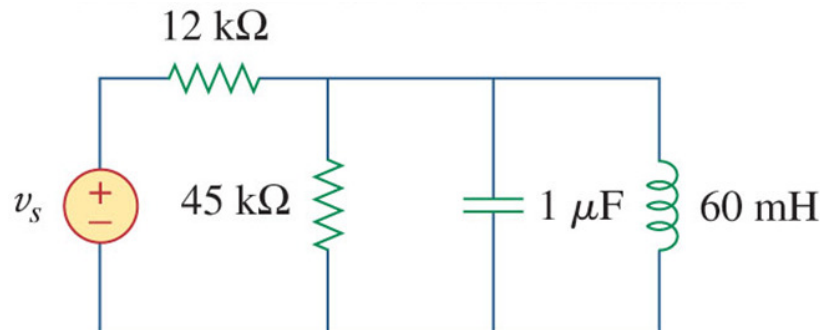



IUPUI ECE 202 Spring 2015:  
Homework #5 (SOLUTIONS)      Name: \_\_\_\_\_

---

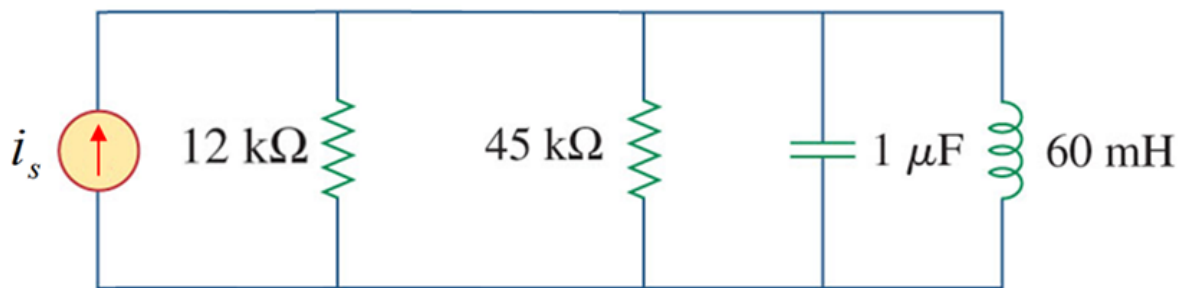1. (Prob. 14.29 in text) Let  $v_s = 20 \cos(\omega t)$  V in the circuit below. Find resonant frequency  $\omega_o$ , quality factor  $\mathbf{Q}$ , and bandwidth  $\mathbf{B}$ , as seen by the capacitor.



First, perform a source transform on the circuit and combine the parallel resistors:



$$i_s = \frac{20}{12} \cos \omega t = 1.66 \cos \omega t$$

$$\mathbf{R} = 12 \text{ k}\Omega \parallel 45 \text{ k}\Omega = \frac{(12)(45)}{(12 + 45)} \text{ k}\Omega = 9.47 \text{ k}\Omega$$

$$(a) \quad \omega_o = \frac{1}{\sqrt{\mathbf{LC}}} = \frac{1}{\sqrt{(60 \times 10^{-3})(1 \times 10^{-6})}} = \boxed{4.082 \text{ krad/s}}$$

$$(b) \quad \mathbf{B} = \frac{1}{\mathbf{RC}} = \frac{1}{(9.47 \times 10^3)(1 \times 10^{-6})} = \boxed{105.6 \text{ rad/s}}$$

$$(c) \quad \mathbf{Q} = \frac{\omega_o}{\mathbf{B}} = \frac{4082}{105.6} = \boxed{38.7}$$

IUPUI ECE 202 Spring 2015:  
Homework #5 (**SOLUTIONS**)      Name: \_\_\_\_\_

---

2. (Prob. 14.35 from Text) A parallel  $RLC$  circuit has  $R = 5 \text{ k}\Omega$ ,  $L = 8 \text{ mH}$ , and  $C = 60 \text{ }\mu\text{F}$ . Determine the following:

- a. The resonant frequency  $\omega_o$
- b. The bandwidth  $\mathbf{B}$
- c. The quality factor  $\mathbf{Q}$


$$(a) \quad \omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(8 \times 10^{-3})(60 \times 10^{-6})}} = \boxed{1.443 \text{ krad/s}}$$

$$(b) \quad \mathbf{B} = \frac{1}{RC} = \frac{1}{(5 \times 10^3)(60 \times 10^{-6})} = \boxed{3.33 \text{ rad/s}}$$

$$(c) \quad \mathbf{Q} = \frac{\omega_o}{\mathbf{B}} = \frac{1443}{3.33} = \boxed{433}$$

IUPUI ECE 202 Spring 2015:  
Homework #5 (SOLUTIONS) Name: \_\_\_\_\_

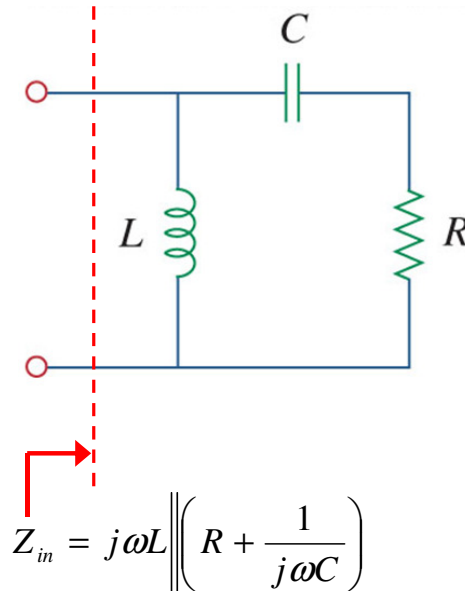3. (Prob. 14.38 from Text) Find the resonant frequency of the circuit in the figure below.



Find the complex impedance and set imaginary part = 0

$$Z_{in} = j\omega L \parallel \left( R - j\frac{1}{\omega C} \right) = \frac{(j\omega L) \left( R - j\frac{1}{\omega C} \right)}{j\omega L + R - j\frac{1}{\omega C}}$$

$$Z_{in} = \frac{\left( j\omega LR + \frac{L}{C} \right)}{R + j\left( \omega L - \frac{1}{\omega C} \right)} \cdot \frac{\left( R - j\left( \omega L - \frac{1}{\omega C} \right) \right)}{R - j\left( \omega L - \frac{1}{\omega C} \right)}$$

$$Z_{in} = \frac{\left( j\omega LR^2 + \frac{LR}{C} \right) - j\left( j\omega LR + \frac{L}{C} \right) \left( \omega L - \frac{1}{\omega C} \right)}{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}$$

$$\text{Im}[Z_{in}] = \frac{\omega LR^2 - \left( \frac{L}{C} \right) \left( \omega L - \frac{1}{\omega C} \right)}{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2} = 0$$

$$\omega LR^2 - \left( \frac{L}{C} \right) \left( \omega L - \frac{1}{\omega C} \right) = 0$$

$$\omega R^2 - \left( \frac{1}{C} \right) \left( \omega L - \frac{1}{\omega C} \right) = 0$$

$$\omega R^2 C - \left( \omega L - \frac{1}{\omega C} \right) = 0$$

$$\omega^2 R^2 C^2 - (\omega^2 LC - 1) = 0$$

$$\omega^2 R^2 C^2 - \omega^2 LC + 1 = 0$$

$$\omega^2 (LC - R^2 C^2) = 1$$

$$\omega = \frac{1}{\sqrt{LC - R^2 C^2}}$$

IUPUI ECE 202 Spring 2015:  
Homework #5 (SOLUTIONS)      Name: \_\_\_\_\_

---

4. (Prob. 14.53 from Text) Design a series *RLC* type **bandpass** filter with cutoff frequencies of 10 kHz and 11 kHz. Assuming  $C = 80 \text{ pF}$  ( $80 \times 10^{-12}$ ), find  $R$ ,  $L$ , and  $Q$ . **Draw** the circuit

Convert frequency into angular frequency:

$$f_1 = 10 \times 10^3 \text{ Hz} \quad \Rightarrow \quad \omega_1 = 2\pi \cdot f_1 = 62,832$$

$$f_2 = 11 \times 10^3 \text{ Hz} \quad \Rightarrow \quad \omega_2 = 2\pi \cdot f_2 = 69,115$$

Find the Bandwidth, center frequency and quality factor “Q”:

$$B = \omega_2 - \omega_1 = 69,115 - 62,832 = 6,283$$

$$\omega_o = \sqrt{\omega_1 \omega_2} = \sqrt{62,832 \times 69,115} = 65,899$$

$$Q = \frac{\omega_o}{B} = \frac{65,899}{6,283} = 10.488$$

Use equation for resonant frequency and known value of C to find L:

$$\omega_o = \frac{1}{\sqrt{LC}} \quad \Rightarrow \quad \omega_o^2 = \frac{1}{LC} \quad \Rightarrow \quad L = \frac{1}{C \omega_o^2}$$

$$L = \frac{1}{80 \times 10^{-12} \times (65,899)^2} = 2.878 \text{ H}$$

Find R from bandwidth equation:


$$B = \frac{R}{L} \quad \Rightarrow \quad R = BL = 6,283 \times 2.878 = 18,086 \text{ } \Omega$$

IUPUI ECE 202 Spring 2015:  
Homework #5 (**SOLUTIONS**)      Name: \_\_\_\_\_

---

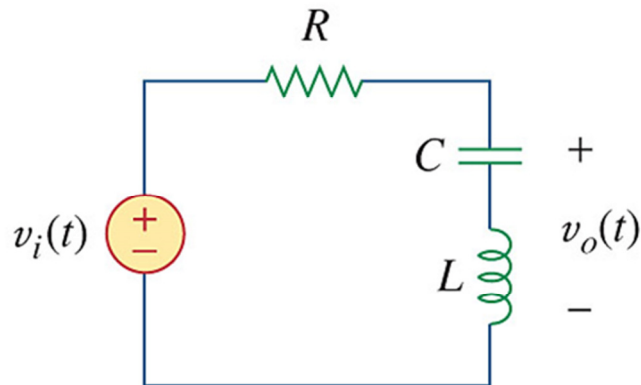5. (Prob. 14.54 from Text) Design passive **bandstop** filter with  $\omega_o = 10$  rad/s and  $Q = 20$ .  
**Draw** the circuit.

Series RLC Bandstop (notch) filter (look at output voltage across L and C)



$$B = \frac{\omega_o}{Q} = \frac{10 \text{ rad/s}}{20} = 0.5 \text{ rad/s}$$

Let  $R = 1 \Omega$

$$B = \frac{R}{L} \Rightarrow L = \frac{R}{B} = \frac{1}{0.5} = 2 \text{ H}$$

$$\omega_o = \frac{1}{\sqrt{LC}} \Rightarrow C = \frac{1}{L \omega_o^2} = \frac{1}{2(10)^2} = 0.005 \text{ F}$$

Choosing different values of R gives the following results:

R	$L = (2)R$	$C = 1/(L \times \omega_o^2)$
1 $\Omega$	2 H	5 mF
5 $\Omega$	10 H	1 mF
8 $\Omega$	16 H	625 $\mu$ F


IUPUI ECE 202 Spring 2015:  
Homework #5 (SOLUTIONS) Name: \_\_\_\_\_

---


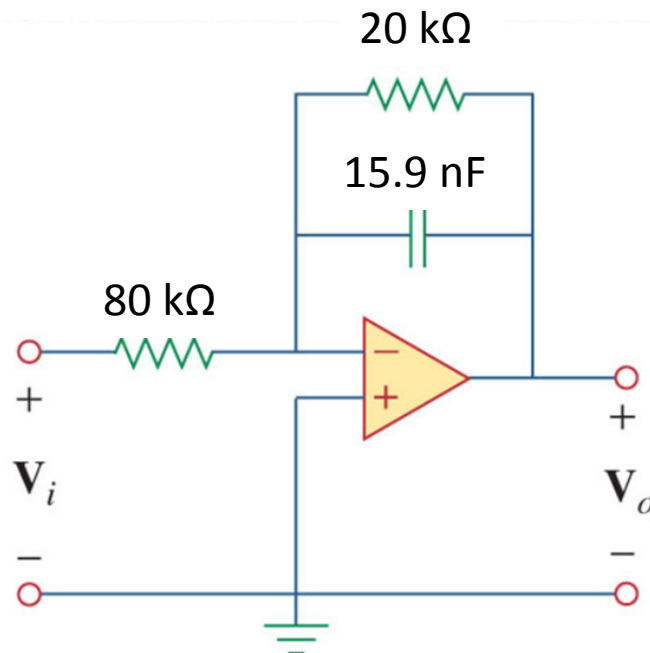
6. (Prob. 14.67 from Text) Design an **active lowpass** filter with dc gain of 0.25 and corner frequency of 500 Hz. (Remember  $\omega = 2\pi f$ )

Start with the equations for Gain and cutoff frequency and “choose” a value for the feedback resistor  $R_f$  (there can be more than one answer to this design problem:

$$\begin{aligned} \text{Gain} &= \frac{R_f}{R_i} = 0.25 & \omega_c &= \frac{1}{R_f C_f} = 2\pi \cdot 500 \\ &\downarrow & &\downarrow \\ &\text{Choose } R_f = 20 \text{ k}\Omega & & \\ &\downarrow & &\downarrow \\ R_i &= \frac{R_f}{0.25} = \frac{20,000}{0.25} = 80 \text{ k}\Omega & C_f &= \frac{1}{\omega_c R_f} \\ & & C_f &= \frac{1}{2\pi \cdot 500 \times 20,000} \\ & & C_f &= 15.9 \times 10^{-9} \text{ F} \end{aligned}$$



### Problem 14.67 - Pspice Simulation

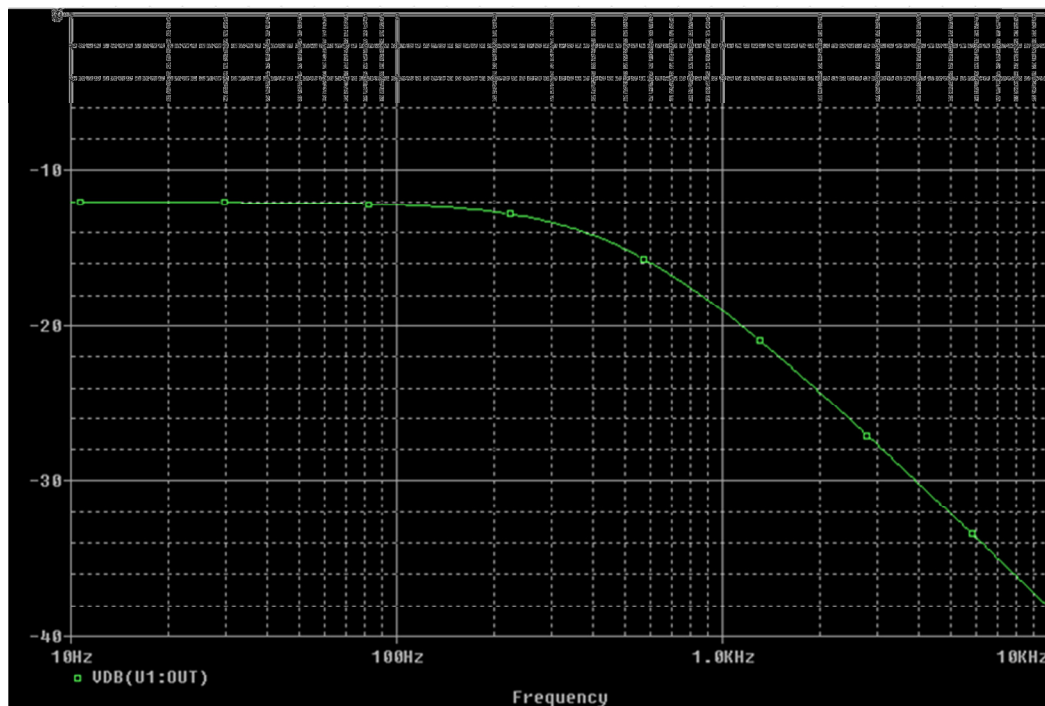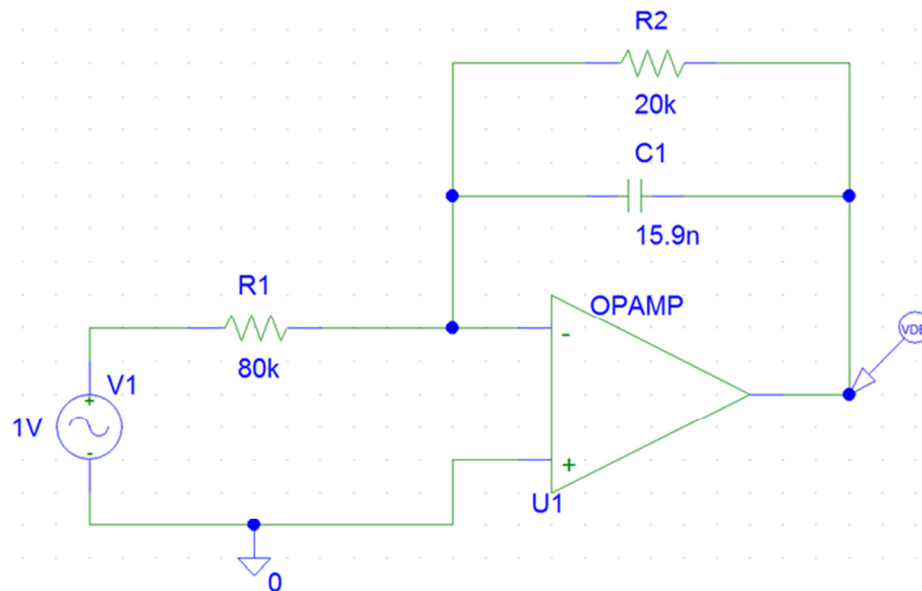

# IUPUI ECE 202 Spring 2015:

## Homework #5 (SOLUTIONS)      Name: \_\_\_\_\_

---

7. (“Based on” Prob. 14.68 from Text) Design an **active highpass** filter with dc voltage gain of +6 dB and corner frequency of 3000 Hz. (Remember  $\omega = 2\pi f$ )

A voltage gain of +6 dB is equivalent to a 2x voltage gain ( $V_{out} = 2 V_{in}$ )

$$20 \log_{10} H = +6 \Rightarrow H = 10^{\frac{6}{20}} \approx 2$$

The magnitude of the voltage gain as  $\omega \rightarrow \infty$  is

$$|H(\infty)| = \frac{R_f}{R_i} = 2 \Rightarrow R_f = (2)R_i$$

Note: We can ignore the 180 degree phase shift caused by going into the inverting terminal if all we care about is the amplitude.

Choose a value for the input impedance  $R_i$


$$R_i = 8 \Omega$$

$$R_f = (2)R_i = 16 \Omega$$

The corner frequency now can be used to find the capacitance value:

$$\omega_c = 2\pi \cdot 3000 = 18850 \text{ rad/s}$$
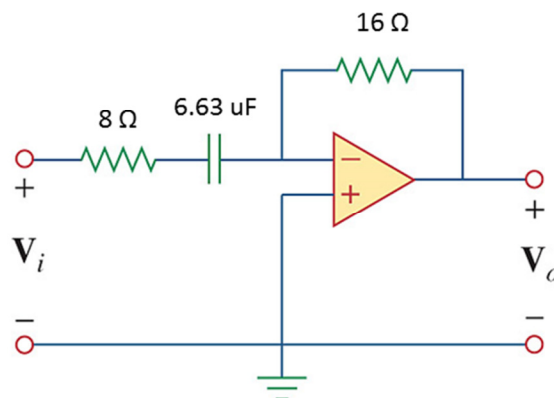
$$\omega_c = \frac{1}{R_i C_i} \Rightarrow C_i = \frac{1}{R_i \omega_c} = \frac{1}{(8)(18850)} = 6.63 \times 10^{-6} \text{ F}$$



Choosing different values of  $R_i$  gives the following results:

$R_i$	$C=1/(R_i\omega_c)$	$R_f$
8 $\Omega$	6.63 $\mu\text{F}$	16 $\Omega$
16 $\Omega$	3.32 $\mu\text{F}$	32 $\Omega$
150 $\Omega$	354 nF	300 $\Omega$



## Problem 14.68 - Pspice Simulation

