


Chapter 19: Two-Port Networks

- 19.1 Introduction
- 19.2 Impedance Parameters (z)
- 19.3 Admittance Parameters (y)
- 19.4 Hybrid Parameters (h)
- 19.5 Transmission Parameters (T)
- 19.6 Relationships between Parameters
- 19.7 Interconnection of Networks
- 19.9 Applications

19.1 Introduction (1)

- A port is an access to the network and consists of a pair of terminals; the current entering one terminal leaves through the other terminal so that the net current entering the port equals zero.
- One port networks include two-terminal devices such as resistors, capacitors, and inductors.
- A two-port network has two separate ports for input and output.
- Two port networks include op amps, transistors and transformers.

19.1 Introduction (2)

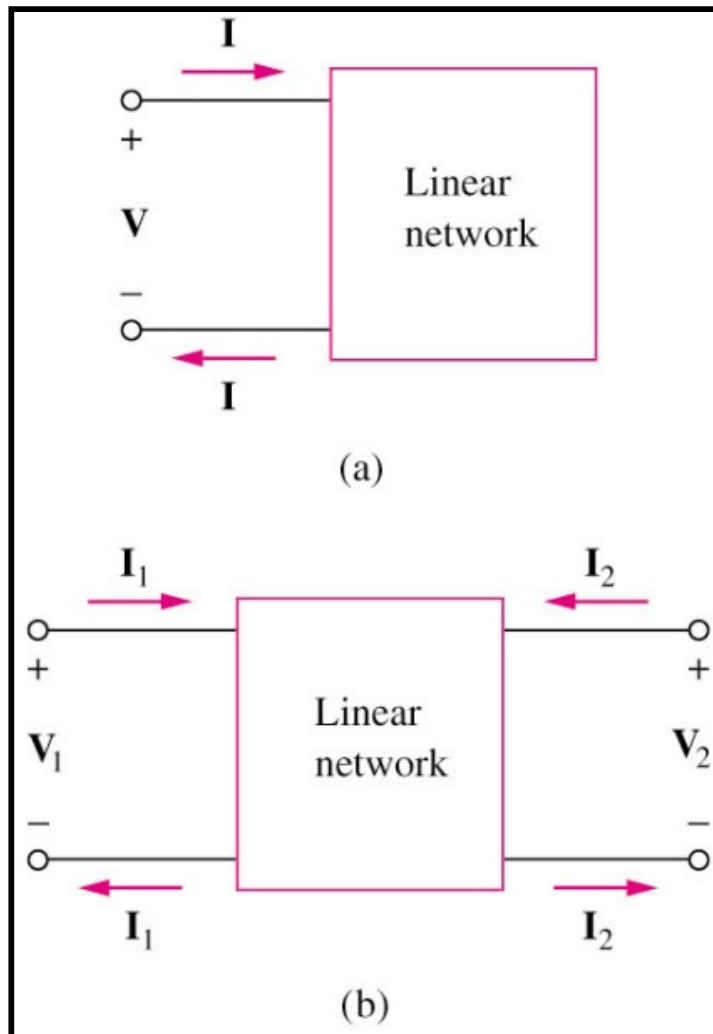

**One port or two
terminal circuit**

**Two port or four
terminal circuit**


- It is an electrical network with two separate ports for input and output.
- No independent sources.

19.1 Introduction (3)

- Characterizing a two-port network requires that we relate the terminal quantities \mathbf{V}_1 , \mathbf{V}_2 , \mathbf{I}_1 , \mathbf{I}_2 out of which two are independent. Six sets of voltage and current parameters will be derived.
- Two port networks are useful in communications, control systems, power systems, and electronics.
- They are used in electronics to model transistors and to facilitate cascaded design.
- Additionally, if we know the parameters of a two-port network it can be treated as a “black box” when embedded within a larger network.

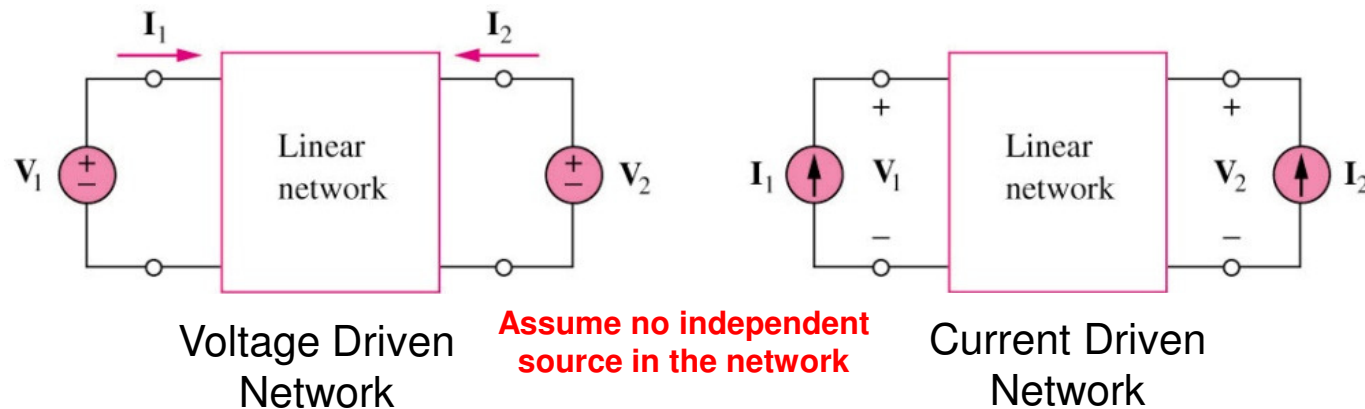19.2 Impedance Parameters (1)

- Often called “**Z-parameters**” since their units are in **ohms** and they represent an impedance relationship between V_1 , V_2 , I_1 , I_2 for the two port network shown below:



$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$




$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

- Z-parameters are commonly used in filter synthesis, impedance matching networks design, and power distribution networks analysis.

19.2 Impedance Parameters (2)

The values of parameters can be evaluated by setting $I_1=0$ or $I_2=0$ (open circuit)

Setting $I_2 = 0$

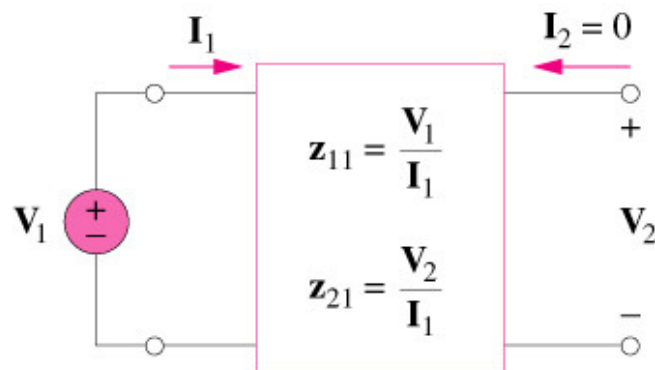


(a)

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

z_{11} = Open-circuit input impedance
 z_{21} = Open-circuit transfer impedance
from port 2 to port 1

Setting $I_1 = 0$

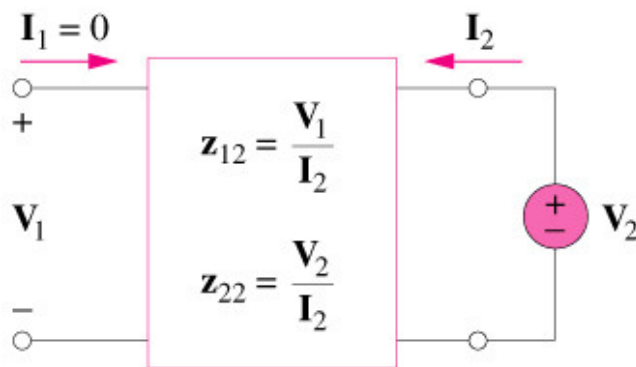

(b)


$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

z_{12} = Open-circuit transfer impedance from port 1 to port 2
 z_{22} = Open-circuit output impedance

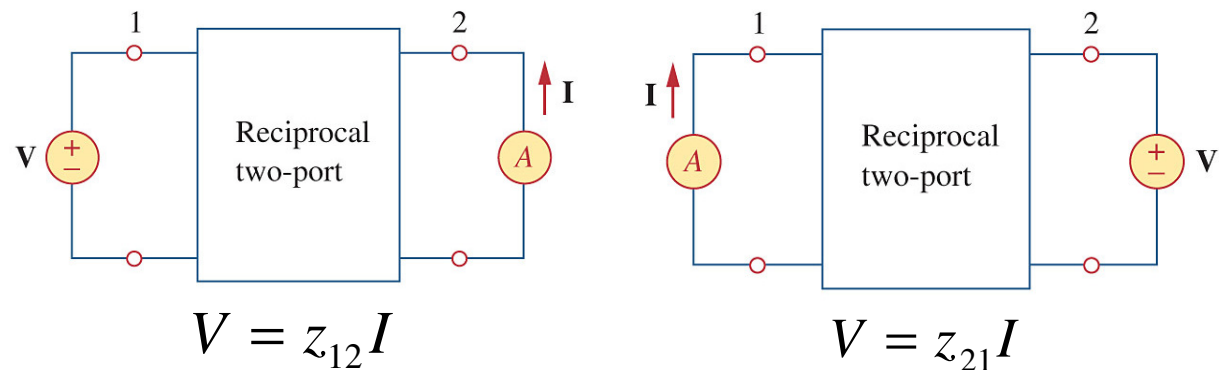19.2 Impedance Parameters (3)


Properties of Z-parameters

- Symmetrical networks $z_{11} = z_{22}$
 - Implies a mirror like symmetry
- Reciprocal networks $z_{12} = z_{21}$
 - Any network made up entirely of resistors, capacitors, and inductors must be reciprocal.
 - Linear networks with no dependant sources are reciprocal.
 - Interchanging an ideal voltage source at one port with an ideal ammeter at the other port gives the same ammeter reading.



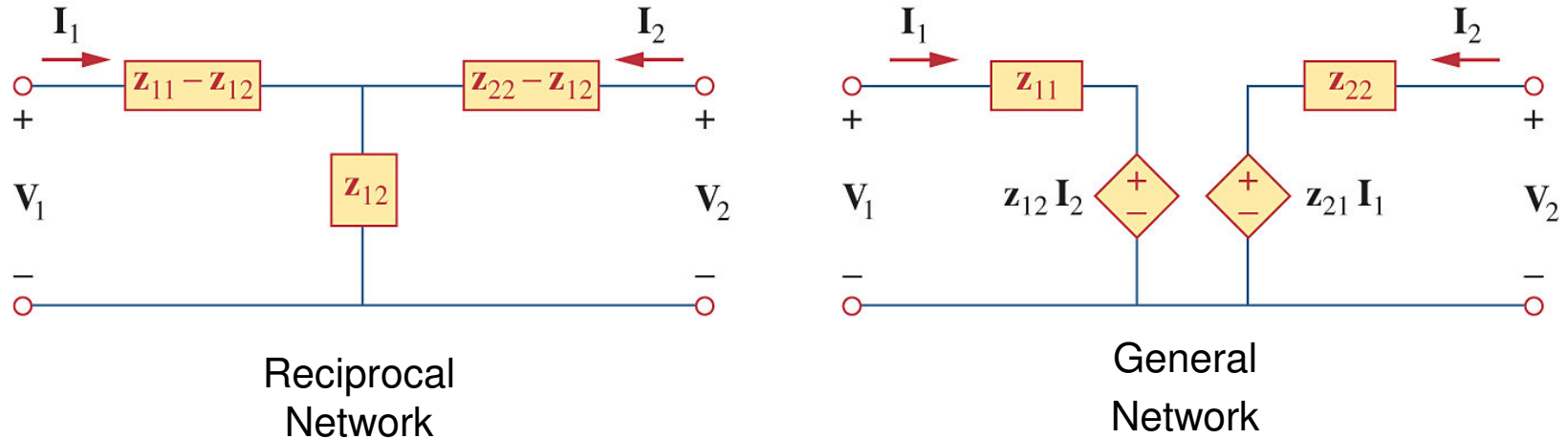19.2 Impedance Parameters (4)


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



- A reciprocal network can be replaced by the T-network shown above
- If not reciprocal, the General network is the T-equivalent.

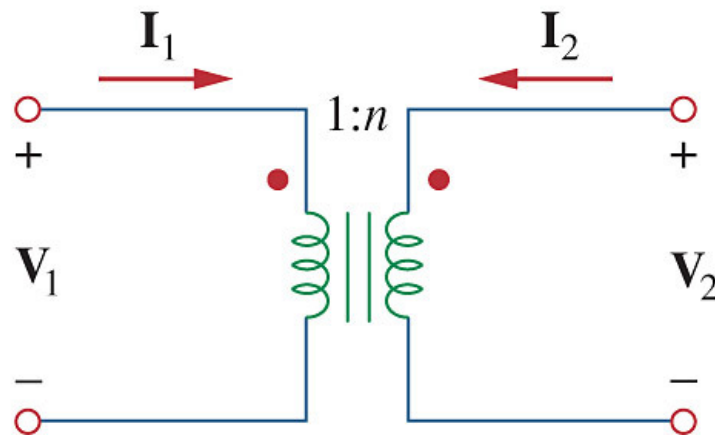19.2 Impedance Parameters (5)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



- Note: some circuits do not have z-parameter equivalents. (they may have other 2-port equivalents, as we shall see)

- Consider an ideal transformer:

$$V_1 = V_2/n \text{ and } I_1 = -nI_2.$$

- This cannot be expressed by:


$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

19.2 Impedance Parameters (6)

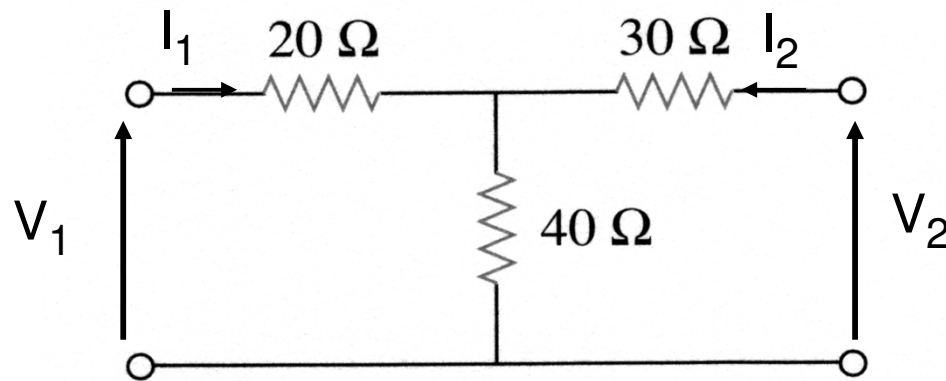Example 19.1

Determine the z-parameters of the following circuit.



$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$



Answer:
$$z = \begin{bmatrix} 60 & 40 \\ 40 & 70 \end{bmatrix} \Omega$$


$$Z = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \Omega$$

19.2 Impedance Parameters (7)

Practice Problem 19.2

Determine I_1 and I_2 in the following circuit.

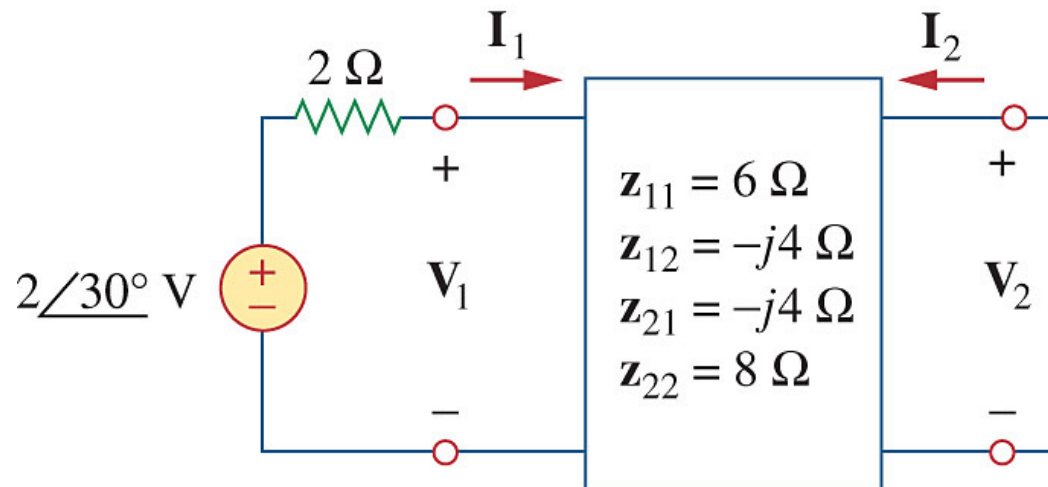
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

Answer: $I_1 = 200\angle 30^\circ \text{ mA}$
 $I_2 = 100\angle 120^\circ \text{ mA}$

19.3 Admittance Parameters (1)

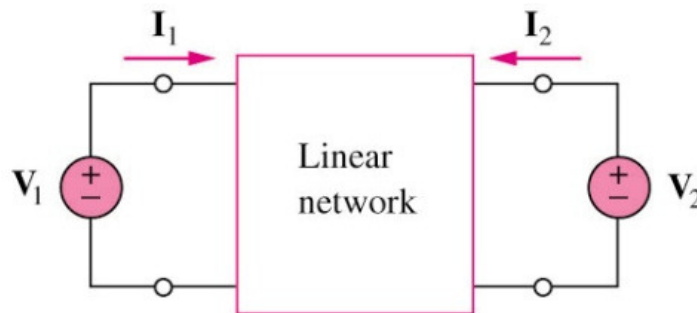

(a)

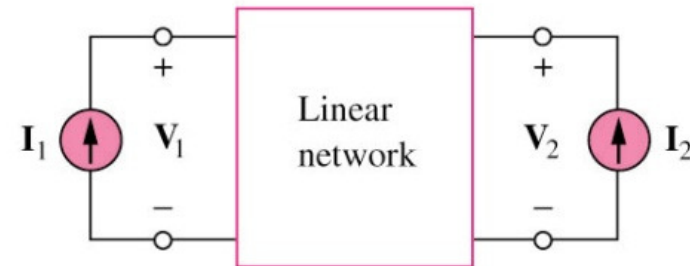

(b)

Assume no independent source in the network


$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$




$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

where the **y** terms are called the admittance parameters, or simply **y** parameters, and they have units of Siemens.

19.3 Admittance Parameters (2)

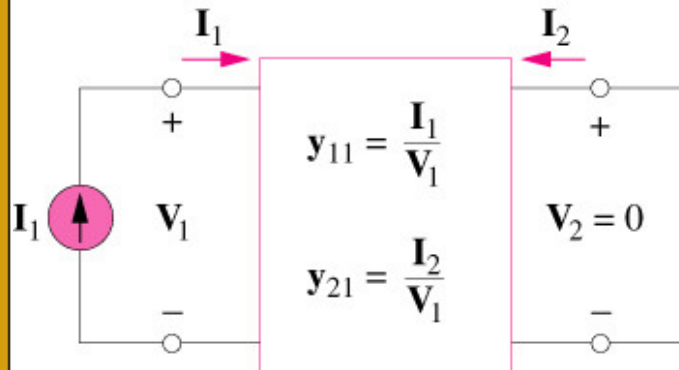

(a)

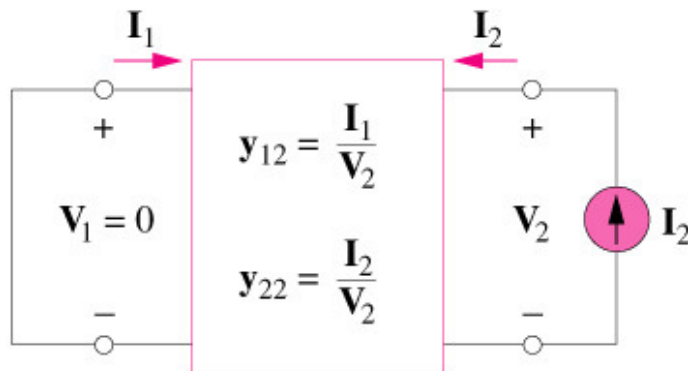

(b)

Setting $V_2 = 0$ (Shorting the output)

$$y_{11} = \frac{I_1}{V_1} \bigg|_{V_2=0} \quad \text{and} \quad y_{21} = \frac{I_2}{V_1} \bigg|_{V_2=0}$$


y_{11} = Short-circuit input admittance
 y_{21} = Short-circuit transfer admittance from port 1 to port 2

Setting $V_1 = 0$ (Shorting the input)

$$y_{12} = \frac{I_1}{V_2} \bigg|_{V_1=0} \quad \text{and} \quad y_{22} = \frac{I_2}{V_2} \bigg|_{V_1=0}$$

y_{12} = Short-circuit transfer admittance from port 2 to port 1
 y_{22} = Short-circuit output admittance

19.3 Admittance Parameters (3)

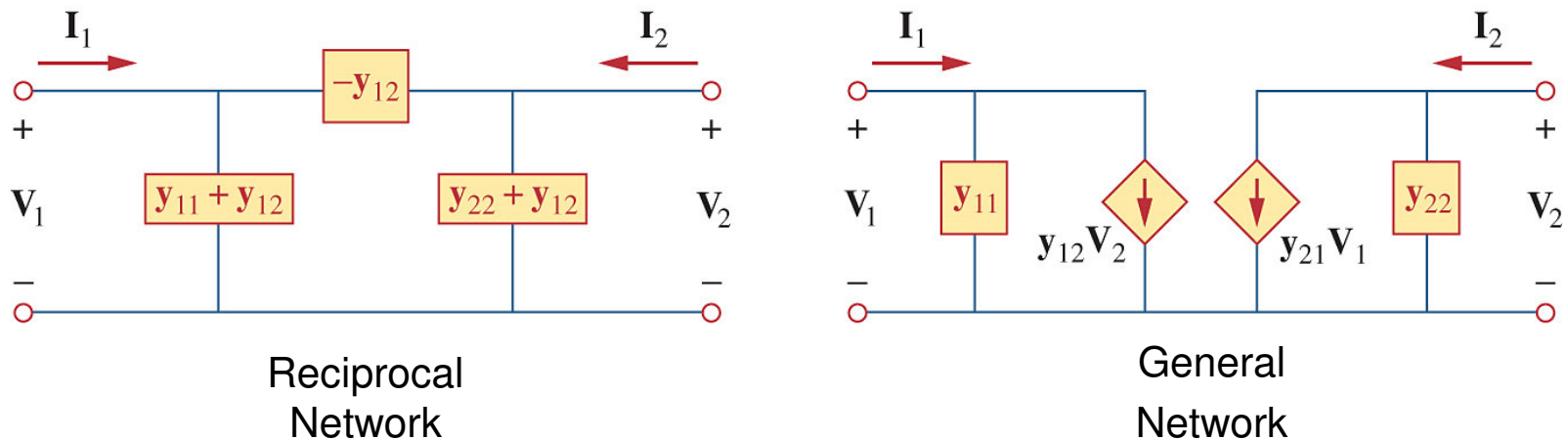


- A reciprocal network ($y_{12} = y_{21}$) can be replaced by the Pi-network in figure (a).
- If not reciprocal, the network in figure (b) is the Pi-equivalent.

19.3 Admittance Parameters (4)

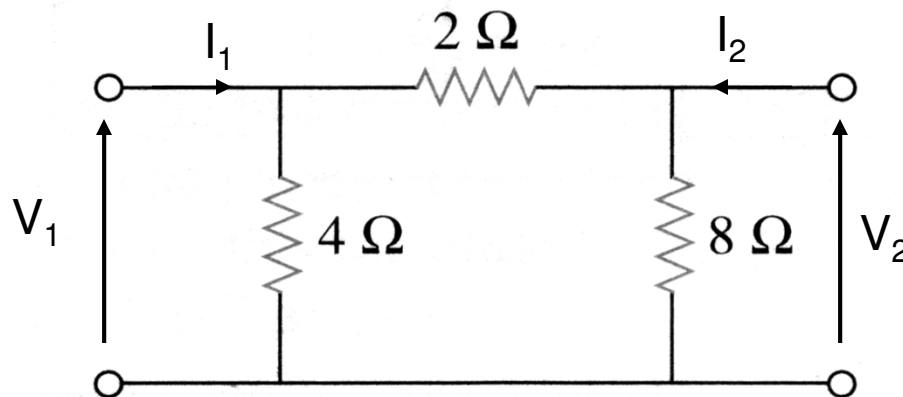Example 19.3

Determine the y-parameters of the following circuit.



Answer: $y = \begin{bmatrix} 0.75 & -0.5 \\ -0.5 & 0.625 \end{bmatrix} \text{S}$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$




$$y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \text{S}$$

19.3 Admittance Parameters (5)

Practice Problem 19.3

Practice Problem 19.3

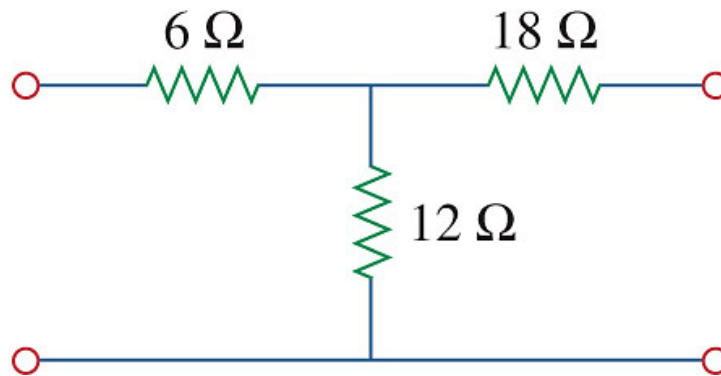Determine the y-parameters of the following circuit.



Answer: $y = \begin{bmatrix} 75.77 & -30.3 \\ -30.3 & 45.47 \end{bmatrix} \text{ mS}$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$



$$y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \text{ S}$$

19.3 Admittance Parameters (6)

Practice Problem 19.3

Practice Problem 19.3 (Solution)

- Short the output
- Put a 1 volt source at input
- Find I_1 and I_2

$$y_{11} = \frac{I_1}{(1)} \bigg|_{V_2=0} \quad \text{and} \quad y_{21} = \frac{I_2}{(1)} \bigg|_{V_2=0}$$

Find Input Impedance

$$Z_{in} = 6 + 12 \parallel 18 = 13.2$$

$$I_1 = \frac{V_1}{Z_{in}} = \frac{1}{13.2} = 0.07576$$


$$y_{11} = 0.07576$$

Similarly at Output

$$Z_{out} = 18 + 6 \parallel 12 = 22$$

$$I_2 = \frac{V_2}{Z_{in}} = \frac{1}{22} = 0.04545$$

$$y_{22} = 0.04545$$

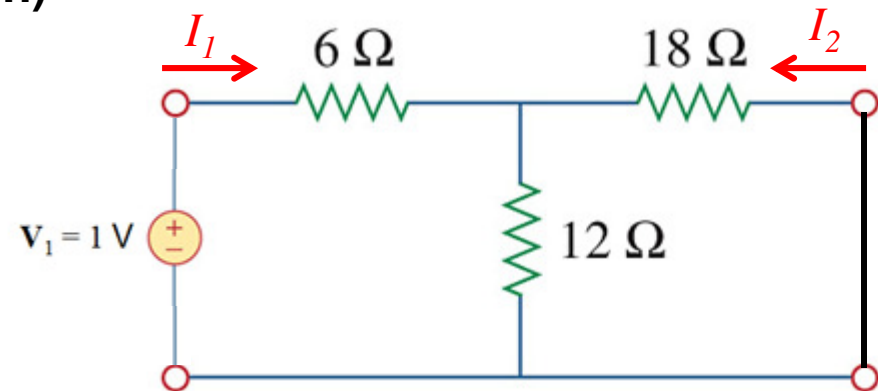

Find I_2 from current divider equation

$$I_2 = \frac{-12}{12 + 18} I_1$$

$$I_2 = (-0.4)0.07576 = -0.0303$$

$$y_{21} = -0.0303$$

$$y_{12} = y_{21} = -0.0303$$


Reciprocal Network

19.3 Admittance Parameters (7)

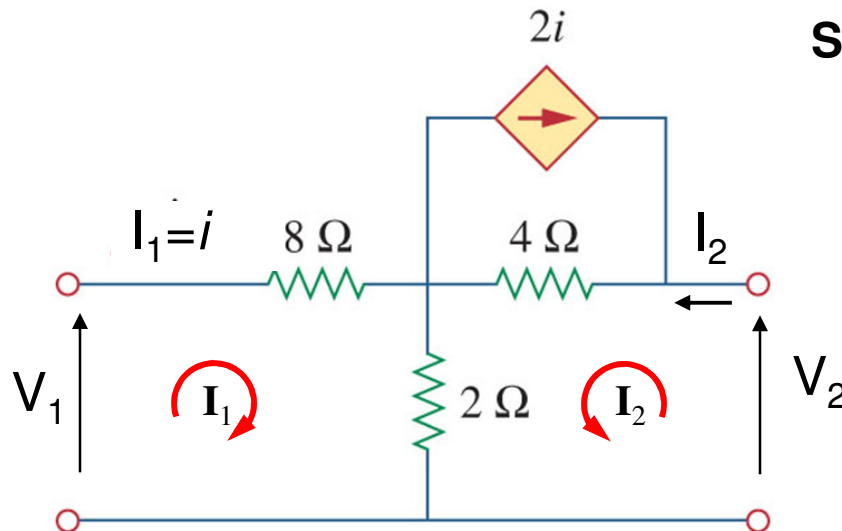Example 19.4

Determine the y-parameters of the following circuit.

$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$



Answer: $y = \begin{bmatrix} 0.15 & -0.05 \\ -0.25 & 0.25 \end{bmatrix} \text{S}$

Note: Sometimes two port parameters will fall out directly from mesh equations.

Solution: Apply KVL

Mesh I_1 : $V_1 = 8I_1 + 2(I_1 + I_2)$

$$V_1 = 10I_1 + 2I_2$$

Mesh I_2 : $V_2 = 4(2i + I_2) + 2(I_1 + I_2)$

$$V_2 = 8I_1 + 4I_2 + 2I_1 + 2I_2$$

$$V_2 = 10I_1 + 6I_2$$

Subtract #1 from #2:

$$V_2 - V_1 = 0 + 4I_2$$

$$I_2 = -0.25V_1 + 0.25V_2$$

Substitute back into #1

$$V_1 = 10I_1 - 0.5V_1 + 0.5V_2$$

$$10I_1 = 1.5V_1 - 0.5V_2$$


$$I_1 = 0.15V_1 - 0.05V_2$$

19.3 Admittance Parameters (8)

Practice problem 19.4

Practice Problem 19.4

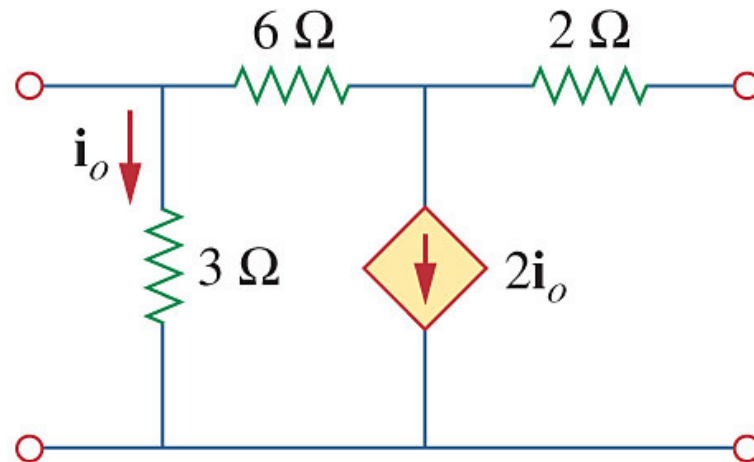Determine the y-parameters of the following circuit.



Answer: $y = \begin{bmatrix} 0.625 & -0.125 \\ 0.375 & 0.125 \end{bmatrix} S$

19.3 Admittance Parameters (9)

Practice problem 19.4

Practice Problem 19.4 (Solution)

- Short the output
- Put a 1 volt source at input
- Find I_1 and I_2

First find i_o :

$$i_o = \frac{1}{3}$$

Dependent current source is then $2/3$, find I_1 by repetitive source transformations of the dependant current source


$$I_1 = 0.625 \Rightarrow y_{11} = 0.625$$

Next find current across $6\ \Omega$ resistor $I_{6\Omega}$:

$$I_{6\Omega} = 0.625 - \frac{1}{3}$$

$$I_2 + I_{6\Omega} = 2i_o$$
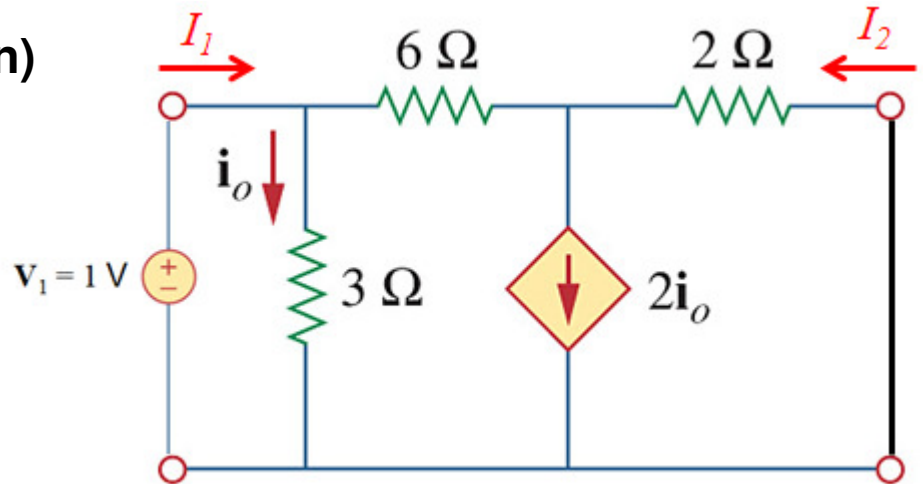
$$I_2 = 2i_o - I_{6\Omega} = \frac{2}{3} - \left(0.625 - \frac{1}{3}\right) = 0.375 \Rightarrow y_{12} = 0.375$$



Z and Y Parameters

Comparison

Z-Parameters


$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

- **Open** one port ($I_1=0$ or $I_2=0$)
- Connect a source to the other port
- Solve to find z-parameters

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

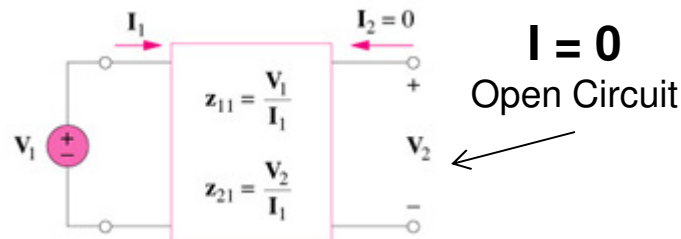

Y-Parameters


$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

- **Short** one port ($V_1=0$ or $V_2=0$)
- Connect a source to the other port
- Solve to find y-parameters

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

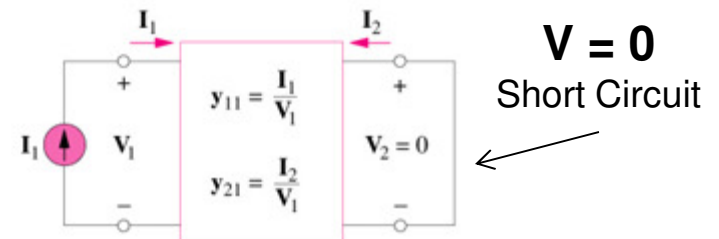


Z and Y parameters

Alternative method (1 Amp / 1 Volt sources)

Z-Parameters

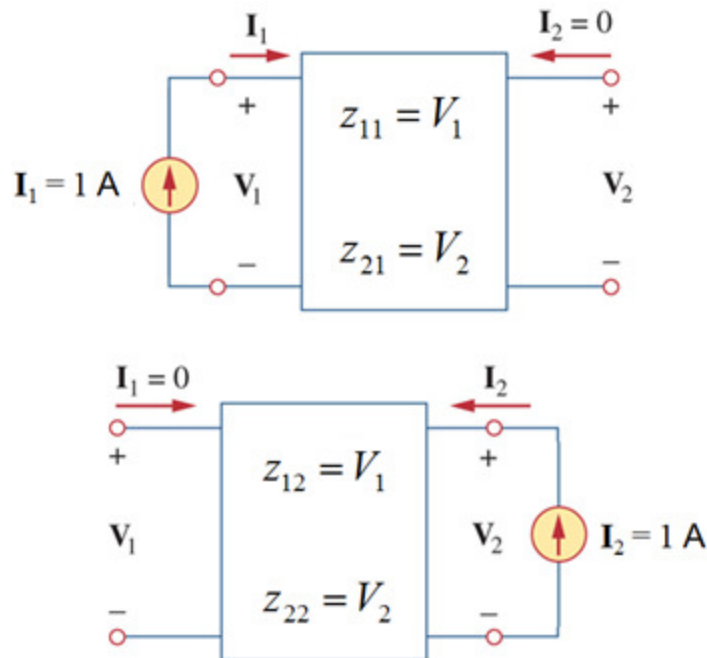
- Open circuit one port
- Put a 1 Amp current source at other port
- Resulting voltages are the z-parameters



$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

Y-Parameters

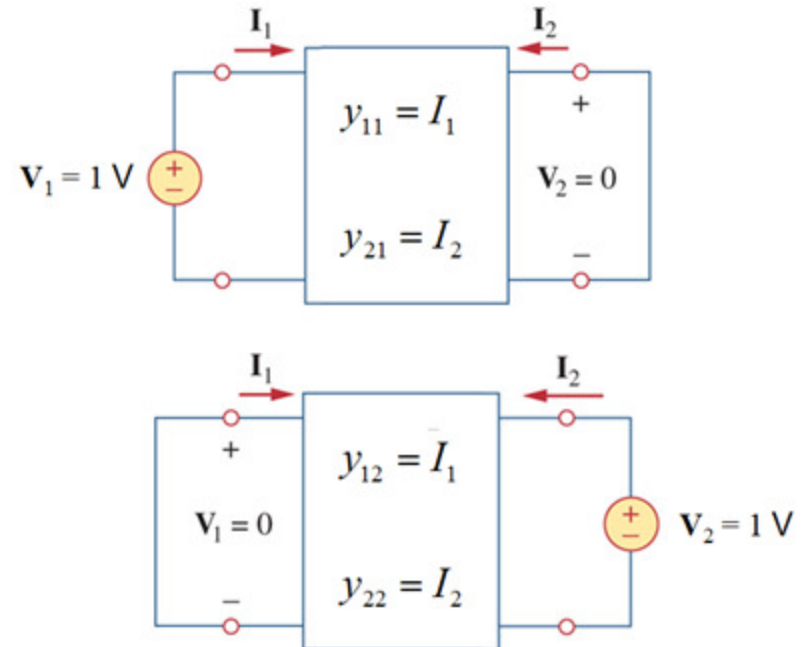
- Short circuit one port
- Put a 1 Volt voltage source at other port
- Resulting current are the y-parameters



$$\begin{aligned} I_1 &= y_{11}V_1 + y_{12}V_2 \\ I_2 &= y_{21}V_1 + y_{22}V_2 \end{aligned}$$

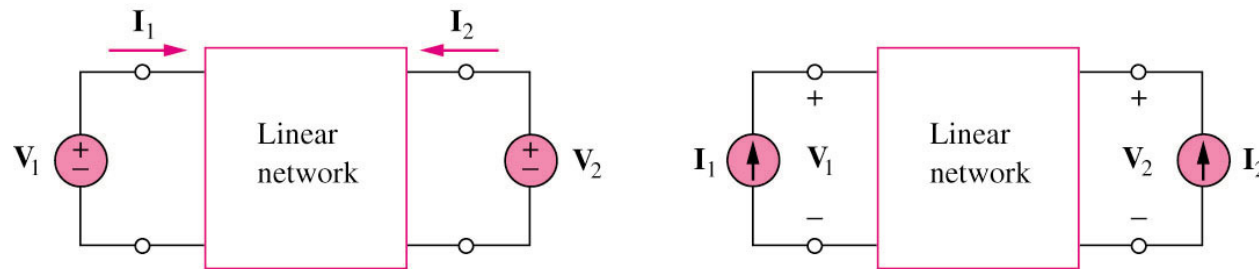19.4 Hybrid Parameters (1)

- The z and y parameters of a two-port network do not always exist. Therefore, there is a need to develop another set of parameters based on making V_1 and I_2 the dependent variables.



Assume no independent source in the network

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$




$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [h] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

where the **h** terms are called the hybrid parameters, or simply h parameters.

- Hybrid parameters are very useful for describing electronic devices such as transistors because it is much easier to measure the h parameters of these devices than to measure their z or y parameters.
- The ideal transformer can also be described by h parameters.

19.4 Hybrid Parameters (2)

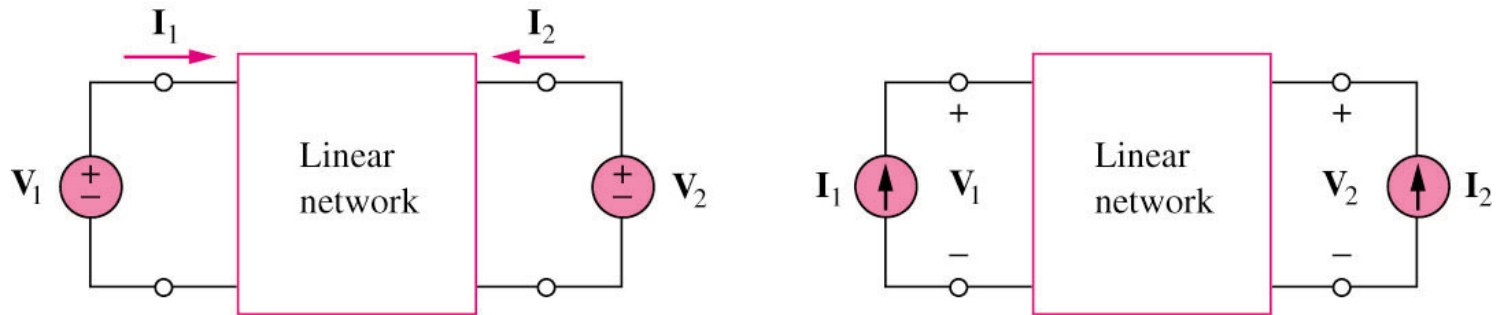

Assume no independent source in the network

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

h_{11} = short-circuit
input impedance (Ω)

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

h_{21} = short-circuit
forward current gain

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$


h_{12} = open-circuit
reverse voltage-gain

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

h_{22} = open-circuit
output admittance (S)


- Note that the h parameters represent an impedance, voltage gain, current gain, and admittance, thereby the term hybrid parameters.
- For reciprocal network, $h_{12} = -h_{21}$

19.4 Hybrid Parameters (3)

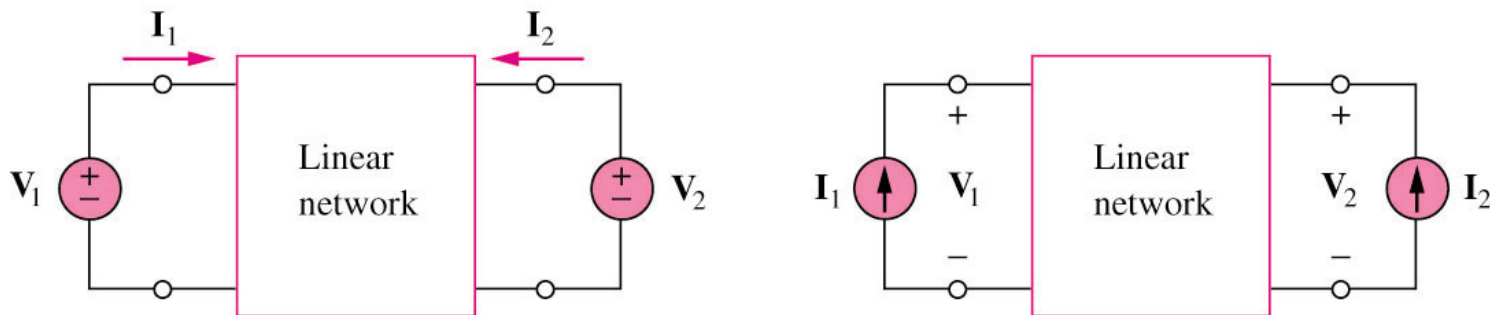

Assume no independent source in the network


Hybrid model of a two-port network:

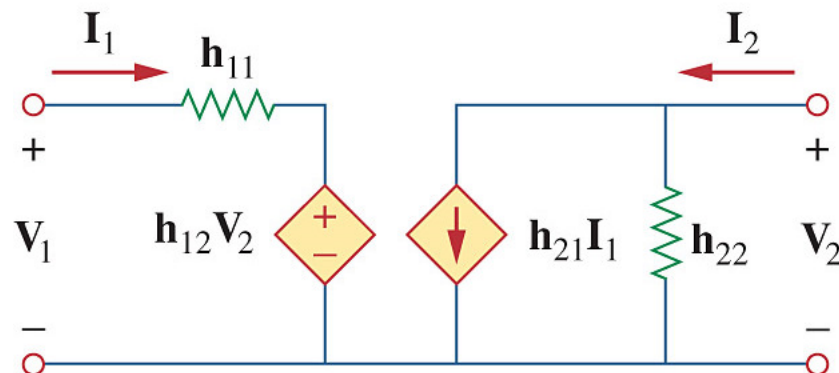

19.4 Hybrid Parameters (4)

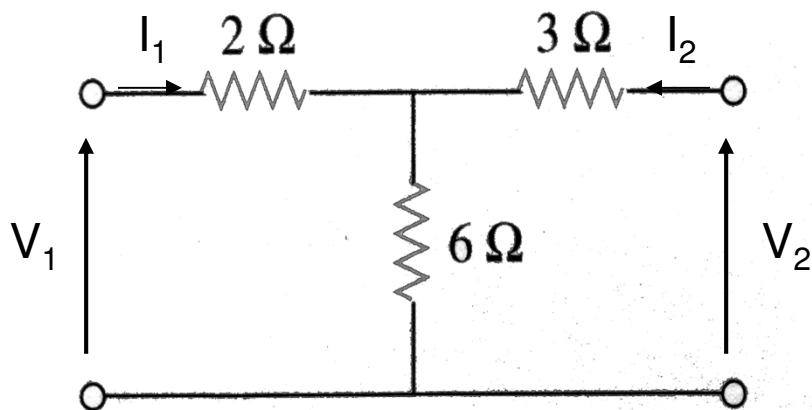Example 19.5:

Determine the h-parameters of the following circuit.



Answer:

$$h = \begin{bmatrix} 4\Omega & \frac{2}{3} \\ -\frac{2}{3} & \frac{1}{9}S \end{bmatrix}$$

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{and} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{and} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$




$$h = \begin{bmatrix} h_{11}\Omega & h_{12} \\ h_{21} & h_{22}S \end{bmatrix}$$

19.4 Hybrid Parameters (5)

Practice Problem 19.5:

Determine the h-parameters of the following circuit.

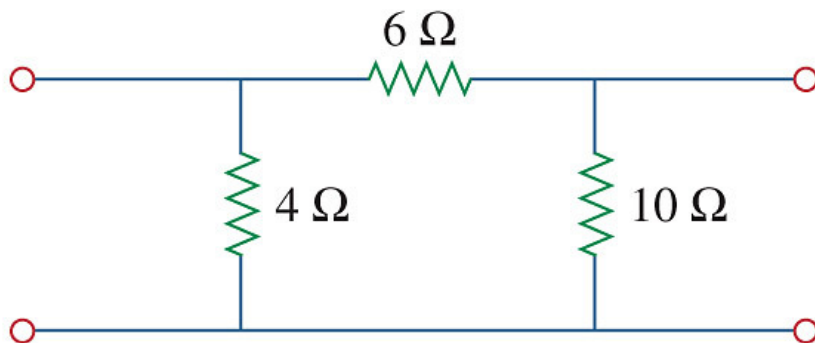Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{and} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{and} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$



Answer:

$$h = \begin{bmatrix} 2.4\Omega & 0.4 \\ -0.4 & 0.2S \end{bmatrix}$$

$$h = \begin{bmatrix} h_{11}\Omega & h_{12} \\ h_{21} & h_{22}S \end{bmatrix}$$

19.9.1 Transistor Circuits (1)

Hybrid Parameters

- H-parameters are often used to model transistor circuits
- The h-parameters vary depending on biasing conditions
- Parameters are given different subscripts:
 - $h_{11} \rightarrow h_{ie}$ = Base input impedance
 - $h_{12} \rightarrow h_{re}$ = Reverse voltage feedback ratio
 - $h_{21} \rightarrow h_{fe}$ = Base-collector current gain
 - $h_{22} \rightarrow h_{oe}$ = Output admittance

Example 2N3904

2N3903 2N3904

h PARAMETERS
($V_{CE} = 10$ Vdc, $f = 1.0$ kHz, $T_A = 25^\circ\text{C}$)

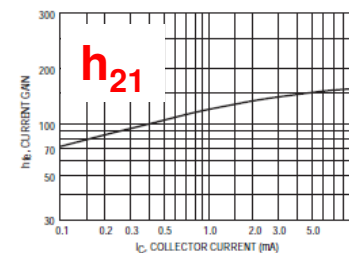
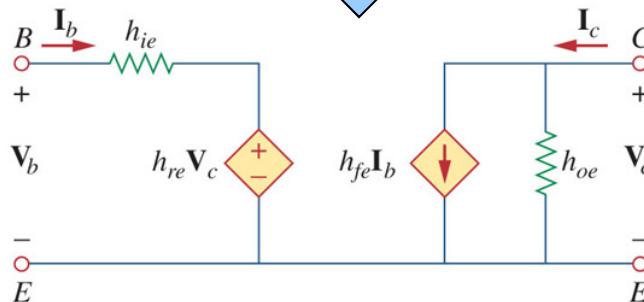
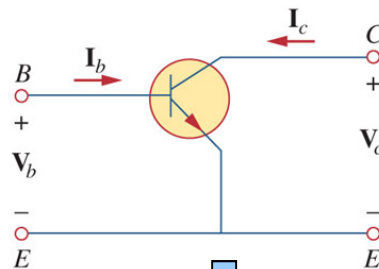


Figure 11. Current Gain

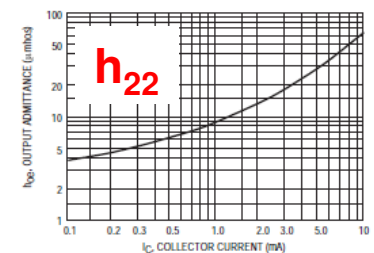


Figure 12. Output Admittance

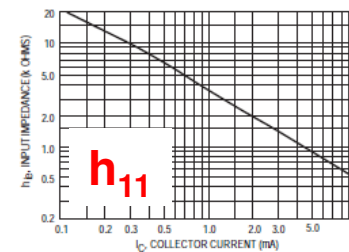


Figure 13. Input Impedance


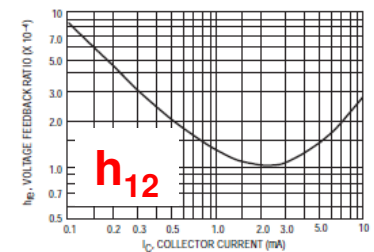


Figure 14. Voltage Feedback Ratio

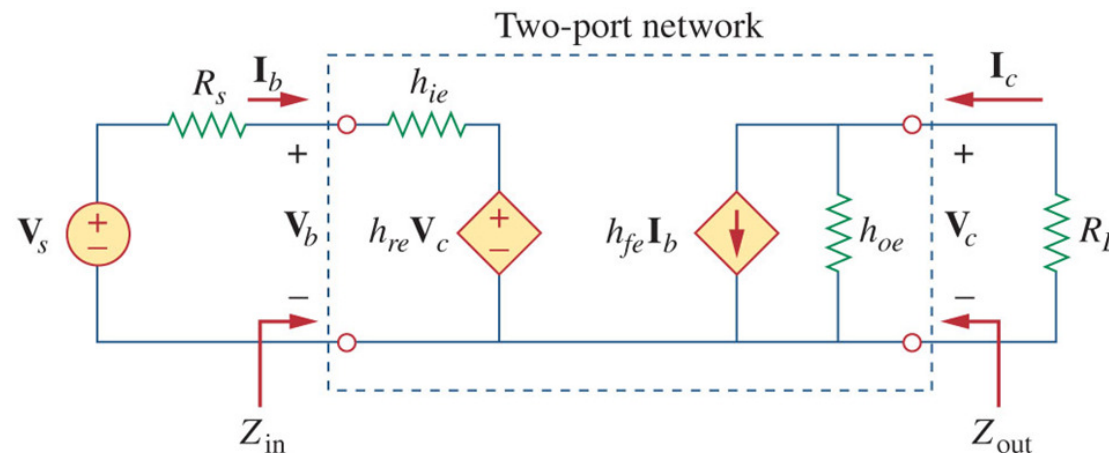19.9.1 Transistor Circuits (2)

Hybrid Parameters

- H parameters are often found in manufacturers spec sheets
- Provide ability to calculate the exact voltage gain, input impedance, and output impedance of the transistor.



Input Impedance

$$Z_{in} = \frac{V_b}{I_b} = h_{ie} - \frac{h_{re} h_{fe} R_L}{1 + h_{oe} R_L}$$

Current Gain

$$A_i = \frac{I_c}{I_b} = \frac{h_{fe}}{1 + h_{oe} R_L}$$


Output Impedance

$$Z_{out} = \frac{V_c}{I_c} \bigg|_{V_s=0} = \frac{R_s + h_{ie}}{(R_s + h_{ie})h_{oe} - h_{re} h_{fe}}$$

Voltage Gain

$$A_v = \frac{V_c}{V_b} = \frac{-h_{fe} R_L}{h_{ie} + (h_{ie} h_{oe} - h_{re} h_{fe}) R_L}$$

19.5 Transmission Parameters (1)

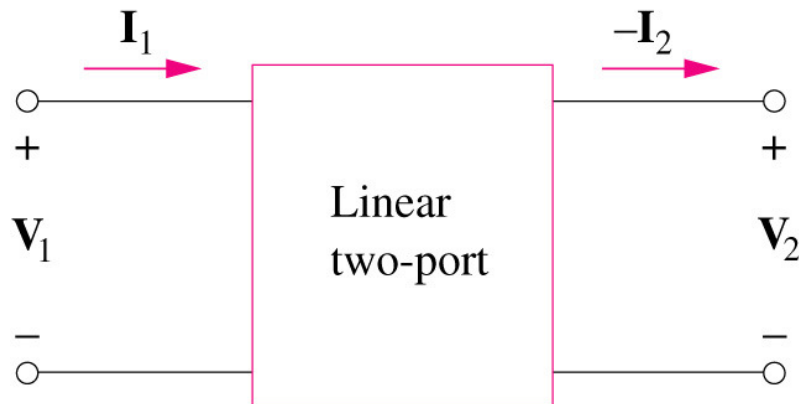

**Assume no
independent source
in the network**

$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = [T] \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

where the **T** terms are called the transmission parameters, or simply **T** or ABCD parameters.

•Note that $-I_2$ is used since the current is considered to be leaving the network. It is logical to think of I_2 as leaving the two-port; this is customary convention in the power industry.

19.5 Transmission Parameters (2)

- These two-port transmission parameters provide a measure of how a circuit transmits voltage and current from a source to a load.
- They are useful in the analysis of transmission lines and are therefore called transmission parameters.
- They are also known as ABCD parameters and are used in the design of telephone systems, microwave networks, and radars.

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

A=open-circuit
voltage ratio

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

C= open-circuit
transfer admittance
(S)

$$B = - \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

B= negative short-
circuit transfer
impedance (Ω)

$$D = - \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

D=negative short-
circuit current ratio

19.5 Transmission Parameters (3)

Solving for Transmission Parameters

- To find the transmission parameters, analyze the circuit as follows:
- Perform the analysis with the output Open Circuited ($I_2=0$)

$$\begin{array}{l} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{array} \xrightarrow{\substack{\text{red arrow} \\ \text{0}}} \begin{array}{l} V_1 = AV_2 \\ I_1 = CV_2 \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} A = \frac{V_1}{V_2} \\ C = \frac{I_1}{V_2} \end{array}$$


- Perform the analysis with the output Short Circuited ($V_2=0$)

$$\begin{array}{l} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{array} \xrightarrow{\substack{\text{red arrow} \\ \text{0}}} \begin{array}{l} V_1 = -BI_2 \\ I_1 = -DI_2 \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} B = -\frac{V_1}{I_2} \\ D = -\frac{I_1}{I_2} \end{array}$$

19.5 Transmission Parameters (4)

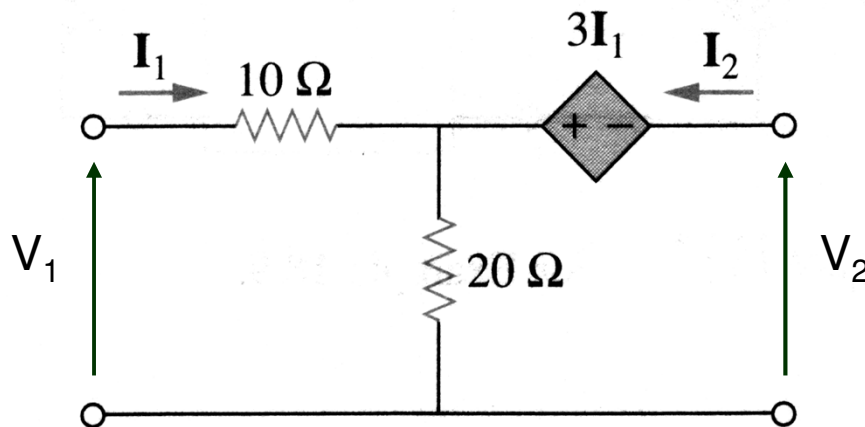Example 19.8

Determine the T-parameters of the following circuit.



$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$

Apply KVL

$$\begin{aligned} V_1 &= 10I_1 + 20(I_1 + I_2) \\ V_2 &= -3I_1 + 20(I_1 + I_2) \end{aligned}$$



Answer:

$$T = \begin{bmatrix} 1.765 & 15.294\Omega \\ 0.059S & 1.176 \end{bmatrix}$$

$$\begin{aligned} V_1 &= \frac{30}{17}V_2 - \frac{260}{17}I_2 \\ I_1 &= \frac{1}{17}V_2 - \frac{20}{17}I_2 \end{aligned}$$

19.5 Transmission Parameters (5)

Example 19.8

From KVL:

$$V_1 = 10I_1 + 20(I_1 + I_2) = 30I_1 + 20I_2$$

$$V_2 = -3I_1 + 20(I_1 + I_2) = 17I_1 + 20I_2$$


If we “open circuit” the output we get:

$$V_1 = 30I_1 + 20\overset{0}{I_2}$$

$$V_1 = 30I_1$$

$$V_2 = 17I_1 + 20\overset{0}{I_2}$$

$$V_2 = 17I_1$$

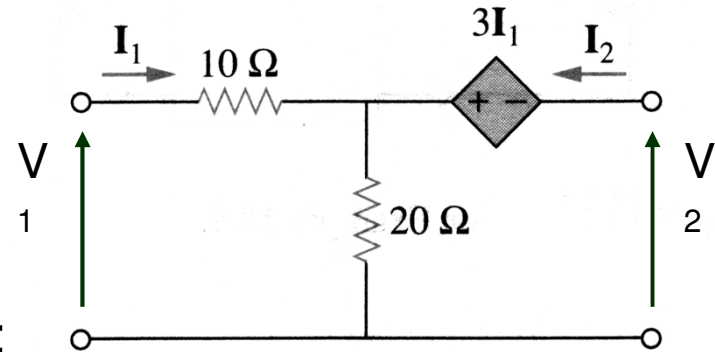

$$A = \frac{V_1}{V_2} = \frac{30I_1}{17I_1} = \frac{30}{17} = 1.765$$

$$C = \frac{1}{17} = 0.0588$$

If we “short circuit” the output we get:

$$V_1 = 30I_1 + 20I_2$$

$$V_1 = 30I_1 + 20I_2$$

$$\overset{0}{V_2} = 17I_1 + 20I_2$$

$$0 = 17I_1 + 20I_2$$

$$V_1 = 30\left(\frac{-20}{17}\right)I_2 + 20I_2$$


$$I_1 = \frac{-20}{17}I_2$$

$$B = -\frac{V_1}{I_2} = -\frac{(30\left(\frac{-20}{17}\right) + 20)I_2}{I_2} = 15.29$$

$$D = -\frac{I_1}{I_2} = \frac{20}{17} = 1.176$$

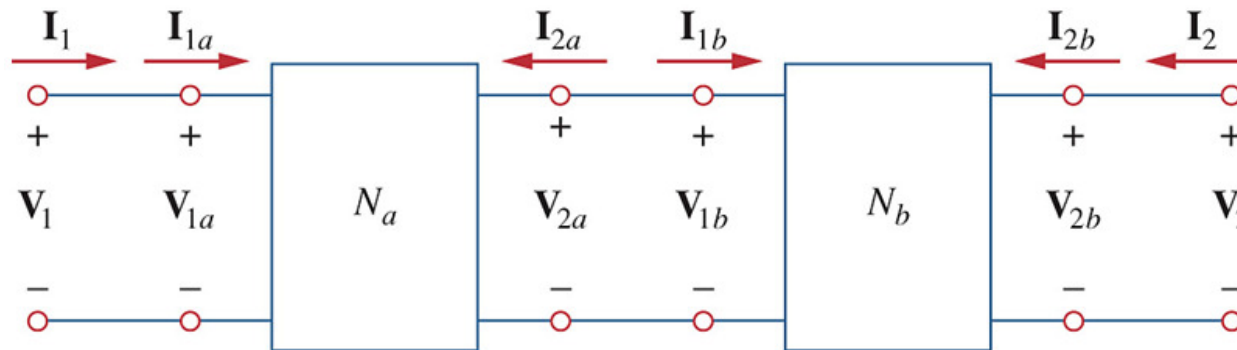19.5 Transmission Parameters (6)

- Transmission Parameters can be cascaded with the result found through simple matrix multiplication



$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$-I_{2a} = I_{1b}$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

19.5 Transmission Parameters (7)

Properties: Building Block Circuits

Consider the following
simple circuits

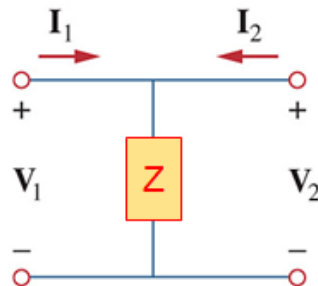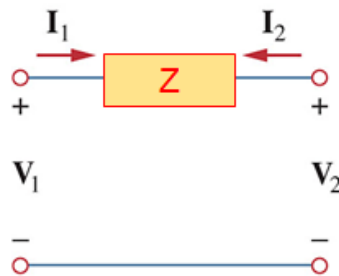


We can find their T
Parameters to be:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{Z} & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Note, following
is equivalent

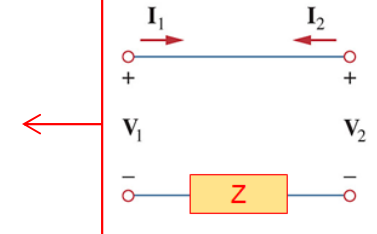

19.5 Transmission Parameters (8)

Properties: Building Block Circuits

- We can use this to construct the following “building block T parameters” to find the T parameters for any ladder type circuit.

$$\begin{bmatrix} 1 & R \\ 0 & 1 \end{bmatrix}$$




$$\begin{bmatrix} 1 & \frac{1}{sC} \\ 0 & 1 \end{bmatrix}$$




$$\begin{bmatrix} 1 & sL \\ 0 & 1 \end{bmatrix}$$



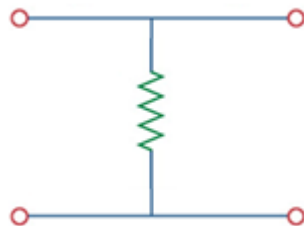
$$\begin{bmatrix} 1 & 0 \\ \frac{1}{R} & 1 \end{bmatrix}$$


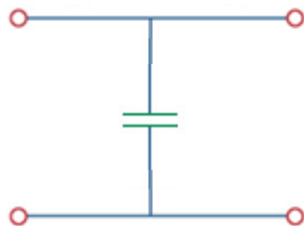
$$\begin{bmatrix} 1 & 0 \\ sC & 1 \end{bmatrix}$$


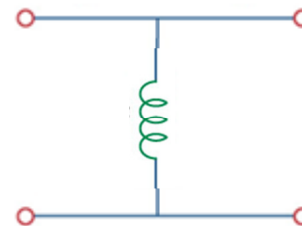
$$\begin{bmatrix} 1 & 0 \\ \frac{1}{sL} & 1 \end{bmatrix}$$



19.5 Transmission Parameters (9)

Properties: Transfer function / Thevenin Equivalent

- The “A” parameter can be used to provide the inverse of the voltage Transfer Function $H(s)$.

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

- Parameters “A” and “B” can be used to find a relationship between the Open Circuit Voltage (V_2) and the Short Circuit Current ($-I_2$).
- We can use this to find the parameters for the Thevenin Equivalent Circuit.


$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{V_1}{V_{oc}}$$

$$V_{Th} = V_{oc} = \frac{V_1}{A}$$


$$Z_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{B}{A}$$

$$B = - \left. \frac{V_1}{I_2} \right|_{V_2=0} = \frac{V_1}{I_{sc}}$$

$$I_N = I_{sc} = \frac{V_1}{B}$$

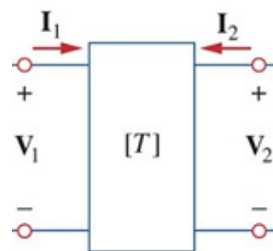

$$V_{Th} = \frac{V_1}{A}$$

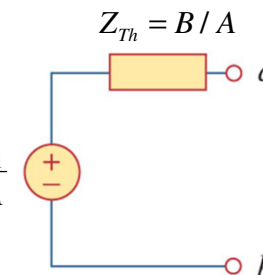


19.5 Transmission Parameters (10)

Transfer Function - Example

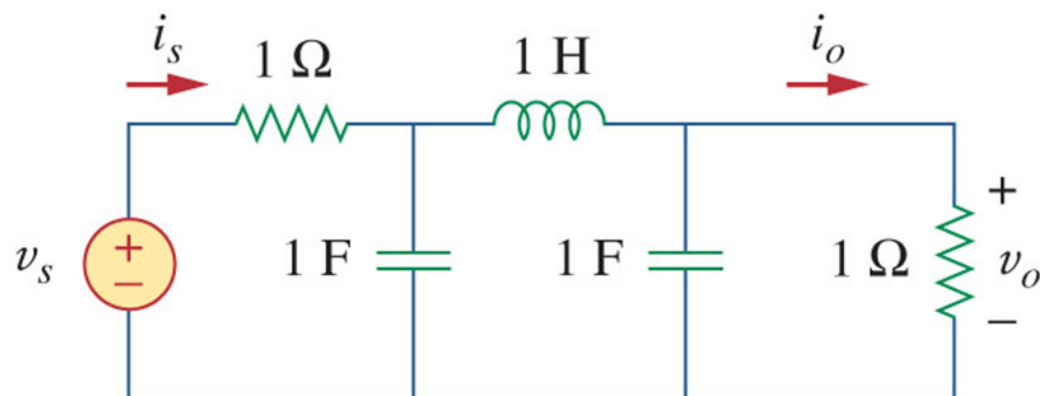Problem 16.80(a)

Find the transfer function $V_o(s)/V_s(s)$ for the following circuit



Answer:


$$H(s) = \frac{1}{s^3 + 2s^2 + 3s + 2}$$

19.5 Transmission Parameters (11)

Transfer Function - Example

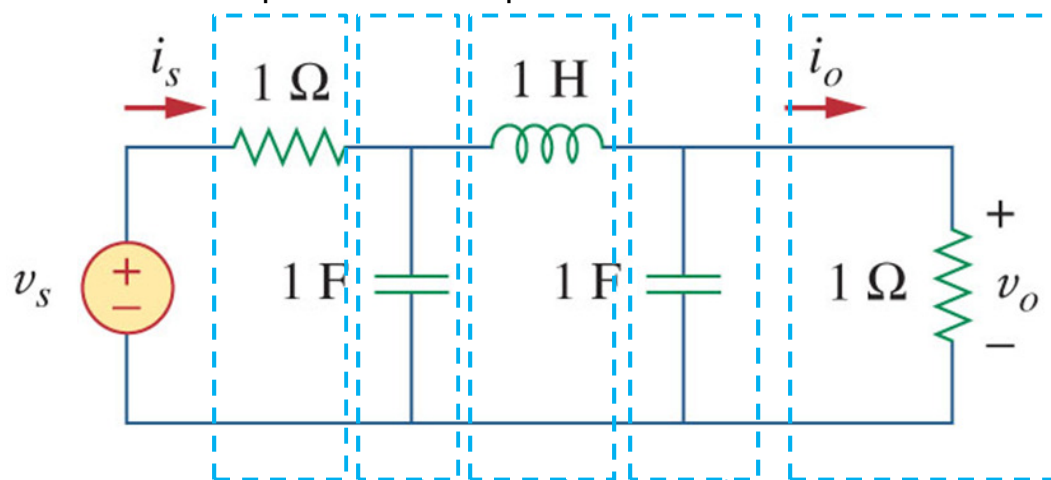Problem 16.80(a) Solution:

- Break up the circuit into a series of cascaded series and shunt components
- Find the composite "T" parameters for the circuit
- Use the relationship between the parameter "A" and the Transfer function



$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

19.5 Transmission Parameters (12)

Transfer Function - Example

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix}$$

Finding the
combined T-matrix

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ (s+1) & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1+s(s+1) & s \\ (s+1) & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1+s(s+1) & s \\ s+s^2(s+1)+(s+1) & s^2 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} s^2+s+1 & s \\ s^3+s^2+2s+1 & s^2 \end{bmatrix}$$

$$\begin{bmatrix} s^3+2s^2+3s+2 & s+s^2 \\ s^3+s^2+2s+1 & s^2 \end{bmatrix}$$

The transfer function can be found
directly from the Transmission
Parameter "A" !

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

$$H(s) = \frac{1}{s^3+2s^2+3s+2}$$


19.5 Transmission Parameters (13)

Example 19.9

The ABCD parameters of the two-port network at right are




$$\mathbf{T} = \begin{bmatrix} 4 & 20 \, \Omega \\ 0.1 \text{ S} & 2 \end{bmatrix}$$

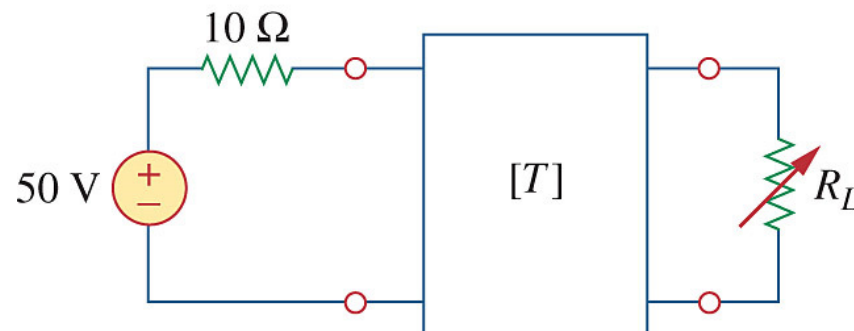Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



The output port is connected to a variable load for maximum power transfer. Find R_L and the maximum power transferred.

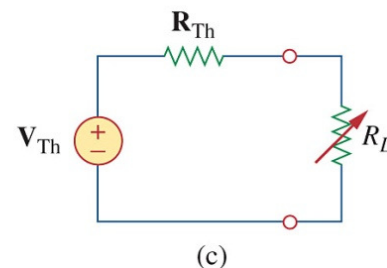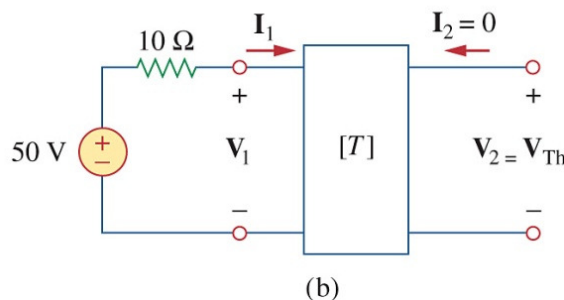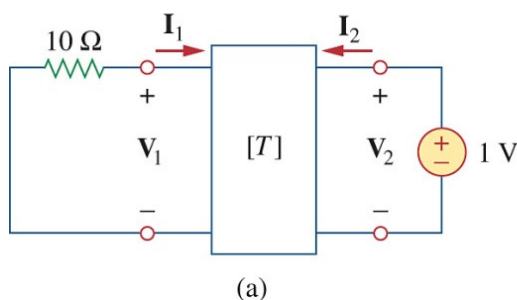Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Answer: $V_{TH} = 10 \text{ V}$; $R_L = 8 \Omega$; $P_m = 3.125 \text{ W}$.

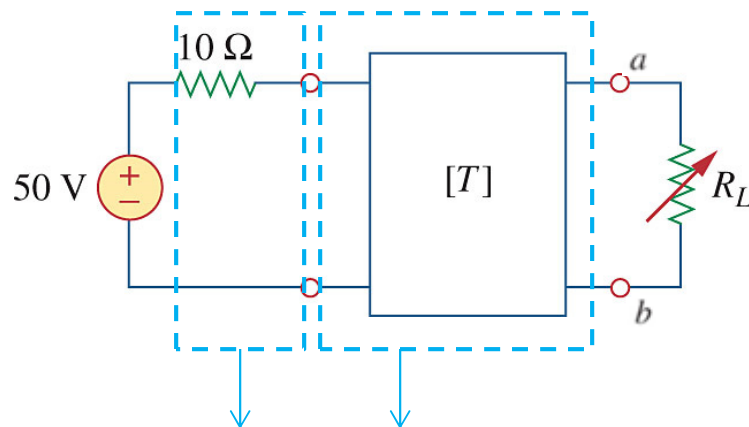19.5 Transmission Parameters (14)


Solution: Example 19.9

- Cascade the Series Resistor with the network
- Find the composite "T" parameters for the circuit
- Use the relationships to find V_{Th} and Z_{Th}



$$[T'] = \begin{bmatrix} 1 & 10 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 4 & 20 \\ 0.1 & 2 \end{bmatrix} = \begin{bmatrix} 5 & 40 \\ 0.1 & 2 \end{bmatrix}$$

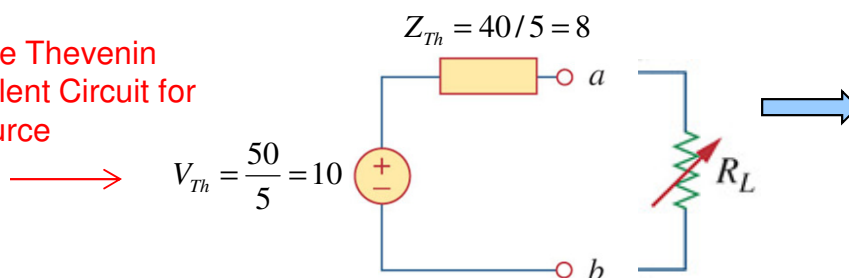Find the Thevenin
Equivalent Circuit for
the source



For Max Power Transfer

$$R_L = Z_{Th} = 8 \Omega$$

$$P_{\max} = I^2 R_L$$


$$P_{\max} = \left(\frac{V_{Th}}{R_L + Z_{Th}} \right)^2 R_L$$

$$P_{\max} = \left(\frac{10}{16} \right)^2 8 = 3.125 \text{ W}$$

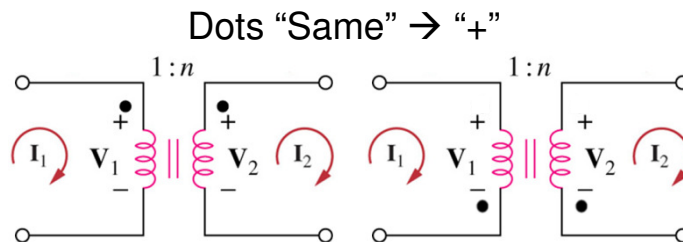19.5 Transmission Parameters (15)

Properties: Building Block Circuits – Ideal Transformer

- We can also use these “building blocks” to model ideal transformers. Remember from Chapter 13




$$V_2 = nV_1$$

$$I_2 = \frac{I_1}{n}$$


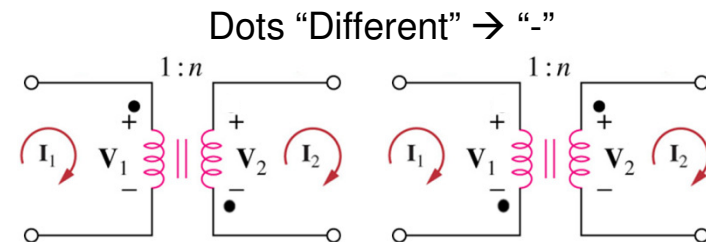
$$\begin{bmatrix} \frac{1}{n} & 0 \\ 0 & n \end{bmatrix}$$



$$V_2 = -nV_1$$

$$I_2 = -\frac{I_1}{n}$$



$$\begin{bmatrix} -\frac{1}{n} & 0 \\ 0 & -n \end{bmatrix}$$


T - parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

19.5 Transmission Parameters (16)

Example 13.8 Revisited

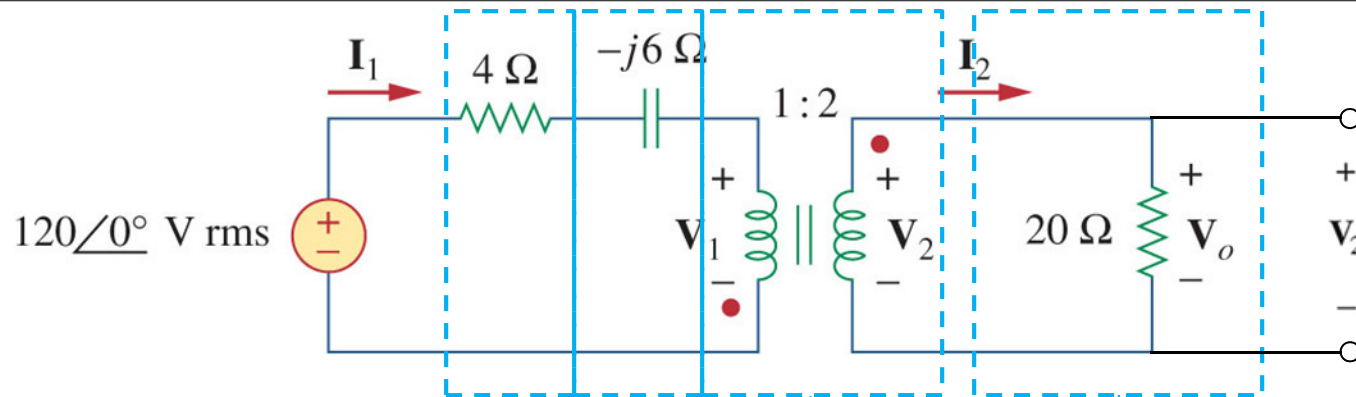

Cascaded T parameters →

$$\begin{bmatrix} 1 & 4 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & -j6 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} -\frac{1}{2} & 0 \\ 0 & -2 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0.05 & 1 \end{bmatrix}$$

a b c d

Using MATLAB: →

```
>> T=a*b*c*d


T =

-0.9000 + 0.6000i -8.0000 + 12.0000i
-0.1000 + 0.0000i -2.0000 + 0.0000i
```

$$V_0 = V_2 = \frac{1}{A} V_1 = \left(\frac{1}{-0.9 + 0.6j} \right) (120 \angle 0^\circ) = 110.94 \angle -146.31^\circ \text{ V}$$

19.5 Transmission Parameters (17)

Example 13.8 Revisited

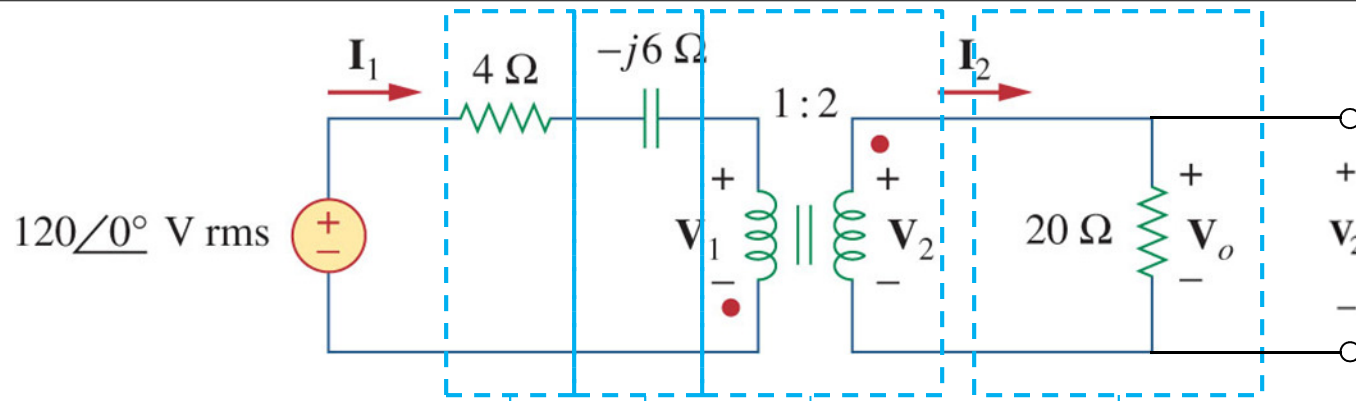

```
>> T=a*b*c*d
```

```
T =
```


```
-0.9000 + 0.6000i  -8.0000 +12.0000i  
-0.1000 + 0.0000i  -2.0000 + 0.0000i
```

$$I_1 = CV_2 = (-0.1)(110.94\angle -146.31^\circ) = 11.09\angle 33.69^\circ \text{ A}$$

$$I_2 = \frac{V_2}{20} = \frac{(110.94\angle -146.31^\circ)}{20} = 5.55\angle -146.31^\circ \text{ A}$$

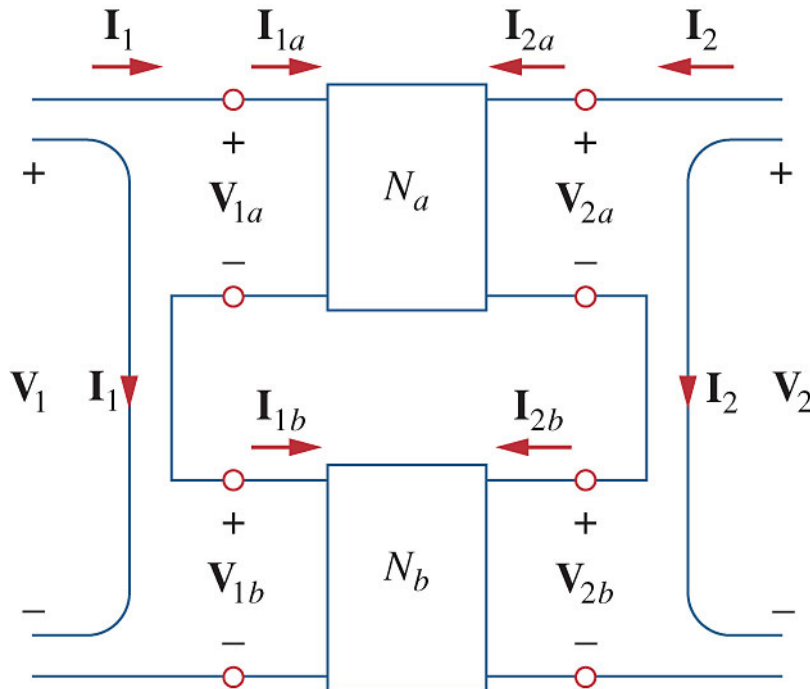19.7 Interconnection of Networks (1)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Series Connection of
two-port networks:

For Impedances; ADD
matrices.

$$Z = Z_a + Z_b$$

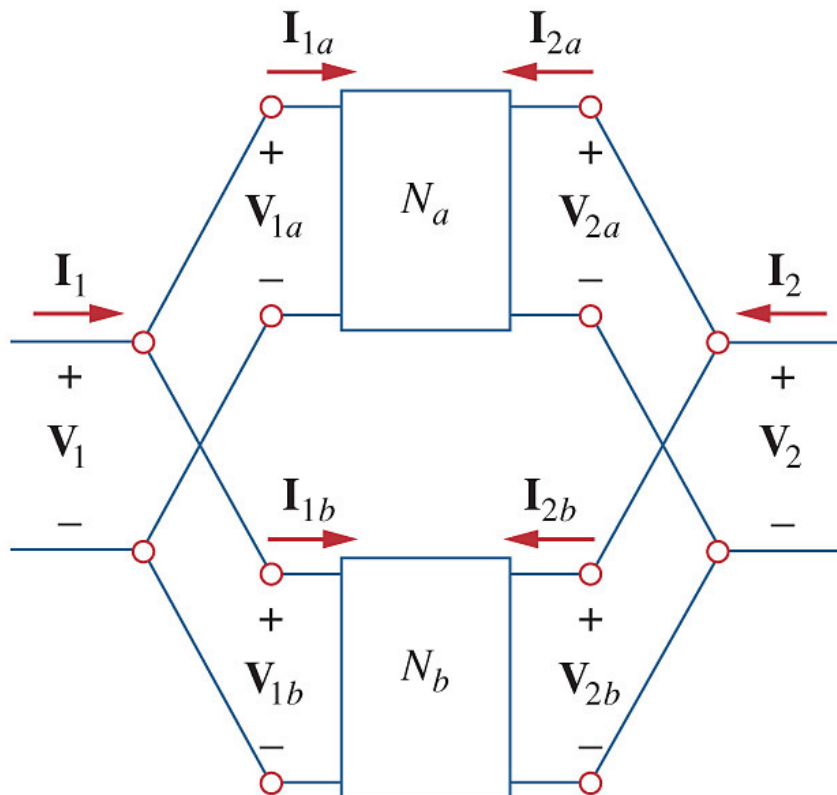19.7 Interconnection of Networks (2)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Parallel Connection of
two-port networks:

For Admittances; ADD
matrices.

$$Y = Y_a + Y_b$$

19.6 Relationships Between Networks

- Use this table to convert between two port parameters

	z		y		h		T	
z	z_{11}	z_{12}	$\frac{y_{22}}{\Delta_y}$	$-\frac{y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$
	z_{21}	z_{22}	$-\frac{y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{C}$	$\frac{D}{C}$
y	$\frac{z_{22}}{\Delta_z}$	$-\frac{z_{12}}{\Delta_z}$	y_{11}	y_{12}	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$	$\frac{D}{B}$	$-\frac{\Delta_T}{B}$
	$-\frac{z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	y_{21}	y_{22}	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$-\frac{1}{B}$	$\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	h_{11}	h_{12}	$\frac{B}{D}$	$\frac{\Delta_T}{D}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	h_{21}	h_{22}	$-\frac{1}{D}$	$\frac{C}{D}$
T	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$-\frac{h_{11}}{h_{21}}$	A	B
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta_y}{y_{21}}$	$-\frac{y_{11}}{y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$-\frac{1}{h_{21}}$	C	D

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21} \quad \Delta_z = z_{11}z_{22} - z_{12}z_{21} \quad \Delta_h = h_{11}h_{22} - h_{12}h_{21} \quad \Delta_T = AD - BC$$

Chapter 19 Review

Z-Parameters

- Parameters:
$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$


- Open circuit the **output** to find z_{11} and z_{21}

$$\begin{aligned} V_1 &= z_{11}I_1 + \cancel{z_{12}I_2}^0 \\ V_2 &= z_{21}I_1 + \cancel{z_{22}I_2}^0 \end{aligned}$$



$$\begin{aligned} V_1 &= z_{11}I_1 \\ V_2 &= z_{21}I_1 \end{aligned}$$

Set $I_1 = 1$ then solve for V_1 and V_2

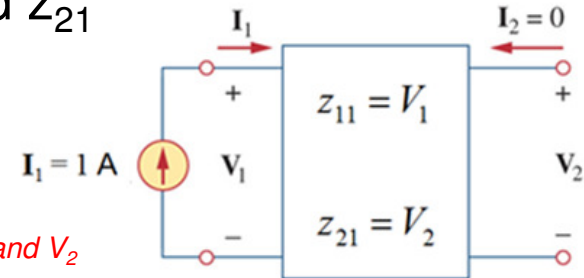


- Open circuit the **input** to find z_{21} and z_{22}

$$\begin{aligned} V_1 &= \cancel{z_{11}I_1}^0 + z_{12}I_2 \\ V_2 &= \cancel{z_{21}I_1}^0 + z_{22}I_2 \end{aligned}$$



$$\begin{aligned} V_1 &= z_{12}I_2 \\ V_2 &= z_{22}I_2 \end{aligned}$$

Set $I_2 = 1$ then solve for V_1 and V_2

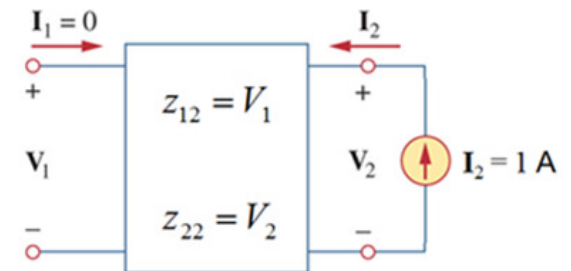


Chapter 19 Review

Z-Parameters (Given a circuit, find Z-parameters)

- Solving problems to find z-parameters:

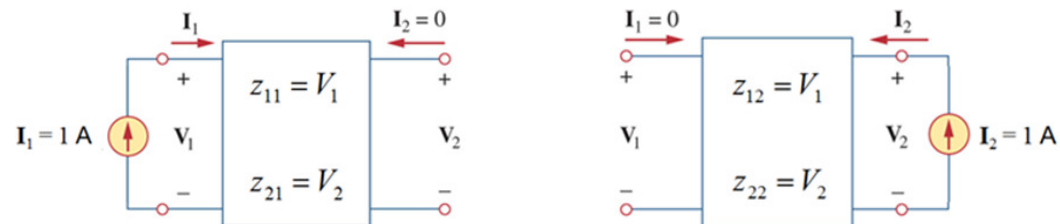1. Refer to definition, apply 1 amp source at input and output with opposite port left open (see previous slide)




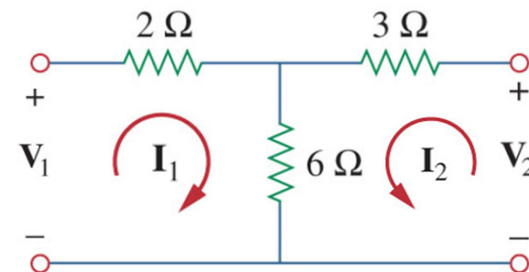2. Sometimes, KVL (mesh current equations) will cause z-parameters to fall right out! :

$$V_1 = 2I_1 + 6(I_1 + I_2) = 8I_1 + 6I_2$$
$$V_2 = 6(I_1 + I_2) + 3I_2 = 6I_1 + 9I_2$$



$$\mathbf{z} = \begin{bmatrix} 8 & 6 \\ 6 & 9 \end{bmatrix} \Omega$$





This mesh defined in counter clockwise direction for convenience

Chapter 19 Review

Z-Parameters (Given Z parameters, find circuit parameters)

- If given, z-parameters can use following techniques to find other circuit parameters (V_1 , V_2 , I_1 , I_2 , etc.):

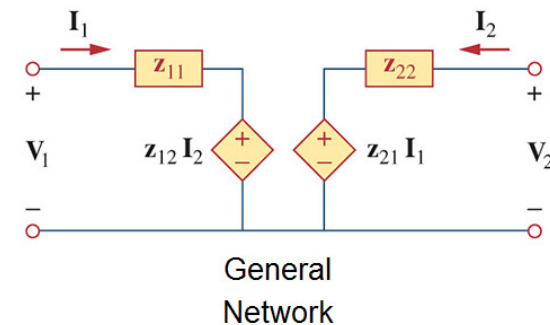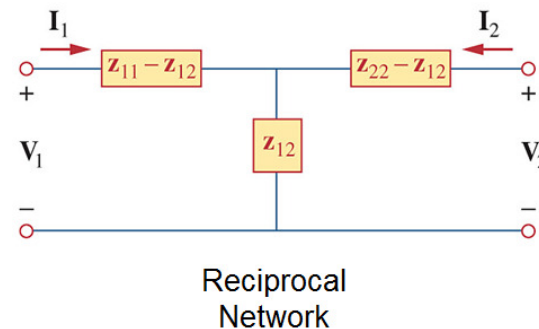1. Apply the model and solve the circuit:



2. Substitute the defining equations into your analysis:

Mesh Analysis


$$10 = 5I_1 + V_1 + 10(I_1 + I_2)$$

$$0 = V_2 + 10(I_1 + I_2) + 20I_2$$

Substitute for V_1 and V_2

$$10 = 5I_1 + (12I_1 + 8I_2) + 10(I_1 + I_2)$$
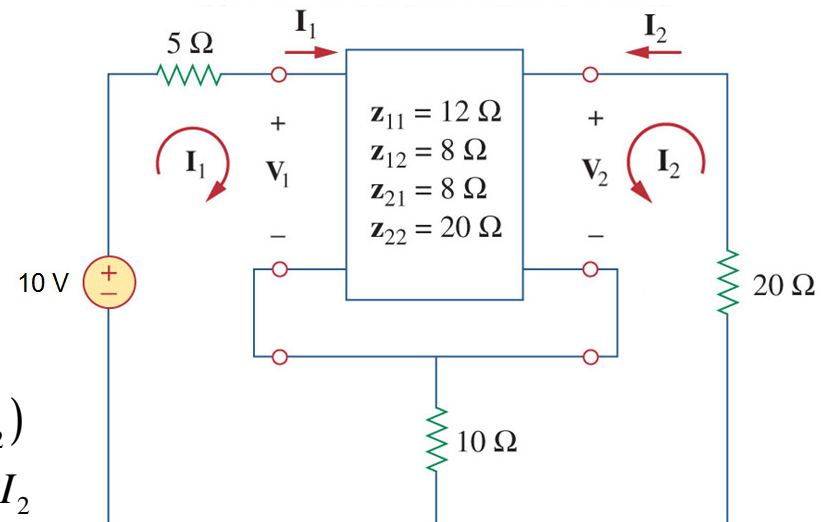
$$0 = (8I_1 + 20I_2) + 10(I_1 + I_2) + 20I_2$$



Chapter 19 Review

Y-Parameters

- Parameters:
$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$


- Short circuit the **output** to find y_{11} and y_{21}

$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} \cancel{V_2}^0 \\ I_2 &= y_{21} V_1 + y_{22} \cancel{V_2}^0 \end{aligned}$$



$$\begin{aligned} I_1 &= y_{11} V_1 \\ I_2 &= y_{21} V_1 \end{aligned}$$

Set $V_1 = 1$ then solve for I_1 and I_2

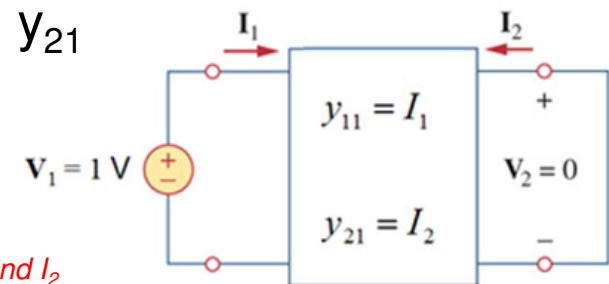


- Short circuit the **input** to find y_{21} and y_{22}

$$\begin{aligned} I_1 &= y_{11} \cancel{V_1}^0 + y_{12} V_2 \\ I_2 &= y_{21} \cancel{V_1}^0 + y_{22} V_2 \end{aligned}$$



$$\begin{aligned} I_1 &= y_{12} V_2 \\ I_2 &= y_{22} V_2 \end{aligned}$$

Set $V_2 = 1$ then solve for I_1 and I_2

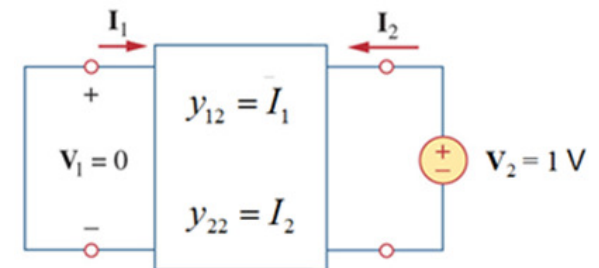


Chapter 19 Review


Y-Parameters (Solving Problems)

- To solve Y-parameter problems, can use these techniques

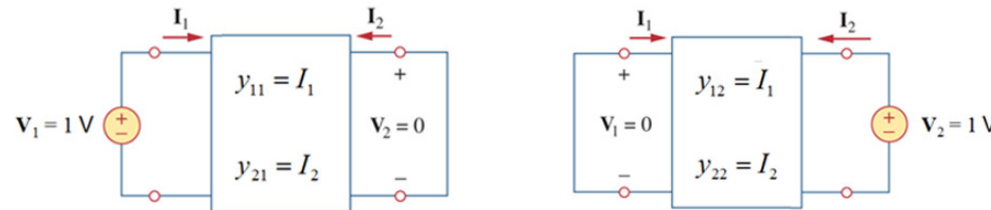1. Apply method from previous slide. Apply 1 Volt source at input and output while shorting opposite port



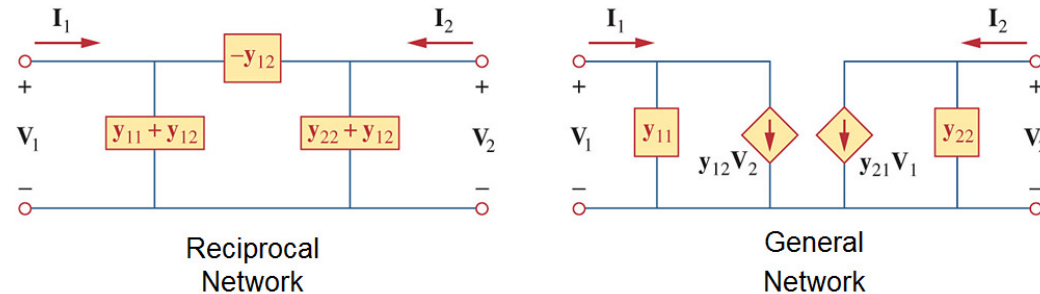2. If given Y parameters can apply the model and solve the circuit:



3. Make it easy on yourself! Use conversions from $Z \rightarrow Y$ or $Y \rightarrow Z$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \left(\frac{1}{\Delta_y} \right) \begin{bmatrix} y_{22} & -y_{12} \\ -y_{21} & y_{11} \end{bmatrix}$$

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21}$$

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \left(\frac{1}{\Delta_z} \right) \begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix}$$

$$\Delta_z = z_{11}z_{22} - z_{12}z_{21}$$

Chapter 19 Review

H-Parameters

- Parameters (hybrid of z and y):

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$


- Short circuit the **output** to find h_{11} and h_{21}

$$\begin{aligned} V_1 &= h_{11} I_1 + \cancel{h_{12} V_2}^0 \\ I_2 &= h_{21} I_1 + \cancel{h_{22} V_2}^0 \end{aligned}$$



$$\begin{aligned} V_1 &= h_{11} I_1 \\ I_2 &= h_{21} I_1 \end{aligned}$$

Set $I_1 = 1$ then solve for V_1 and I_2

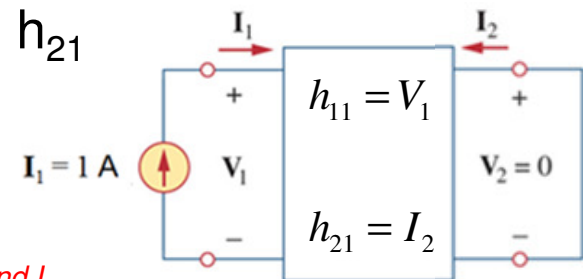


- Open circuit the **input** to find h_{21} and h_{22}

$$\begin{aligned} V_1 &= \cancel{h_{11} I_1}^0 + h_{12} V_2 \\ I_2 &= \cancel{h_{21} I_1}^0 + h_{22} V_2 \end{aligned}$$



$$\begin{aligned} V_1 &= h_{12} V_2 \\ I_2 &= h_{22} V_2 \end{aligned}$$

Set $V_2 = 1$ then solve for V_1 and I_2

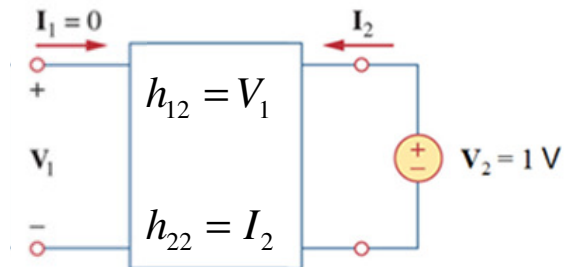


Chapter 19 Review

H-Parameters (Solving Problems)


- To solve H-parameter problems, can use these techniques

1. Apply methods from previous slide.

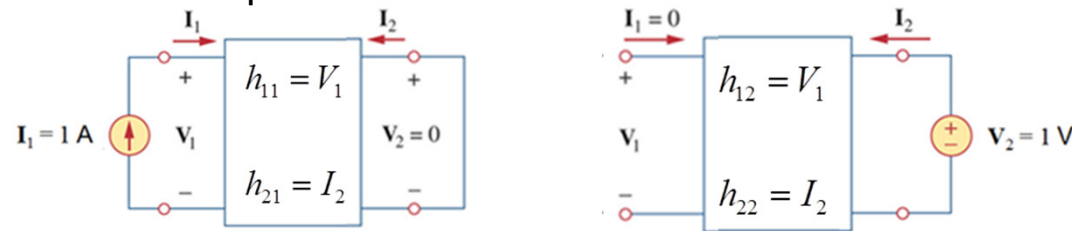

2. H parameters can be found by performing a set of tests on the device
 - a) Shorting the output and applying a current
 - b) Leaving the input open and applying a voltage across the output

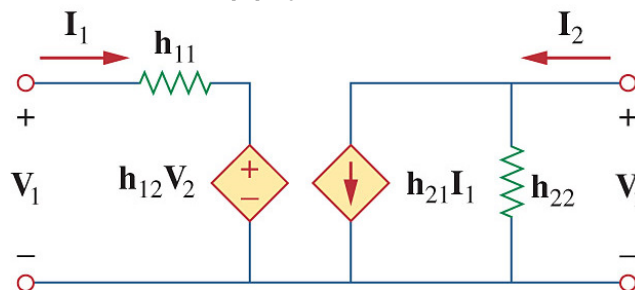3. If given H parameters can apply the model and solve the circuit:




4. If helpful, use conversion tables

Chapter 19 Review

H-Parameters (Transistor Model)

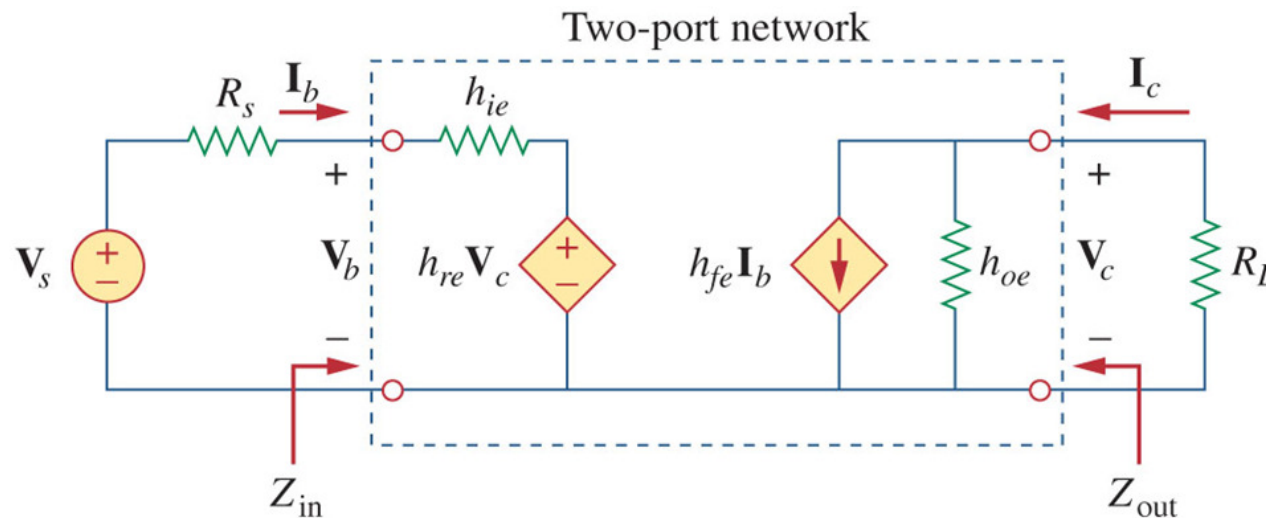
- H parameters are often used in modeling transistors
- Parameters vary depending on biasing conditions
- Spec sheets often use different subscripts:
 - $h_{11} \rightarrow h_{ie}$ = Base input impedance
 - $h_{12} \rightarrow h_{re}$ = Reverse voltage feedback ration
 - $h_{21} \rightarrow h_{fe}$ = Base-collector current gain
 - $h_{22} \rightarrow h_{oe}$ = Output admittance



Chapter 19 Review

H-Parameters (Transistor Model)

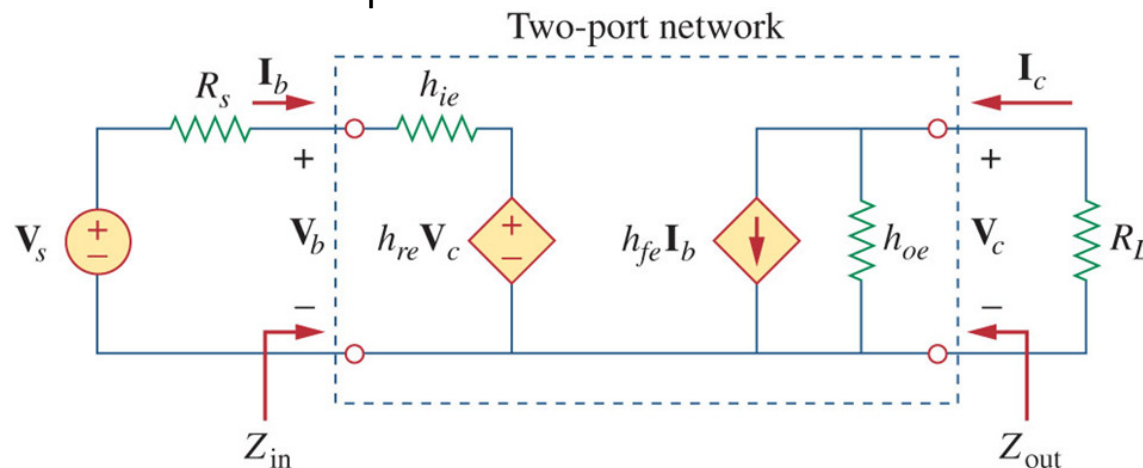- Equations for calculating input impedance, output impedance, voltage gain, and current gain for simple transistor circuit:
 - V_s and R_s can be the Thevenin equivalent source driving the input.
 - R_L can be the input impedance looking into the load of the circuit connected to the output



Input Impedance

$$Z_{in} = \frac{V_b}{I_b} = h_{ie} - \frac{h_{re} h_{fe} R_L}{1 + h_{oe} R_L}$$

Output Impedance

$$Z_{out} = \frac{V_c}{I_c} \bigg|_{V_s=0} = \frac{R_s + h_{ie}}{(R_s + h_{ie}) h_{oe} - h_{re} h_{fe}}$$

Current Gain

$$A_i = \frac{I_c}{I_b} = \frac{h_{fe}}{1 + h_{oe} R_L}$$

Voltage Gain

$$A_v = \frac{V_c}{V_b} = \frac{-h_{fe} R_L}{h_{ie} + (h_{ie} h_{oe} - h_{re} h_{fe}) R_L}$$

Chapter 19 Review

Transmission ("T") Parameters

- Parameters: $V_1 = AV_2 - BI_2$
 $I_1 = CV_2 - DI_2$

- Perform the analysis with the **output** Open Circuited ($I_2=0$)

$$\begin{array}{l} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{array} \xrightarrow{I_2=0} \begin{array}{l} V_1 = AV_2 \\ I_1 = CV_2 \end{array} \xrightarrow{} \begin{array}{l} A = \frac{V_1}{V_2} \\ C = \frac{I_1}{V_2} \end{array}$$


- Perform the analysis with the **output** Short Circuited ($V_2=0$)

$$\begin{array}{l} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{array} \xrightarrow{V_2=0} \begin{array}{l} V_1 = -BI_2 \\ I_1 = -DI_2 \end{array} \xrightarrow{} \begin{array}{l} B = -\frac{V_1}{I_2} \\ D = -\frac{I_1}{I_2} \end{array}$$

Chapter 19 Review

Transmission ("T") Parameters (Cascading)

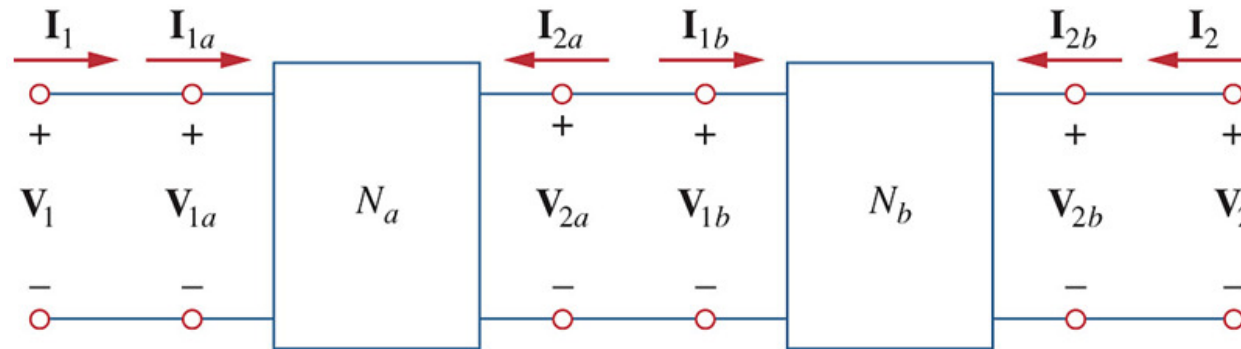- Primary benefit of "T"-Parameters is their ability to be cascaded.



$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$-I_{2a} = I_{1b}$$




$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Chapter 19 Review

T - Parameters (Building Block models)

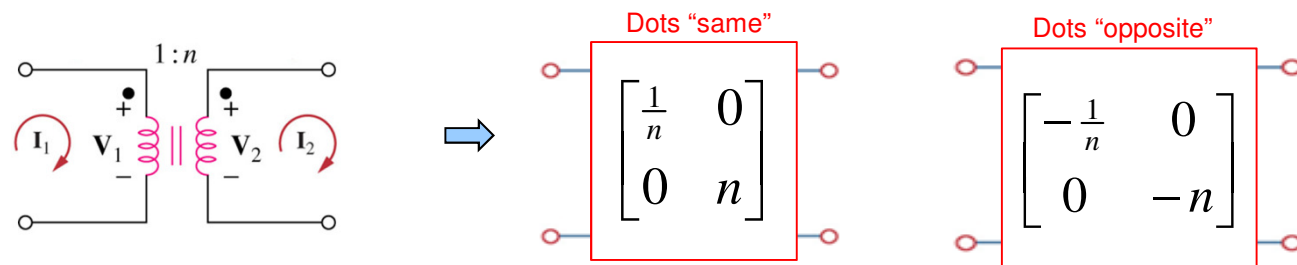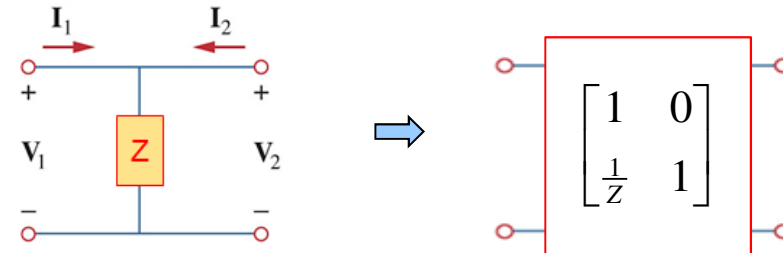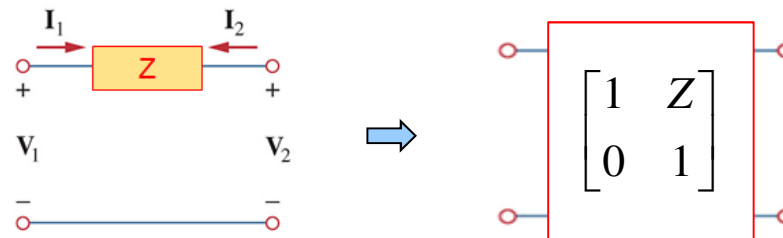
- We can create “building block” models of components by finding their T-parameters and use the cascading property to find the T-parameters for the complete circuit/system.



Chapter 19 Review

T - Parameters (Building Block models)

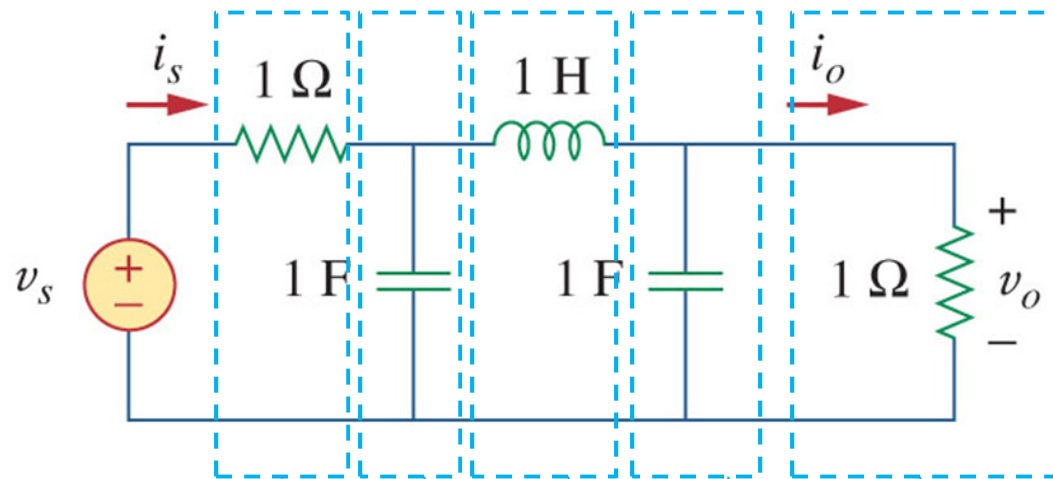- With “Building Block” approach, circuits can be broke up into discrete components and analyzed using T-parameters



$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$\rightarrow A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

Chapter 19 Review


T - Parameters (Useful Properties)

- The T parameters give us useful properties in the analysis of circuits:
 - Open Circuit Voltage Transfer Function:

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

$$H(s) = \frac{1}{A}$$

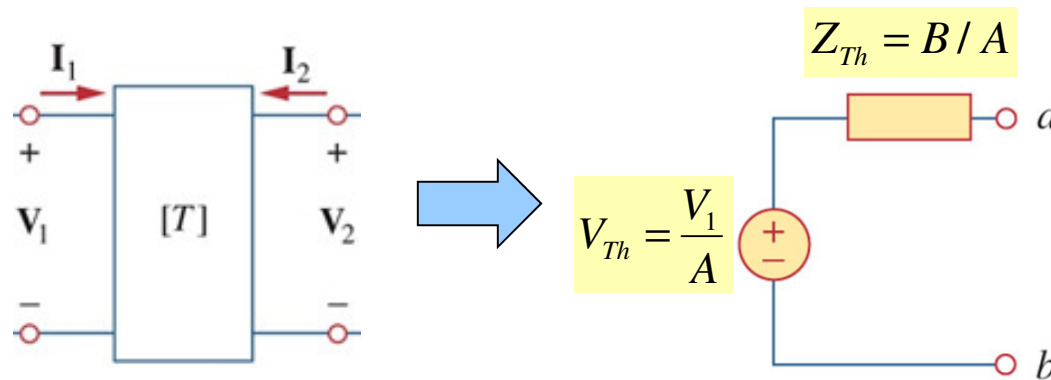- Thevenin Equivalent Circuit (Replace circuit as a source)



Chapter 19 Review

Conversion between Parameters

- Conversion tables exist to convert between parameters

	z		y		h		T	
z	z ₁₁	z ₁₂	$\frac{y_{22}}{\Delta_y}$	$-\frac{y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$
	z ₂₁	z ₂₂	$-\frac{y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{C}$	$\frac{D}{C}$
y	$\frac{z_{22}}{\Delta_z}$	$-\frac{z_{12}}{\Delta_z}$	y ₁₁	y ₁₂	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$	$\frac{D}{B}$	$-\frac{\Delta_T}{B}$
	$-\frac{z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	y ₂₁	y ₂₂	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$-\frac{1}{B}$	$\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	h ₁₁	h ₁₂	$\frac{B}{D}$	$\frac{\Delta_T}{D}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	h ₂₁	h ₂₂	$-\frac{1}{D}$	$\frac{C}{D}$
T	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$-\frac{h_{11}}{h_{21}}$	A	B
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta_y}{y_{21}}$	$-\frac{y_{11}}{y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$-\frac{1}{h_{21}}$	C	D

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21} \quad \Delta_z = z_{11}z_{22} - z_{12}z_{21} \quad \Delta_h = h_{11}h_{22} - h_{12}h_{21} \quad \Delta_T = AD - BC$$


Chapter 19: Two-Port Networks

- 19.1 Introduction
- 19.2 Impedance Parameters (z)
- 19.3 Admittance Parameters (y)
- 19.4 Hybrid Parameters (h)
- 19.5 Transmission Parameters (T)
- 19.6 Relationships between Parameters
- 19.7 Interconnection of Networks
- 19.9 Applications

19.1 Introduction (1)

- A port is an access to the network and consists of a pair of terminals; the current entering one terminal leaves through the other terminal so that the net current entering the port equals zero.
- One port networks include two-terminal devices such as resistors, capacitors, and inductors.
- A two-port network has two separate ports for input and output.
- Two port networks include op amps, transistors and transformers.

19.1 Introduction (2)

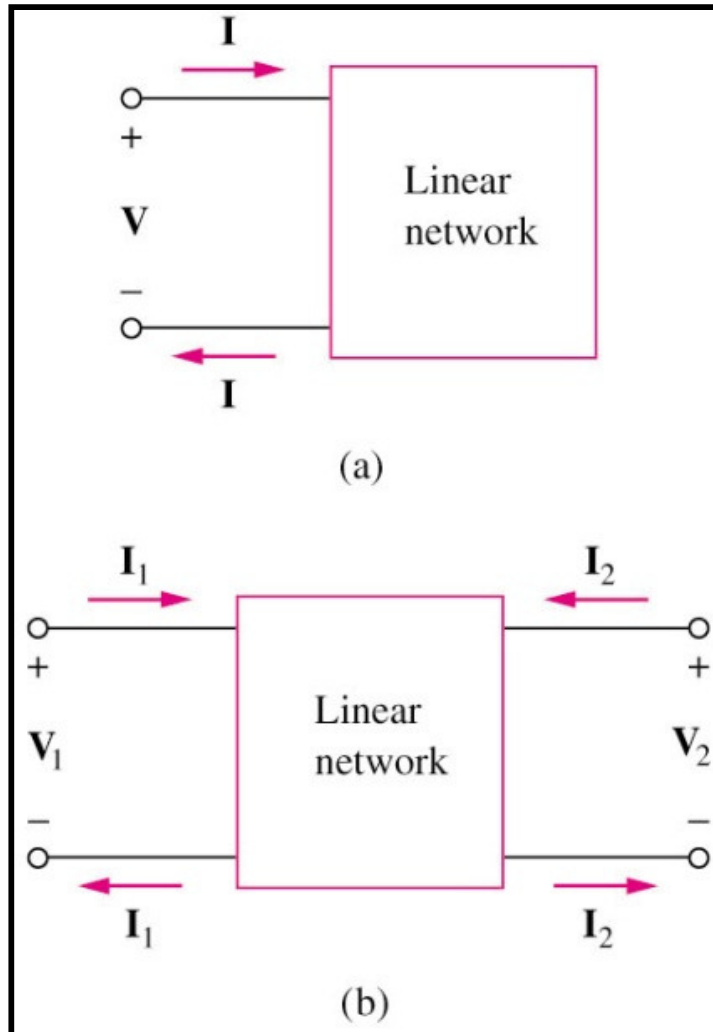

**One port or two
terminal circuit**

**Two port or four
terminal circuit**


- It is an electrical network with two separate ports for input and output.
- No independent sources.

19.1 Introduction (3)

- Characterizing a two-port network requires that we relate the terminal quantities \mathbf{V}_1 , \mathbf{V}_2 , \mathbf{I}_1 , \mathbf{I}_2 out of which two are independent. Six sets of voltage and current parameters will be derived.
- Two port networks are useful in communications, control systems, power systems, and electronics.
- They are used in electronics to model transistors and to facilitate cascaded design.
- Additionally, if we know the parameters of a two-port network it can be treated as a “black box” when embedded within a larger network.

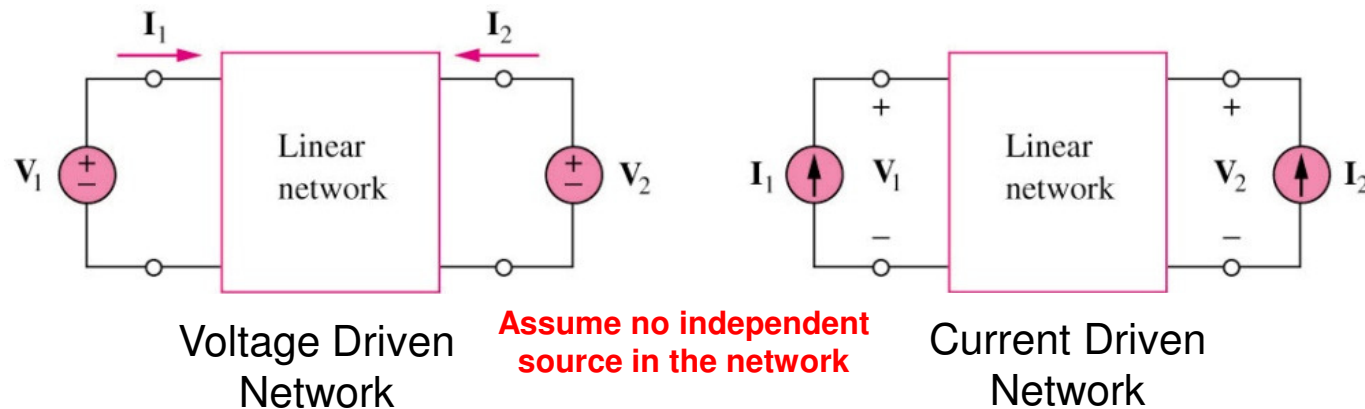19.2 Impedance Parameters (1)

- Often called “**Z-parameters**” since their units are in **ohms** and they represent an impedance relationship between V_1 , V_2 , I_1 , I_2 for the two port network shown below:



$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$




$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

- Z-parameters are commonly used in filter synthesis, impedance matching networks design, and power distribution networks analysis.

19.2 Impedance Parameters (2)

The values of parameters can be evaluated by setting $I_1=0$ or $I_2=0$ (open circuit)

Setting $I_2 = 0$

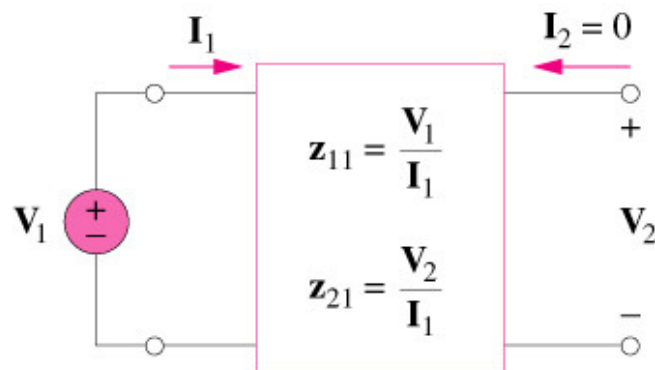


(a)

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

z_{11} = Open-circuit input impedance
 z_{21} = Open-circuit transfer impedance
from port 2 to port 1

Setting $I_1 = 0$

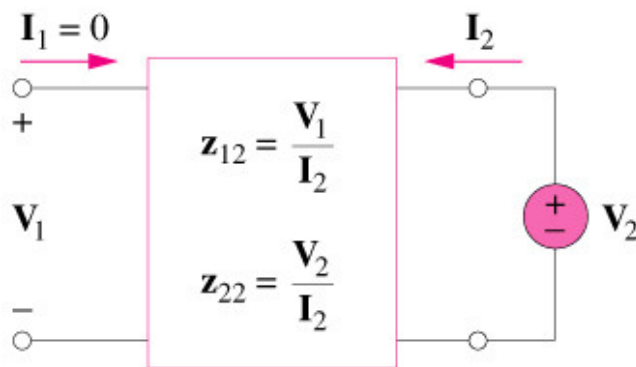

(b)


$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

z_{12} = Open-circuit transfer impedance from port
1 to port 2
 z_{22} = Open-circuit output impedance

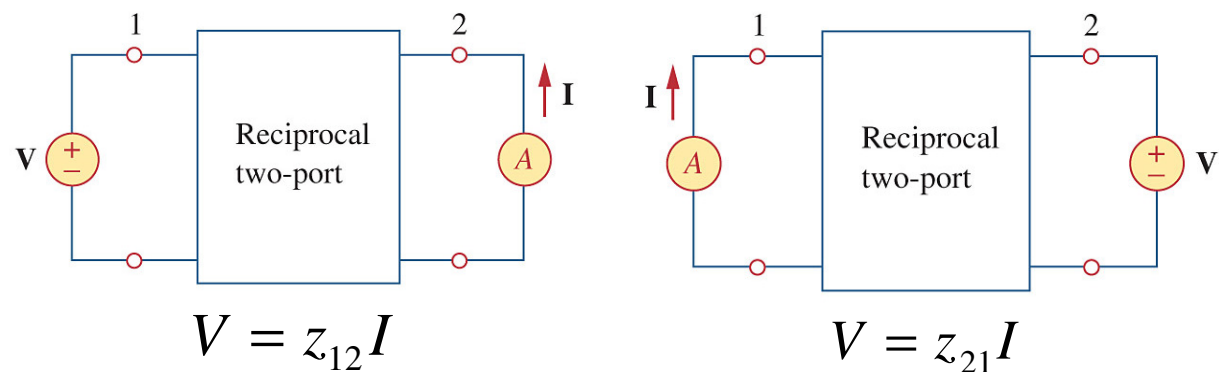19.2 Impedance Parameters (3)


Properties of Z-parameters

- Symmetrical networks $z_{11} = z_{22}$
 - Implies a mirror like symmetry
- Reciprocal networks $z_{12} = z_{21}$
 - Any network made up entirely of resistors, capacitors, and inductors must be reciprocal.
 - Linear networks with no dependant sources are reciprocal.
 - Interchanging an ideal voltage source at one port with an ideal ammeter at the other port gives the same ammeter reading.



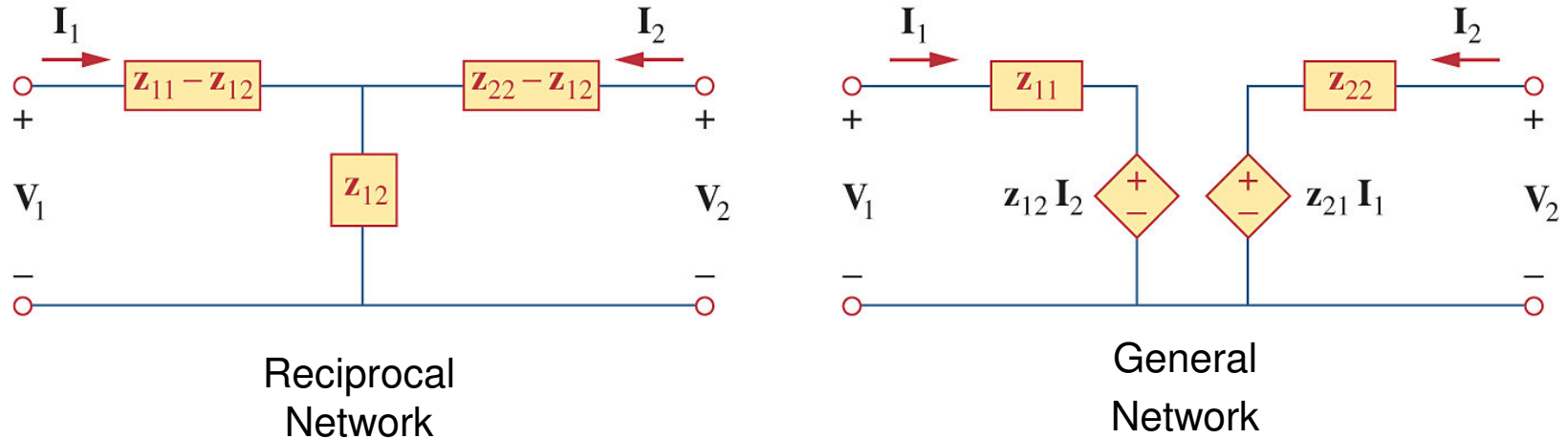19.2 Impedance Parameters (4)


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



- A reciprocal network can be replaced by the T-network shown above
- If not reciprocal, the General network is the T-equivalent.

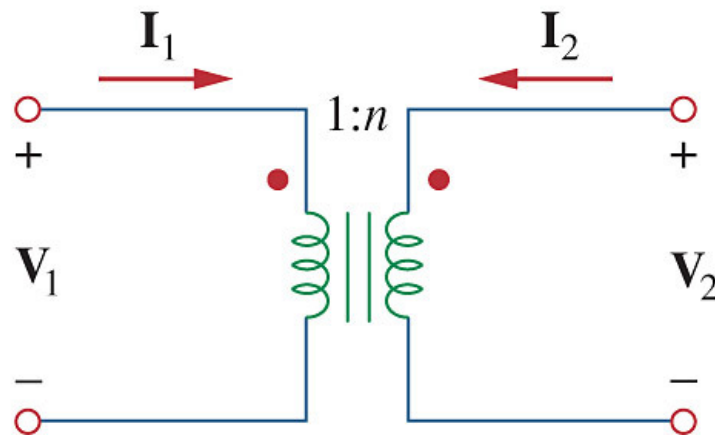19.2 Impedance Parameters (5)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



- Note: some circuits do not have z-parameter equivalents. (they may have other 2-port equivalents, as we shall see)

- Consider an ideal transformer:

$$V_1 = V_2/n \text{ and } I_1 = -nI_2.$$


- This cannot be expressed by:

$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

19.2 Impedance Parameters (6)

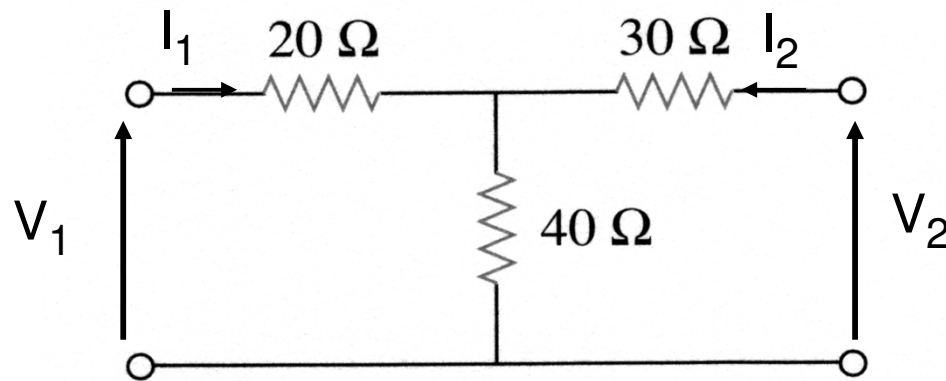Example 19.1

Determine the z-parameters of the following circuit.



$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$



Answer:
$$z = \begin{bmatrix} 60 & 40 \\ 40 & 70 \end{bmatrix} \Omega$$


$$Z = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \Omega$$

19.2 Impedance Parameters (7)

Practice Problem 19.2

Determine I_1 and I_2 in the following circuit.

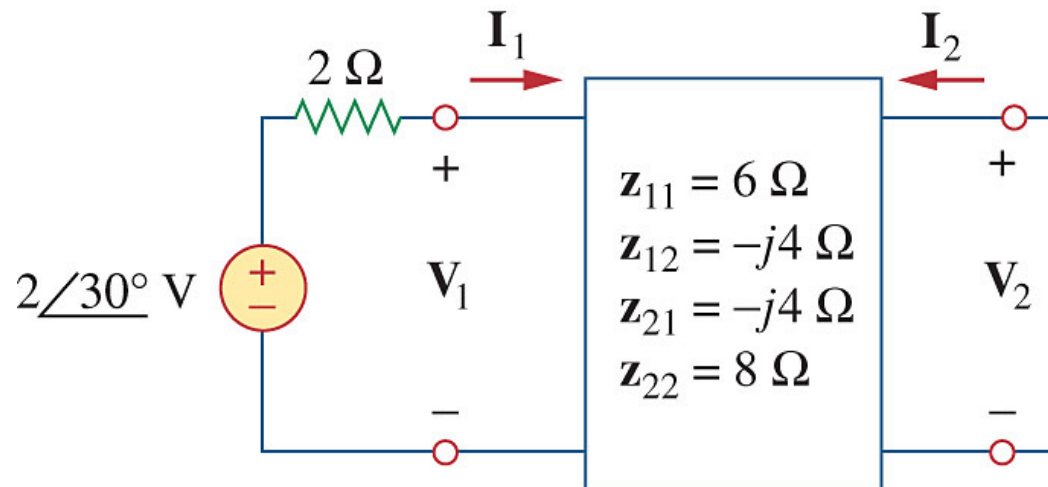Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.





$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

Answer:

$$\begin{aligned} I_1 &= 200\angle 30^\circ \text{ mA} \\ I_2 &= 100\angle 120^\circ \text{ mA} \end{aligned}$$

19.3 Admittance Parameters (1)

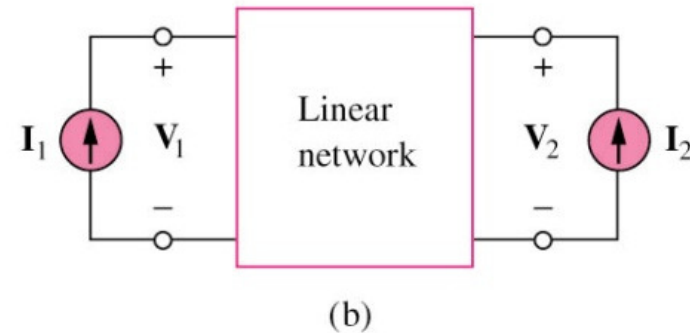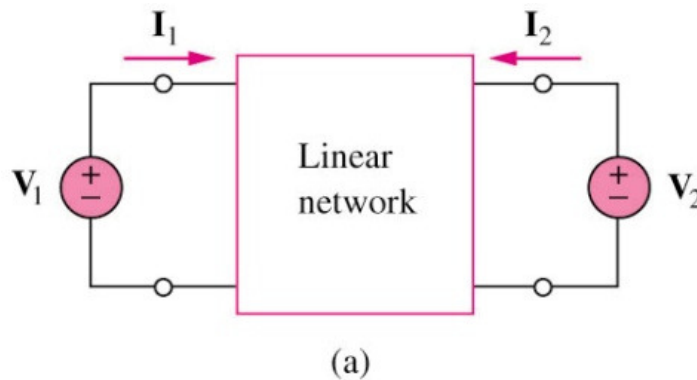

Assume no independent source in the network


$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$




$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

where the **y** terms are called the admittance parameters, or simply **y** parameters, and they have units of Siemens.

19.3 Admittance Parameters (2)

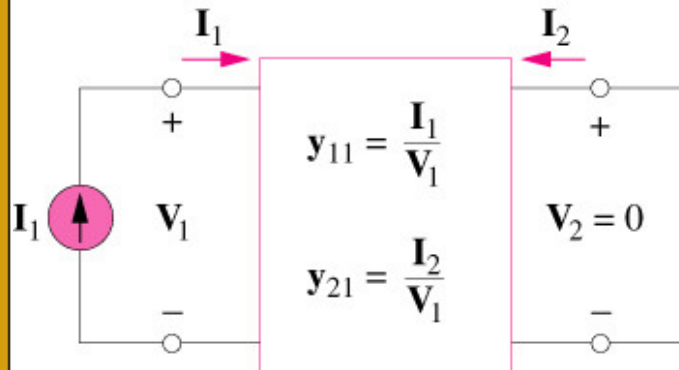

(a)

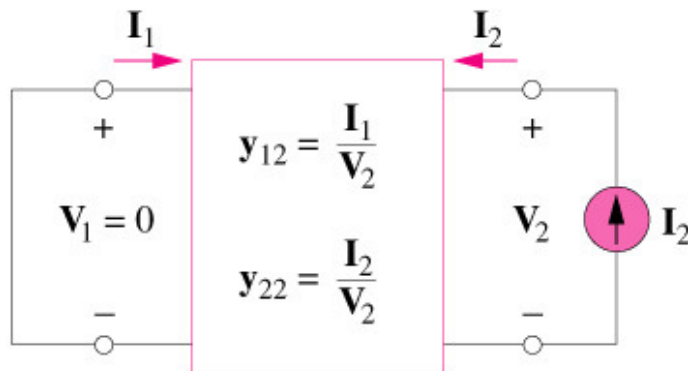

(b)

Setting $V_2 = 0$ (Shorting the output)

$$y_{11} = \frac{I_1}{V_1} \bigg|_{V_2=0} \quad \text{and} \quad y_{21} = \frac{I_2}{V_1} \bigg|_{V_2=0}$$


y_{11} = Short-circuit input admittance
 y_{21} = Short-circuit transfer
admittance from port 1 to port 2

Setting $V_1 = 0$ (Shorting the input)

$$y_{12} = \frac{I_1}{V_2} \bigg|_{V_1=0} \quad \text{and} \quad y_{22} = \frac{I_2}{V_2} \bigg|_{V_1=0}$$

y_{12} = Short-circuit transfer
admittance from port 2 to port 1
 y_{22} = Short-circuit output
admittance

19.3 Admittance Parameters (3)

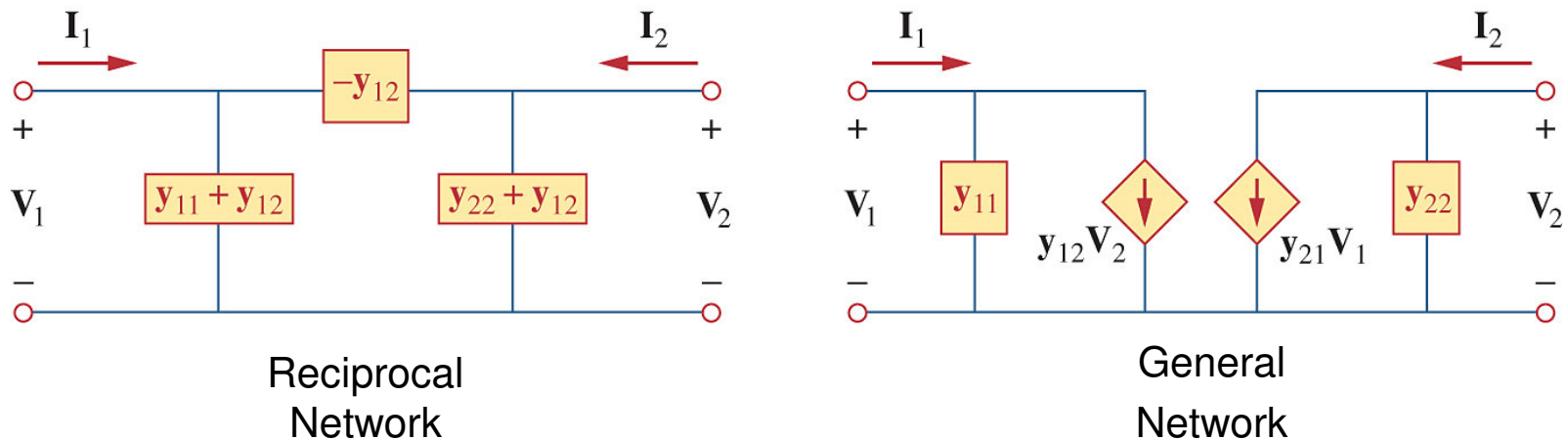


- A reciprocal network ($y_{12} = y_{21}$) can be replaced by the Pi-network in figure (a).
- If not reciprocal, the network in figure (b) is the Pi-equivalent.

19.3 Admittance Parameters (4)

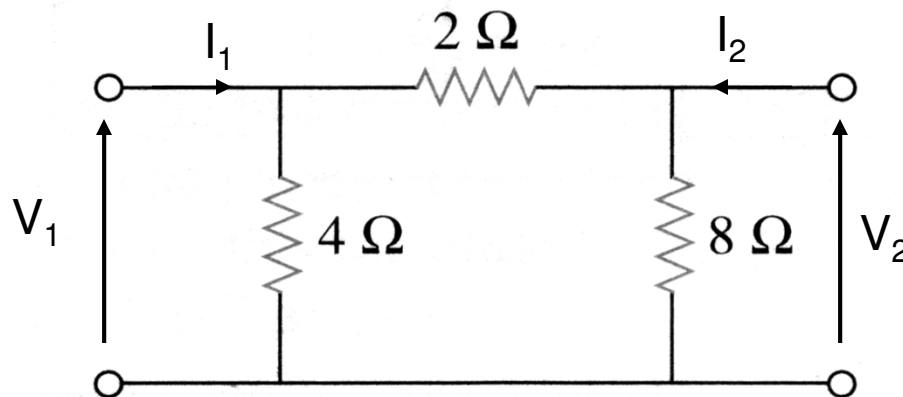Example 19.3

Determine the y-parameters of the following circuit.



Answer: $y = \begin{bmatrix} 0.75 & -0.5 \\ -0.5 & 0.625 \end{bmatrix} \text{S}$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$




$$y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \text{S}$$

19.3 Admittance Parameters (5)

Practice Problem 19.3

Practice Problem 19.3

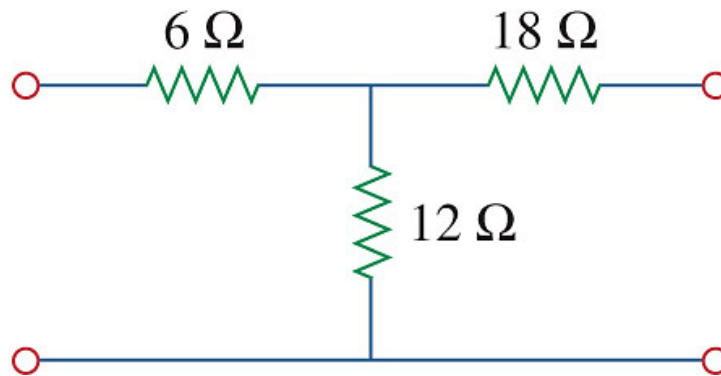Determine the y-parameters of the following circuit.



Answer: $y = \begin{bmatrix} 75.77 & -30.3 \\ -30.3 & 45.47 \end{bmatrix} \text{ mS}$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$



$$y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \text{ S}$$

19.3 Admittance Parameters (6)

Practice Problem 19.3

Practice Problem 19.3 (Solution)

- Short the output
- Put a 1 volt source at input
- Find I_1 and I_2

$$y_{11} = \frac{I_1}{(1)} \bigg|_{V_2=0} \quad \text{and} \quad y_{21} = \frac{I_2}{(1)} \bigg|_{V_2=0}$$

Find Input Impedance

$$Z_{in} = 6 + 12 \parallel 18 = 13.2$$

$$I_1 = \frac{V_1}{Z_{in}} = \frac{1}{13.2} = 0.07576$$


$$y_{11} = 0.07576$$

Similarly at Output

$$Z_{out} = 18 + 6 \parallel 12 = 22$$

$$I_2 = \frac{V_2}{Z_{in}} = \frac{1}{22} = 0.04545$$

$$y_{22} = 0.04545$$

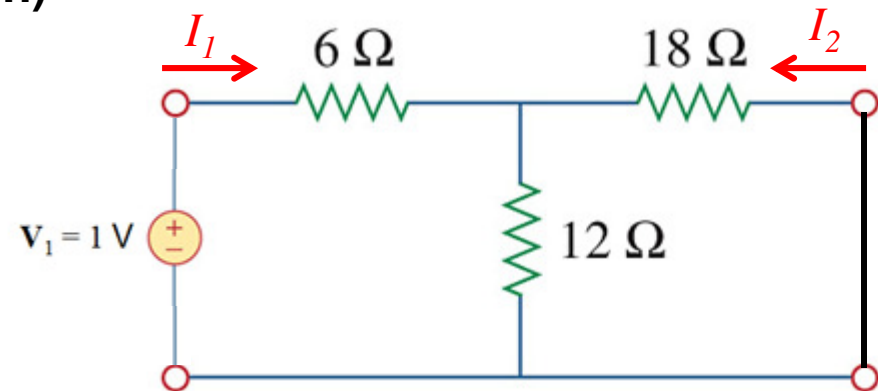

Find I_2 from current divider equation

$$I_2 = \frac{-12}{12 + 18} I_1$$

$$I_2 = (-0.4) 0.07576 = -0.0303$$

$$y_{21} = -0.0303$$

$$y_{12} = y_{21} = -0.0303$$


Reciprocal Network

19.3 Admittance Parameters (7)

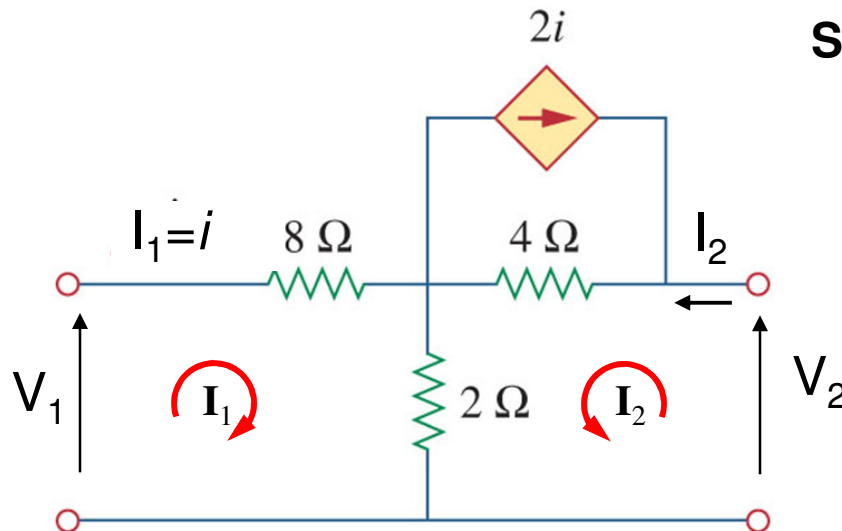Example 19.4

Determine the y-parameters of the following circuit.

$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$



Answer: $y = \begin{bmatrix} 0.15 & -0.05 \\ -0.25 & 0.25 \end{bmatrix} \text{S}$

Note: Sometimes two port parameters will fall out directly from mesh equations.

Solution: Apply KVL

Mesh I_1 : $V_1 = 8I_1 + 2(I_1 + I_2)$

$$V_1 = 10I_1 + 2I_2$$

Mesh I_2 : $V_2 = 4(2i + I_2) + 2(I_1 + I_2)$

$$V_2 = 8I_1 + 4I_2 + 2I_1 + 2I_2$$

$$V_2 = 10I_1 + 6I_2$$

Subtract #1 from #2:

$$V_2 - V_1 = 0 + 4I_2$$

$$I_2 = -0.25V_1 + 0.25V_2$$

Substitute back into #1

$$V_1 = 10I_1 - 0.5V_1 + 0.5V_2$$

$$10I_1 = 1.5V_1 - 0.5V_2$$


$$I_1 = 0.15V_1 - 0.05V_2$$

19.3 Admittance Parameters (8)

Practice problem 19.4

Practice Problem 19.4

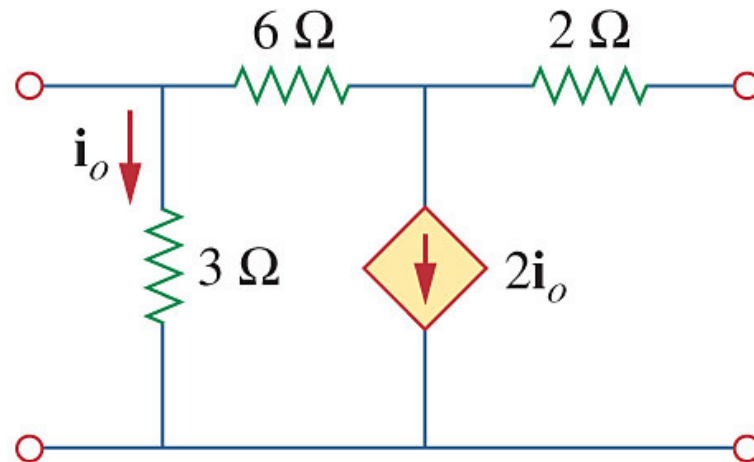Determine the y-parameters of the following circuit.



Answer: $y = \begin{bmatrix} 0.625 & -0.125 \\ 0.375 & 0.125 \end{bmatrix} S$

19.3 Admittance Parameters (9)

Practice problem 19.4

Practice Problem 19.4 (Solution)

- Short the output
- Put a 1 volt source at input
- Find I_1 and I_2

First find i_o :

$$i_o = \frac{1}{3}$$

Dependent current source is then $2/3$, find I_1 by repetitive source transformations of the dependant current source


$$I_1 = 0.625 \Rightarrow y_{11} = 0.625$$

Next find current across $6\ \Omega$ resistor $I_{6\Omega}$:

$$I_{6\Omega} = 0.625 - \frac{1}{3}$$

$$I_2 + I_{6\Omega} = 2i_o$$
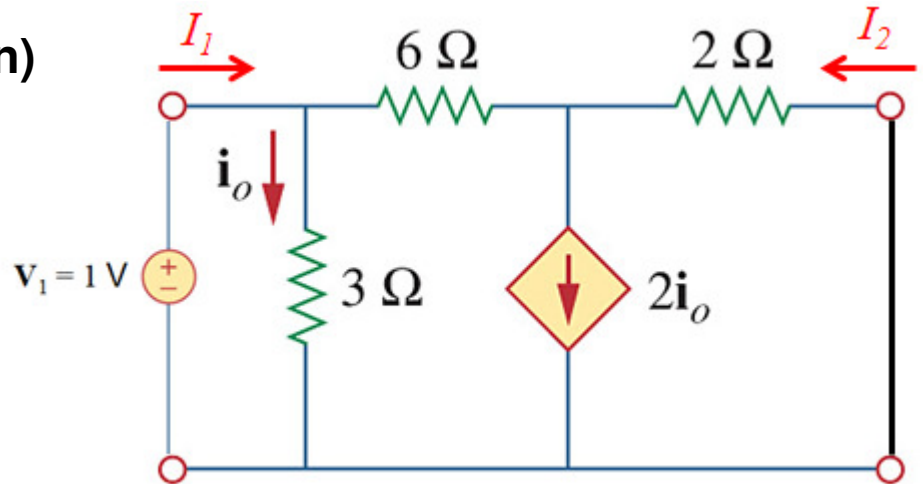
$$I_2 = 2i_o - I_{6\Omega} = \frac{2}{3} - \left(0.625 - \frac{1}{3}\right) = 0.375 \Rightarrow y_{12} = 0.375$$



Z and Y Parameters Comparison

Z-Parameters


$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

- **Open** one port ($I_1=0$ or $I_2=0$)
- Connect a source to the other port
- Solve to find z-parameters

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

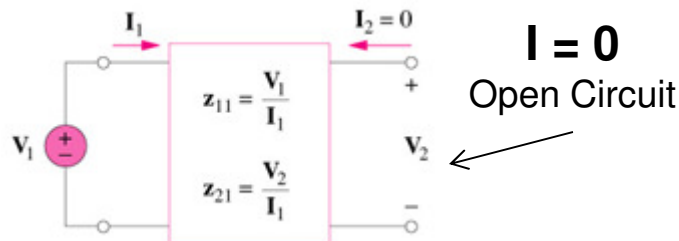

Y-Parameters


$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

- **Short** one port ($V_1=0$ or $V_2=0$)
- Connect a source to the other port
- Solve to find y-parameters

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

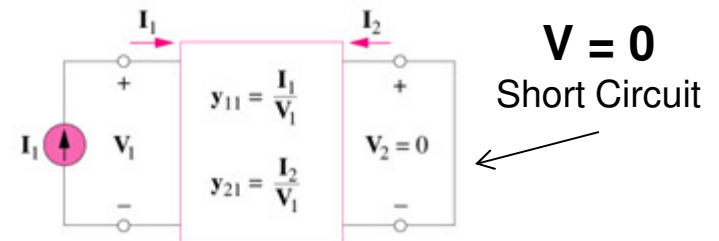


Z and Y parameters

Alternative method (1 Amp / 1 Volt sources)

Z-Parameters

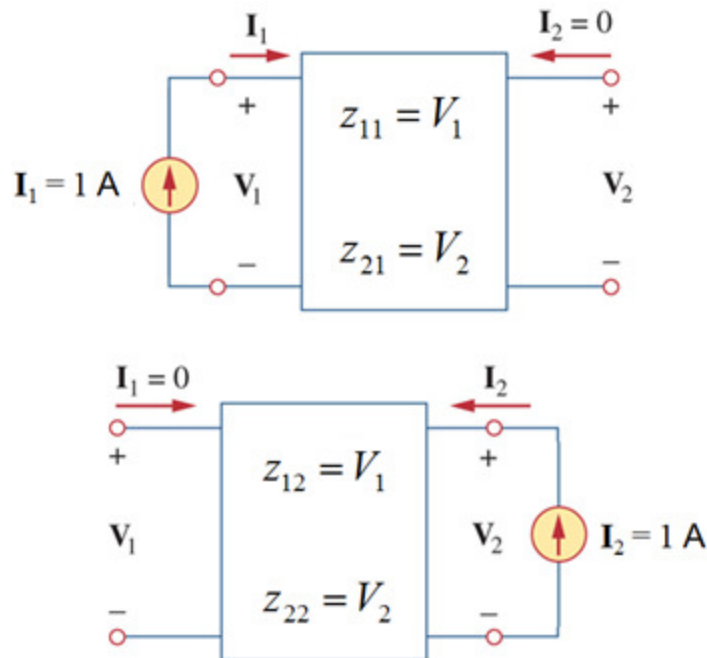
- Open circuit one port
- Put a 1 Amp current source at other port
- Resulting voltages are the z-parameters



$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

Y-Parameters

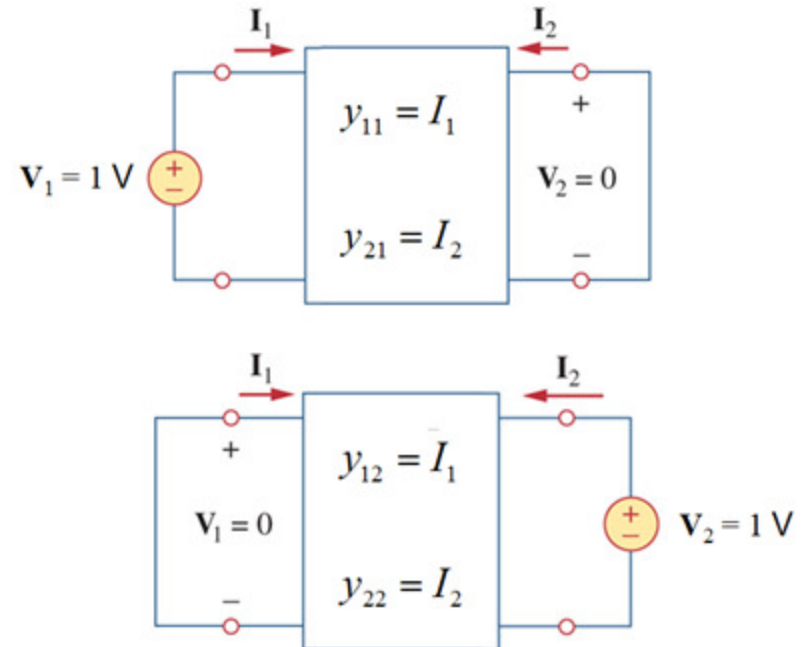
- Short circuit one port
- Put a 1 Volt voltage source at other port
- Resulting current are the y-parameters



$$\begin{aligned} I_1 &= y_{11}V_1 + y_{12}V_2 \\ I_2 &= y_{21}V_1 + y_{22}V_2 \end{aligned}$$

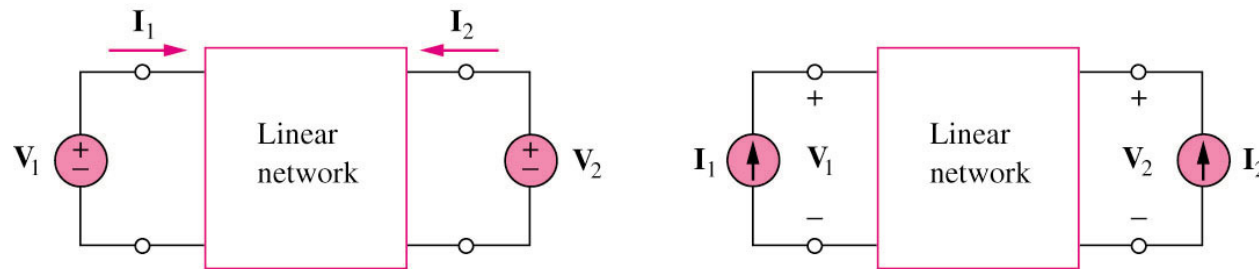19.4 Hybrid Parameters (1)

- The z and y parameters of a two-port network do not always exist. Therefore, there is a need to develop another set of parameters based on making V_1 and I_2 the dependent variables.



Assume no independent source in the network

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$




$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [h] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

where the **h** terms are called the hybrid parameters, or simply h parameters.

- Hybrid parameters are very useful for describing electronic devices such as transistors because it is much easier to measure the h parameters of these devices than to measure their z or y parameters.
- The ideal transformer can also be described by h parameters.

19.4 Hybrid Parameters (2)

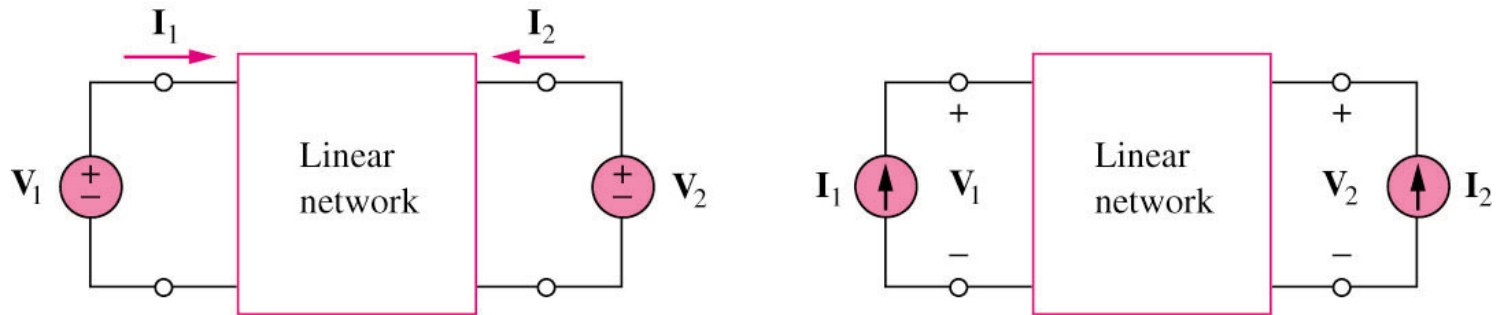

Assume no independent source in the network

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

h_{11} = short-circuit
input impedance (Ω)

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

h_{21} = short-circuit
forward current gain

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$


h_{12} = open-circuit
reverse voltage-gain

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

h_{22} = open-circuit
output admittance (S)


- Note that the h parameters represent an impedance, voltage gain, current gain, and admittance, thereby the term hybrid parameters.
- For reciprocal network, $h_{12} = -h_{21}$

19.4 Hybrid Parameters (3)

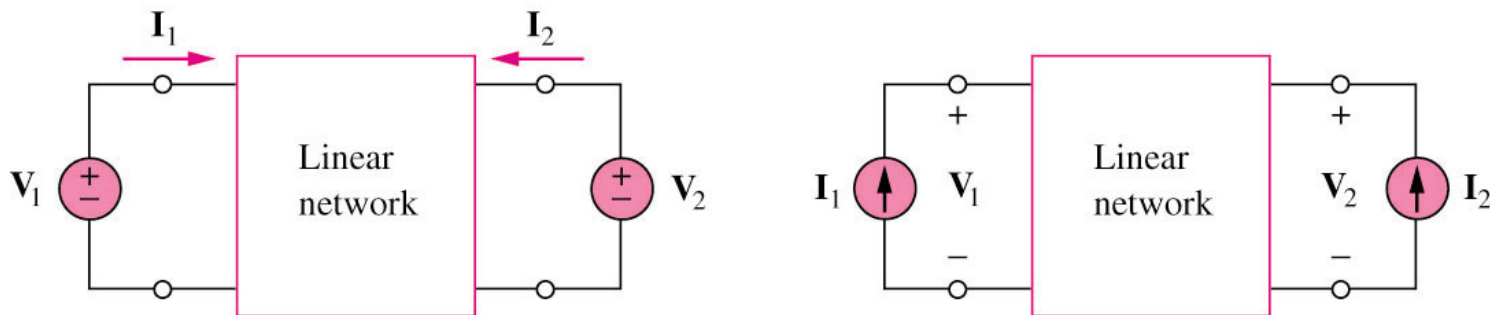

Assume no independent source in the network


Hybrid model of a two-port network:

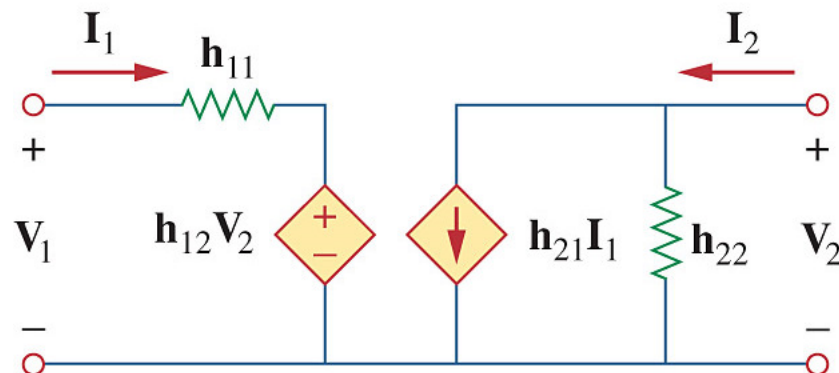

19.4 Hybrid Parameters (4)

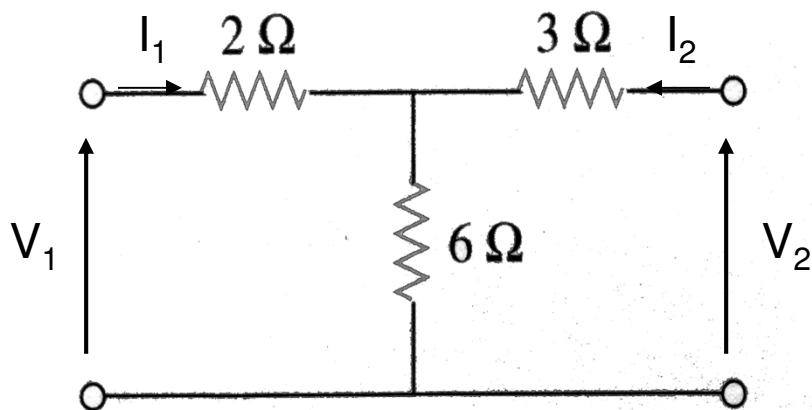Example 19.5:

Determine the h-parameters of the following circuit.



Answer:

$$h = \begin{bmatrix} 4\Omega & \frac{2}{3} \\ -\frac{2}{3} & \frac{1}{9}S \end{bmatrix}$$

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{and} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{and} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$




$$h = \begin{bmatrix} h_{11}\Omega & h_{12} \\ h_{21} & h_{22}S \end{bmatrix}$$

19.4 Hybrid Parameters (5)

Practice Problem 19.5:

Determine the h-parameters of the following circuit.

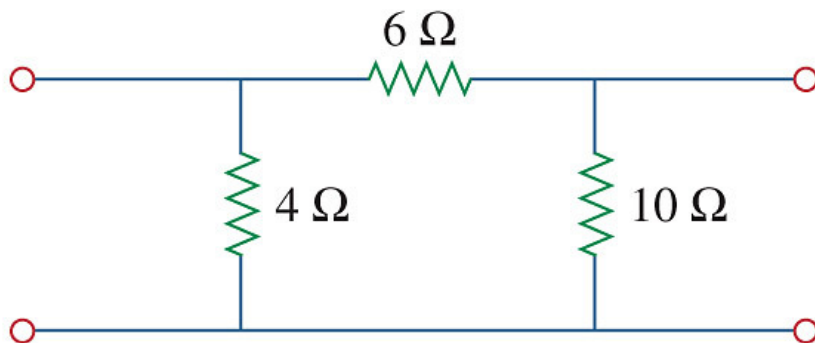Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{and} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{and} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$



Answer:

$$h = \begin{bmatrix} 2.4\Omega & 0.4 \\ -0.4 & 0.2S \end{bmatrix}$$

$$h = \begin{bmatrix} h_{11}\Omega & h_{12} \\ h_{21} & h_{22}S \end{bmatrix}$$

19.9.1 Transistor Circuits (1)

Hybrid Parameters

- H-parameters are often used to model transistor circuits
- The h-parameters vary depending on biasing conditions
- Parameters are given different subscripts:
 - $h_{11} \rightarrow h_{ie}$ = Base input impedance
 - $h_{12} \rightarrow h_{re}$ = Reverse voltage feedback ratio
 - $h_{21} \rightarrow h_{fe}$ = Base-collector current gain
 - $h_{22} \rightarrow h_{oe}$ = Output admittance

Example 2N3904

2N3903 2N3904

h PARAMETERS
($V_{CE} = 10$ Vdc, $f = 1.0$ kHz, $T_A = 25^\circ\text{C}$)

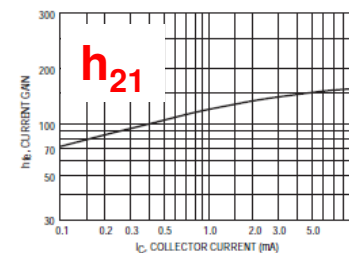
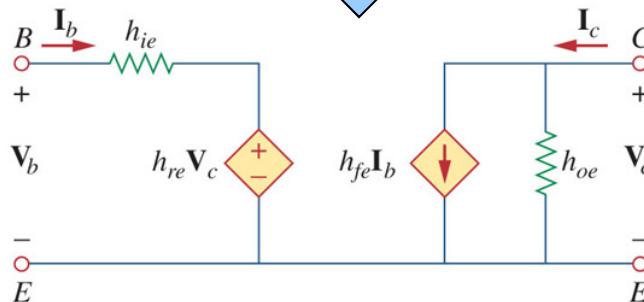
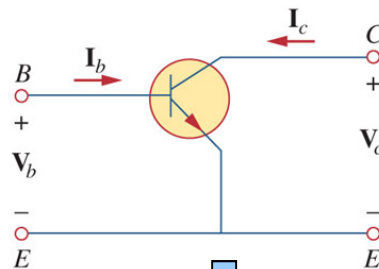


Figure 11. Current Gain

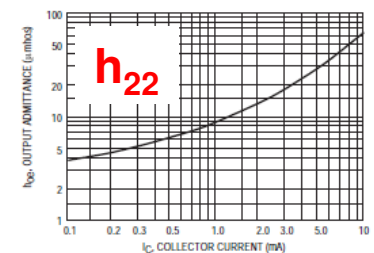


Figure 12. Output Admittance

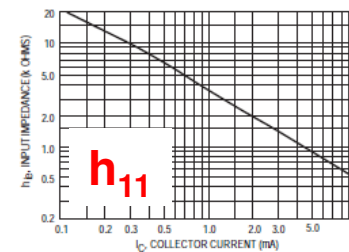


Figure 13. Input Impedance


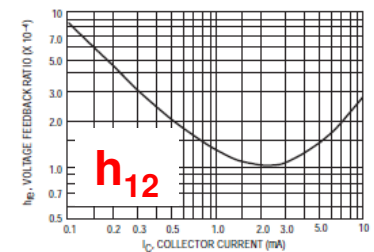


Figure 14. Voltage Feedback Ratio

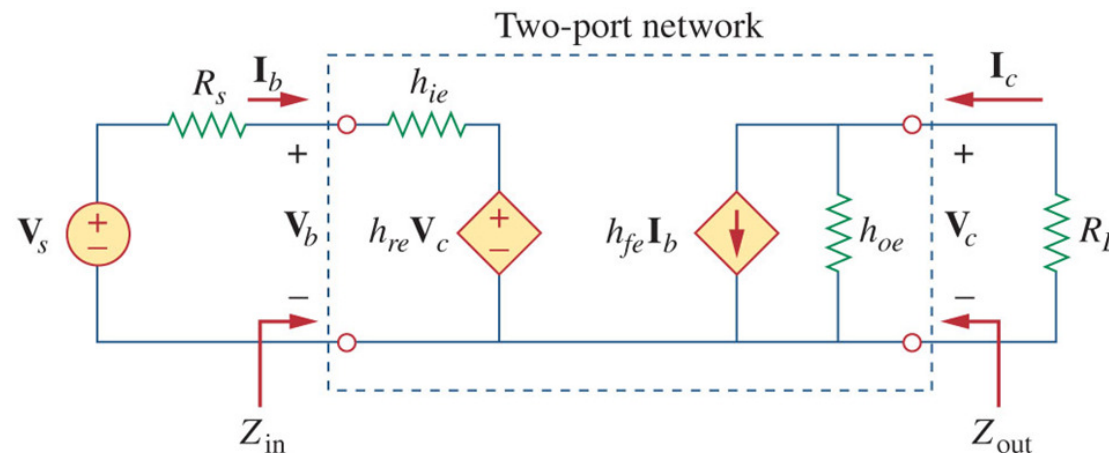19.9.1 Transistor Circuits (2)

Hybrid Parameters

- H parameters are often found in manufacturers spec sheets
- Provide ability to calculate the exact voltage gain, input impedance, and output impedance of the transistor.



Input Impedance

$$Z_{in} = \frac{V_b}{I_b} = h_{ie} - \frac{h_{re} h_{fe} R_L}{1 + h_{oe} R_L}$$

Current Gain

$$A_i = \frac{I_c}{I_b} = \frac{h_{fe}}{1 + h_{oe} R_L}$$


Output Impedance

$$Z_{out} = \frac{V_c}{I_c} \bigg|_{V_s=0} = \frac{R_s + h_{ie}}{(R_s + h_{ie})h_{oe} - h_{re} h_{fe}}$$

Voltage Gain

$$A_v = \frac{V_c}{V_b} = \frac{-h_{fe} R_L}{h_{ie} + (h_{ie} h_{oe} - h_{re} h_{fe}) R_L}$$

19.5 Transmission Parameters (1)

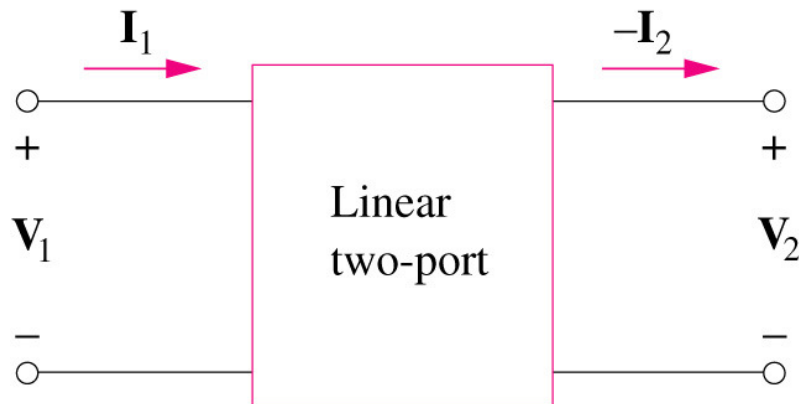

**Assume no
independent source
in the network**

$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = [T] \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

where the **T** terms are called the transmission parameters, or simply **T** or ABCD parameters.

•Note that $-I_2$ is used since the current is considered to be leaving the network. It is logical to think of I_2 as leaving the two-port; this is customary convention in the power industry.

19.5 Transmission Parameters (2)

- These two-port transmission parameters provide a measure of how a circuit transmits voltage and current from a source to a load.
- They are useful in the analysis of transmission lines and are therefore called transmission parameters.
- They are also known as ABCD parameters and are used in the design of telephone systems, microwave networks, and radars.

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

A=open-circuit
voltage ratio

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

C= open-circuit
transfer admittance
(S)

$$B = - \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

B= negative short-
circuit transfer
impedance (Ω)

$$D = - \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

D=negative short-
circuit current ratio

19.5 Transmission Parameters (3)

Solving for Transmission Parameters

- To find the transmission parameters, analyze the circuit as follows:
- Perform the analysis with the output Open Circuited ($I_2=0$)

$$\begin{array}{l} V_1 = AV_2 - \cancel{BI_2} \\ I_1 = CV_2 - \cancel{DI_2} \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} V_1 = AV_2 \\ I_1 = CV_2 \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} A = \frac{V_1}{V_2} \\ C = \frac{I_1}{V_2} \end{array}$$


- Perform the analysis with the output Short Circuited ($V_2=0$)

$$\begin{array}{l} V_1 = \cancel{AV_2} - BI_2 \\ I_1 = \cancel{CV_2} - DI_2 \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} V_1 = -BI_2 \\ I_1 = -DI_2 \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} B = -\frac{V_1}{I_2} \\ D = -\frac{I_1}{I_2} \end{array}$$

19.5 Transmission Parameters (4)

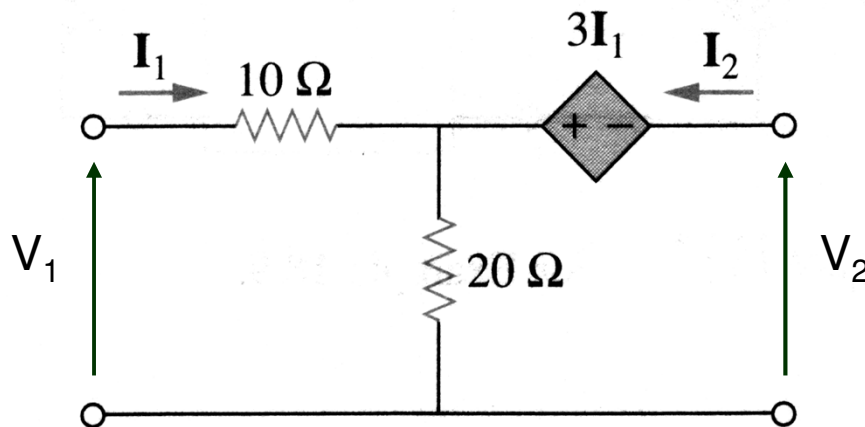Example 19.8

Determine the T-parameters of the following circuit.



$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$

Apply KVL

$$\begin{aligned} V_1 &= 10I_1 + 20(I_1 + I_2) \\ V_2 &= -3I_1 + 20(I_1 + I_2) \end{aligned}$$



Answer:
$$T = \begin{bmatrix} 1.765 & 15.294\Omega \\ 0.059S & 1.176 \end{bmatrix}$$

$$\begin{aligned} V_1 &= \frac{30}{17}V_2 - \frac{260}{17}I_2 \\ I_1 &= \frac{1}{17}V_2 - \frac{20}{17}I_2 \end{aligned}$$

19.5 Transmission Parameters (5)

Example 19.8

From KVL:

$$V_1 = 10I_1 + 20(I_1 + I_2) = 30I_1 + 20I_2$$

$$V_2 = -3I_1 + 20(I_1 + I_2) = 17I_1 + 20I_2$$


If we “open circuit” the output we get:

$$V_1 = 30I_1 + 20\overset{0}{I_2}$$

$$V_1 = 30I_1$$

$$V_2 = 17I_1 + 20\overset{0}{I_2}$$

$$V_2 = 17I_1$$

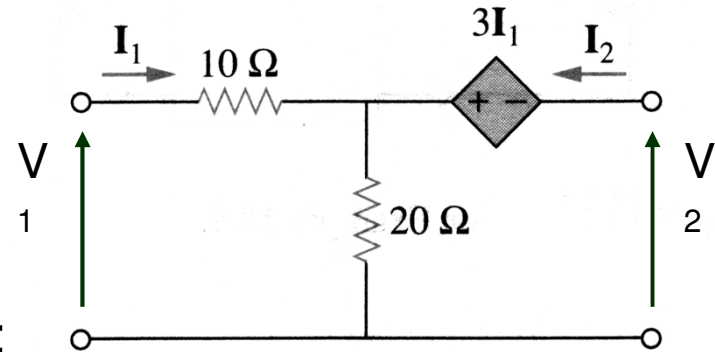

$$A = \frac{V_1}{V_2} = \frac{30I_1}{17I_1} = \frac{30}{17} = 1.765$$

$$C = \frac{1}{17} = 0.0588$$

If we “short circuit” the output we get:

$$V_1 = 30I_1 + 20I_2$$

$$V_1 = 30I_1 + 20I_2$$

$$\overset{0}{V_2} = 17I_1 + 20I_2$$

$$0 = 17I_1 + 20I_2$$

$$V_1 = 30\left(\frac{-20}{17}\right)I_2 + 20I_2$$


$$I_1 = \frac{-20}{17}I_2$$

$$B = -\frac{V_1}{I_2} = -\frac{(30\left(\frac{-20}{17}\right) + 20)I_2}{I_2} = 15.29$$

$$D = -\frac{I_1}{I_2} = \frac{20}{17} = 1.176$$

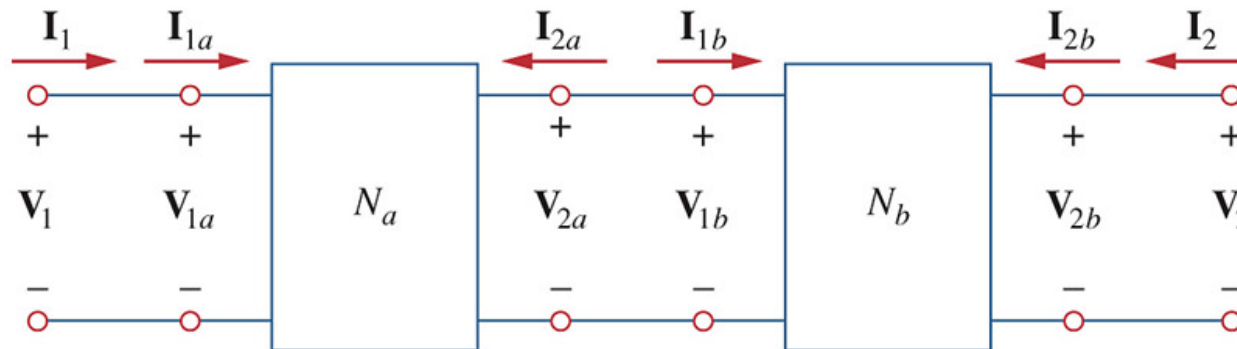19.5 Transmission Parameters (6)

- Transmission Parameters can be cascaded with the result found through simple matrix multiplication



$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$-I_{2a} = I_{1b}$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

19.5 Transmission Parameters (7)

Properties: Building Block Circuits

Consider the following
simple circuits

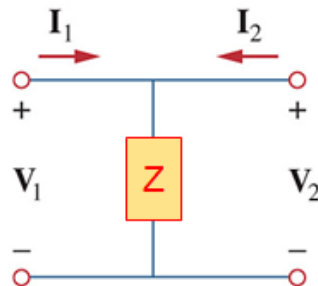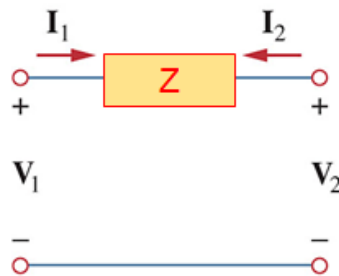


We can find their T
Parameters to be:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{Z} & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Note, following
is equivalent

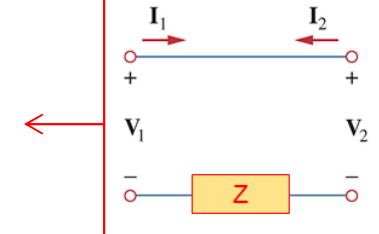

19.5 Transmission Parameters (8)

Properties: Building Block Circuits

- We can use this to construct the following “building block T parameters” to find the T parameters for any ladder type circuit.

$$\begin{bmatrix} 1 & R \\ 0 & 1 \end{bmatrix}$$




$$\begin{bmatrix} 1 & \frac{1}{sC} \\ 0 & 1 \end{bmatrix}$$




$$\begin{bmatrix} 1 & sL \\ 0 & 1 \end{bmatrix}$$



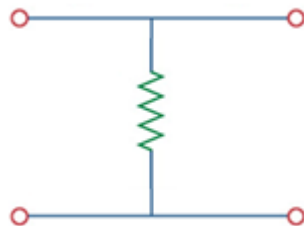
$$\begin{bmatrix} 1 & 0 \\ \frac{1}{R} & 1 \end{bmatrix}$$


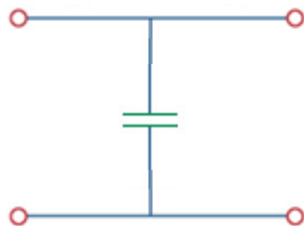
$$\begin{bmatrix} 1 & 0 \\ sC & 1 \end{bmatrix}$$


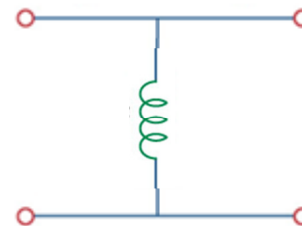
$$\begin{bmatrix} 1 & 0 \\ \frac{1}{sL} & 1 \end{bmatrix}$$



19.5 Transmission Parameters (9)

Properties: Transfer function / Thevenin Equivalent

- The “A” parameter can be used to provide the inverse of the voltage Transfer Function $H(s)$.

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

- Parameters “A” and “B” can be used to find a relationship between the Open Circuit Voltage (V_2) and the Short Circuit Current ($-I_2$).
- We can use this to find the parameters for the Thevenin Equivalent Circuit.


$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{V_1}{V_{oc}}$$

$$V_{Th} = V_{oc} = \frac{V_1}{A}$$


$$Z_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{B}{A}$$

$$B = - \left. \frac{V_1}{I_2} \right|_{V_2=0} = \frac{V_1}{I_{sc}}$$

$$I_N = I_{sc} = \frac{V_1}{B}$$

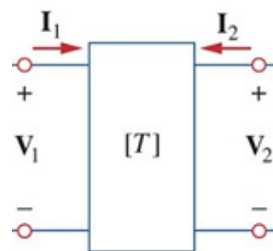

$$V_{Th} = \frac{V_1}{A}$$

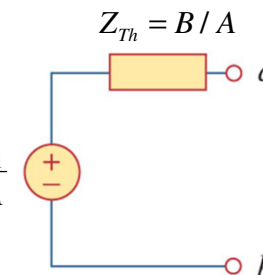


19.5 Transmission Parameters (10)

Transfer Function - Example

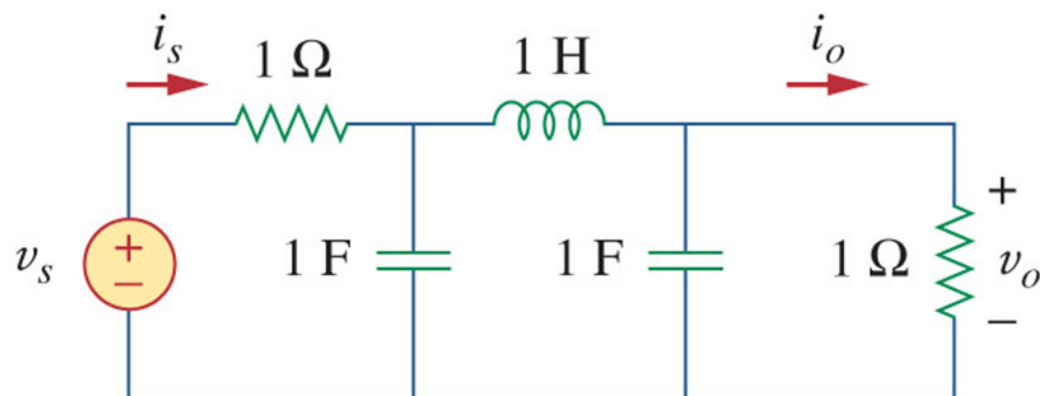Problem 16.80(a)

Find the transfer function $V_o(s)/V_s(s)$ for the following circuit



Answer:


$$H(s) = \frac{1}{s^3 + 2s^2 + 3s + 2}$$

19.5 Transmission Parameters (11)

Transfer Function - Example

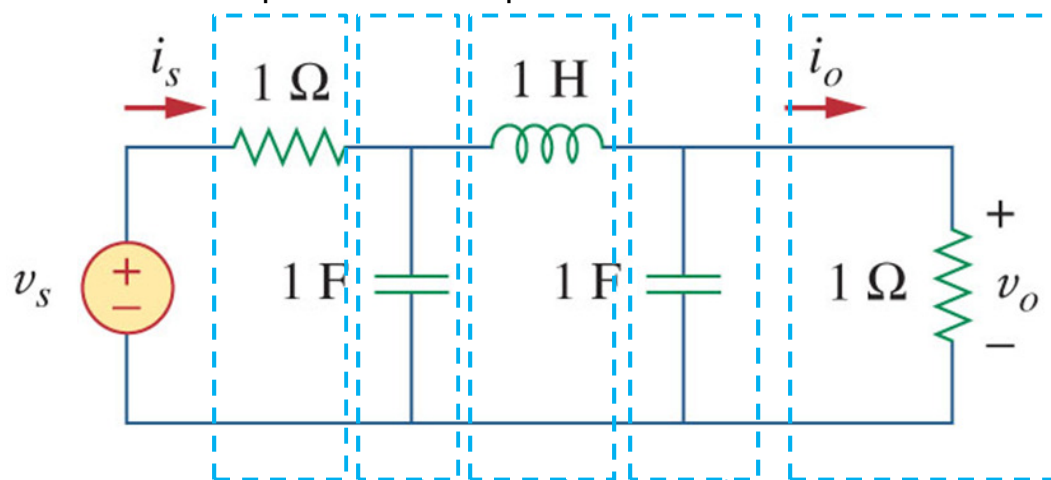Problem 16.80(a) Solution:

- Break up the circuit into a series of cascaded series and shunt components
- Find the composite "T" parameters for the circuit
- Use the relationship between the parameter "A" and the Transfer function



$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

19.5 Transmission Parameters (12)

Transfer Function - Example

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix}$$

Finding the
combined T-matrix

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ (s+1) & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1+s(s+1) & s \\ (s+1) & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1+s(s+1) & s \\ s+s^2(s+1)+(s+1) & s^2 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} s^2+s+1 & s \\ s^3+s^2+2s+1 & s^2 \end{bmatrix}$$

$$\begin{bmatrix} s^3+2s^2+3s+2 & s+s^2 \\ s^3+s^2+2s+1 & s^2 \end{bmatrix}$$

The transfer function can be found
directly from the Transmission
Parameter "A" !

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

$$H(s) = \frac{1}{s^3+2s^2+3s+2}$$


19.5 Transmission Parameters (13)

Example 19.9

The ABCD parameters of the two-port network at right are




$$\mathbf{T} = \begin{bmatrix} 4 & 20 \, \Omega \\ 0.1 \text{ S} & 2 \end{bmatrix}$$

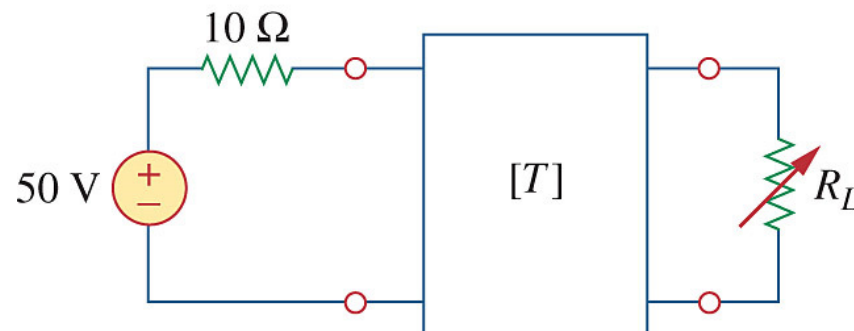Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



The output port is connected to a variable load for maximum power transfer. Find R_L and the maximum power transferred.

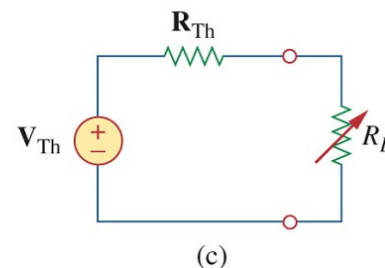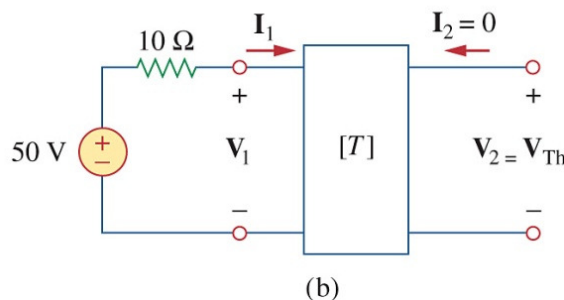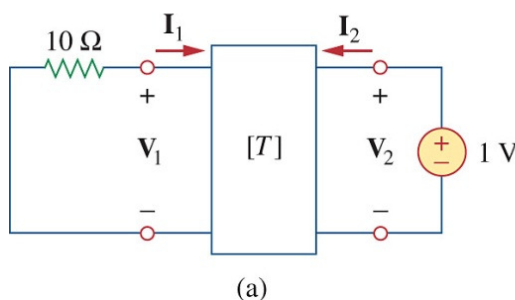Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Answer: $V_{TH} = 10 \text{ V}$; $R_L = 8 \, \Omega$; $P_m = 3.125 \text{ W}$.

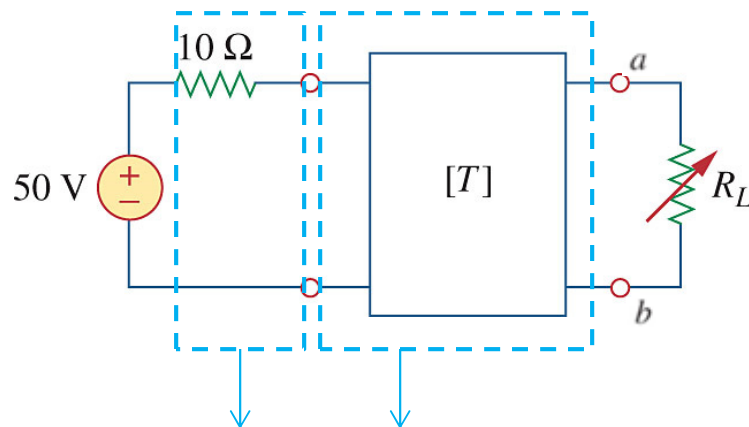19.5 Transmission Parameters (14)


Solution: Example 19.9

- Cascade the Series Resistor with the network
- Find the composite "T" parameters for the circuit
- Use the relationships to find V_{Th} and Z_{Th}



$$[T'] = \begin{bmatrix} 1 & 10 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 4 & 20 \\ 0.1 & 2 \end{bmatrix} = \begin{bmatrix} 5 & 40 \\ 0.1 & 2 \end{bmatrix}$$

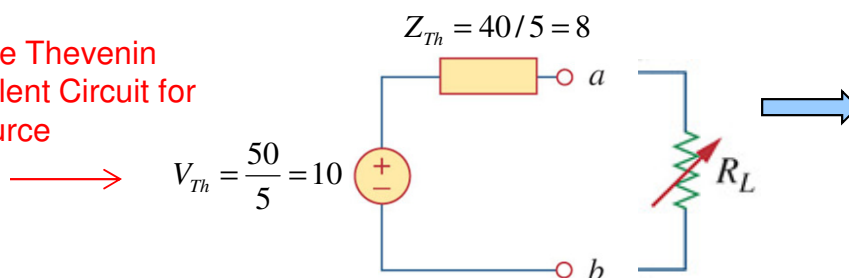Find the Thevenin
Equivalent Circuit for
the source



For Max Power Transfer

$$R_L = Z_{Th} = 8 \Omega$$

$$P_{\max} = I^2 R_L$$


$$P_{\max} = \left(\frac{V_{Th}}{R_L + Z_{Th}} \right)^2 R_L$$

$$P_{\max} = \left(\frac{10}{16} \right)^2 8 = 3.125 \text{ W}$$

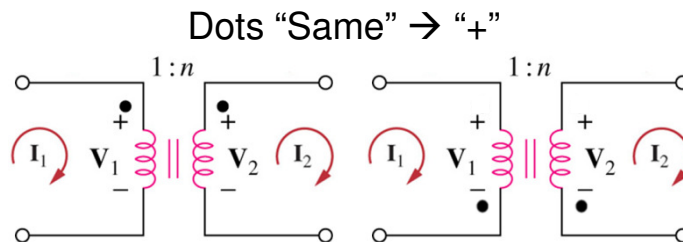19.5 Transmission Parameters (15)

Properties: Building Block Circuits – Ideal Transformer

- We can also use these “building blocks” to model ideal transformers. Remember from Chapter 13




$$V_2 = nV_1$$

$$I_2 = \frac{I_1}{n}$$


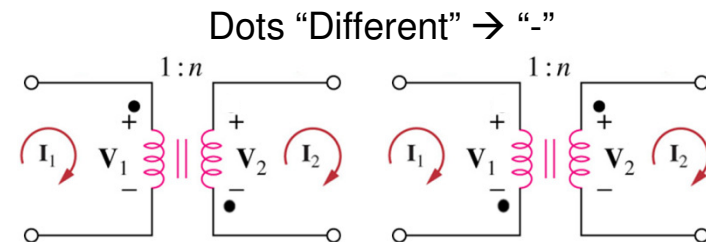
$$\begin{bmatrix} \frac{1}{n} & 0 \\ 0 & n \end{bmatrix}$$



$$V_2 = -nV_1$$

$$I_2 = -\frac{I_1}{n}$$



$$\begin{bmatrix} -\frac{1}{n} & 0 \\ 0 & -n \end{bmatrix}$$


T - parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

19.5 Transmission Parameters (16)

Example 13.8 Revisited

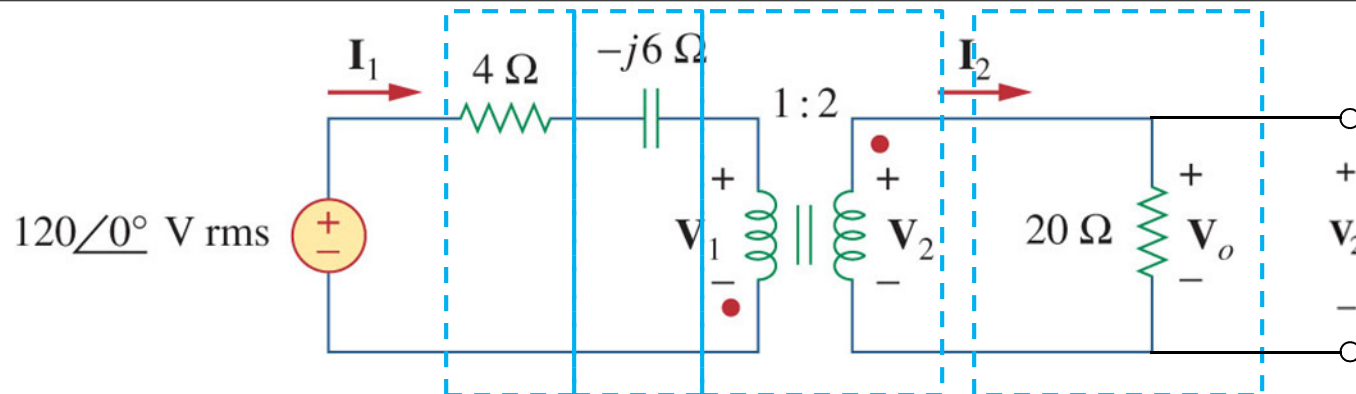

Cascaded T parameters →

$$\begin{bmatrix} 1 & 4 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & -j6 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} -\frac{1}{2} & 0 \\ 0 & -2 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0.05 & 1 \end{bmatrix}$$

a b c d

Using MATLAB: →

```
>> T=a*b*c*d


T =

-0.9000 + 0.6000i -8.0000 + 12.0000i
-0.1000 + 0.0000i -2.0000 + 0.0000i
```

$$V_0 = V_2 = \frac{1}{A} V_1 = \left(\frac{1}{-0.9 + 0.6j} \right) (120 \angle 0^\circ) = 110.94 \angle -146.31^\circ \text{ V}$$

19.5 Transmission Parameters (17)

Example 13.8 Revisited

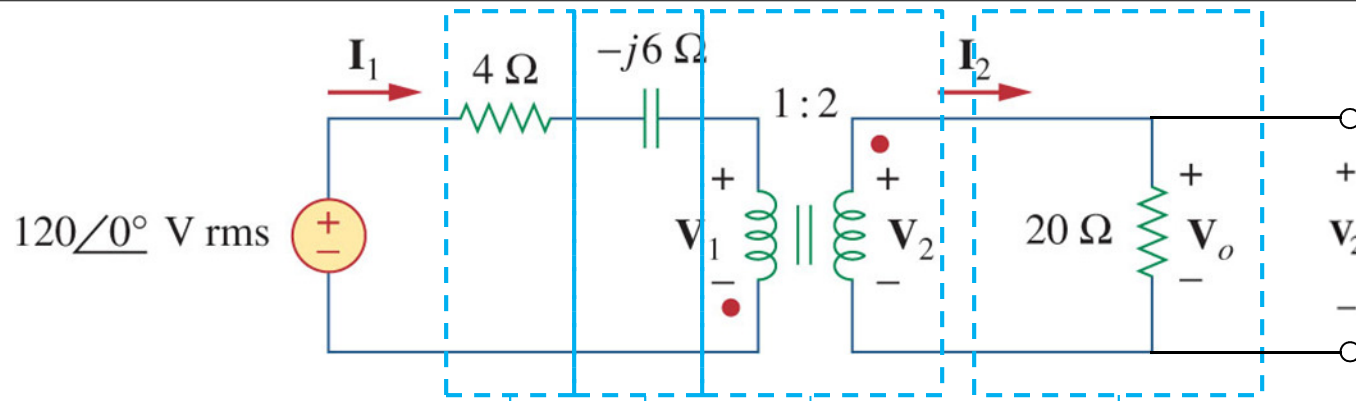

```
>> T=a*b*c*d
```

```
T =
```


```
-0.9000 + 0.6000i  -8.0000 +12.0000i  
-0.1000 + 0.0000i  -2.0000 + 0.0000i
```

$$I_1 = CV_2 = (-0.1)(110.94\angle -146.31^\circ) = 11.09\angle 33.69^\circ \text{ A}$$

$$I_2 = \frac{V_2}{20} = \frac{(110.94\angle -146.31^\circ)}{20} = 5.55\angle -146.31^\circ \text{ A}$$

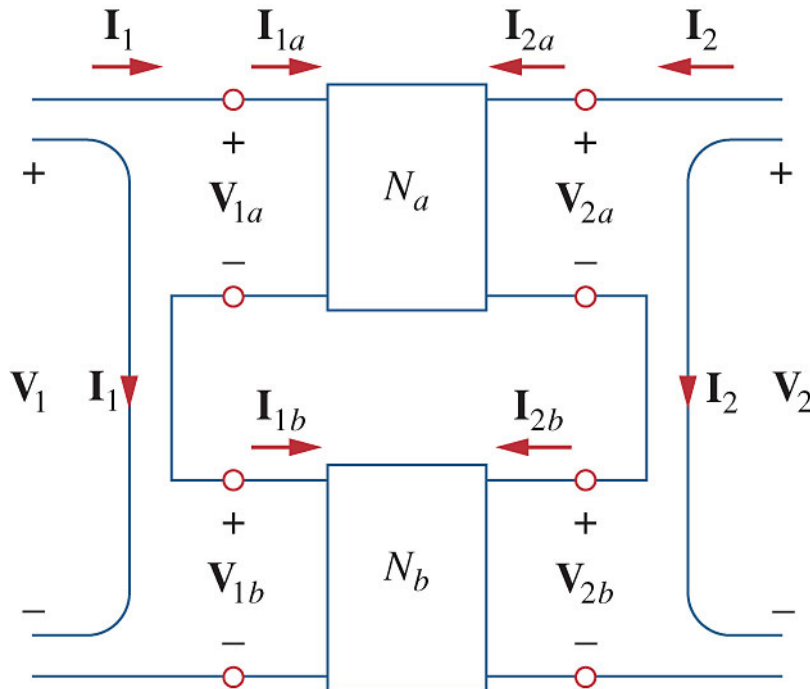19.7 Interconnection of Networks (1)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Series Connection of
two-port networks:

For Impedances; ADD
matrices.

$$Z = Z_a + Z_b$$

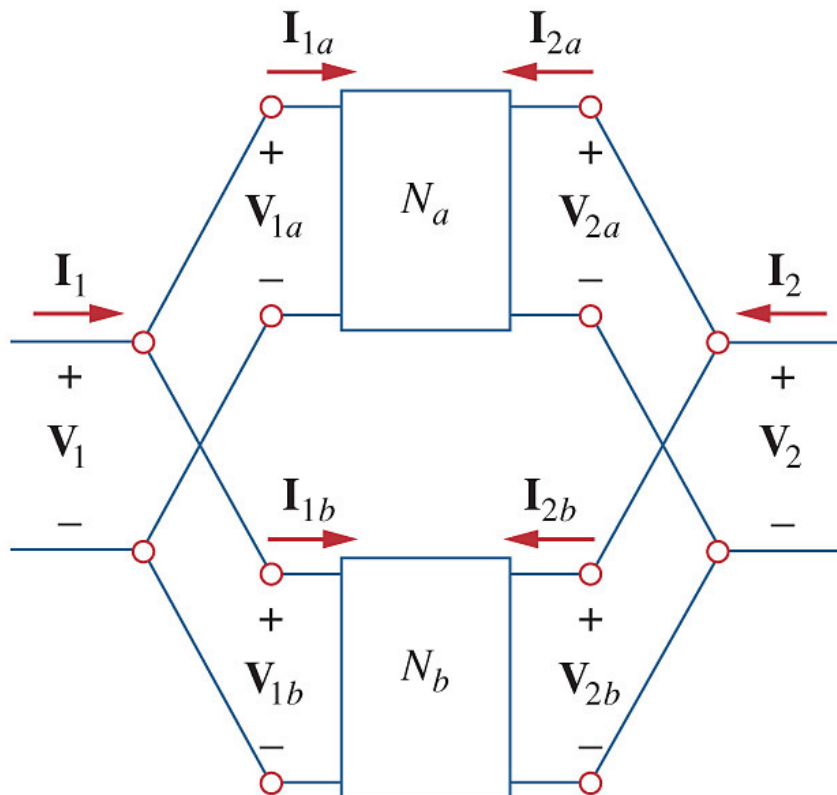19.7 Interconnection of Networks (2)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Parallel Connection of
two-port networks:

For Admittances; ADD
matrices.

$$Y = Y_a + Y_b$$

19.6 Relationships Between Networks

- Use this table to convert between two port parameters

	z		y		h		T	
z	z_{11}	z_{12}	$\frac{y_{22}}{\Delta_y}$	$-\frac{y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$
	z_{21}	z_{22}	$-\frac{y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{C}$	$\frac{D}{C}$
y	$\frac{z_{22}}{\Delta_z}$	$-\frac{z_{12}}{\Delta_z}$	y_{11}	y_{12}	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$	$\frac{D}{B}$	$-\frac{\Delta_T}{B}$
	$-\frac{z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	y_{21}	y_{22}	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$-\frac{1}{B}$	$\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	h_{11}	h_{12}	$\frac{B}{D}$	$\frac{\Delta_T}{D}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	h_{21}	h_{22}	$-\frac{1}{D}$	$\frac{C}{D}$
T	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$-\frac{h_{11}}{h_{21}}$	A	B
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta_y}{y_{21}}$	$-\frac{y_{11}}{y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$-\frac{1}{h_{21}}$	C	D

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21} \quad \Delta_z = z_{11}z_{22} - z_{12}z_{21} \quad \Delta_h = h_{11}h_{22} - h_{12}h_{21} \quad \Delta_T = AD - BC$$

Chapter 19 Review

Z-Parameters

- Parameters:
$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$


- Open circuit the **output** to find z_{11} and z_{21}

$$\begin{aligned} V_1 &= z_{11}I_1 + \cancel{z_{12}I_2}^0 \\ V_2 &= z_{21}I_1 + \cancel{z_{22}I_2}^0 \end{aligned}$$



$$\begin{aligned} V_1 &= z_{11}I_1 \\ V_2 &= z_{21}I_1 \end{aligned}$$

Set $I_1 = 1$ then solve for V_1 and V_2

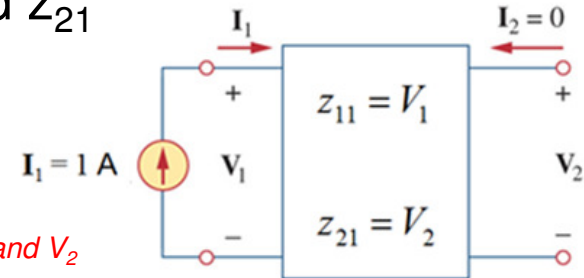


- Open circuit the **input** to find z_{21} and z_{22}

$$\begin{aligned} V_1 &= \cancel{z_{11}I_1}^0 + z_{12}I_2 \\ V_2 &= \cancel{z_{21}I_1}^0 + z_{22}I_2 \end{aligned}$$



$$\begin{aligned} V_1 &= z_{12}I_2 \\ V_2 &= z_{22}I_2 \end{aligned}$$

Set $I_2 = 1$ then solve for V_1 and V_2

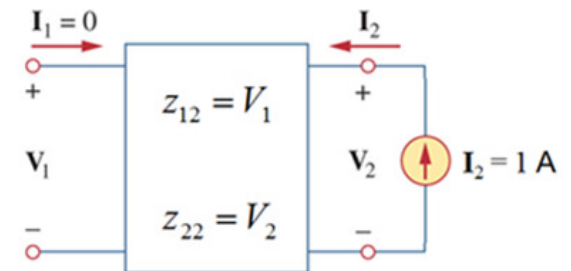


Chapter 19 Review

Z-Parameters (Given a circuit, find Z-parameters)

- Solving problems to find z-parameters:

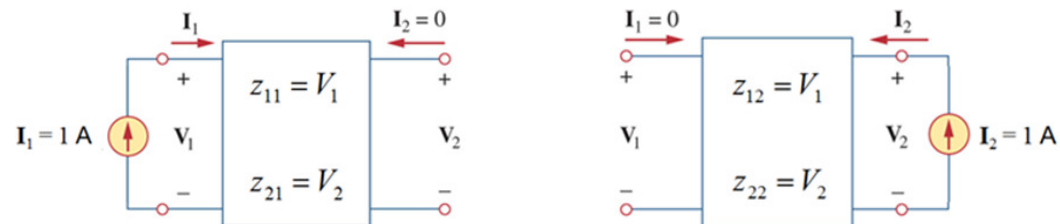1. Refer to definition, apply 1 amp source at input and output with opposite port left open (see previous slide)




2. Sometimes, KVL (mesh current equations) will cause z-parameters to fall right out! :

$$V_1 = 2I_1 + 6(I_1 + I_2) = 8I_1 + 6I_2$$

$$V_2 = 6(I_1 + I_2) + 3I_2 = 6I_1 + 9I_2$$


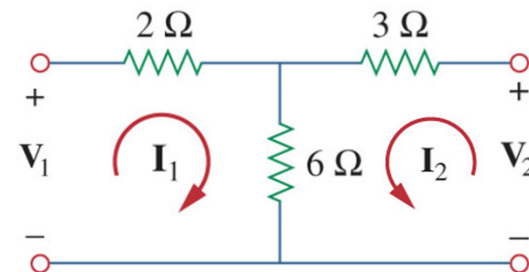
$$\mathbf{z} = \begin{bmatrix} 8 & 6 \\ 6 & 9 \end{bmatrix} \Omega$$




This mesh defined in counter clockwise direction for convenience

Chapter 19 Review


Z-Parameters (Given Z parameters, find circuit parameters)

- If given, z-parameters can use following techniques to find other circuit parameters (V_1 , V_2 , I_1 , I_2 , etc.):

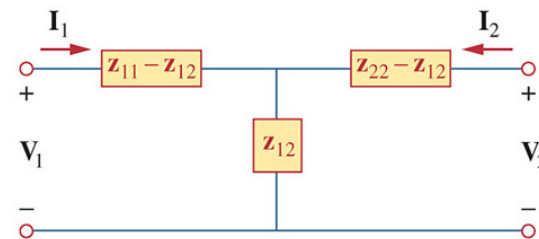1. Apply the model and solve the circuit:



Reciprocal
Network

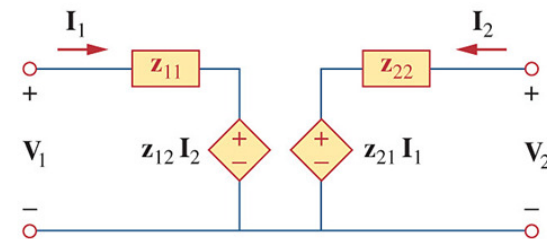

General
Network

2. Substitute the defining equations into your analysis:

Mesh Analysis


$$10 = 5I_1 + V_1 + 10(I_1 + I_2)$$

$$0 = V_2 + 10(I_1 + I_2) + 20I_2$$

Substitute for V_1 and V_2

$$10 = 5I_1 + (12I_1 + 8I_2) + 10(I_1 + I_2)$$
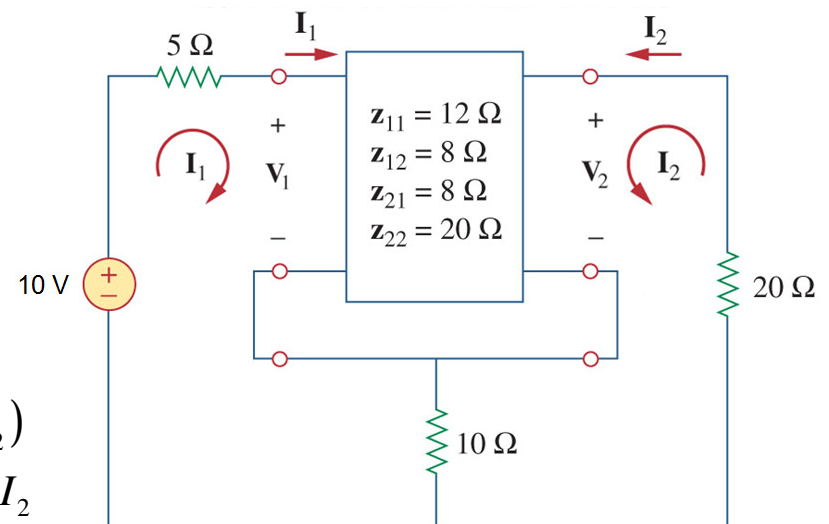
$$0 = (8I_1 + 20I_2) + 10(I_1 + I_2) + 20I_2$$



Chapter 19 Review

Y-Parameters

- Parameters:
$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$


- Short circuit the **output** to find y_{11} and y_{21}

$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} \cancel{V_2}^0 \\ I_2 &= y_{21} V_1 + y_{22} \cancel{V_2}^0 \end{aligned}$$



$$\begin{aligned} I_1 &= y_{11} V_1 \\ I_2 &= y_{21} V_1 \end{aligned}$$

Set $V_1 = 1$ then solve for I_1 and I_2

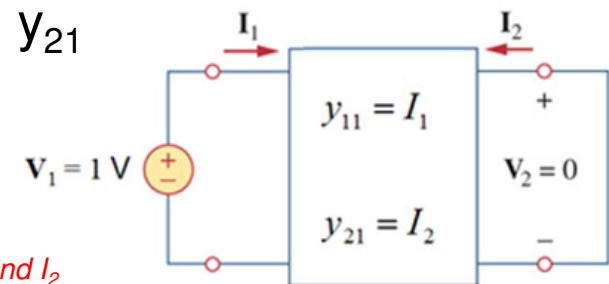


- Short circuit the **input** to find y_{21} and y_{22}

$$\begin{aligned} I_1 &= y_{11} \cancel{V_1}^0 + y_{12} V_2 \\ I_2 &= y_{21} \cancel{V_1}^0 + y_{22} V_2 \end{aligned}$$



$$\begin{aligned} I_1 &= y_{12} V_2 \\ I_2 &= y_{22} V_2 \end{aligned}$$

Set $V_2 = 1$ then solve for I_1 and I_2

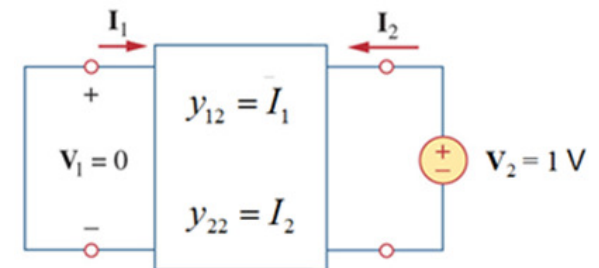


Chapter 19 Review


Y-Parameters (Solving Problems)

- To solve Y-parameter problems, can use these techniques

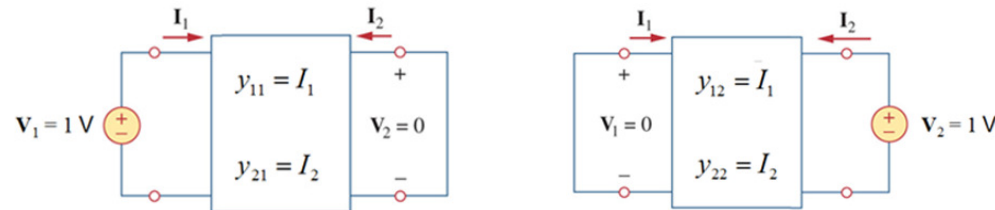1. Apply method from previous slide. Apply 1 Volt source at input and output while shorting opposite port



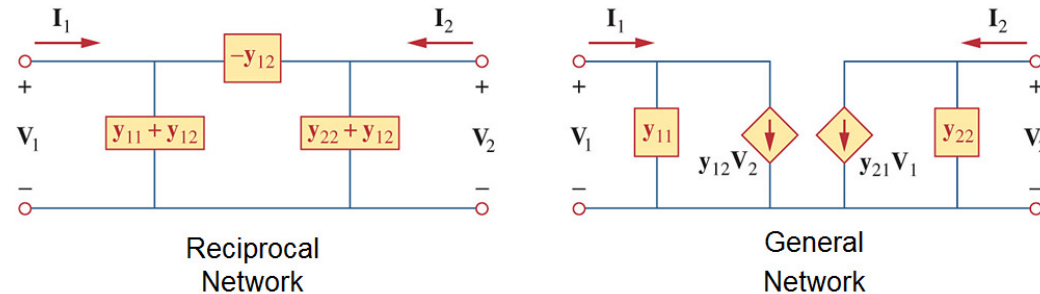2. If given Y parameters can apply the model and solve the circuit:



3. Make it easy on yourself! Use conversions from $Z \rightarrow Y$ or $Y \rightarrow Z$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \left(\frac{1}{\Delta_y} \right) \begin{bmatrix} y_{22} & -y_{12} \\ -y_{21} & y_{11} \end{bmatrix}$$

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21}$$

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \left(\frac{1}{\Delta_z} \right) \begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix}$$

$$\Delta_z = z_{11}z_{22} - z_{12}z_{21}$$

Chapter 19 Review

H-Parameters

- Parameters (hybrid of z and y):

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$


- Short circuit the **output** to find h_{11} and h_{21}

$$\begin{aligned} V_1 &= h_{11} I_1 + \cancel{h_{12} V_2}^0 \\ I_2 &= h_{21} I_1 + \cancel{h_{22} V_2}^0 \end{aligned}$$



$$\begin{aligned} V_1 &= h_{11} I_1 \\ I_2 &= h_{21} I_1 \end{aligned}$$

Set $I_1 = 1$ then solve for V_1 and I_2

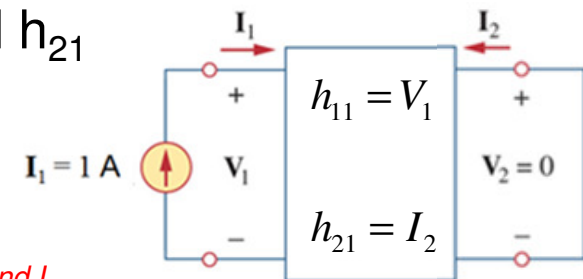


- Open circuit the **input** to find h_{21} and h_{22}

$$\begin{aligned} V_1 &= \cancel{h_{11} I_1}^0 + h_{12} V_2 \\ I_2 &= \cancel{h_{21} I_1}^0 + h_{22} V_2 \end{aligned}$$



$$\begin{aligned} V_1 &= h_{12} V_2 \\ I_2 &= h_{22} V_2 \end{aligned}$$

Set $V_2 = 1$ then solve for V_1 and I_2

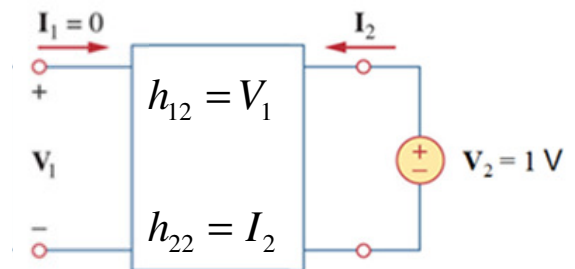


Chapter 19 Review

H-Parameters (Solving Problems)


- To solve H-parameter problems, can use these techniques

1. Apply methods from previous slide.

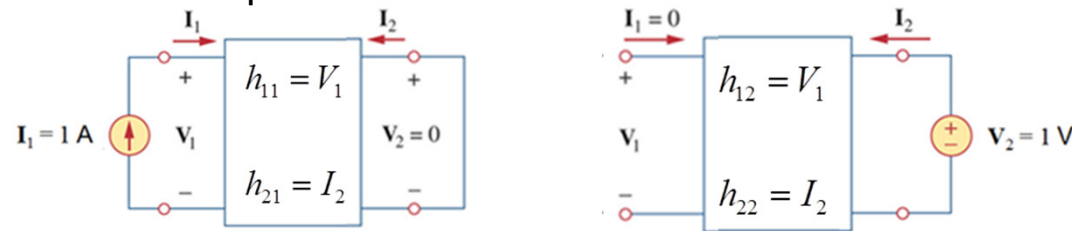

2. H parameters can be found by performing a set of tests on the device
 - a) Shorting the output and applying a current
 - b) Leaving the input open and applying a voltage across the output

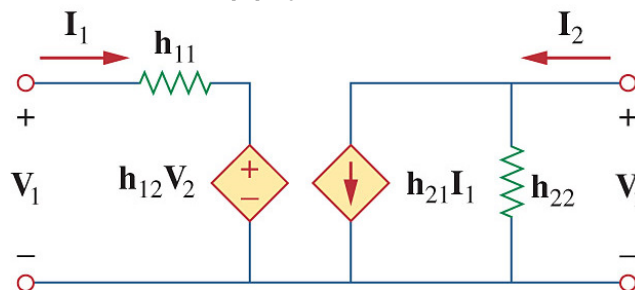3. If given H parameters can apply the model and solve the circuit:




4. If helpful, use conversion tables

Chapter 19 Review

H-Parameters (Transistor Model)

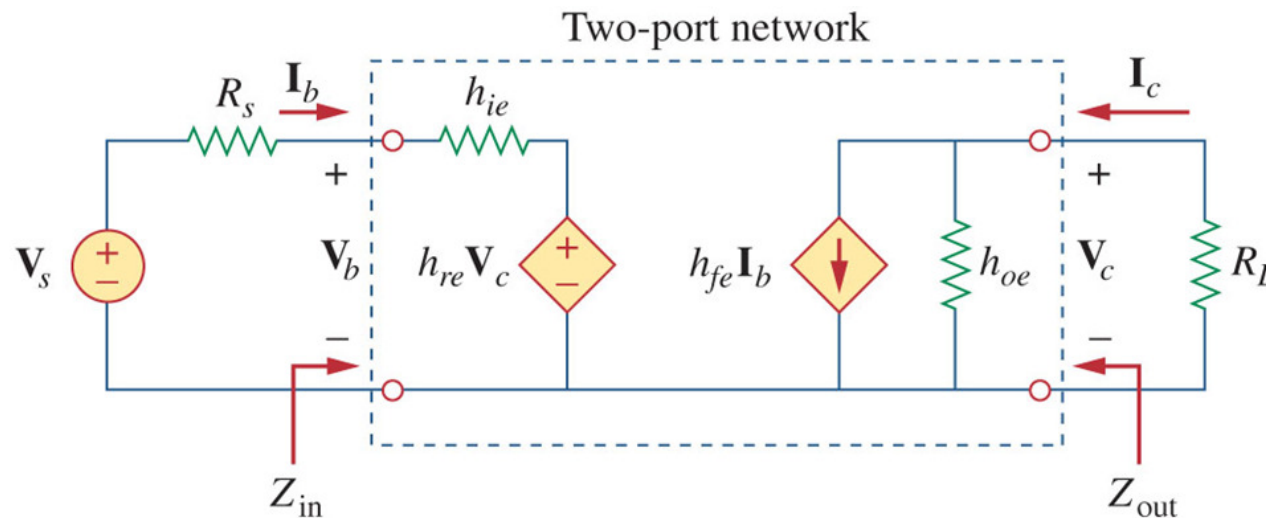
- H parameters are often used in modeling transistors
- Parameters vary depending on biasing conditions
- Spec sheets often use different subscripts:
 - $h_{11} \rightarrow h_{ie}$ = Base input impedance
 - $h_{12} \rightarrow h_{re}$ = Reverse voltage feedback ration
 - $h_{21} \rightarrow h_{fe}$ = Base-collector current gain
 - $h_{22} \rightarrow h_{oe}$ = Output admittance



Chapter 19 Review

H-Parameters (Transistor Model)

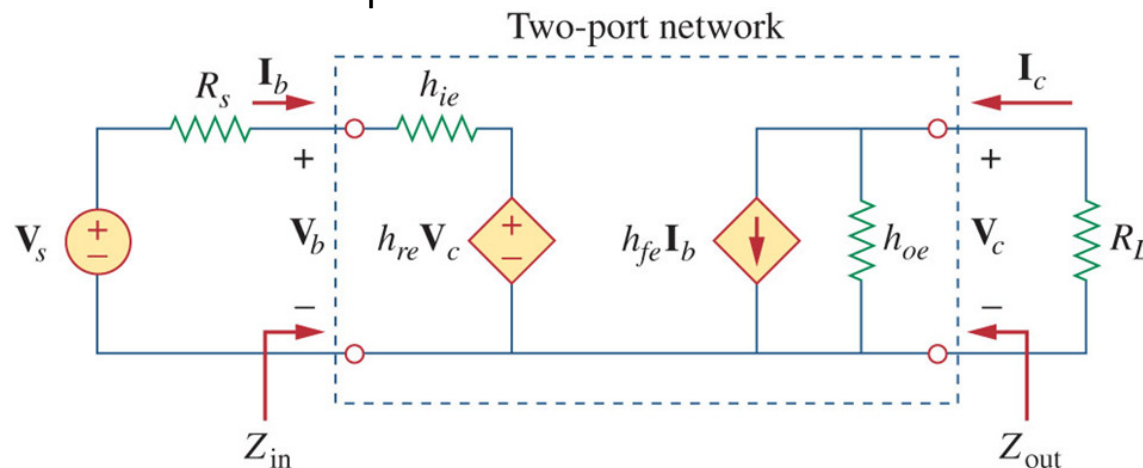- Equations for calculating input impedance, output impedance, voltage gain, and current gain for simple transistor circuit:
 - V_s and R_s can be the Thevenin equivalent source driving the input.
 - R_L can be the input impedance looking into the load of the circuit connected to the output



Input Impedance

$$Z_{in} = \frac{V_b}{I_b} = h_{ie} - \frac{h_{re} h_{fe} R_L}{1 + h_{oe} R_L}$$

Output Impedance

$$Z_{out} = \frac{V_c}{I_c} \bigg|_{V_s=0} = \frac{R_s + h_{ie}}{(R_s + h_{ie})h_{oe} - h_{re} h_{fe}}$$

Current Gain

$$A_i = \frac{I_c}{I_b} = \frac{h_{fe}}{1 + h_{oe} R_L}$$

Voltage Gain

$$A_v = \frac{V_c}{V_b} = \frac{-h_{fe} R_L}{h_{ie} + (h_{ie} h_{oe} - h_{re} h_{fe}) R_L}$$

Chapter 19 Review

Transmission ("T") Parameters

- Parameters: $V_1 = AV_2 - BI_2$
 $I_1 = CV_2 - DI_2$

- Perform the analysis with the **output** Open Circuited ($I_2=0$)

$$\begin{array}{l} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{array} \xrightarrow{I_2=0} \begin{array}{l} V_1 = AV_2 \\ I_1 = CV_2 \end{array} \xrightarrow{} \begin{array}{l} A = \frac{V_1}{V_2} \\ C = \frac{I_1}{V_2} \end{array}$$


- Perform the analysis with the **output** Short Circuited ($V_2=0$)

$$\begin{array}{l} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{array} \xrightarrow{V_2=0} \begin{array}{l} V_1 = -BI_2 \\ I_1 = -DI_2 \end{array} \xrightarrow{} \begin{array}{l} B = -\frac{V_1}{I_2} \\ D = -\frac{I_1}{I_2} \end{array}$$

Chapter 19 Review

Transmission ("T") Parameters (Cascading)

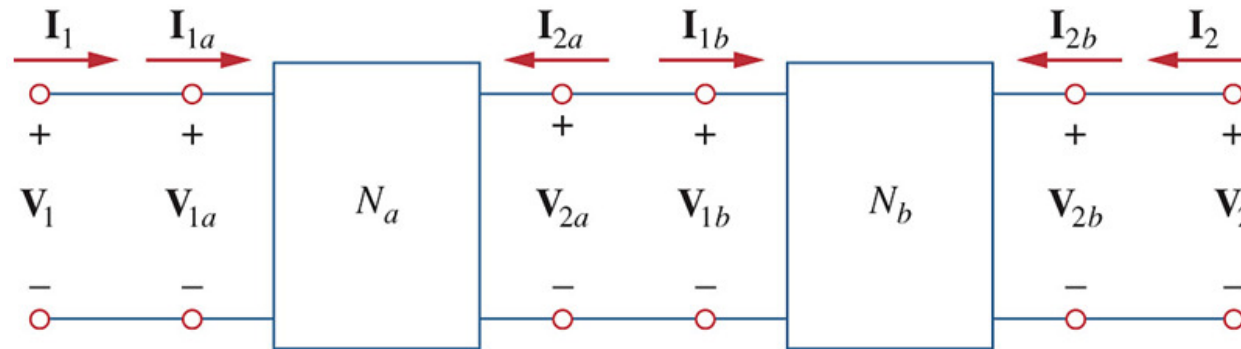- Primary benefit of "T"-Parameters is their ability to be cascaded.



$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$-I_{2a} = I_{1b}$$




$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Chapter 19 Review

T - Parameters (Building Block models)

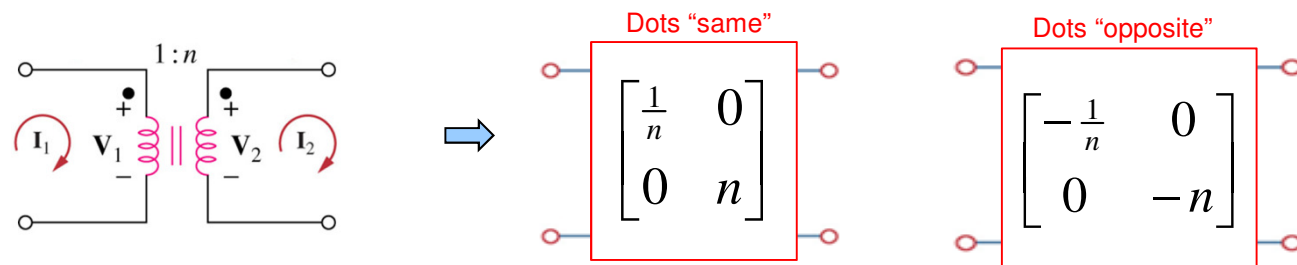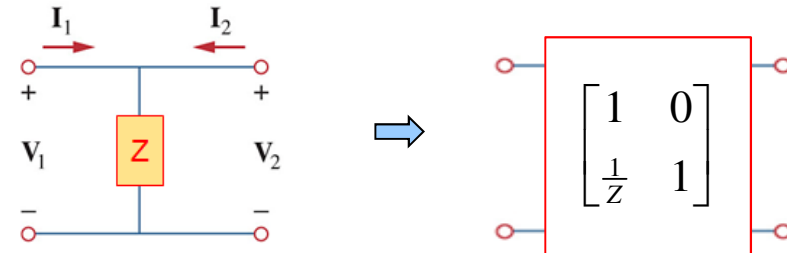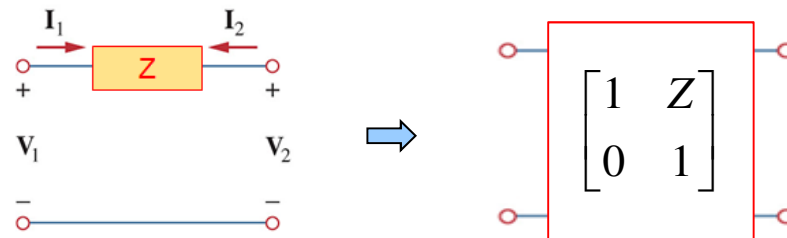
- We can create “building block” models of components by finding their T-parameters and use the cascading property to find the T-parameters for the complete circuit/system.



Chapter 19 Review

T - Parameters (Building Block models)

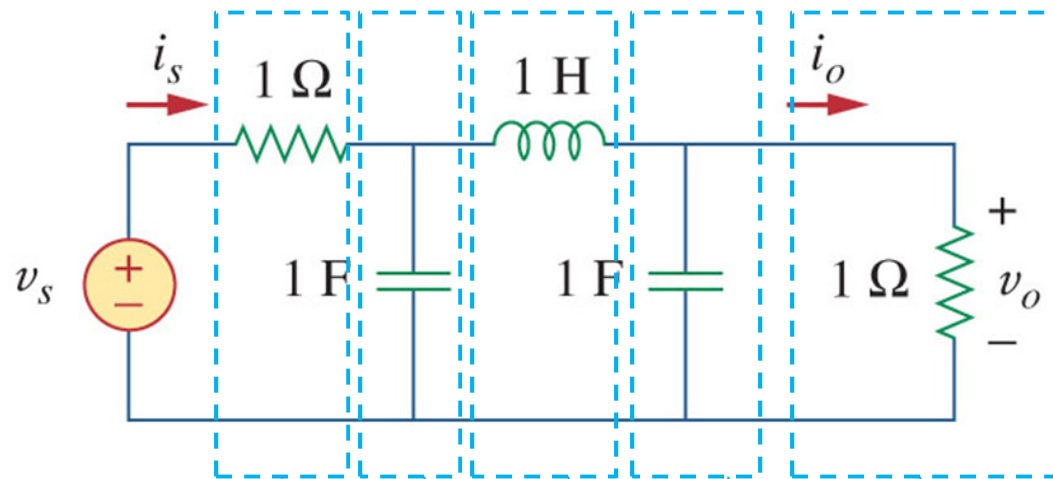- With “Building Block” approach, circuits can be broke up into discrete components and analyzed using T-parameters



$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$\rightarrow A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

Chapter 19 Review


T - Parameters (Useful Properties)

- The T parameters give us useful properties in the analysis of circuits:

- Open Circuit Voltage Transfer Function:

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)} \quad H(s) = \frac{1}{A}$$

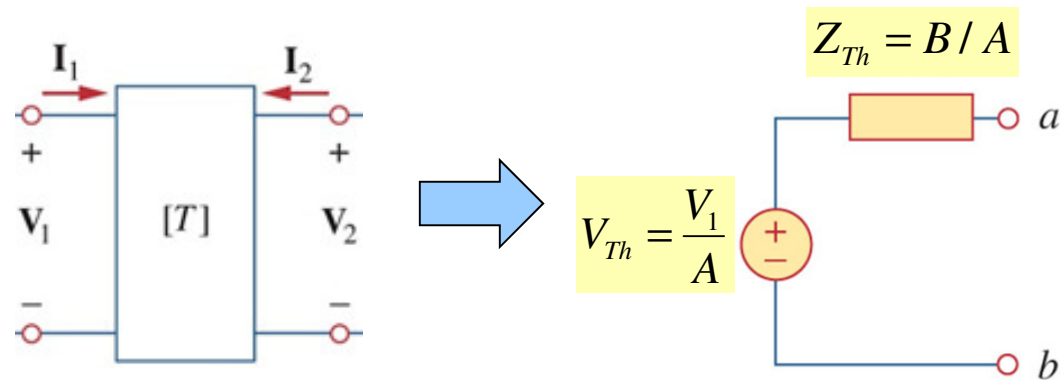- Thevenin Equivalent Circuit (Replace circuit as a source)



Chapter 19 Review

Conversion between Parameters

- Conversion tables exist to convert between parameters

	z		y		h		T	
z	z ₁₁	z ₁₂	$\frac{y_{22}}{\Delta_y}$	$-\frac{y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$
	z ₂₁	z ₂₂	$-\frac{y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{C}$	$\frac{D}{C}$
y	$\frac{z_{22}}{\Delta_z}$	$-\frac{z_{12}}{\Delta_z}$	y ₁₁	y ₁₂	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$	$\frac{D}{B}$	$-\frac{\Delta_T}{B}$
	$-\frac{z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	y ₂₁	y ₂₂	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$-\frac{1}{B}$	$\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	h ₁₁	h ₁₂	$\frac{B}{D}$	$\frac{\Delta_T}{D}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	h ₂₁	h ₂₂	$-\frac{1}{D}$	$\frac{C}{D}$
T	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$-\frac{h_{11}}{h_{21}}$	A	B
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta_y}{y_{21}}$	$-\frac{y_{11}}{y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$-\frac{1}{h_{21}}$	C	D

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21} \quad \Delta_z = z_{11}z_{22} - z_{12}z_{21} \quad \Delta_h = h_{11}h_{22} - h_{12}h_{21} \quad \Delta_T = AD - BC$$


Chapter 19: Two-Port Networks

- 19.1 Introduction
- 19.2 Impedance Parameters (z)
- 19.3 Admittance Parameters (y)
- 19.4 Hybrid Parameters (h)
- 19.5 Transmission Parameters (T)
- 19.6 Relationships between Parameters
- 19.7 Interconnection of Networks
- 19.9 Applications

19.1 Introduction (1)

- A port is an access to the network and consists of a pair of terminals; the current entering one terminal leaves through the other terminal so that the net current entering the port equals zero.
- One port networks include two-terminal devices such as resistors, capacitors, and inductors.
- A two-port network has two separate ports for input and output.
- Two port networks include op amps, transistors and transformers.

19.1 Introduction (2)

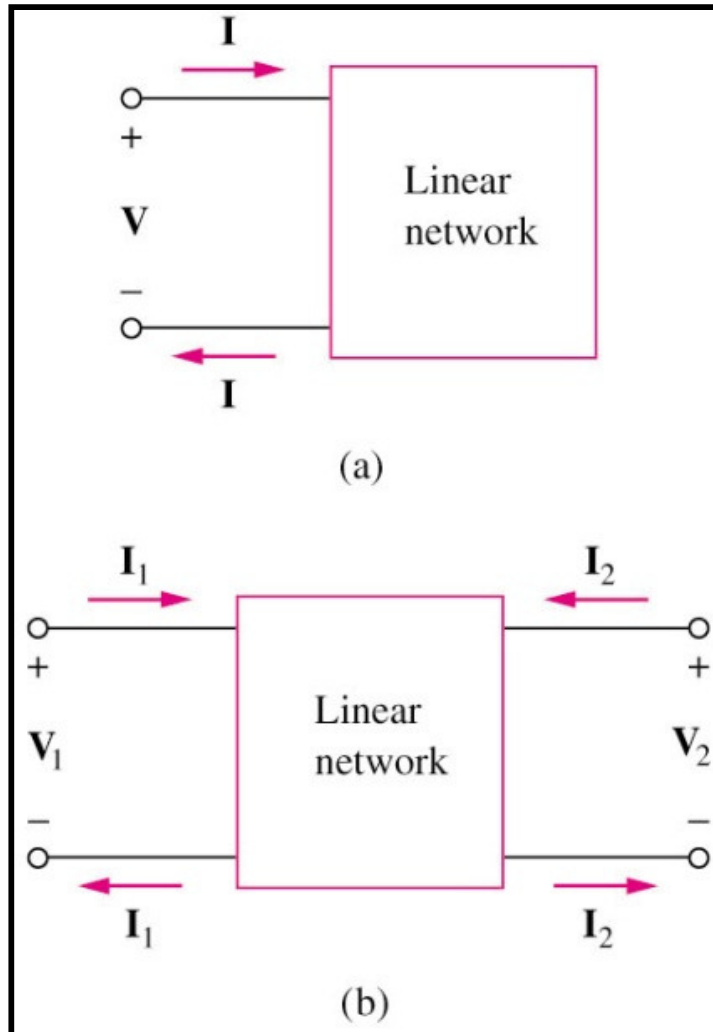

**One port or two
terminal circuit**

**Two port or four
terminal circuit**


- It is an electrical network with two separate ports for input and output.
- No independent sources.

19.1 Introduction (3)

- Characterizing a two-port network requires that we relate the terminal quantities \mathbf{V}_1 , \mathbf{V}_2 , \mathbf{I}_1 , \mathbf{I}_2 out of which two are independent. Six sets of voltage and current parameters will be derived.
- Two port networks are useful in communications, control systems, power systems, and electronics.
- They are used in electronics to model transistors and to facilitate cascaded design.
- Additionally, if we know the parameters of a two-port network it can be treated as a “black box” when embedded within a larger network.

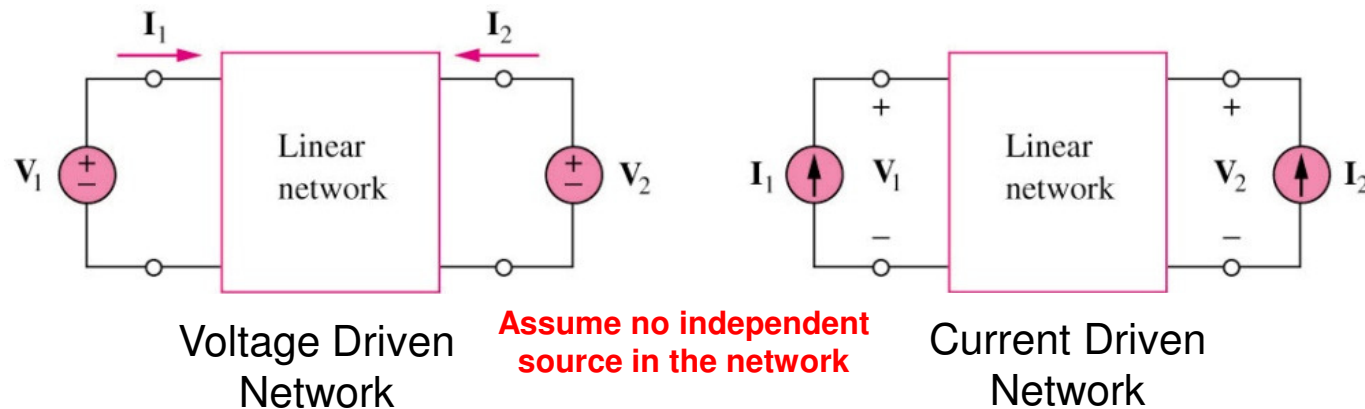19.2 Impedance Parameters (1)

- Often called “**Z-parameters**” since their units are in **ohms** and they represent an impedance relationship between V_1 , V_2 , I_1 , I_2 for the two port network shown below:



$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$




$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

- Z-parameters are commonly used in filter synthesis, impedance matching networks design, and power distribution networks analysis.

19.2 Impedance Parameters (2)

The values of parameters can be evaluated by setting $I_1=0$ or $I_2=0$ (open circuit)

Setting $I_2 = 0$

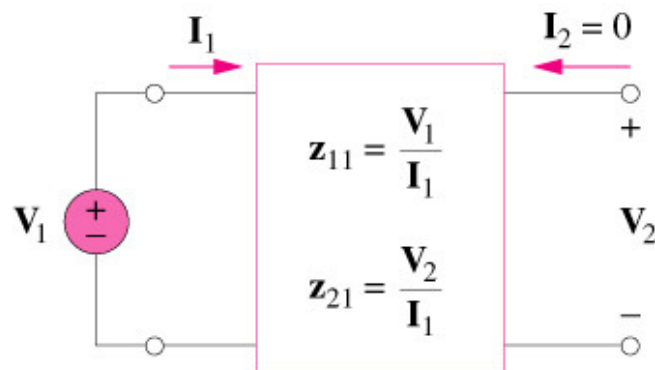


(a)

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

z_{11} = Open-circuit input impedance
 z_{21} = Open-circuit transfer impedance
from port 2 to port 1

Setting $I_1 = 0$

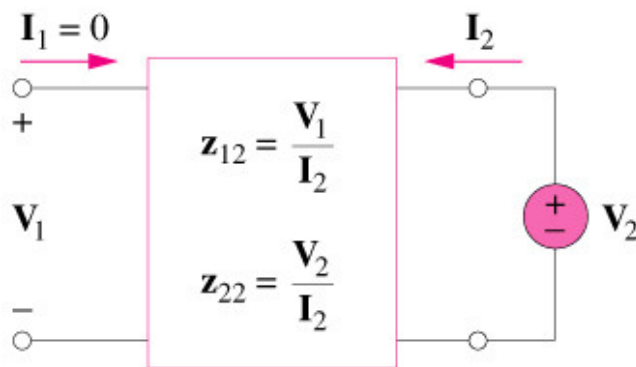

(b)


$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

z_{12} = Open-circuit transfer impedance from port 1 to port 2
 z_{22} = Open-circuit output impedance

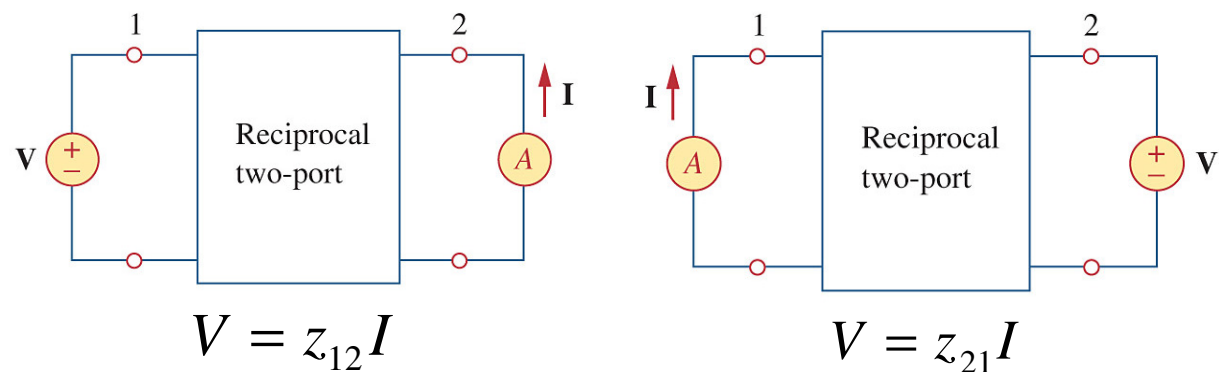19.2 Impedance Parameters (3)


Properties of Z-parameters

- Symmetrical networks $z_{11} = z_{22}$
 - Implies a mirror like symmetry
- Reciprocal networks $z_{12} = z_{21}$
 - Any network made up entirely of resistors, capacitors, and inductors must be reciprocal.
 - Linear networks with no dependant sources are reciprocal.
 - Interchanging an ideal voltage source at one port with an ideal ammeter at the other port gives the same ammeter reading.



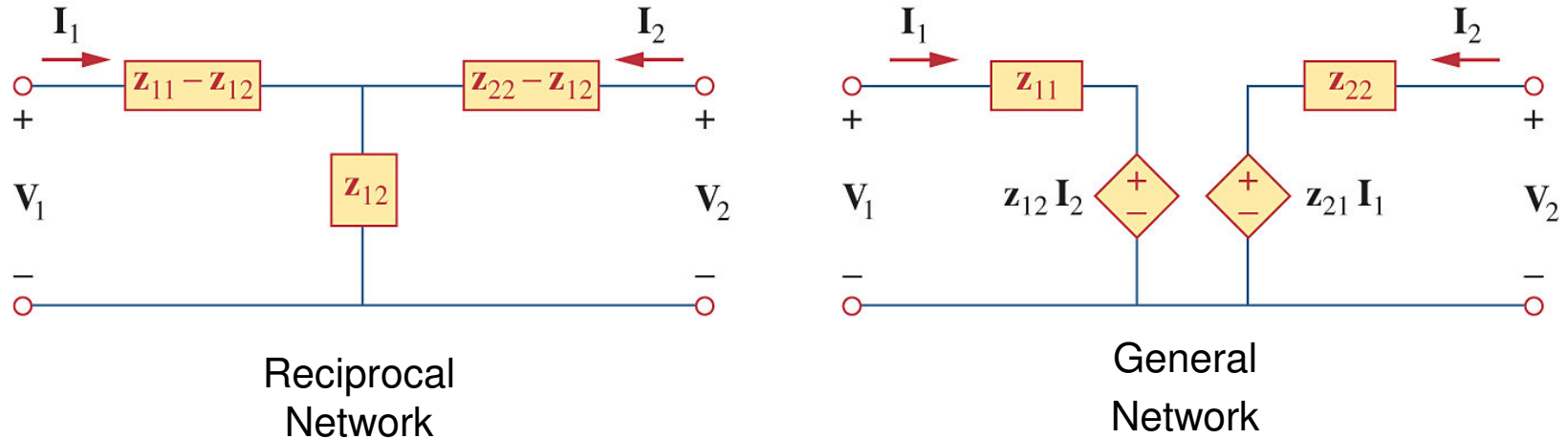19.2 Impedance Parameters (4)


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



- A reciprocal network can be replaced by the T-network shown above
- If not reciprocal, the General network is the T-equivalent.

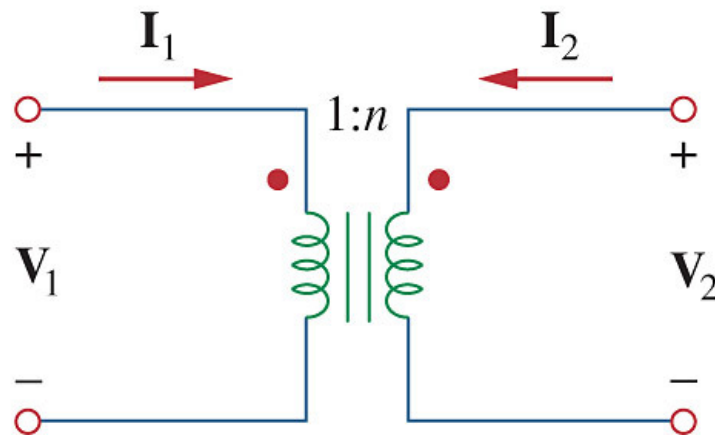19.2 Impedance Parameters (5)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



- Note: some circuits do not have z-parameter equivalents. (they may have other 2-port equivalents, as we shall see)

- Consider an ideal transformer:

$$V_1 = V_2/n \text{ and } I_1 = -nI_2.$$


- This cannot be expressed by:

$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

19.2 Impedance Parameters (6)

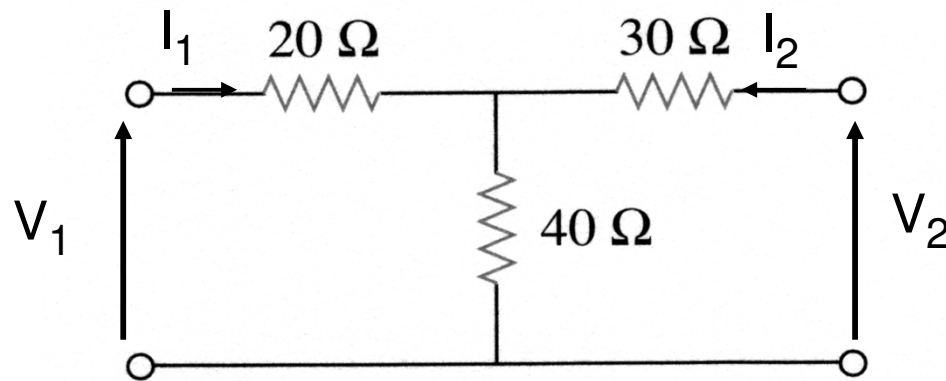Example 19.1

Determine the z-parameters of the following circuit.



$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$



Answer:
$$z = \begin{bmatrix} 60 & 40 \\ 40 & 70 \end{bmatrix} \Omega$$


$$Z = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \Omega$$

19.2 Impedance Parameters (7)

Practice Problem 19.2

Determine I_1 and I_2 in the following circuit.

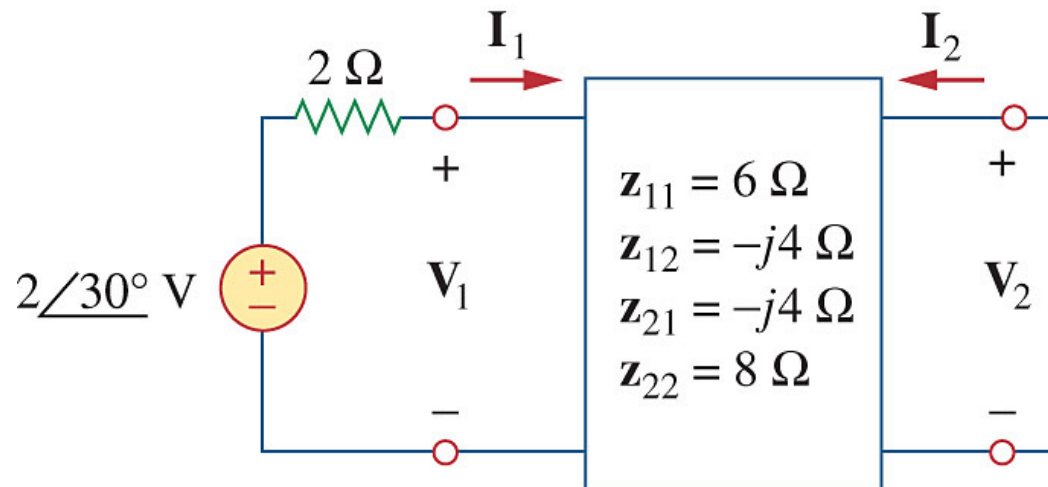
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

Answer: $I_1 = 200\angle 30^\circ \text{ mA}$
 $I_2 = 100\angle 120^\circ \text{ mA}$

19.3 Admittance Parameters (1)

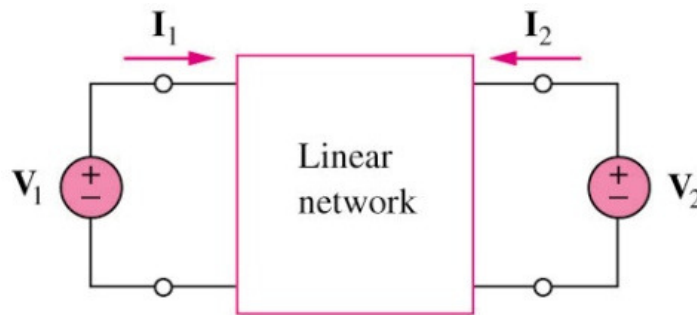

(a)

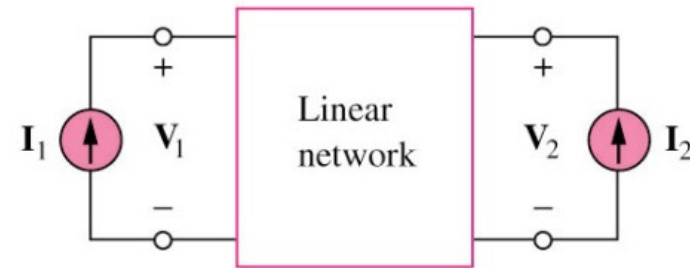

(b)

Assume no independent source in the network


$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$




$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

where the **y** terms are called the admittance parameters, or simply **y** parameters, and they have units of Siemens.

19.3 Admittance Parameters (2)

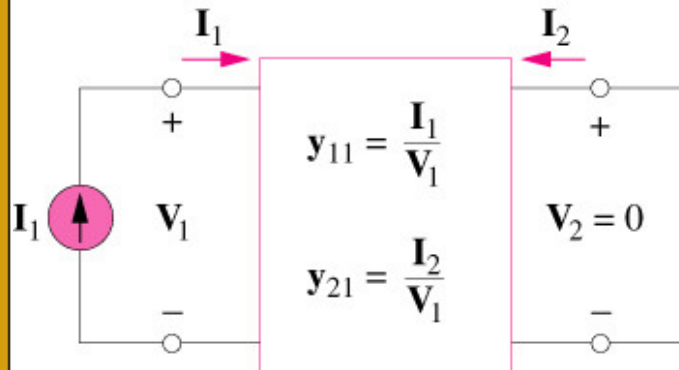

(a)

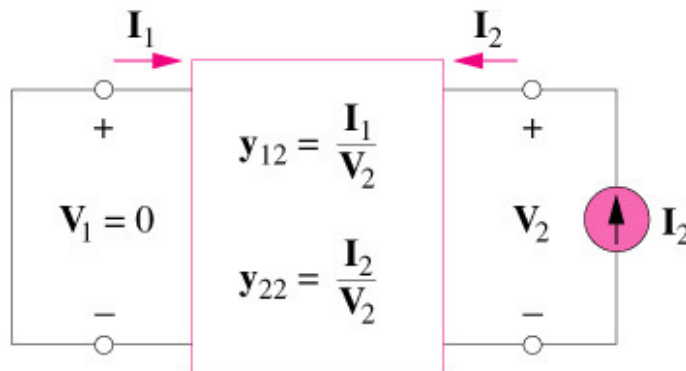

(b)

Setting $V_2 = 0$ (Shorting the output)

$$y_{11} = \frac{I_1}{V_1} \bigg|_{V_2=0} \quad \text{and} \quad y_{21} = \frac{I_2}{V_1} \bigg|_{V_2=0}$$


y_{11} = Short-circuit input admittance
 y_{21} = Short-circuit transfer admittance from port 1 to port 2

Setting $V_1 = 0$ (Shorting the input)

$$y_{12} = \frac{I_1}{V_2} \bigg|_{V_1=0} \quad \text{and} \quad y_{22} = \frac{I_2}{V_2} \bigg|_{V_1=0}$$

y_{12} = Short-circuit transfer admittance from port 2 to port 1
 y_{22} = Short-circuit output admittance

19.3 Admittance Parameters (3)

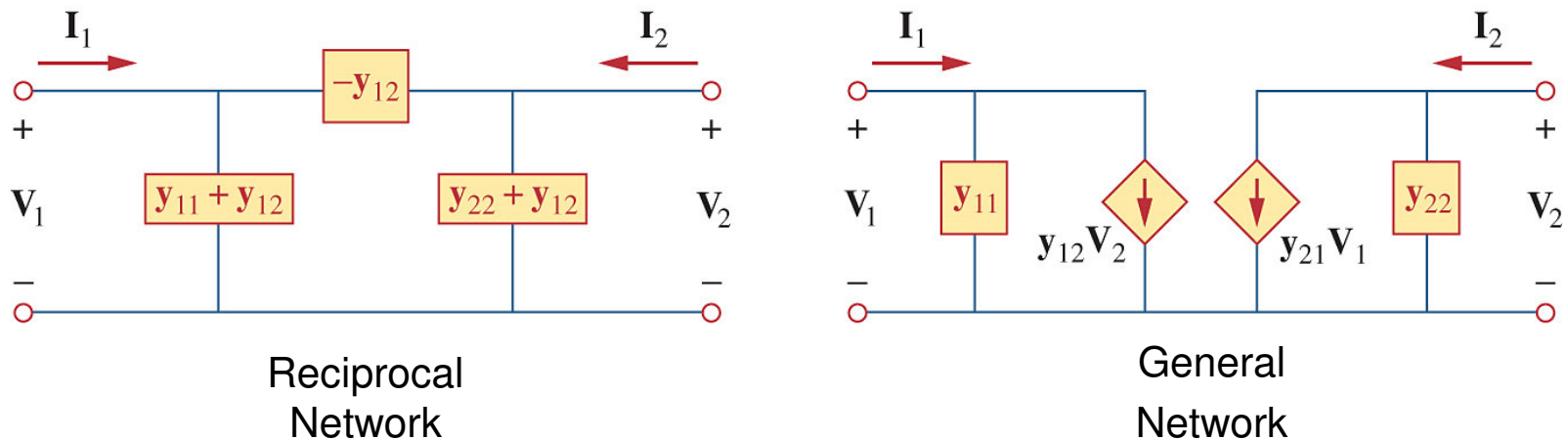


- A reciprocal network ($y_{12} = y_{21}$) can be replaced by the Pi-network in figure (a).
- If not reciprocal, the network in figure (b) is the Pi-equivalent.

19.3 Admittance Parameters (4)

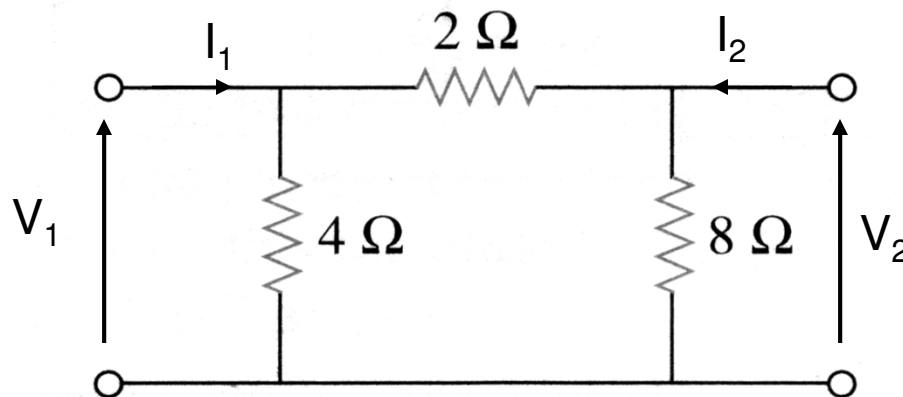Example 19.3

Determine the y-parameters of the following circuit.



Answer: $y = \begin{bmatrix} 0.75 & -0.5 \\ -0.5 & 0.625 \end{bmatrix} \text{S}$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$




$$y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \text{S}$$

19.3 Admittance Parameters (5)

Practice Problem 19.3

Practice Problem 19.3

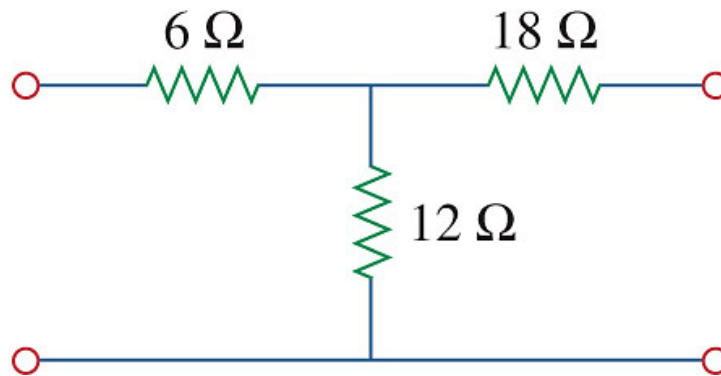Determine the y-parameters of the following circuit.



$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$



$$y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \text{S}$$

Answer: $y = \begin{bmatrix} 75.77 & -30.3 \\ -30.3 & 45.47 \end{bmatrix} \text{mS}$

19.3 Admittance Parameters (6)

Practice Problem 19.3

Practice Problem 19.3 (Solution)

- Short the output
- Put a 1 volt source at input
- Find I_1 and I_2

$$y_{11} = \frac{I_1}{(1)} \bigg|_{V_2=0} \quad \text{and} \quad y_{21} = \frac{I_2}{(1)} \bigg|_{V_2=0}$$

Find Input Impedance

$$Z_{in} = 6 + 12 \parallel 18 = 13.2$$

$$I_1 = \frac{V_1}{Z_{in}} = \frac{1}{13.2} = 0.07576$$


$$y_{11} = 0.07576$$

Similarly at Output

$$Z_{out} = 18 + 6 \parallel 12 = 22$$

$$I_2 = \frac{V_2}{Z_{in}} = \frac{1}{22} = 0.04545$$

$$y_{22} = 0.04545$$

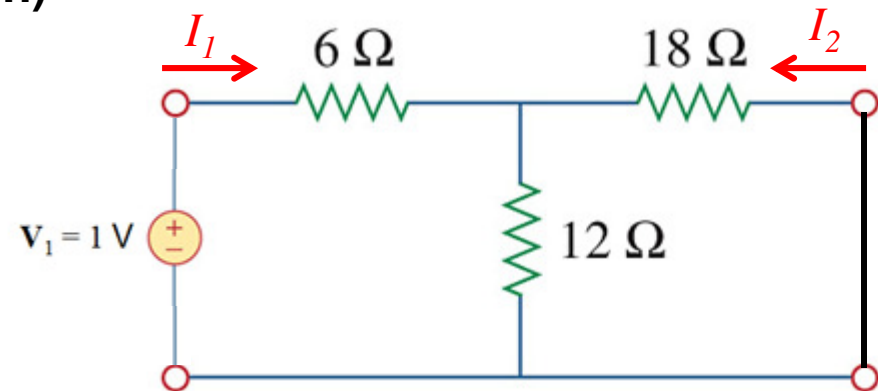

Find I_2 from current divider equation

$$I_2 = \frac{-12}{12 + 18} I_1$$

$$I_2 = (-0.4)0.07576 = -0.0303$$

$$y_{21} = -0.0303$$

$$y_{12} = y_{21} = -0.0303$$


Reciprocal Network

19.3 Admittance Parameters (7)

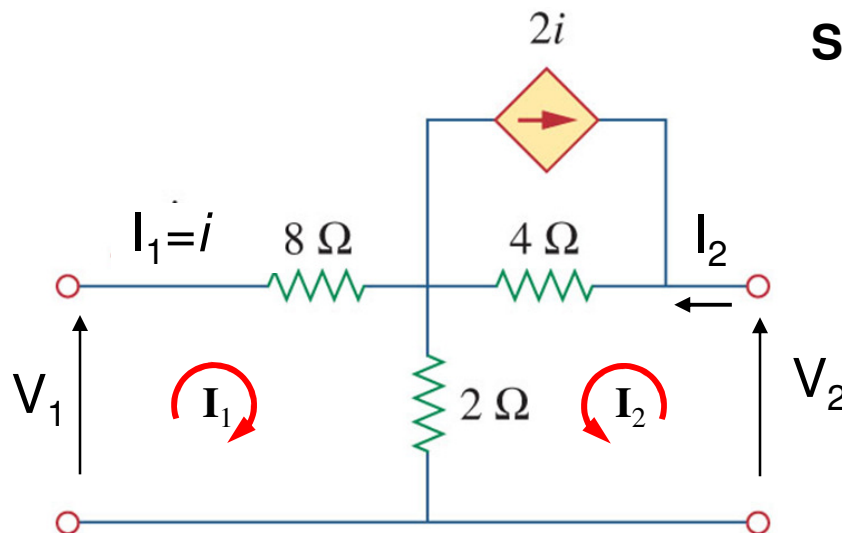Example 19.4

Determine the y-parameters of the following circuit.

$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$



Answer: $y = \begin{bmatrix} 0.15 & -0.05 \\ -0.25 & 0.25 \end{bmatrix} \text{S}$

Note: Sometimes two port parameters will fall out directly from mesh equations.

Solution: Apply KVL

Mesh I_1 : $V_1 = 8I_1 + 2(I_1 + I_2)$

$$V_1 = 10I_1 + 2I_2$$

Mesh I_2 : $V_2 = 4(2i + I_2) + 2(I_1 + I_2)$

$$V_2 = 8I_1 + 4I_2 + 2I_1 + 2I_2$$

$$V_2 = 10I_1 + 6I_2$$

Subtract #1 from #2:

$$V_2 - V_1 = 0 + 4I_2$$

$$I_2 = -0.25V_1 + 0.25V_2$$

Substitute back into #1

$$V_1 = 10I_1 - 0.5V_1 + 0.5V_2$$

$$10I_1 = 1.5V_1 - 0.5V_2$$


$$I_1 = 0.15V_1 - 0.05V_2$$

19.3 Admittance Parameters (8)

Practice problem 19.4

Practice Problem 19.4

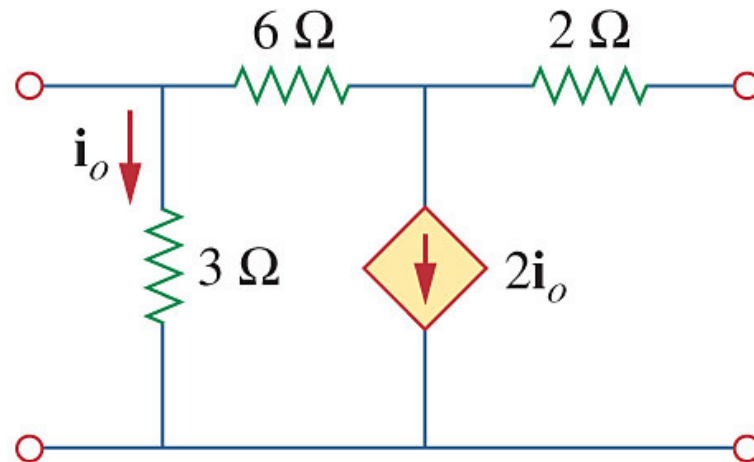Determine the y-parameters of the following circuit.



Answer: $y = \begin{bmatrix} 0.625 & -0.125 \\ 0.375 & 0.125 \end{bmatrix} S$

19.3 Admittance Parameters (9)

Practice problem 19.4

Practice Problem 19.4 (Solution)

- Short the output
- Put a 1 volt source at input
- Find I_1 and I_2

First find i_o :

$$i_o = \frac{1}{3}$$

Dependent current source is then $2/3$, find I_1 by repetitive source transformations of the dependant current source


$$I_1 = 0.625 \Rightarrow y_{11} = 0.625$$

Next find current across $6\ \Omega$ resistor $I_{6\Omega}$:

$$I_{6\Omega} = 0.625 - \frac{1}{3}$$

$$I_2 + I_{6\Omega} = 2i_o$$
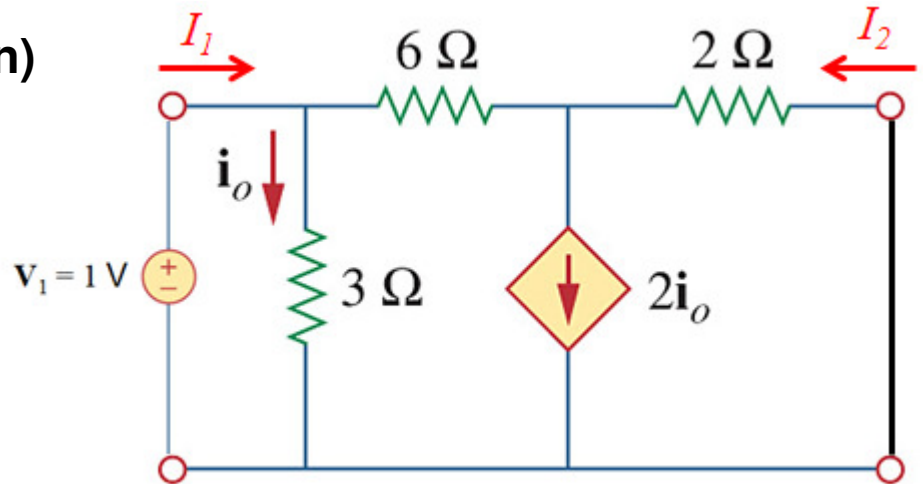
$$I_2 = 2i_o - I_{6\Omega} = \frac{2}{3} - \left(0.625 - \frac{1}{3}\right) = 0.375 \Rightarrow y_{12} = 0.375$$



Z and Y Parameters Comparison

Z-Parameters


$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

- **Open** one port ($I_1=0$ or $I_2=0$)
- Connect a source to the other port
- Solve to find z-parameters

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

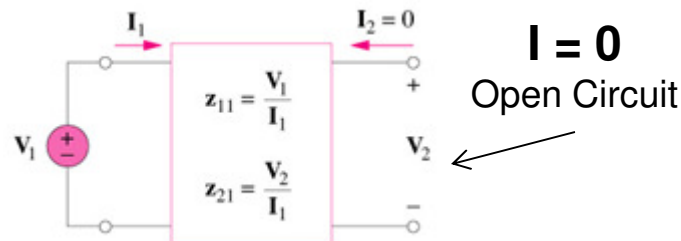

Y-Parameters


$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

- **Short** one port ($V_1=0$ or $V_2=0$)
- Connect a source to the other port
- Solve to find y-parameters

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

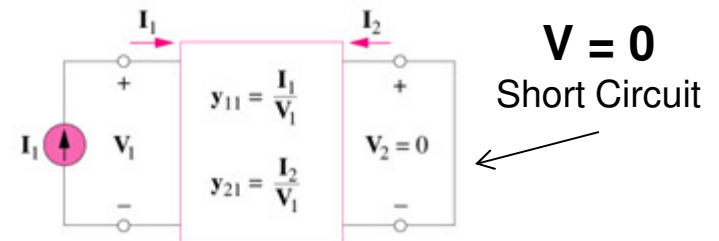


Z and Y parameters

Alternative method (1 Amp / 1 Volt sources)

Z-Parameters

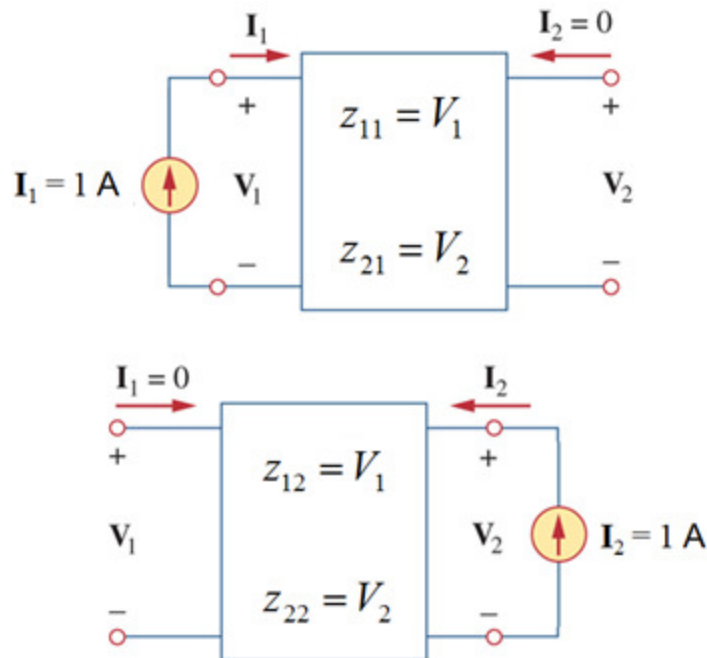
- Open circuit one port
- Put a 1 Amp current source at other port
- Resulting voltages are the z-parameters



$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

Y-Parameters

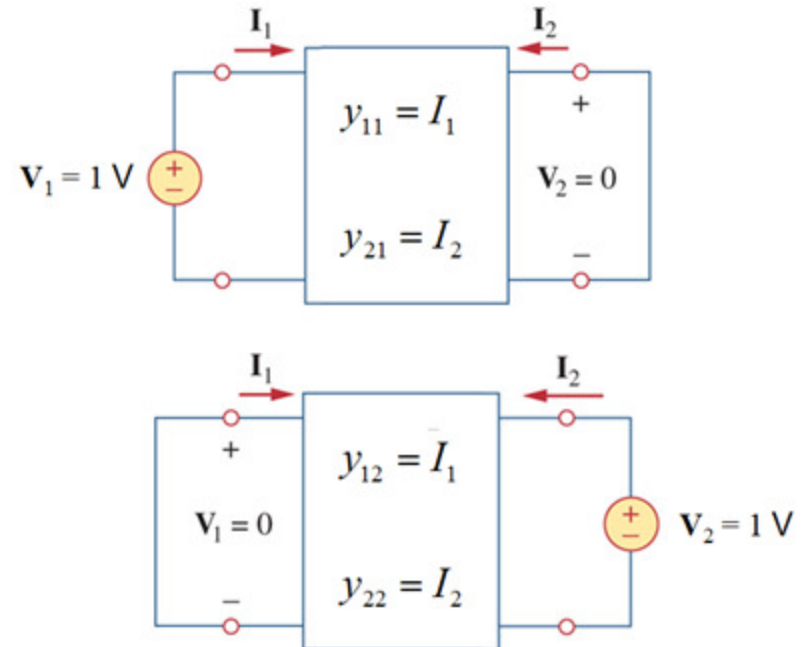
- Short circuit one port
- Put a 1 Volt voltage source at other port
- Resulting current are the y-parameters



$$\begin{aligned} I_1 &= y_{11}V_1 + y_{12}V_2 \\ I_2 &= y_{21}V_1 + y_{22}V_2 \end{aligned}$$

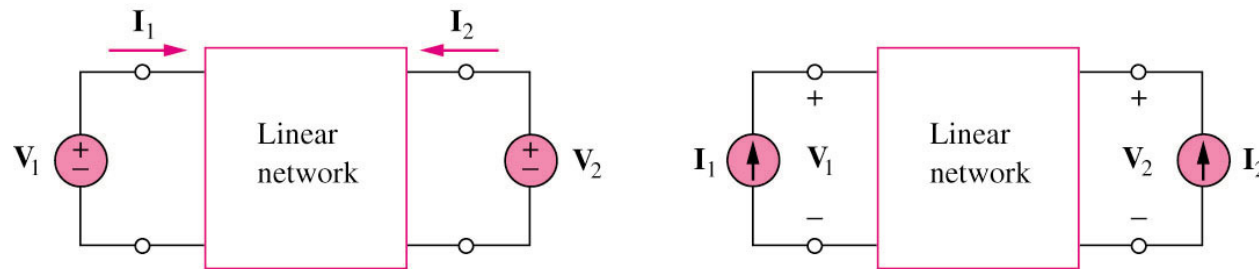19.4 Hybrid Parameters (1)

- The z and y parameters of a two-port network do not always exist. Therefore, there is a need to develop another set of parameters based on making V_1 and I_2 the dependent variables.



Assume no independent source in the network

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$




$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [h] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

where the **h** terms are called the hybrid parameters, or simply h parameters.

- Hybrid parameters are very useful for describing electronic devices such as transistors because it is much easier to measure the h parameters of these devices than to measure their z or y parameters.
- The ideal transformer can also be described by h parameters.

19.4 Hybrid Parameters (2)

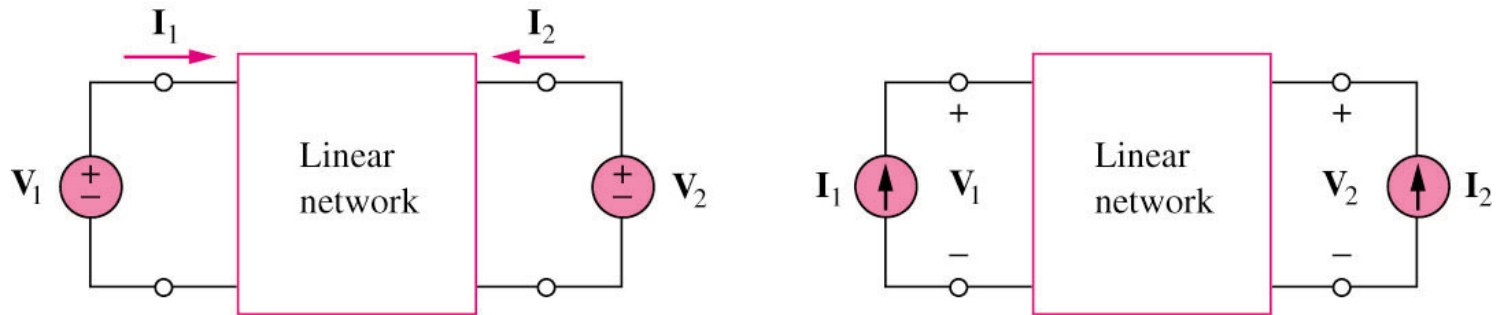

Assume no independent source in the network

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

h_{11} = short-circuit
input impedance (Ω)

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

h_{21} = short-circuit
forward current gain

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$


h_{12} = open-circuit
reverse voltage-gain

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

h_{22} = open-circuit
output admittance (S)


- Note that the h parameters represent an impedance, voltage gain, current gain, and admittance, thereby the term hybrid parameters.
- For reciprocal network, $h_{12} = -h_{21}$

19.4 Hybrid Parameters (3)

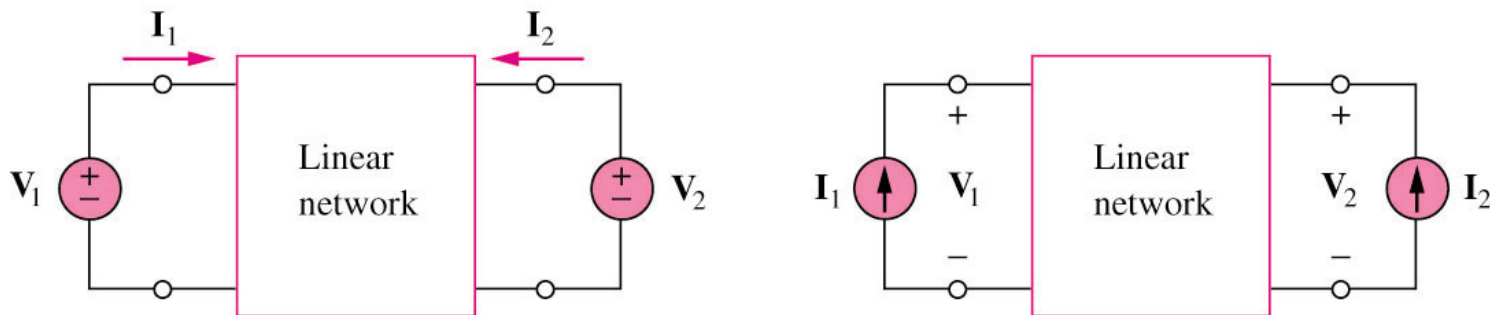

Assume no independent source in the network


Hybrid model of a two-port network:

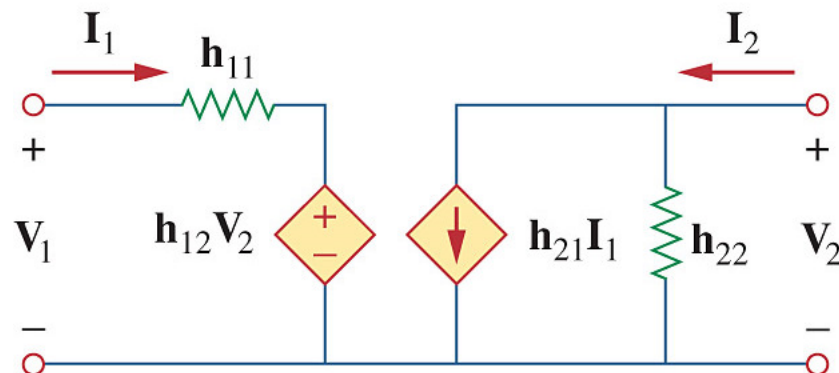

19.4 Hybrid Parameters (4)

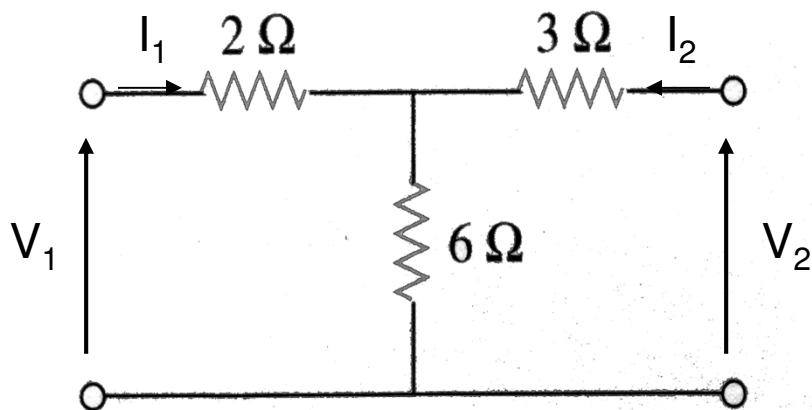Example 19.5:

Determine the h-parameters of the following circuit.



Answer:

$$h = \begin{bmatrix} 4\Omega & \frac{2}{3} \\ -\frac{2}{3} & \frac{1}{9}S \end{bmatrix}$$

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{and} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{and} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$




$$h = \begin{bmatrix} h_{11}\Omega & h_{12} \\ h_{21} & h_{22}S \end{bmatrix}$$

19.4 Hybrid Parameters (5)

Practice Problem 19.5:

Determine the h-parameters of the following circuit.

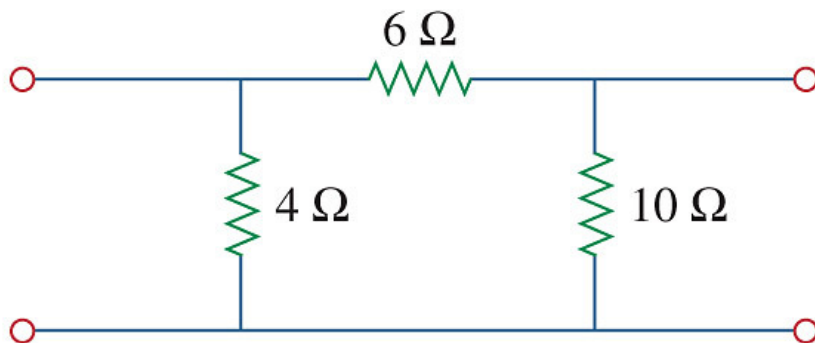Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{and} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{and} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$



Answer:

$$h = \begin{bmatrix} 2.4\Omega & 0.4 \\ -0.4 & 0.2S \end{bmatrix}$$

$$h = \begin{bmatrix} h_{11}\Omega & h_{12} \\ h_{21} & h_{22}S \end{bmatrix}$$

19.9.1 Transistor Circuits (1)

Hybrid Parameters

- H-parameters are often used to model transistor circuits
- The h-parameters vary depending on biasing conditions
- Parameters are given different subscripts:
 - $h_{11} \rightarrow h_{ie}$ = Base input impedance
 - $h_{12} \rightarrow h_{re}$ = Reverse voltage feedback ratio
 - $h_{21} \rightarrow h_{fe}$ = Base-collector current gain
 - $h_{22} \rightarrow h_{oe}$ = Output admittance

Example 2N3904

2N3903 2N3904

h PARAMETERS
($V_{CE} = 10$ Vdc, $f = 1.0$ kHz, $T_A = 25^\circ\text{C}$)

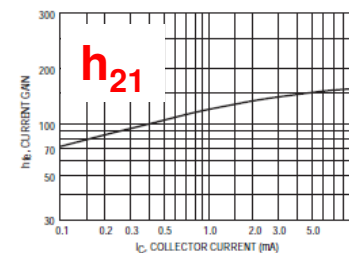
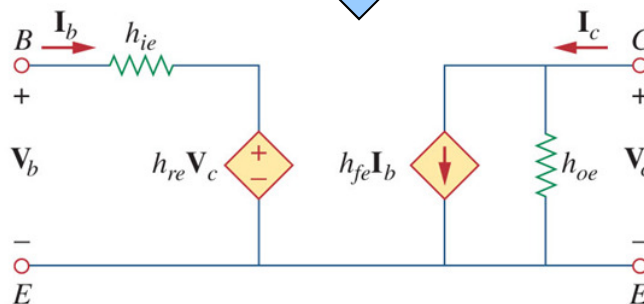
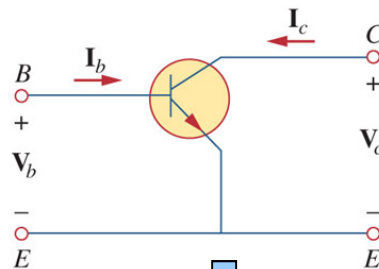


Figure 11. Current Gain

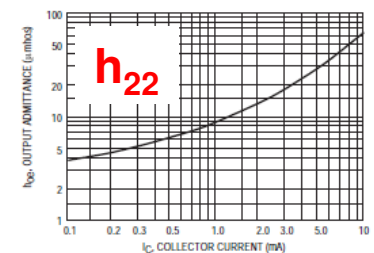


Figure 12. Output Admittance

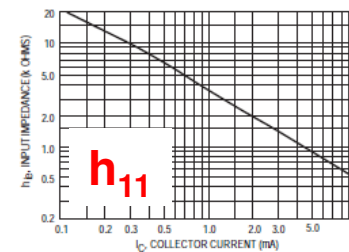


Figure 13. Input Impedance


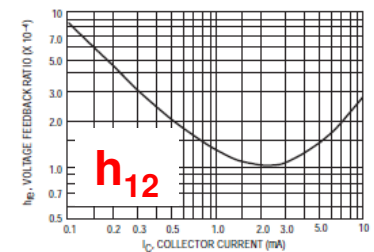


Figure 14. Voltage Feedback Ratio

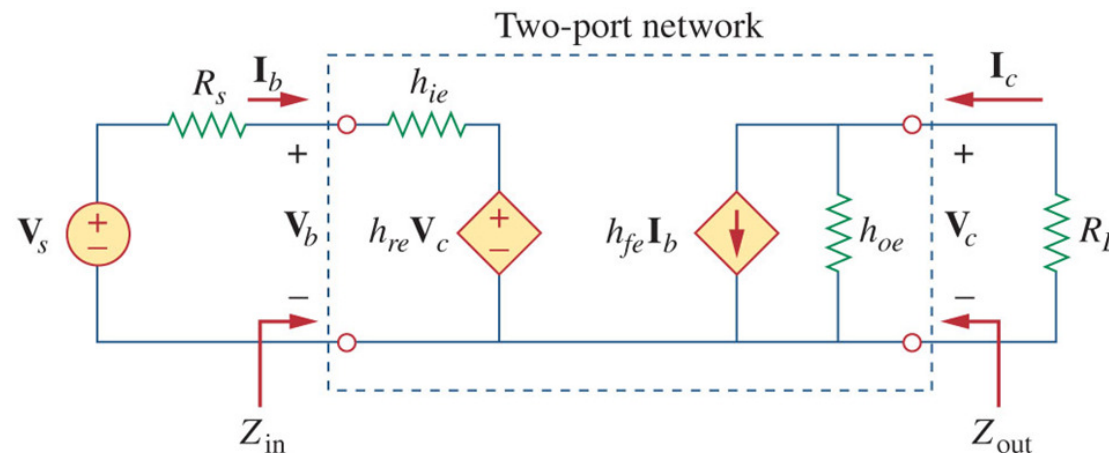19.9.1 Transistor Circuits (2)

Hybrid Parameters

- H parameters are often found in manufacturers spec sheets
- Provide ability to calculate the exact voltage gain, input impedance, and output impedance of the transistor.



Input Impedance

$$Z_{in} = \frac{V_b}{I_b} = h_{ie} - \frac{h_{re} h_{fe} R_L}{1 + h_{oe} R_L}$$

Current Gain

$$A_i = \frac{I_c}{I_b} = \frac{h_{fe}}{1 + h_{oe} R_L}$$


Output Impedance

$$Z_{out} = \frac{V_c}{I_c} \bigg|_{V_s=0} = \frac{R_s + h_{ie}}{(R_s + h_{ie})h_{oe} - h_{re} h_{fe}}$$

Voltage Gain

$$A_v = \frac{V_c}{V_b} = \frac{-h_{fe} R_L}{h_{ie} + (h_{ie} h_{oe} - h_{re} h_{fe}) R_L}$$

19.5 Transmission Parameters (1)

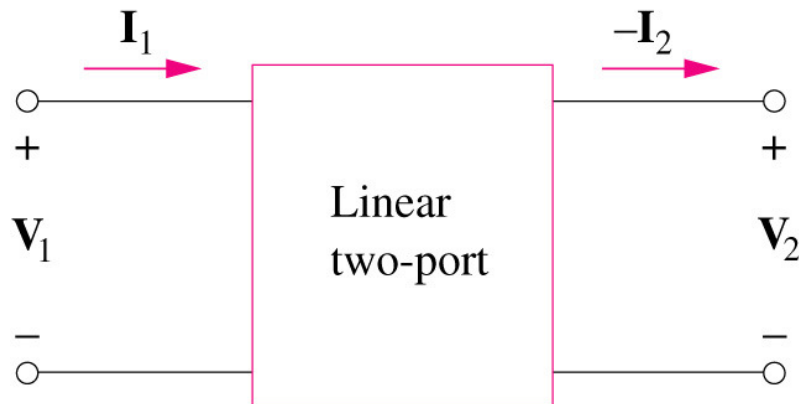

**Assume no
independent source
in the network**

$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = [T] \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

where the **T** terms are called the transmission parameters, or simply **T** or ABCD parameters.

•Note that $-I_2$ is used since the current is considered to be leaving the network. It is logical to think of I_2 as leaving the two-port; this is customary convention in the power industry.

19.5 Transmission Parameters (2)

- These two-port transmission parameters provide a measure of how a circuit transmits voltage and current from a source to a load.
- They are useful in the analysis of transmission lines and are therefore called transmission parameters.
- They are also known as ABCD parameters and are used in the design of telephone systems, microwave networks, and radars.

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

A=open-circuit
voltage ratio

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

C= open-circuit
transfer admittance
(S)

$$B = - \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

B= negative short-
circuit transfer
impedance (Ω)

$$D = - \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

D=negative short-
circuit current ratio

19.5 Transmission Parameters (3)

Solving for Transmission Parameters

- To find the transmission parameters, analyze the circuit as follows:
- Perform the analysis with the output Open Circuited ($I_2=0$)

$$\begin{array}{l} V_1 = AV_2 - \cancel{BI_2} \\ I_1 = CV_2 - \cancel{DI_2} \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} V_1 = AV_2 \\ I_1 = CV_2 \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} A = \frac{V_1}{V_2} \\ C = \frac{I_1}{V_2} \end{array}$$


- Perform the analysis with the output Short Circuited ($V_2=0$)

$$\begin{array}{l} V_1 = \cancel{AV_2} - BI_2 \\ I_1 = \cancel{CV_2} - DI_2 \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} V_1 = -BI_2 \\ I_1 = -DI_2 \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} B = -\frac{V_1}{I_2} \\ D = -\frac{I_1}{I_2} \end{array}$$

19.5 Transmission Parameters (4)

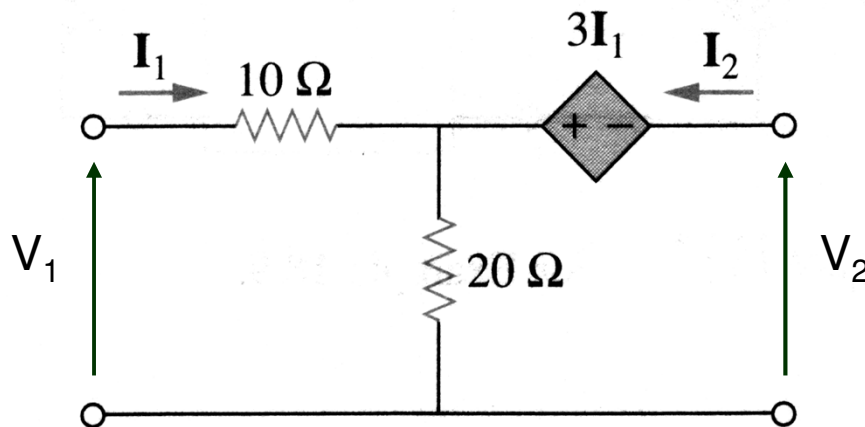Example 19.8

Determine the T-parameters of the following circuit.



Answer:

$$T = \begin{bmatrix} 1.765 & 15.294\Omega \\ 0.059S & 1.176 \end{bmatrix}$$

$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$

Apply KVL

$$\begin{aligned} V_1 &= 10I_1 + 20(I_1 + I_2) \\ V_2 &= -3I_1 + 20(I_1 + I_2) \end{aligned}$$



$$\begin{aligned} V_1 &= \frac{30}{17}V_2 - \frac{260}{17}I_2 \\ I_1 &= \frac{1}{17}V_2 - \frac{20}{17}I_2 \end{aligned}$$

19.5 Transmission Parameters (5)

Example 19.8

From KVL:

$$V_1 = 10I_1 + 20(I_1 + I_2) = 30I_1 + 20I_2$$

$$V_2 = -3I_1 + 20(I_1 + I_2) = 17I_1 + 20I_2$$


If we “open circuit” the output we get:

$$V_1 = 30I_1 + 20\overset{0}{I_2}$$

$$V_1 = 30I_1$$

$$V_2 = 17I_1 + 20\overset{0}{I_2}$$

$$V_2 = 17I_1$$

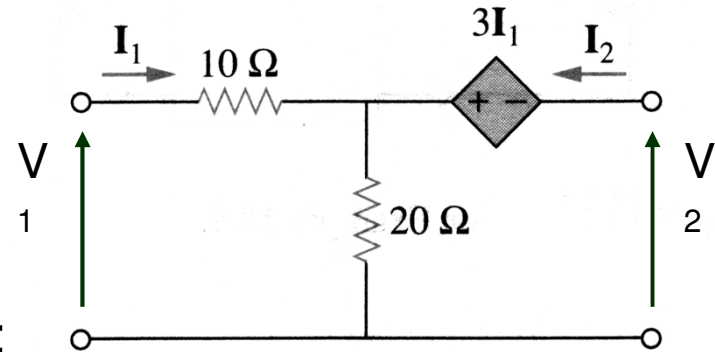

$$A = \frac{V_1}{V_2} = \frac{30I_1}{17I_1} = \frac{30}{17} = 1.765$$

$$C = \frac{1}{17} = 0.0588$$

If we “short circuit” the output we get:

$$V_1 = 30I_1 + 20I_2$$

$$\overset{0}{V_2} = 17I_1 + 20I_2$$

$$V_1 = 30I_1 + 20I_2$$

$$0 = 17I_1 + 20I_2$$

$$V_1 = 30\left(\frac{-20}{17}\right)I_2 + 20I_2$$


$$I_1 = \frac{-20}{17}I_2$$

$$B = -\frac{V_1}{I_2} = -\frac{(30\left(\frac{-20}{17}\right) + 20)I_2}{I_2} = 15.29$$

$$D = -\frac{I_1}{I_2} = \frac{20}{17} = 1.176$$

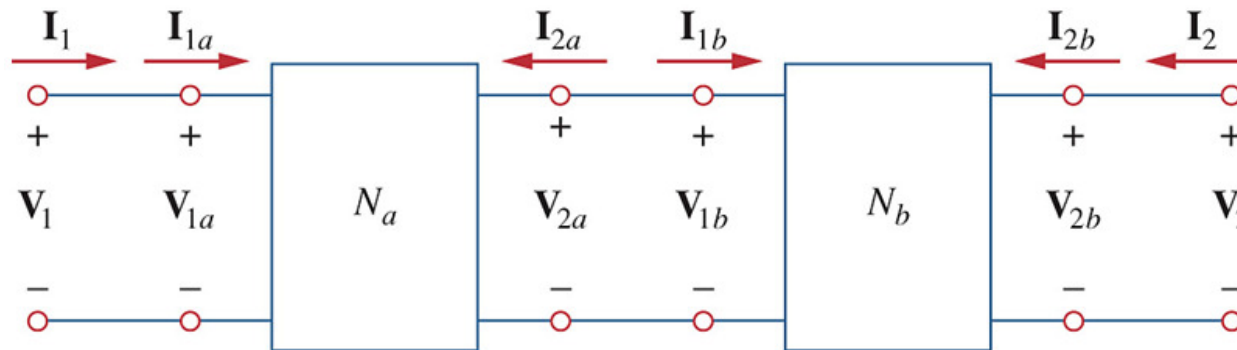19.5 Transmission Parameters (6)

- Transmission Parameters can be cascaded with the result found through simple matrix multiplication



$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$-I_{2a} = I_{1b}$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

19.5 Transmission Parameters (7)

Properties: Building Block Circuits

Consider the following
simple circuits

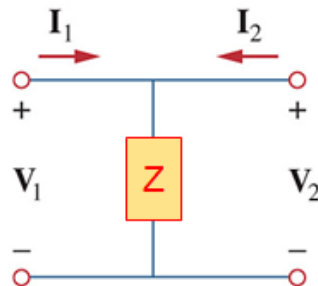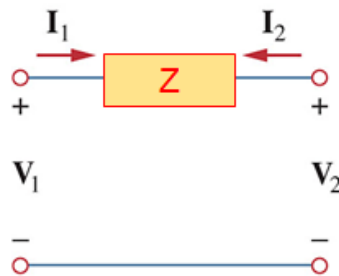


We can find their T
Parameters to be:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{Z} & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Note, following
is equivalent

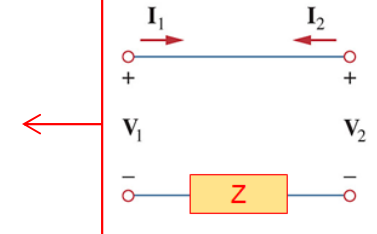

19.5 Transmission Parameters (8)

Properties: Building Block Circuits

- We can use this to construct the following “building block T parameters” to find the T parameters for any ladder type circuit.

$$\begin{bmatrix} 1 & R \\ 0 & 1 \end{bmatrix}$$




$$\begin{bmatrix} 1 & \frac{1}{sC} \\ 0 & 1 \end{bmatrix}$$




$$\begin{bmatrix} 1 & sL \\ 0 & 1 \end{bmatrix}$$



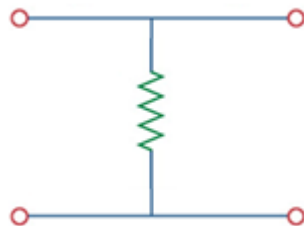
$$\begin{bmatrix} 1 & 0 \\ \frac{1}{R} & 1 \end{bmatrix}$$


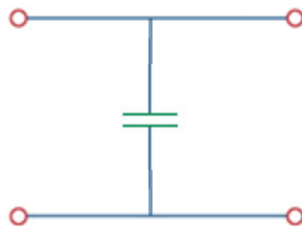
$$\begin{bmatrix} 1 & 0 \\ sC & 1 \end{bmatrix}$$


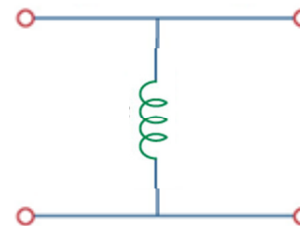
$$\begin{bmatrix} 1 & 0 \\ \frac{1}{sL} & 1 \end{bmatrix}$$



19.5 Transmission Parameters (9)

Properties: Transfer function / Thevenin Equivalent

- The “A” parameter can be used to provide the inverse of the voltage Transfer Function $H(s)$.

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

- Parameters “A” and “B” can be used to find a relationship between the Open Circuit Voltage (V_2) and the Short Circuit Current ($-I_2$).
- We can use this to find the parameters for the Thevenin Equivalent Circuit.


$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{V_1}{V_{oc}}$$

$$V_{Th} = V_{oc} = \frac{V_1}{A}$$


$$Z_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{B}{A}$$

$$B = - \left. \frac{V_1}{I_2} \right|_{V_2=0} = \frac{V_1}{I_{sc}}$$

$$I_N = I_{sc} = \frac{V_1}{B}$$

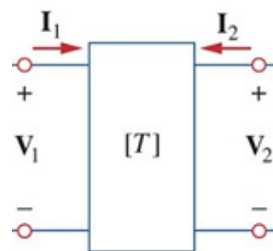

$$V_{Th} = \frac{V_1}{A}$$

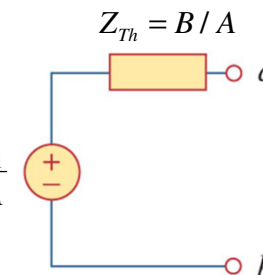


19.5 Transmission Parameters (10)

Transfer Function - Example

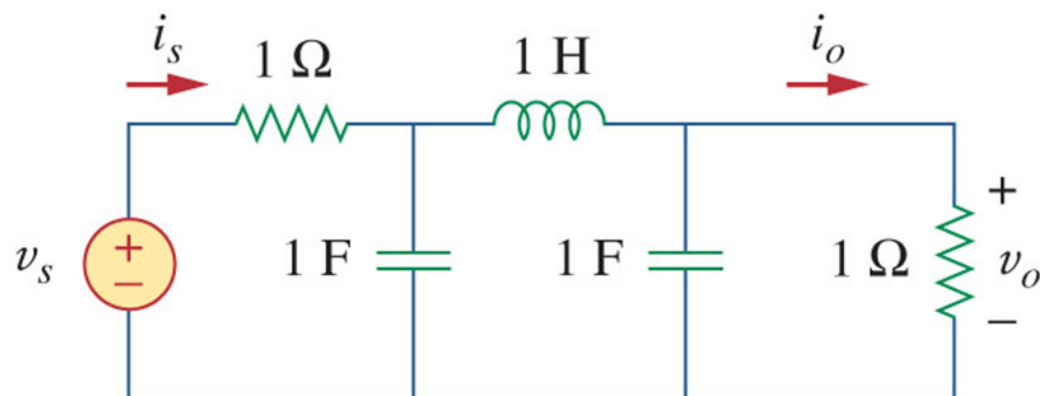Problem 16.80(a)

Find the transfer function $V_o(s)/V_s(s)$ for the following circuit



Answer:


$$H(s) = \frac{1}{s^3 + 2s^2 + 3s + 2}$$

19.5 Transmission Parameters (11)

Transfer Function - Example

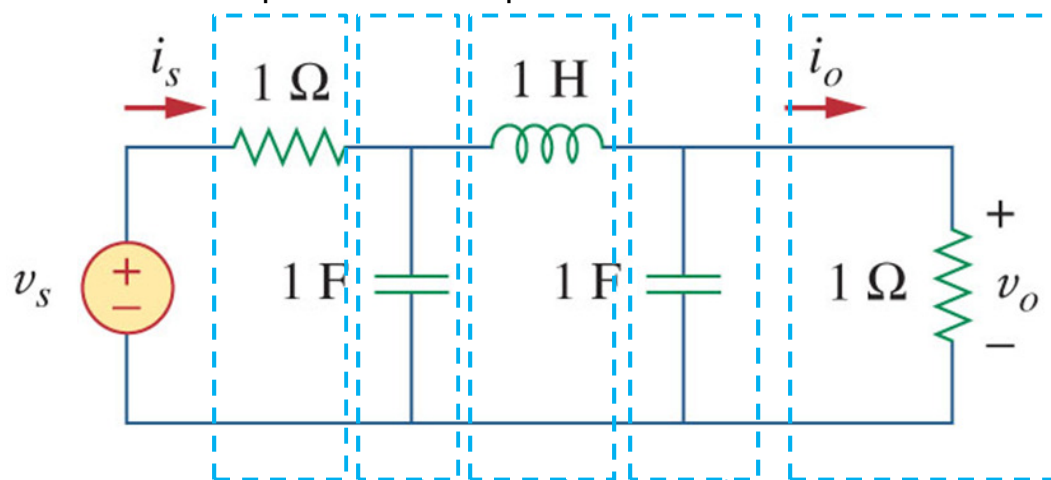Problem 16.80(a) Solution:

- Break up the circuit into a series of cascaded series and shunt components
- Find the composite "T" parameters for the circuit
- Use the relationship between the parameter "A" and the Transfer function



$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

19.5 Transmission Parameters (12)

Transfer Function - Example

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix}$$

Finding the
combined T-matrix

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ (s+1) & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1+s(s+1) & s \\ (s+1) & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1+s(s+1) & s \\ s+s^2(s+1)+(s+1) & s^2 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} s^2+s+1 & s \\ s^3+s^2+2s+1 & s^2 \end{bmatrix}$$

$$\begin{bmatrix} s^3+2s^2+3s+2 & s+s^2 \\ s^3+s^2+2s+1 & s^2 \end{bmatrix}$$

The transfer function can be found
directly from the Transmission
Parameter "A" !

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

$$H(s) = \frac{1}{s^3+2s^2+3s+2}$$


19.5 Transmission Parameters (13)

Example 19.9

The ABCD parameters of the two-port network at right are




$$\mathbf{T} = \begin{bmatrix} 4 & 20 \, \Omega \\ 0.1 \text{ S} & 2 \end{bmatrix}$$

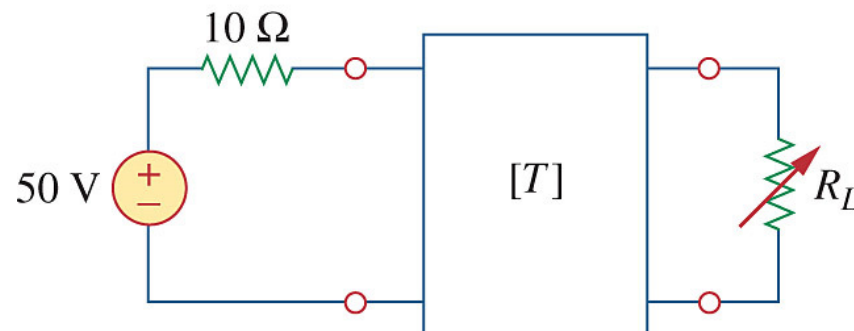Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



The output port is connected to a variable load for maximum power transfer. Find R_L and the maximum power transferred.

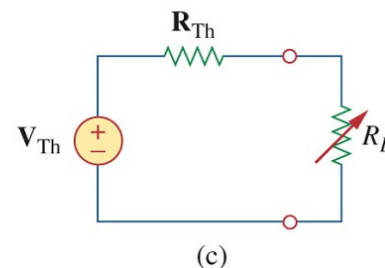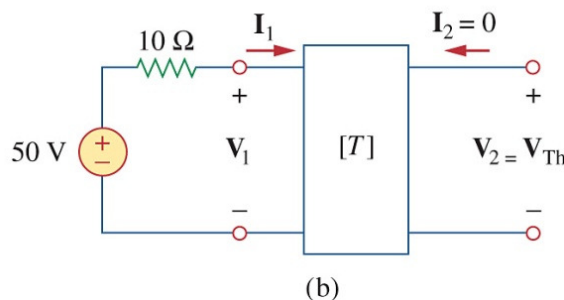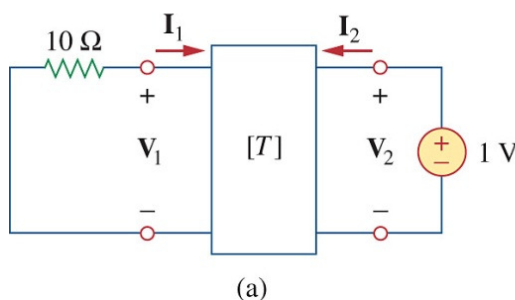Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Answer: $V_{TH} = 10 \text{ V}$; $R_L = 8 \Omega$; $P_m = 3.125 \text{ W}$.

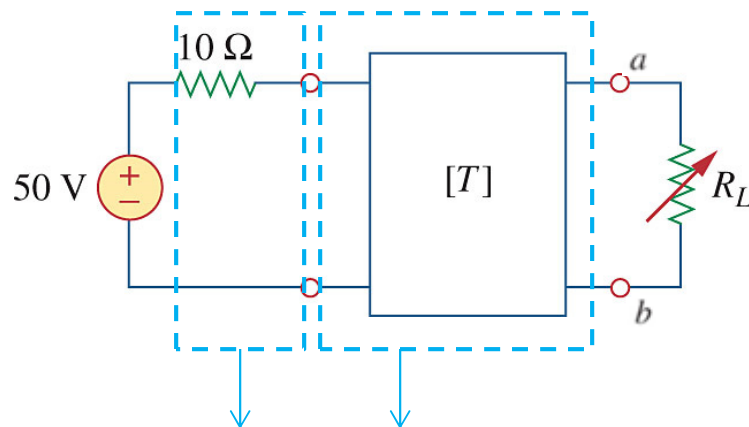19.5 Transmission Parameters (14)


Solution: Example 19.9

- Cascade the Series Resistor with the network
- Find the composite "T" parameters for the circuit
- Use the relationships to find V_{Th} and Z_{Th}



$$[T'] = \begin{bmatrix} 1 & 10 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 4 & 20 \\ 0.1 & 2 \end{bmatrix} = \begin{bmatrix} 5 & 40 \\ 0.1 & 2 \end{bmatrix}$$

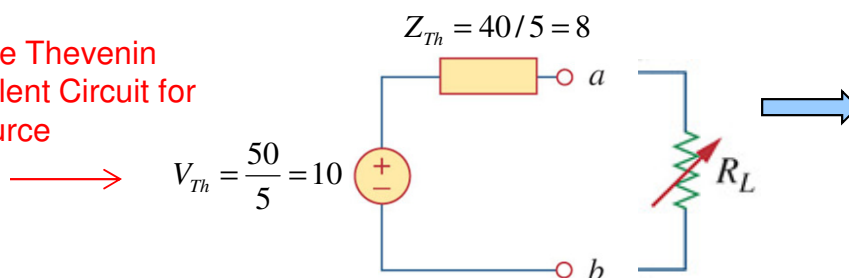Find the Thevenin
Equivalent Circuit for
the source



For Max Power Transfer

$$R_L = Z_{Th} = 8 \Omega$$

$$P_{\max} = I^2 R_L$$


$$P_{\max} = \left(\frac{V_{Th}}{R_L + Z_{Th}} \right)^2 R_L$$

$$P_{\max} = \left(\frac{10}{16} \right)^2 8 = 3.125 \text{ W}$$

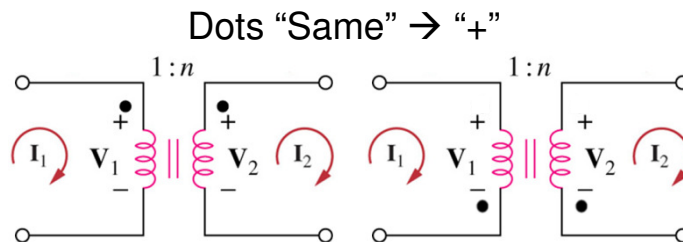19.5 Transmission Parameters (15)

Properties: Building Block Circuits – Ideal Transformer

- We can also use these “building blocks” to model ideal transformers. Remember from Chapter 13




$$V_2 = nV_1$$

$$I_2 = \frac{I_1}{n}$$


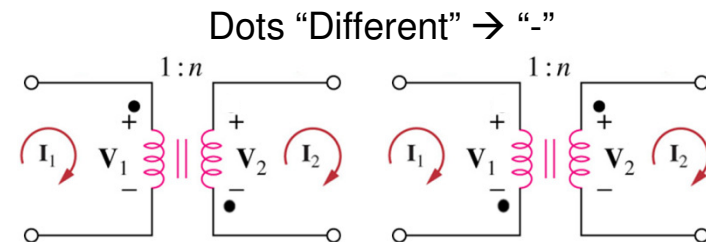
$$\begin{bmatrix} \frac{1}{n} & 0 \\ 0 & n \end{bmatrix}$$



$$V_2 = -nV_1$$

$$I_2 = -\frac{I_1}{n}$$



$$\begin{bmatrix} -\frac{1}{n} & 0 \\ 0 & -n \end{bmatrix}$$


T - parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

19.5 Transmission Parameters (16)

Example 13.8 Revisited

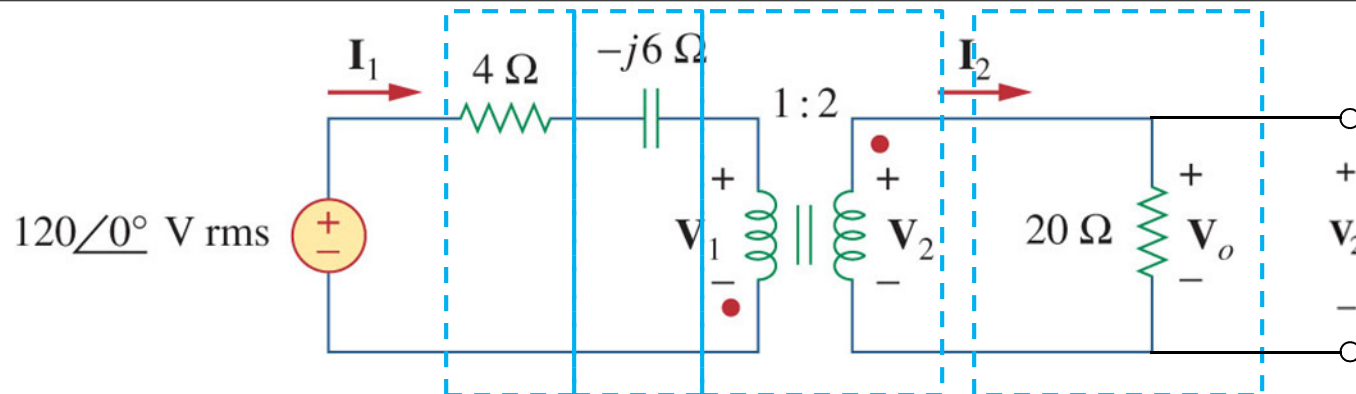

Cascaded T parameters →

$$\begin{bmatrix} 1 & 4 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & -j6 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} -\frac{1}{2} & 0 \\ 0 & -2 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0.05 & 1 \end{bmatrix}$$

a b c d

Using MATLAB: →

```
>> T=a*b*c*d


T =

-0.9000 + 0.6000i -8.0000 + 12.0000i
-0.1000 + 0.0000i -2.0000 + 0.0000i
```

$$V_0 = V_2 = \frac{1}{A} V_1 = \left(\frac{1}{-0.9 + 0.6j} \right) (120 \angle 0^\circ) = 110.94 \angle -146.31^\circ \text{ V}$$

19.5 Transmission Parameters (17)

Example 13.8 Revisited

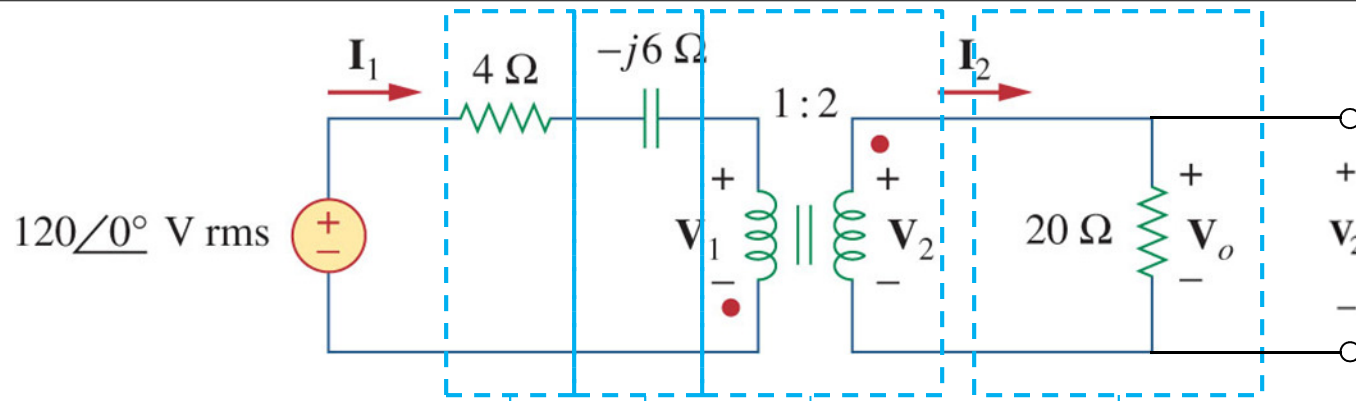


```
>> T=a*b*c*d
T =
-0.9000 + 0.6000i -8.0000 +12.0000i
-0.1000 + 0.0000i -2.0000 + 0.0000i
```

$$I_1 = CV_2 = (-0.1)(110.94\angle -146.31^\circ) = 11.09\angle 33.69^\circ \text{ A}$$

$$I_2 = \frac{V_2}{20} = \frac{(110.94\angle -146.31^\circ)}{20} = 5.55\angle -146.31^\circ \text{ A}$$

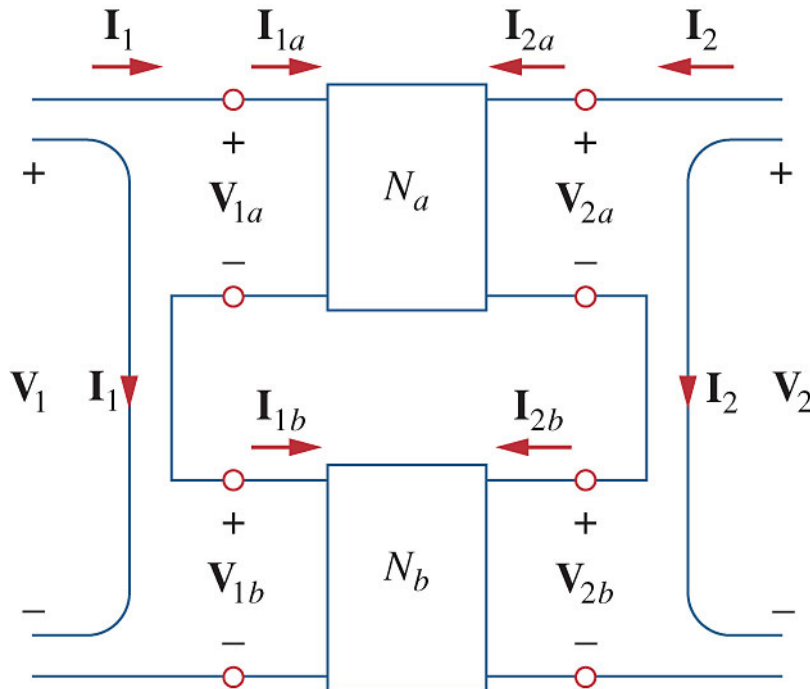19.7 Interconnection of Networks (1)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Series Connection of
two-port networks:

For Impedances; ADD
matrices.

$$Z = Z_a + Z_b$$

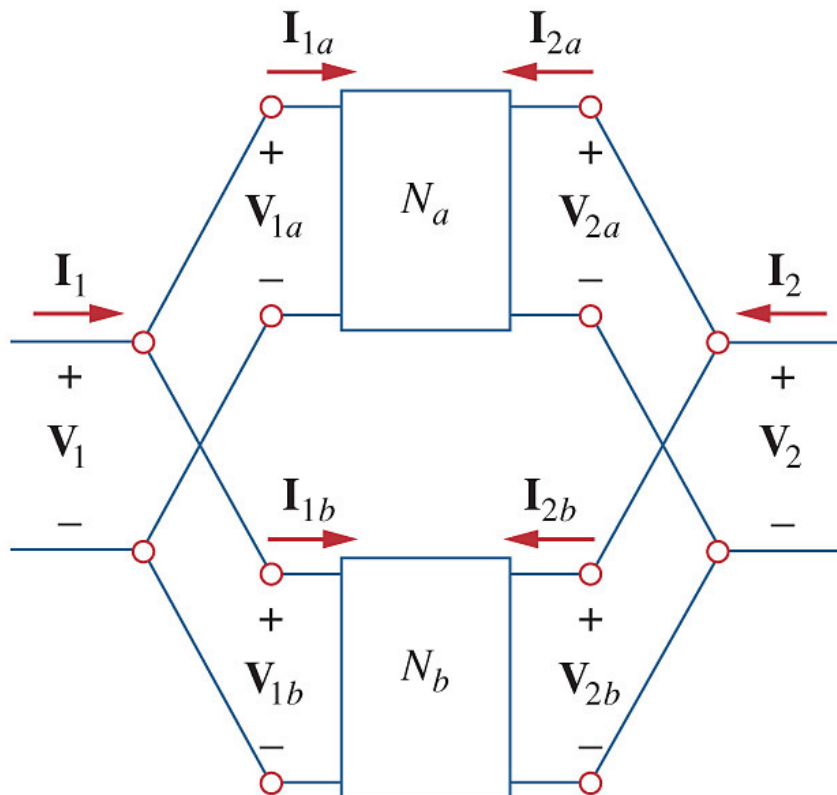19.7 Interconnection of Networks (2)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Parallel Connection of
two-port networks:

For Admittances; ADD
matrices.

$$Y = Y_a + Y_b$$

19.6 Relationships Between Networks

- Use this table to convert between two port parameters

	z		y		h		T	
z	z_{11}	z_{12}	$\frac{y_{22}}{\Delta_y}$	$-\frac{y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$
	z_{21}	z_{22}	$-\frac{y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{C}$	$\frac{D}{C}$
y	$\frac{z_{22}}{\Delta_z}$	$-\frac{z_{12}}{\Delta_z}$	y_{11}	y_{12}	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$	$\frac{D}{B}$	$-\frac{\Delta_T}{B}$
	$-\frac{z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	y_{21}	y_{22}	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$-\frac{1}{B}$	$\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	h_{11}	h_{12}	$\frac{B}{D}$	$\frac{\Delta_T}{D}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	h_{21}	h_{22}	$-\frac{1}{D}$	$\frac{C}{D}$
T	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$-\frac{h_{11}}{h_{21}}$	A	B
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta_y}{y_{21}}$	$-\frac{y_{11}}{y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$-\frac{1}{h_{21}}$	C	D

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21} \quad \Delta_z = z_{11}z_{22} - z_{12}z_{21} \quad \Delta_h = h_{11}h_{22} - h_{12}h_{21} \quad \Delta_T = AD - BC$$

Chapter 19 Review

Z-Parameters

- Parameters:
$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$


- Open circuit the **output** to find z_{11} and z_{21}

$$\begin{aligned} V_1 &= z_{11}I_1 + \cancel{z_{12}I_2}^0 \\ V_2 &= z_{21}I_1 + \cancel{z_{22}I_2}^0 \end{aligned}$$



$$\begin{aligned} V_1 &= z_{11}I_1 \\ V_2 &= z_{21}I_1 \end{aligned}$$

Set $I_1 = 1$ then solve for V_1 and V_2

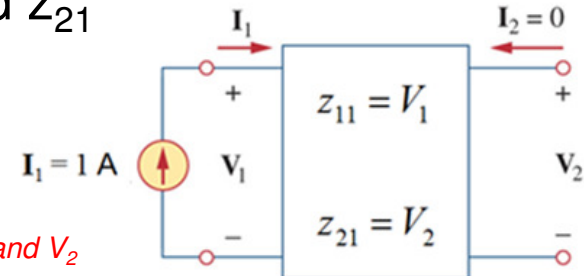


- Open circuit the **input** to find z_{21} and z_{22}

$$\begin{aligned} V_1 &= \cancel{z_{11}I_1}^0 + z_{12}I_2 \\ V_2 &= \cancel{z_{21}I_1}^0 + z_{22}I_2 \end{aligned}$$



$$\begin{aligned} V_1 &= z_{12}I_2 \\ V_2 &= z_{22}I_2 \end{aligned}$$

Set $I_2 = 1$ then solve for V_1 and V_2

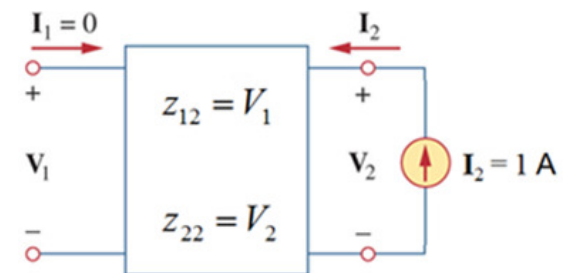


Chapter 19 Review

Z-Parameters (Given a circuit, find Z-parameters)

- Solving problems to find z-parameters:

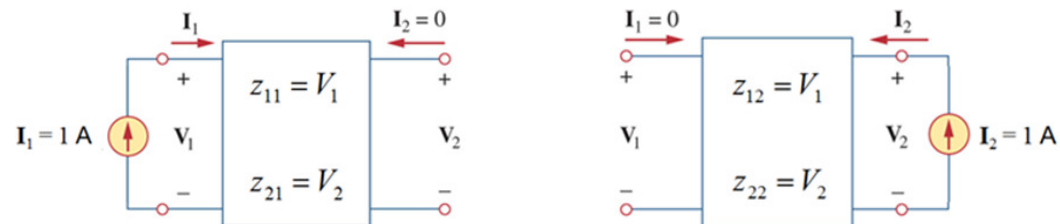1. Refer to definition, apply 1 amp source at input and output with opposite port left open (see previous slide)




2. Sometimes, KVL (mesh current equations) will cause z-parameters to fall right out! :

$$V_1 = 2I_1 + 6(I_1 + I_2) = 8I_1 + 6I_2$$

$$V_2 = 6(I_1 + I_2) + 3I_2 = 6I_1 + 9I_2$$


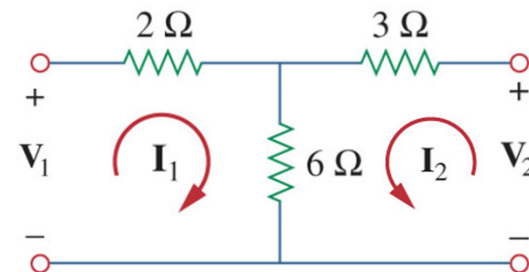
$$\mathbf{z} = \begin{bmatrix} 8 & 6 \\ 6 & 9 \end{bmatrix} \Omega$$




This mesh defined in counter clockwise direction for convenience

Chapter 19 Review


Z-Parameters (Given Z parameters, find circuit parameters)

- If given, z-parameters can use following techniques to find other circuit parameters (V_1 , V_2 , I_1 , I_2 , etc.):

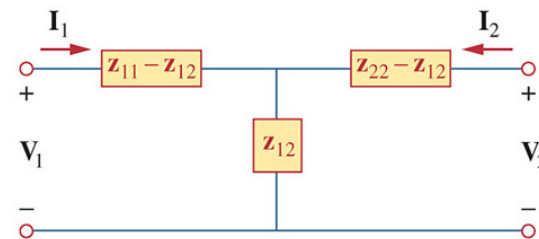1. Apply the model and solve the circuit:



Reciprocal
Network

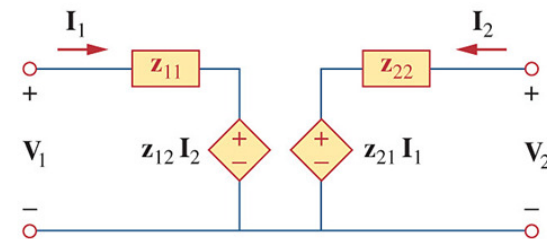

General
Network

2. Substitute the defining equations into your analysis:

Mesh Analysis


$$10 = 5I_1 + V_1 + 10(I_1 + I_2)$$

$$0 = V_2 + 10(I_1 + I_2) + 20I_2$$

Substitute for V_1 and V_2

$$10 = 5I_1 + (12I_1 + 8I_2) + 10(I_1 + I_2)$$
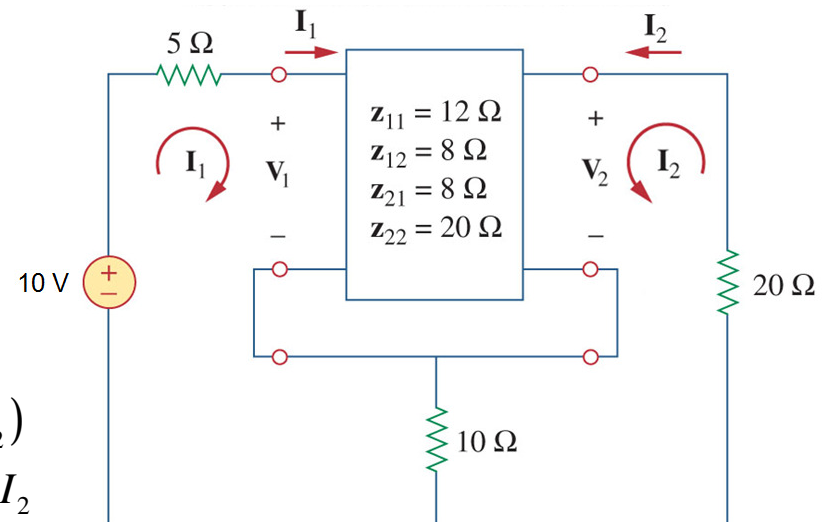
$$0 = (8I_1 + 20I_2) + 10(I_1 + I_2) + 20I_2$$



Chapter 19 Review

Y-Parameters

- Parameters:
$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$


- Short circuit the **output** to find y_{11} and y_{21}

$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} \cancel{V_2}^0 \\ I_2 &= y_{21} V_1 + y_{22} \cancel{V_2}^0 \end{aligned}$$



$$\begin{aligned} I_1 &= y_{11} V_1 \\ I_2 &= y_{21} V_1 \end{aligned}$$

Set $V_1 = 1$ then solve for I_1 and I_2

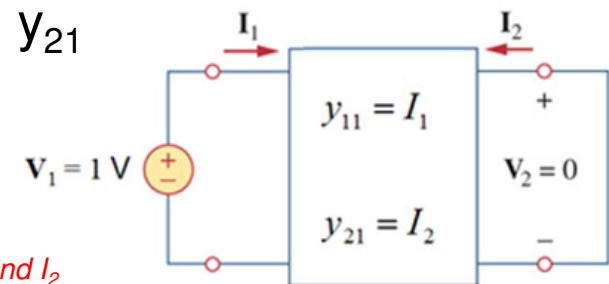


- Short circuit the **input** to find y_{21} and y_{22}

$$\begin{aligned} I_1 &= y_{11} \cancel{V_1}^0 + y_{12} V_2 \\ I_2 &= y_{21} \cancel{V_1}^0 + y_{22} V_2 \end{aligned}$$



$$\begin{aligned} I_1 &= y_{12} V_2 \\ I_2 &= y_{22} V_2 \end{aligned}$$

Set $V_2 = 1$ then solve for I_1 and I_2

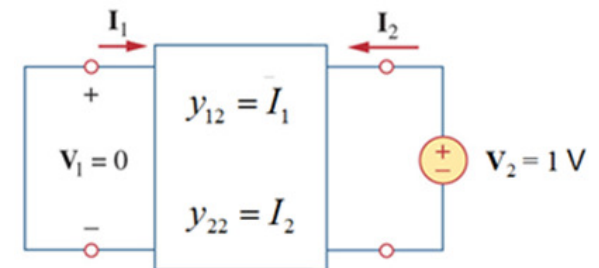


Chapter 19 Review


Y-Parameters (Solving Problems)

- To solve Y-parameter problems, can use these techniques

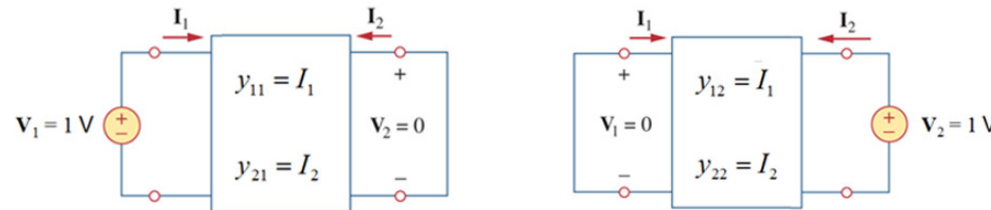1. Apply method from previous slide. Apply 1 Volt source at input and output while shorting opposite port



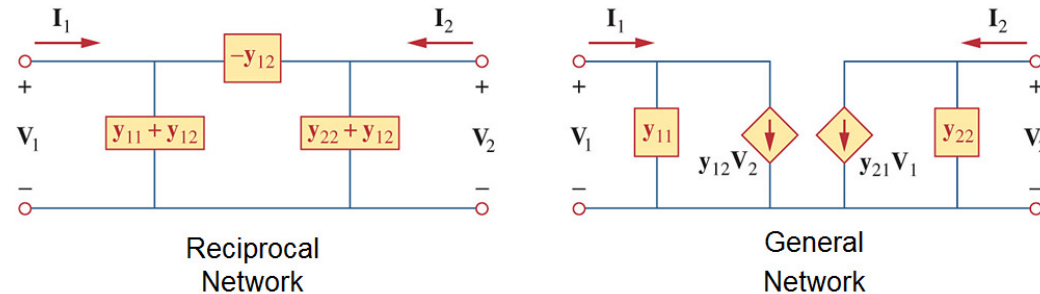2. If given Y parameters can apply the model and solve the circuit:



3. Make it easy on yourself! Use conversions from $Z \rightarrow Y$ or $Y \rightarrow Z$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \left(\frac{1}{\Delta_y} \right) \begin{bmatrix} y_{22} & -y_{12} \\ -y_{21} & y_{11} \end{bmatrix}$$

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21}$$

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \left(\frac{1}{\Delta_z} \right) \begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix}$$

$$\Delta_z = z_{11}z_{22} - z_{12}z_{21}$$

Chapter 19 Review

H-Parameters

- Parameters (hybrid of z and y):

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$


- Short circuit the **output** to find h_{11} and h_{21}

$$\begin{aligned} V_1 &= h_{11}I_1 + \cancel{h_{12}V_2}^0 \\ I_2 &= h_{21}I_1 + \cancel{h_{22}V_2}^0 \end{aligned}$$



$$\begin{aligned} V_1 &= h_{11}I_1 \\ I_2 &= h_{21}I_1 \end{aligned}$$

Set $I_1 = 1$ then solve for V_1 and I_2

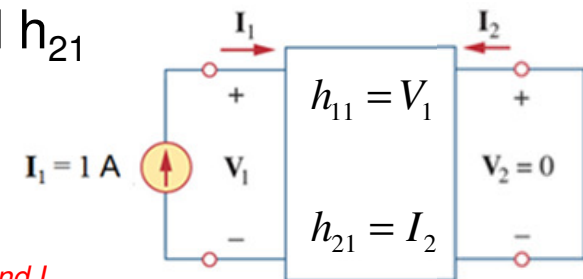


- Open circuit the **input** to find h_{21} and h_{22}

$$\begin{aligned} V_1 &= \cancel{h_{11}I_1}^0 + h_{12}V_2 \\ I_2 &= \cancel{h_{21}I_1}^0 + h_{22}V_2 \end{aligned}$$



$$\begin{aligned} V_1 &= h_{12}V_2 \\ I_2 &= h_{22}V_2 \end{aligned}$$

Set $V_2 = 1$ then solve for V_1 and I_2

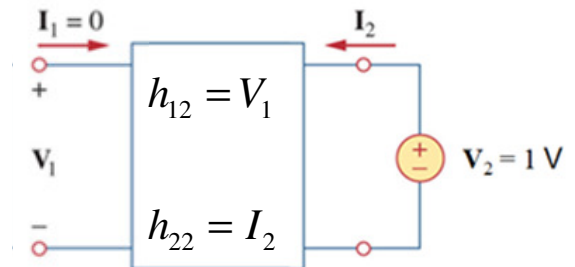


Chapter 19 Review

H-Parameters (Solving Problems)


- To solve H-parameter problems, can use these techniques

1. Apply methods from previous slide.

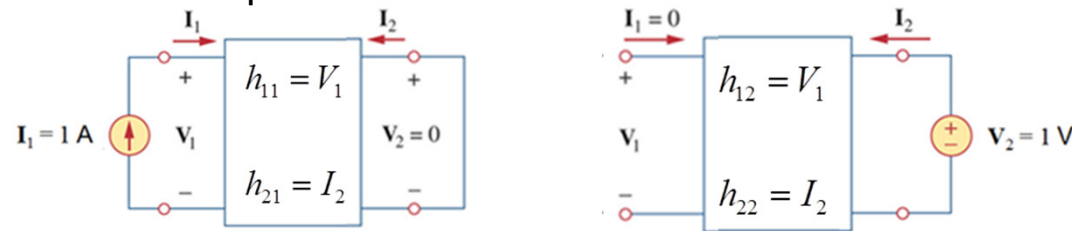

2. H parameters can be found by performing a set of tests on the device
 - a) Shorting the output and applying a current
 - b) Leaving the input open and applying a voltage across the output

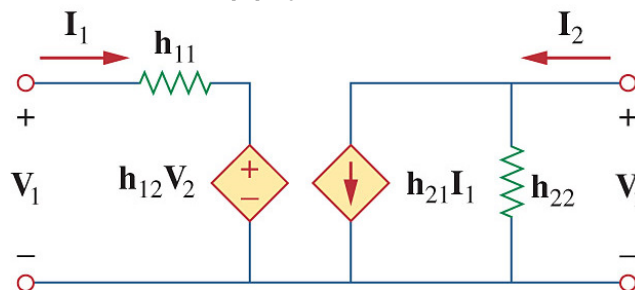3. If given H parameters can apply the model and solve the circuit:




4. If helpful, use conversion tables

Chapter 19 Review

H-Parameters (Transistor Model)

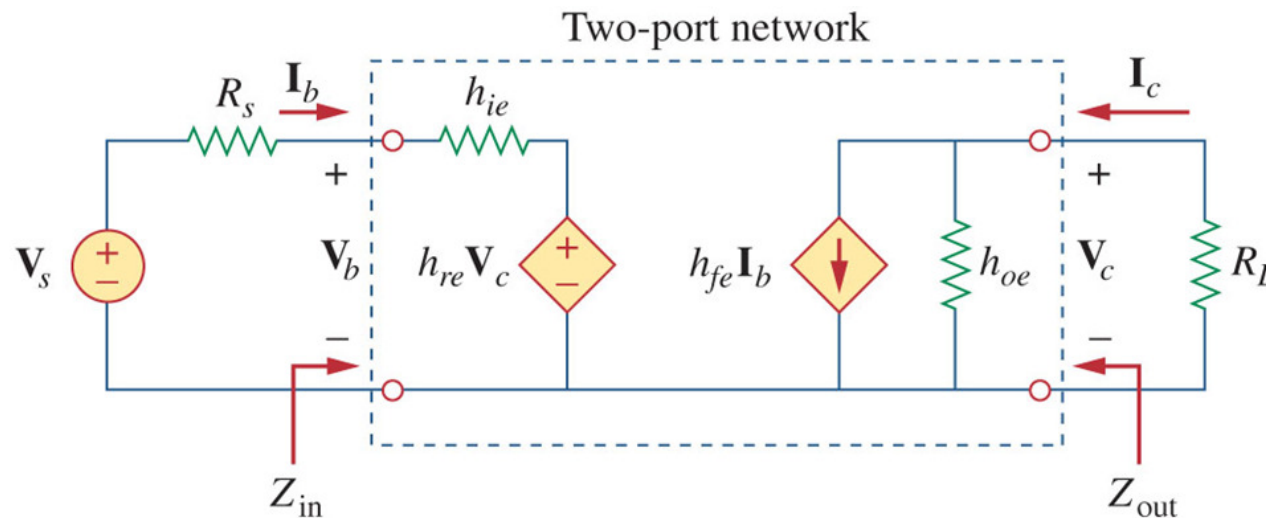
- H parameters are often used in modeling transistors
- Parameters vary depending on biasing conditions
- Spec sheets often use different subscripts:
 - $h_{11} \rightarrow h_{ie}$ = Base input impedance
 - $h_{12} \rightarrow h_{re}$ = Reverse voltage feedback ration
 - $h_{21} \rightarrow h_{fe}$ = Base-collector current gain
 - $h_{22} \rightarrow h_{oe}$ = Output admittance



Chapter 19 Review

H-Parameters (Transistor Model)

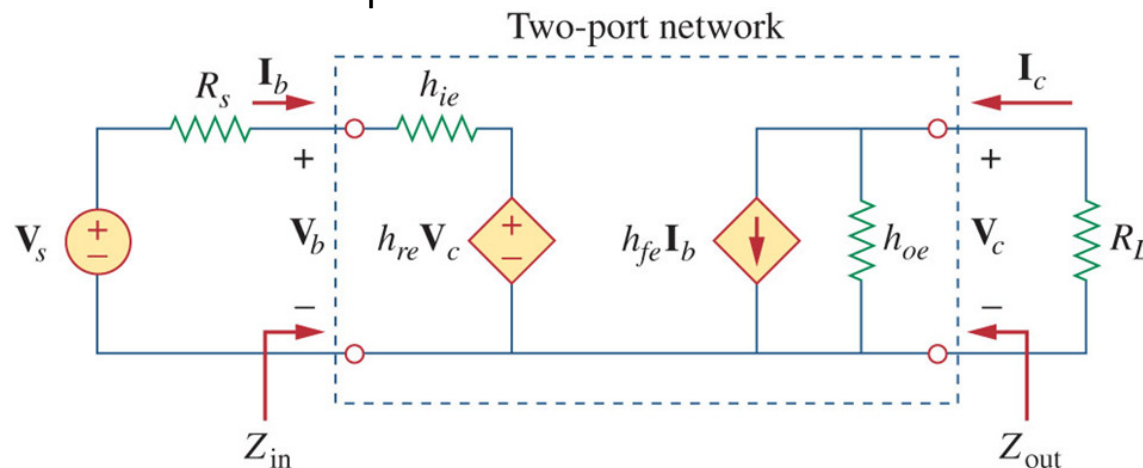- Equations for calculating input impedance, output impedance, voltage gain, and current gain for simple transistor circuit:
 - V_s and R_s can be the Thevenin equivalent source driving the input.
 - R_L can be the input impedance looking into the load of the circuit connected to the output



Input Impedance

$$Z_{in} = \frac{V_b}{I_b} = h_{ie} - \frac{h_{re} h_{fe} R_L}{1 + h_{oe} R_L}$$

Current Gain

$$A_i = \frac{I_c}{I_b} = \frac{h_{fe}}{1 + h_{oe} R_L}$$

Output Impedance

$$Z_{out} = \frac{V_c}{I_c} \bigg|_{V_s=0} = \frac{R_s + h_{ie}}{(R_s + h_{ie}) h_{oe} - h_{re} h_{fe}}$$

Voltage Gain

$$A_v = \frac{V_c}{V_b} = \frac{-h_{fe} R_L}{h_{ie} + (h_{ie} h_{oe} - h_{re} h_{fe}) R_L}$$

Chapter 19 Review

Transmission ("T") Parameters

- Parameters: $V_1 = AV_2 - BI_2$
 $I_1 = CV_2 - DI_2$

- Perform the analysis with the **output** Open Circuited ($I_2=0$)

$$\begin{array}{l} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{array} \xrightarrow{I_2=0} \begin{array}{l} V_1 = AV_2 \\ I_1 = CV_2 \end{array} \xrightarrow{} \begin{array}{l} A = \frac{V_1}{V_2} \\ C = \frac{I_1}{V_2} \end{array}$$


- Perform the analysis with the **output** Short Circuited ($V_2=0$)

$$\begin{array}{l} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{array} \xrightarrow{V_2=0} \begin{array}{l} V_1 = -BI_2 \\ I_1 = -DI_2 \end{array} \xrightarrow{} \begin{array}{l} B = -\frac{V_1}{I_2} \\ D = -\frac{I_1}{I_2} \end{array}$$

Chapter 19 Review

Transmission ("T") Parameters (Cascading)

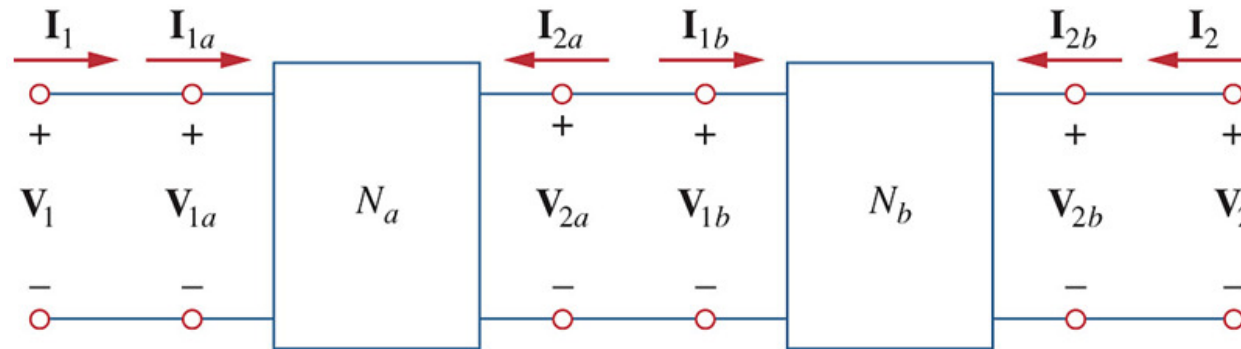- Primary benefit of "T"-Parameters is their ability to be cascaded.



$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$-I_{2a} = I_{1b}$$




$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Chapter 19 Review

T - Parameters (Building Block models)

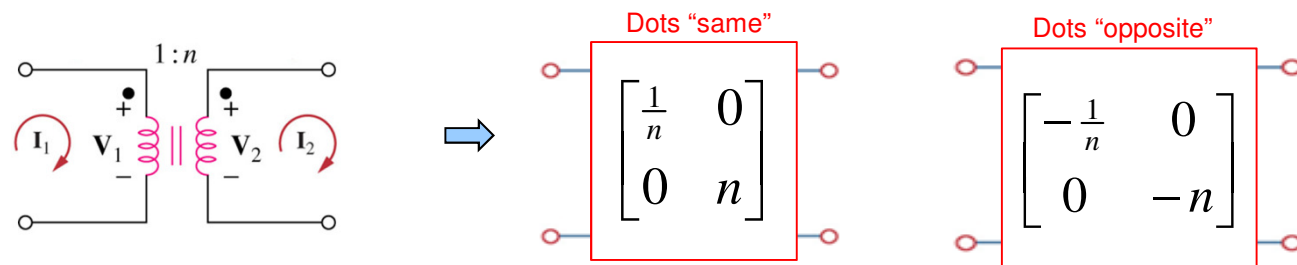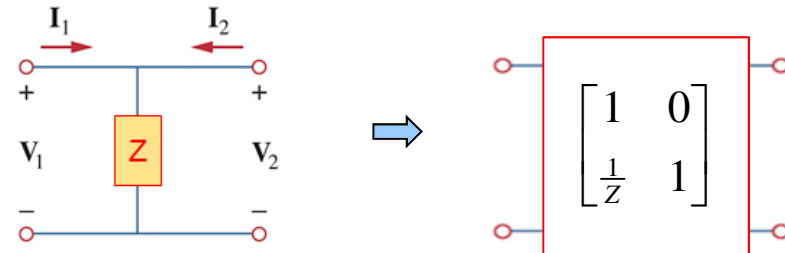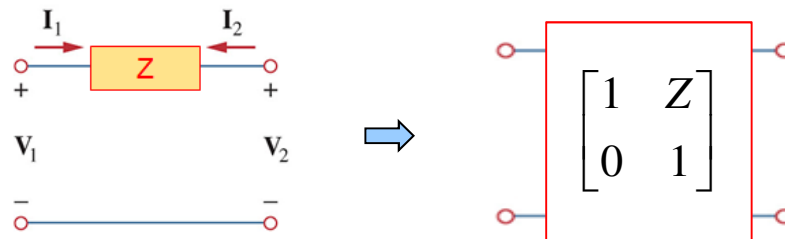
- We can create “building block” models of components by finding their T-parameters and use the cascading property to find the T-parameters for the complete circuit/system.



Chapter 19 Review

T - Parameters (Building Block models)

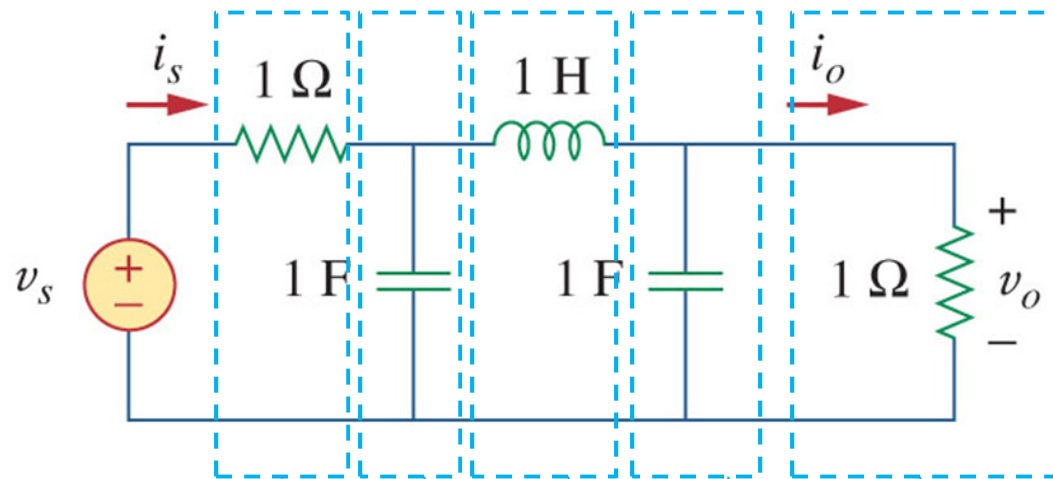- With “Building Block” approach, circuits can be broke up into discrete components and analyzed using T-parameters



$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

Chapter 19 Review


T - Parameters (Useful Properties)

- The T parameters give us useful properties in the analysis of circuits:

- Open Circuit Voltage Transfer Function:

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)} \quad H(s) = \frac{1}{A}$$

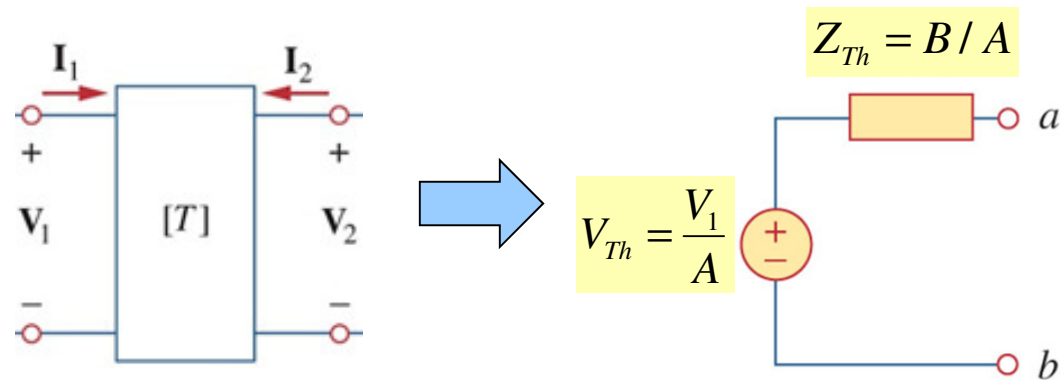- Thevenin Equivalent Circuit (Replace circuit as a source)



Chapter 19 Review

Conversion between Parameters

- Conversion tables exist to convert between parameters

	z		y		h		T	
z	z ₁₁	z ₁₂	$\frac{y_{22}}{\Delta_y}$	$-\frac{y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$
	z ₂₁	z ₂₂	$-\frac{y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{C}$	$\frac{D}{C}$
y	$\frac{z_{22}}{\Delta_z}$	$-\frac{z_{12}}{\Delta_z}$	y ₁₁	y ₁₂	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$	$\frac{D}{B}$	$-\frac{\Delta_T}{B}$
	$-\frac{z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	y ₂₁	y ₂₂	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$-\frac{1}{B}$	$\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	h ₁₁	h ₁₂	$\frac{B}{D}$	$\frac{\Delta_T}{D}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	h ₂₁	h ₂₂	$-\frac{1}{D}$	$\frac{C}{D}$
T	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$-\frac{h_{11}}{h_{21}}$	A	B
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta_y}{y_{21}}$	$-\frac{y_{11}}{y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$-\frac{1}{h_{21}}$	C	D

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21} \quad \Delta_z = z_{11}z_{22} - z_{12}z_{21} \quad \Delta_h = h_{11}h_{22} - h_{12}h_{21} \quad \Delta_T = AD - BC$$


Chapter 19: Two-Port Networks

- 19.1 Introduction
- 19.2 Impedance Parameters (z)
- 19.3 Admittance Parameters (y)
- 19.4 Hybrid Parameters (h)
- 19.5 Transmission Parameters (T)
- 19.6 Relationships between Parameters
- 19.7 Interconnection of Networks
- 19.9 Applications

19.1 Introduction (1)

- A port is an access to the network and consists of a pair of terminals; the current entering one terminal leaves through the other terminal so that the net current entering the port equals zero.
- One port networks include two-terminal devices such as resistors, capacitors, and inductors.
- A two-port network has two separate ports for input and output.
- Two port networks include op amps, transistors and transformers.

19.1 Introduction (2)

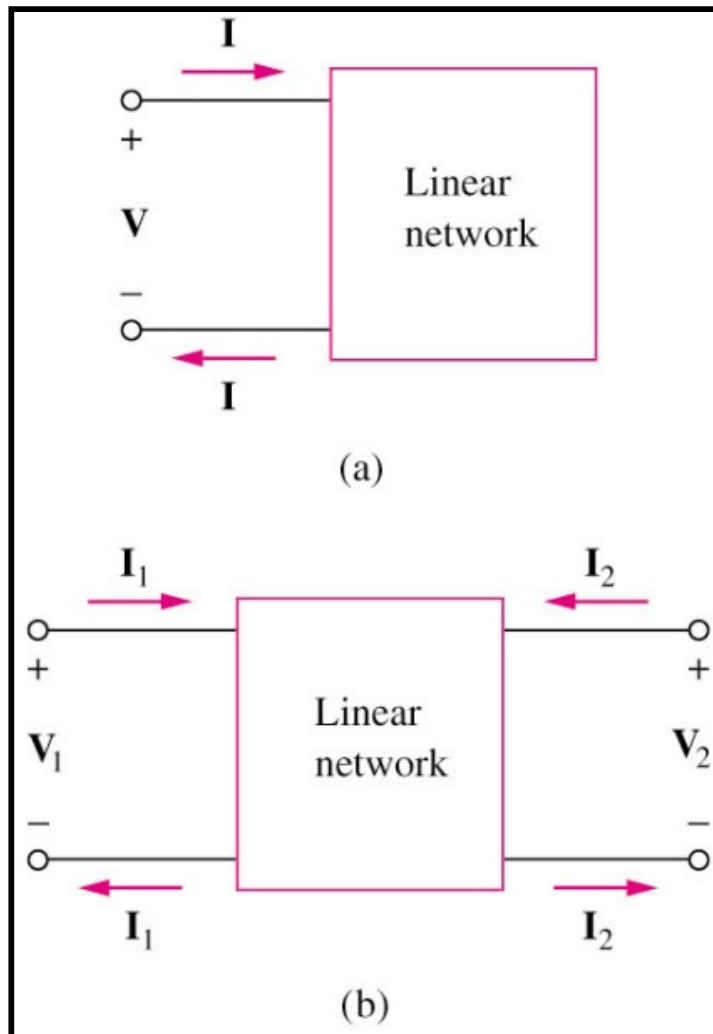

**One port or two
terminal circuit**

**Two port or four
terminal circuit**


- It is an electrical network with two separate ports for input and output.
- No independent sources.

19.1 Introduction (3)

- Characterizing a two-port network requires that we relate the terminal quantities \mathbf{V}_1 , \mathbf{V}_2 , \mathbf{I}_1 , \mathbf{I}_2 out of which two are independent. Six sets of voltage and current parameters will be derived.
- Two port networks are useful in communications, control systems, power systems, and electronics.
- They are used in electronics to model transistors and to facilitate cascaded design.
- Additionally, if we know the parameters of a two-port network it can be treated as a “black box” when embedded within a larger network.

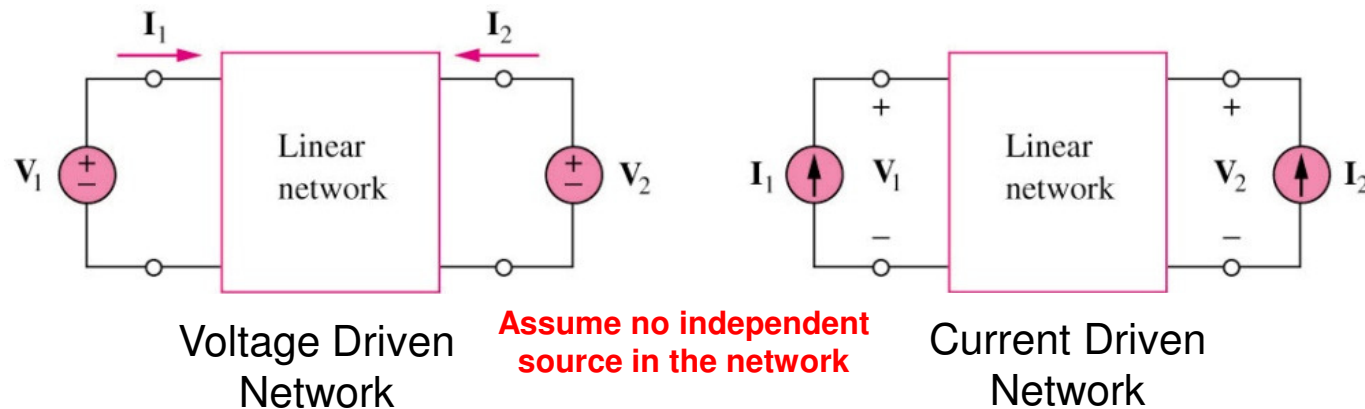19.2 Impedance Parameters (1)

- Often called “**Z-parameters**” since their units are in **ohms** and they represent an impedance relationship between V_1 , V_2 , I_1 , I_2 for the two port network shown below:



$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$




$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

- Z-parameters are commonly used in filter synthesis, impedance matching networks design, and power distribution networks analysis.

19.2 Impedance Parameters (2)

The values of parameters can be evaluated by setting $I_1=0$ or $I_2=0$ (open circuit)

Setting $I_2 = 0$

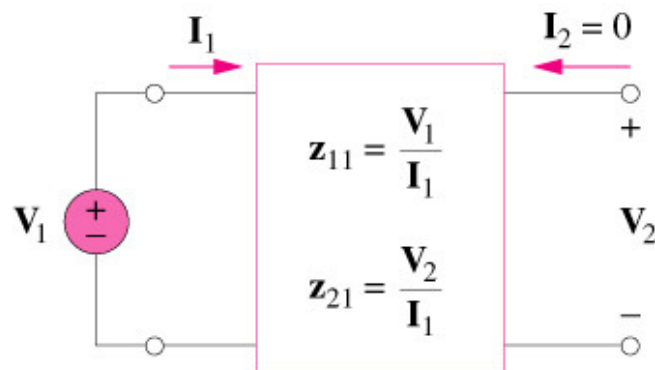


(a)

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

z_{11} = Open-circuit input impedance
 z_{21} = Open-circuit transfer impedance
from port 2 to port 1

Setting $I_1 = 0$

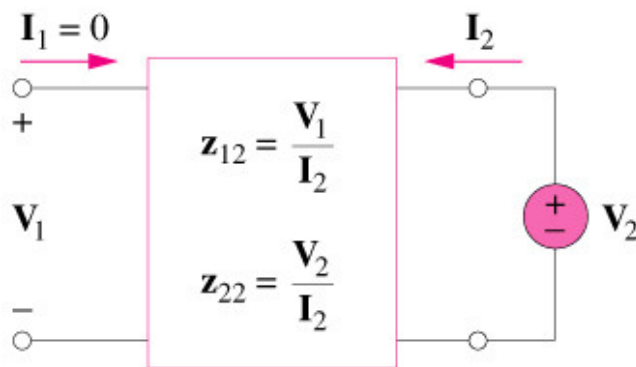

(b)


$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

z_{12} = Open-circuit transfer impedance from port
1 to port 2
 z_{22} = Open-circuit output impedance

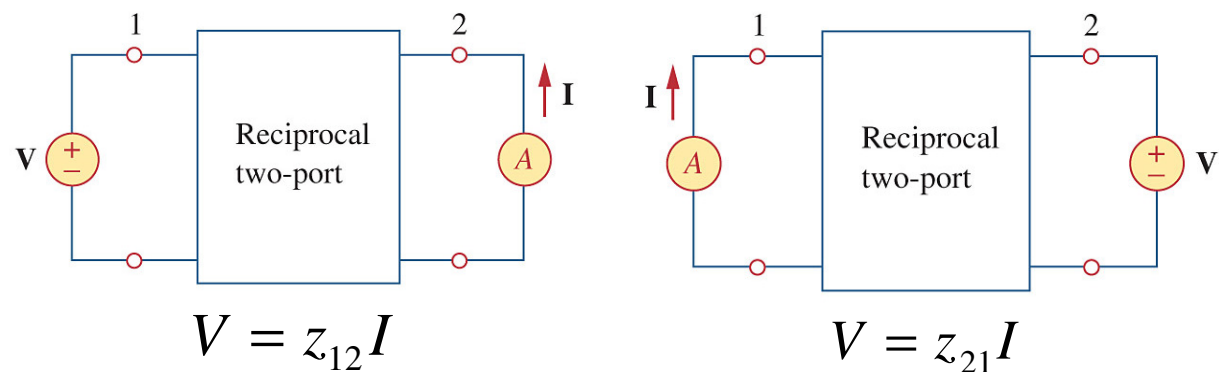19.2 Impedance Parameters (3)


Properties of Z-parameters

- Symmetrical networks $z_{11} = z_{22}$
 - Implies a mirror like symmetry
- Reciprocal networks $z_{12} = z_{21}$
 - Any network made up entirely of resistors, capacitors, and inductors must be reciprocal.
 - Linear networks with no dependant sources are reciprocal.
 - Interchanging an ideal voltage source at one port with an ideal ammeter at the other port gives the same ammeter reading.



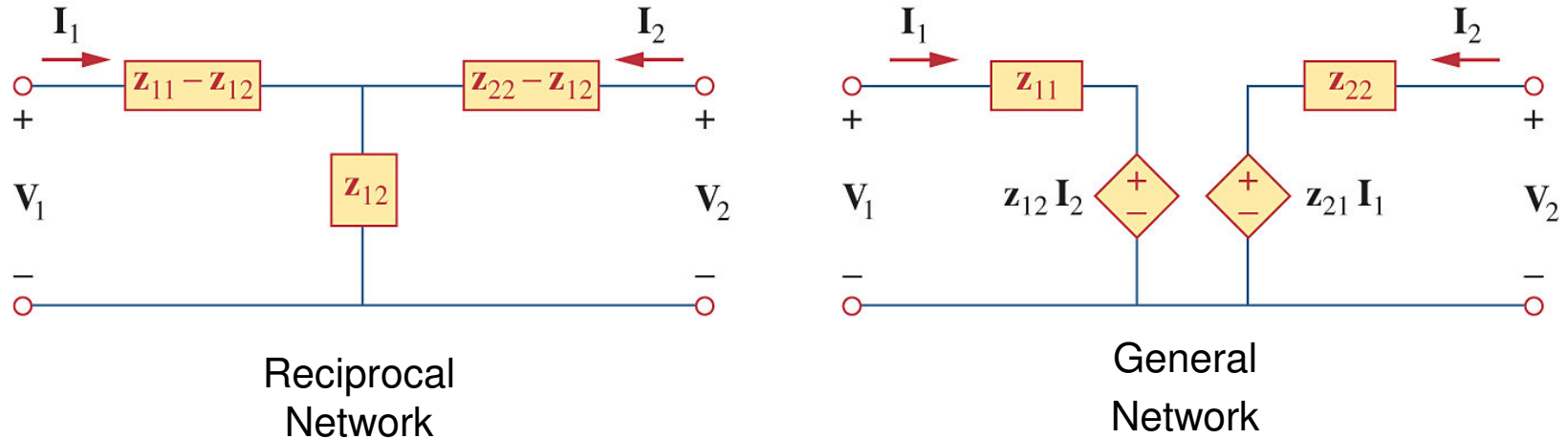19.2 Impedance Parameters (4)


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



- A reciprocal network can be replaced by the T-network shown above
- If not reciprocal, the General network is the T-equivalent.

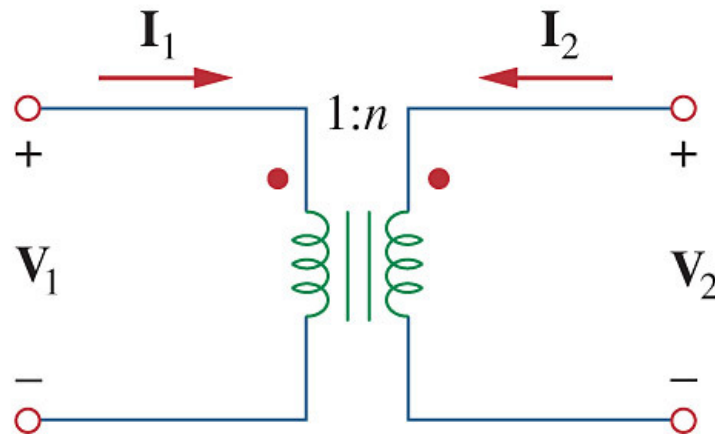19.2 Impedance Parameters (5)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



- Note: some circuits do not have z-parameter equivalents. (they may have other 2-port equivalents, as we shall see)

- Consider an ideal transformer:

$$V_1 = V_2/n \text{ and } I_1 = -nI_2.$$


- This cannot be expressed by:

$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

19.2 Impedance Parameters (6)

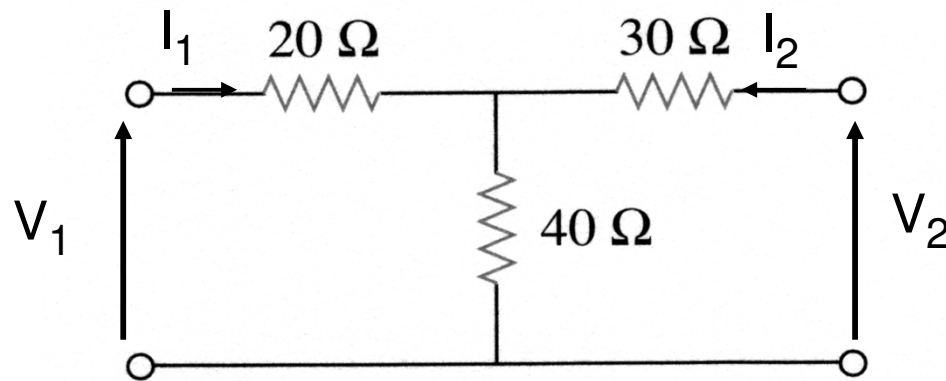Example 19.1

Determine the z-parameters of the following circuit.



$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$



Answer:
$$z = \begin{bmatrix} 60 & 40 \\ 40 & 70 \end{bmatrix} \Omega$$


$$Z = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \Omega$$

19.2 Impedance Parameters (7)

Practice Problem 19.2

Determine I_1 and I_2 in the following circuit.

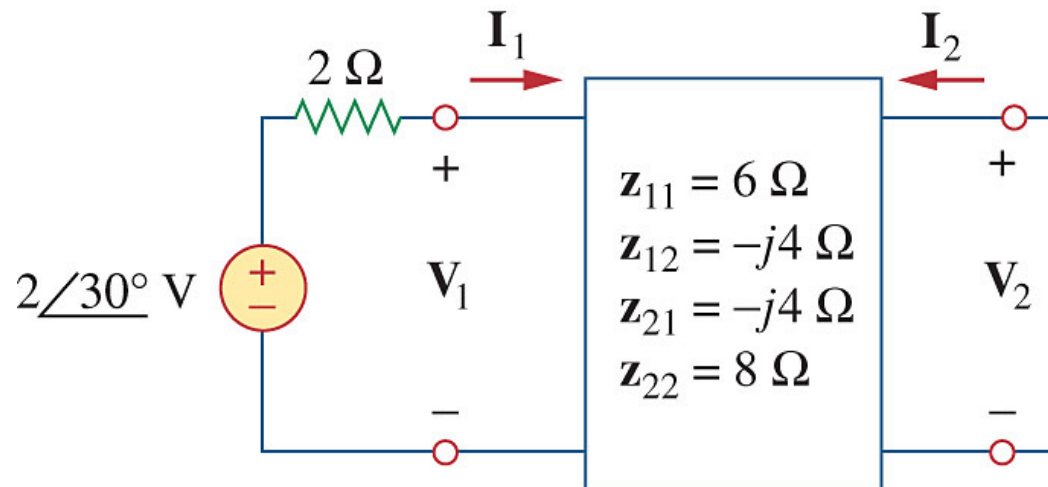
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

Answer: $I_1 = 200\angle 30^\circ \text{ mA}$
 $I_2 = 100\angle 120^\circ \text{ mA}$

19.3 Admittance Parameters (1)

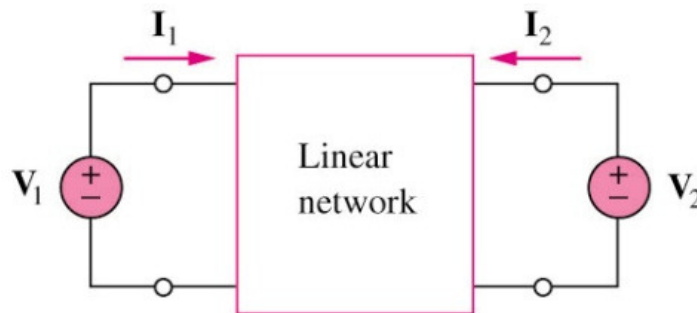

(a)

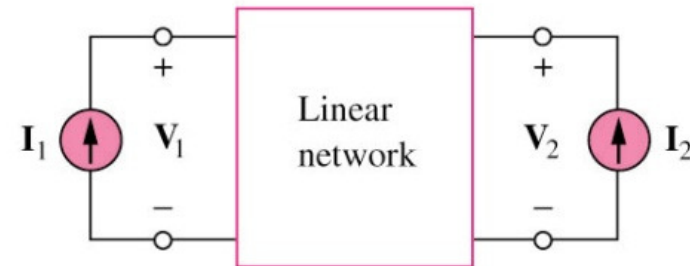

(b)

Assume no independent source in the network


$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$




$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

where the **y** terms are called the admittance parameters, or simply **y** parameters, and they have units of Siemens.

19.3 Admittance Parameters (2)

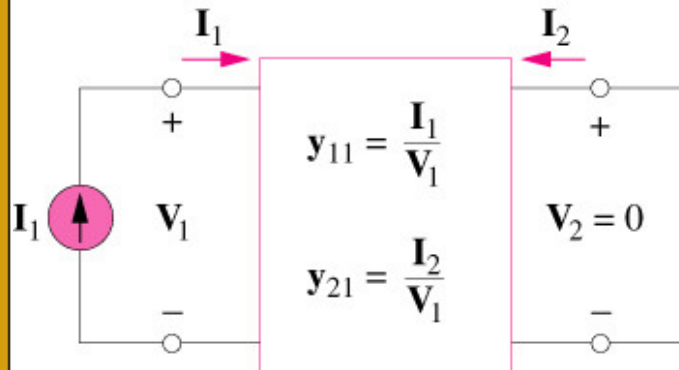

(a)

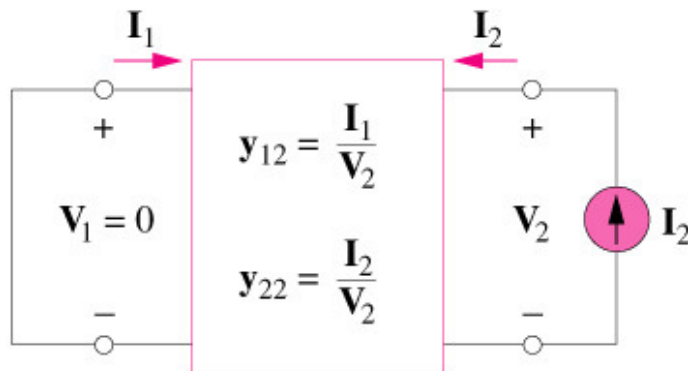

(b)

Setting $V_2 = 0$ (Shorting the output)

$$y_{11} = \frac{I_1}{V_1} \bigg|_{V_2=0} \quad \text{and} \quad y_{21} = \frac{I_2}{V_1} \bigg|_{V_2=0}$$


y_{11} = Short-circuit input admittance
 y_{21} = Short-circuit transfer admittance from port 1 to port 2

Setting $V_1 = 0$ (Shorting the input)

$$y_{12} = \frac{I_1}{V_2} \bigg|_{V_1=0} \quad \text{and} \quad y_{22} = \frac{I_2}{V_2} \bigg|_{V_1=0}$$

y_{12} = Short-circuit transfer admittance from port 2 to port 1
 y_{22} = Short-circuit output admittance

19.3 Admittance Parameters (3)

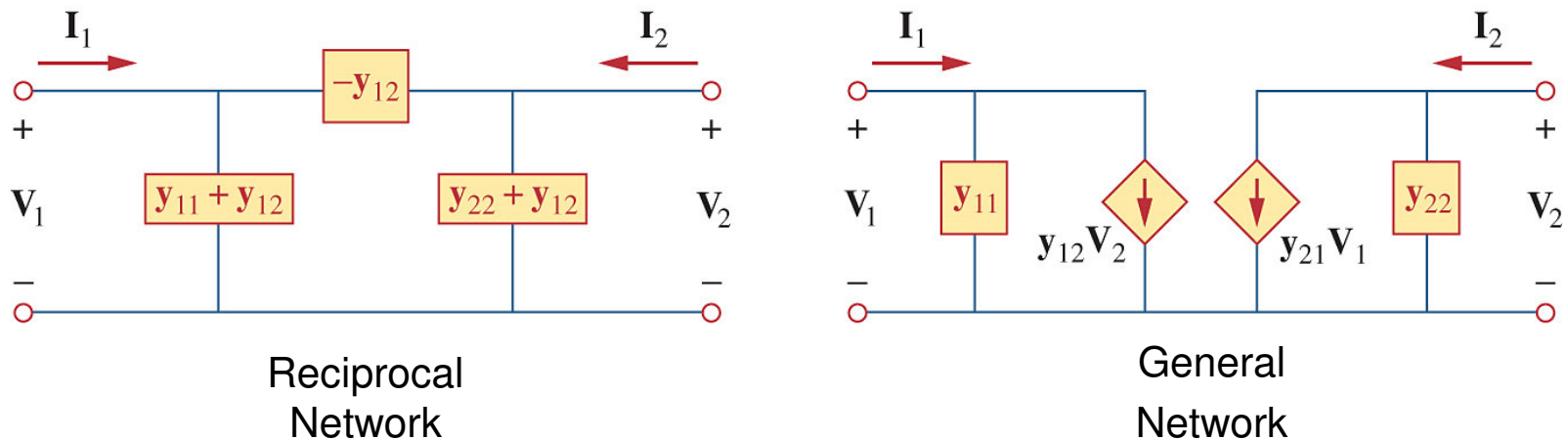


- A reciprocal network ($y_{12} = y_{21}$) can be replaced by the Pi-network in figure (a).
- If not reciprocal, the network in figure (b) is the Pi-equivalent.

19.3 Admittance Parameters (4)

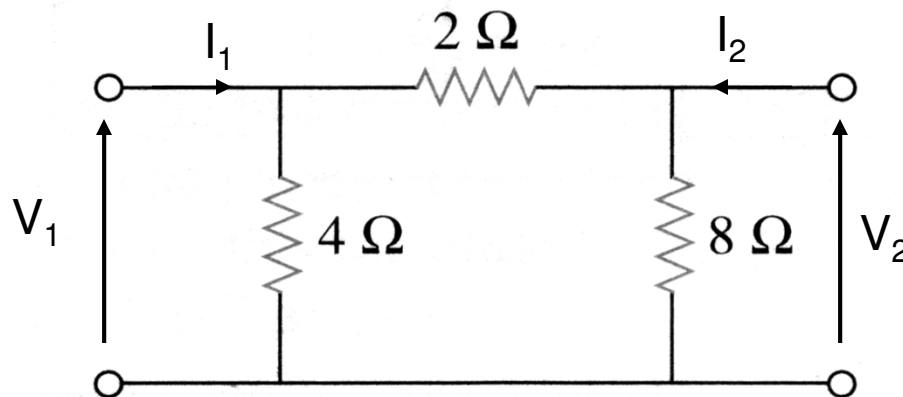Example 19.3

Determine the y-parameters of the following circuit.



Answer: $y = \begin{bmatrix} 0.75 & -0.5 \\ -0.5 & 0.625 \end{bmatrix} \text{S}$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$




$$y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \text{S}$$

19.3 Admittance Parameters (5)

Practice Problem 19.3

Practice Problem 19.3

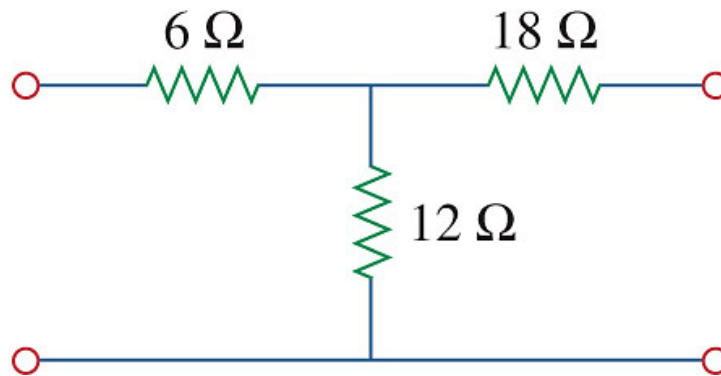Determine the y-parameters of the following circuit.



Answer: $y = \begin{bmatrix} 75.77 & -30.3 \\ -30.3 & 45.47 \end{bmatrix} \text{ mS}$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$



$$y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \text{ S}$$

19.3 Admittance Parameters (6)

Practice Problem 19.3

Practice Problem 19.3 (Solution)

- Short the output
- Put a 1 volt source at input
- Find I_1 and I_2

$$y_{11} = \frac{I_1}{(1)} \bigg|_{V_2=0} \quad \text{and} \quad y_{21} = \frac{I_2}{(1)} \bigg|_{V_2=0}$$

Find Input Impedance

$$Z_{in} = 6 + 12 \parallel 18 = 13.2$$

$$I_1 = \frac{V_1}{Z_{in}} = \frac{1}{13.2} = 0.07576$$


$$y_{11} = 0.07576$$

Similarly at Output

$$Z_{out} = 18 + 6 \parallel 12 = 22$$

$$I_2 = \frac{V_2}{Z_{in}} = \frac{1}{22} = 0.04545$$

$$y_{22} = 0.04545$$

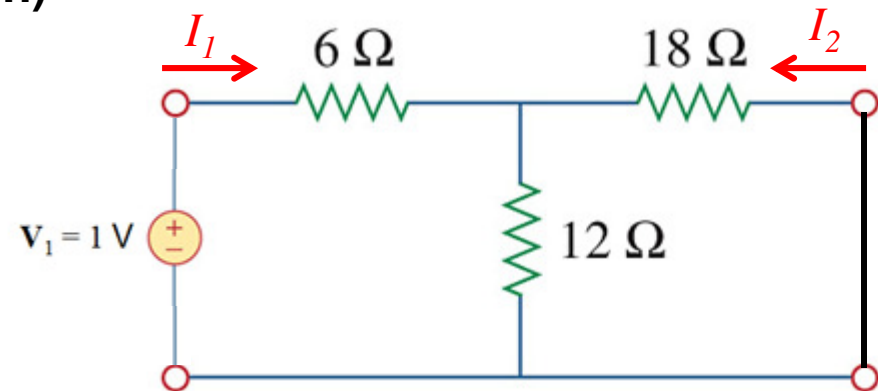

Find I_2 from current divider equation

$$I_2 = \frac{-12}{12 + 18} I_1$$

$$I_2 = (-0.4) 0.07576 = -0.0303$$

$$y_{21} = -0.0303$$

$$y_{12} = y_{21} = -0.0303$$


Reciprocal Network

19.3 Admittance Parameters (7)

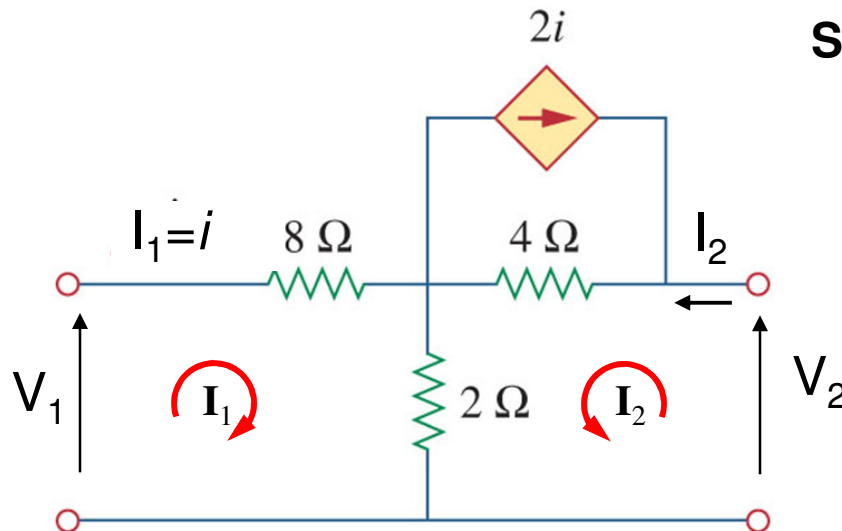Example 19.4

Determine the y-parameters of the following circuit.

$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$



Answer: $y = \begin{bmatrix} 0.15 & -0.05 \\ -0.25 & 0.25 \end{bmatrix} \text{S}$

Note: Sometimes two port parameters will fall out directly from mesh equations.

Solution: Apply KVL

Mesh I_1 : $V_1 = 8I_1 + 2(I_1 + I_2)$

$$V_1 = 10I_1 + 2I_2$$

Mesh I_2 : $V_2 = 4(2i + I_2) + 2(I_1 + I_2)$

$$V_2 = 8I_1 + 4I_2 + 2I_1 + 2I_2$$

$$V_2 = 10I_1 + 6I_2$$

Subtract #1 from #2:

$$V_2 - V_1 = 0 + 4I_2$$

$$I_2 = -0.25V_1 + 0.25V_2$$

Substitute back into #1

$$V_1 = 10I_1 - 0.5V_1 + 0.5V_2$$

$$10I_1 = 1.5V_1 - 0.5V_2$$


$$I_1 = 0.15V_1 - 0.05V_2$$

19.3 Admittance Parameters (8)

Practice problem 19.4

Practice Problem 19.4

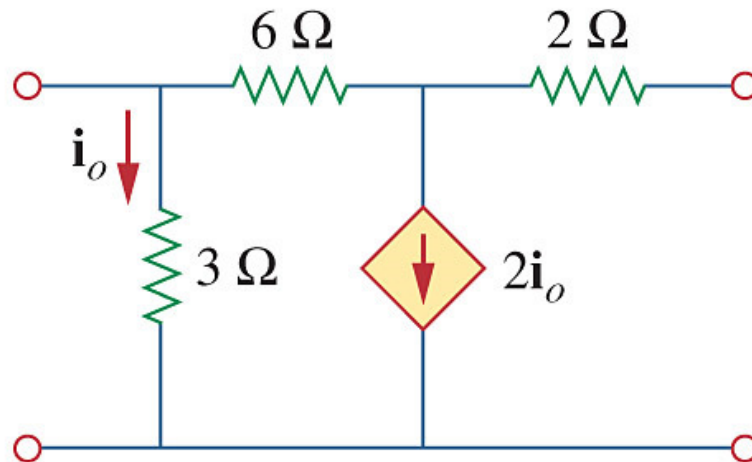Determine the y-parameters of the following circuit.



Answer: $y = \begin{bmatrix} 0.625 & -0.125 \\ 0.375 & 0.125 \end{bmatrix} S$

19.3 Admittance Parameters (9)

Practice problem 19.4

Practice Problem 19.4 (Solution)

- Short the output
- Put a 1 volt source at input
- Find I_1 and I_2

First find i_o :

$$i_o = \frac{1}{3}$$

Dependent current source is then $2/3$, find I_1 by repetitive source transformations of the dependant current source


$$I_1 = 0.625 \Rightarrow y_{11} = 0.625$$

Next find current across $6\ \Omega$ resistor $I_{6\Omega}$:

$$I_{6\Omega} = 0.625 - \frac{1}{3}$$

$$I_2 + I_{6\Omega} = 2i_o$$
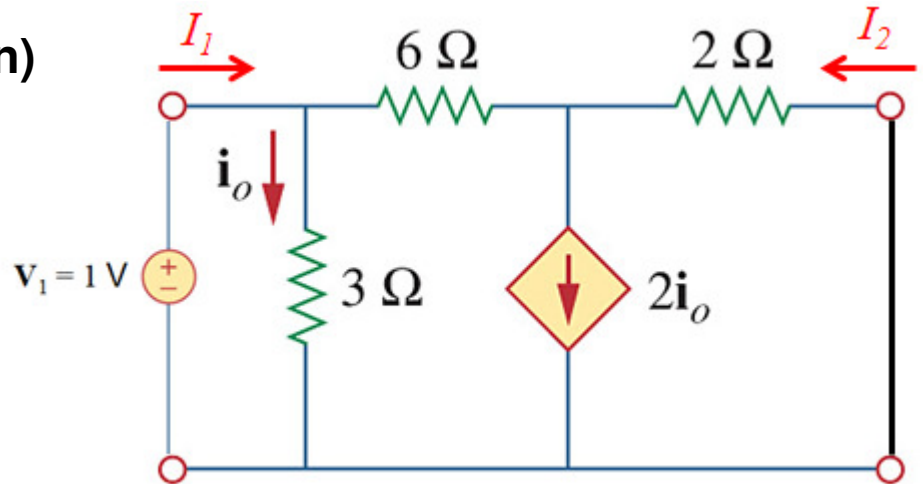
$$I_2 = 2i_o - I_{6\Omega} = \frac{2}{3} - \left(0.625 - \frac{1}{3}\right) = 0.375 \Rightarrow y_{12} = 0.375$$



Z and Y Parameters Comparison

Z-Parameters


$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

- **Open** one port ($I_1=0$ or $I_2=0$)
- Connect a source to the other port
- Solve to find z-parameters

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

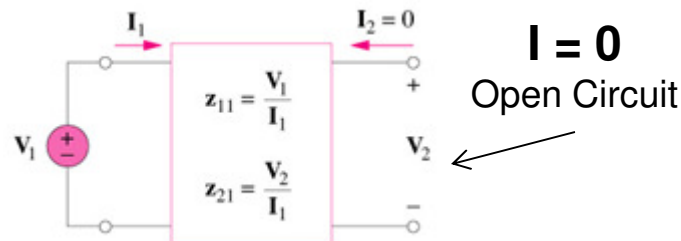

Y-Parameters


$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

- **Short** one port ($V_1=0$ or $V_2=0$)
- Connect a source to the other port
- Solve to find y-parameters

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

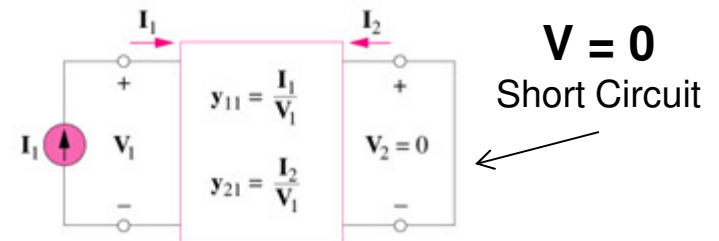


Z and Y parameters

Alternative method (1 Amp / 1 Volt sources)

Z-Parameters

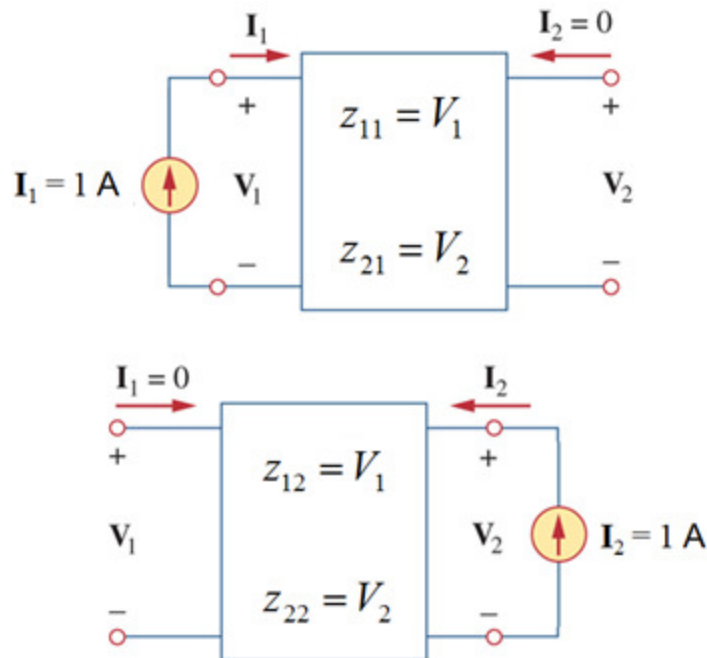
- Open circuit one port
- Put a 1 Amp current source at other port
- Resulting voltages are the z-parameters



$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

Y-Parameters

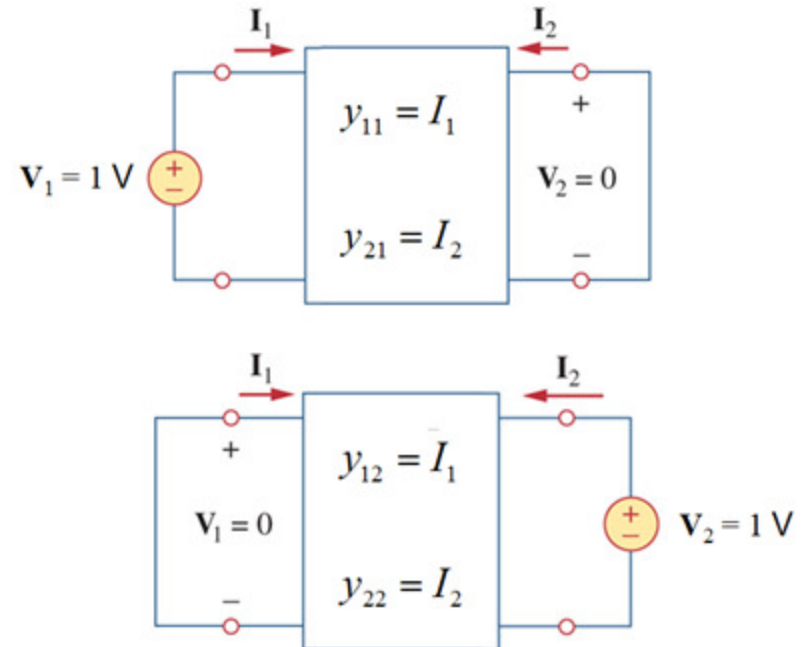
- Short circuit one port
- Put a 1 Volt voltage source at other port
- Resulting current are the y-parameters



$$\begin{aligned} I_1 &= y_{11}V_1 + y_{12}V_2 \\ I_2 &= y_{21}V_1 + y_{22}V_2 \end{aligned}$$

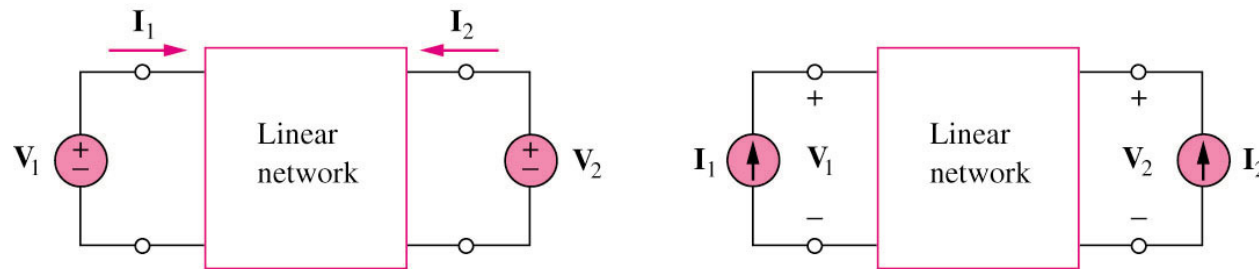19.4 Hybrid Parameters (1)

- The z and y parameters of a two-port network do not always exist. Therefore, there is a need to develop another set of parameters based on making V_1 and I_2 the dependent variables.



Assume no independent source in the network

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$




$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [h] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

where the **h** terms are called the hybrid parameters, or simply h parameters.

- Hybrid parameters are very useful for describing electronic devices such as transistors because it is much easier to measure the h parameters of these devices than to measure their z or y parameters.
- The ideal transformer can also be described by h parameters.

19.4 Hybrid Parameters (2)

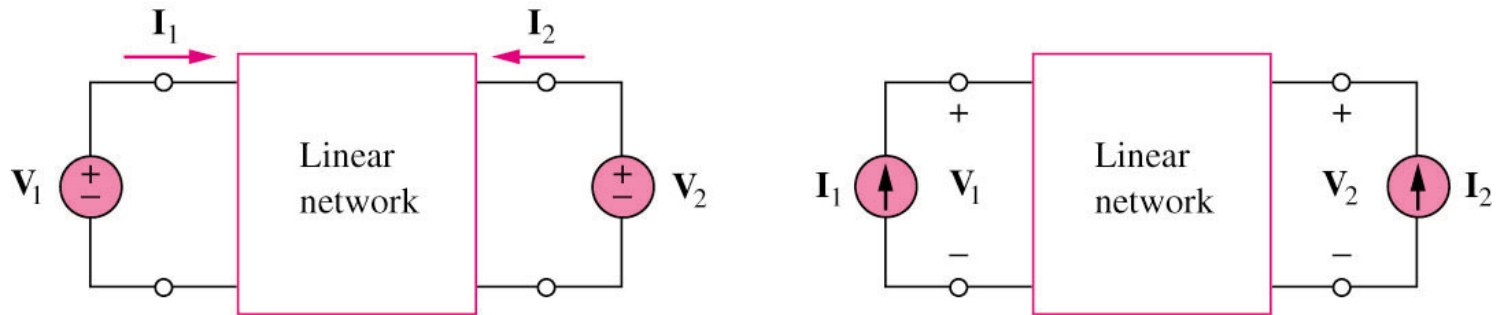

Assume no independent source in the network

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

h_{11} = short-circuit
input impedance (Ω)

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

h_{21} = short-circuit
forward current gain

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$


h_{12} = open-circuit
reverse voltage-gain

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

h_{22} = open-circuit
output admittance (S)


- Note that the h parameters represent an impedance, voltage gain, current gain, and admittance, thereby the term hybrid parameters.
- For reciprocal network, $h_{12} = -h_{21}$

19.4 Hybrid Parameters (3)

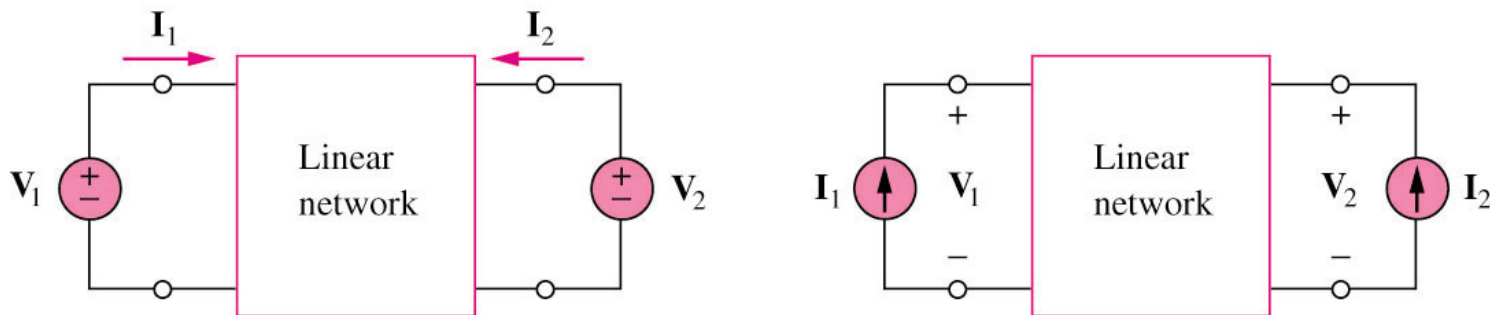

Assume no independent source in the network


Hybrid model of a two-port network:

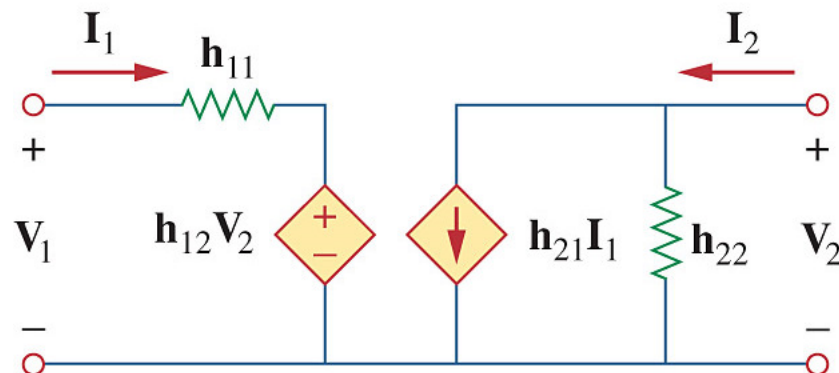

19.4 Hybrid Parameters (4)

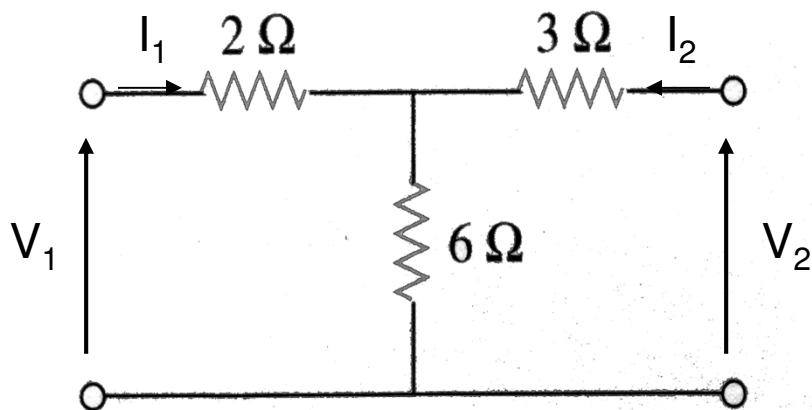Example 19.5:

Determine the h-parameters of the following circuit.



Answer:

$$h = \begin{bmatrix} 4\Omega & \frac{2}{3} \\ -\frac{2}{3} & \frac{1}{9}S \end{bmatrix}$$

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{and} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{and} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$




$$h = \begin{bmatrix} h_{11}\Omega & h_{12} \\ h_{21} & h_{22}S \end{bmatrix}$$

19.4 Hybrid Parameters (5)

Practice Problem 19.5:

Determine the h-parameters of the following circuit.

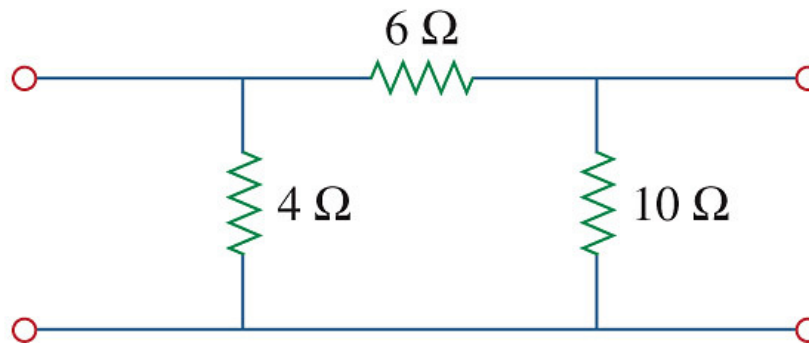Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{and} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{and} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$



Answer:

$$h = \begin{bmatrix} 2.4\Omega & 0.4 \\ -0.4 & 0.2S \end{bmatrix}$$

$$h = \begin{bmatrix} h_{11}\Omega & h_{12} \\ h_{21} & h_{22}S \end{bmatrix}$$

19.9.1 Transistor Circuits (1)

Hybrid Parameters

- H-parameters are often used to model transistor circuits
- The h-parameters vary depending on biasing conditions
- Parameters are given different subscripts:
 - $h_{11} \rightarrow h_{ie}$ = Base input impedance
 - $h_{12} \rightarrow h_{re}$ = Reverse voltage feedback ratio
 - $h_{21} \rightarrow h_{fe}$ = Base-collector current gain
 - $h_{22} \rightarrow h_{oe}$ = Output admittance

Example 2N3904

2N3903 2N3904

h PARAMETERS
($V_{CE} = 10$ Vdc, $f = 1.0$ kHz, $T_A = 25^\circ\text{C}$)

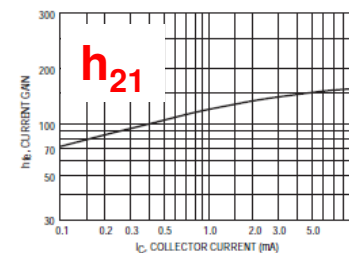
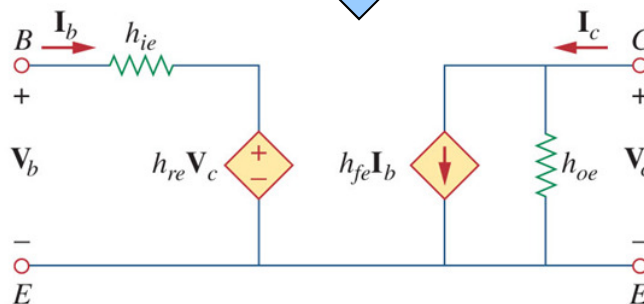
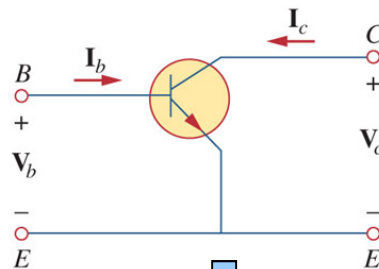


Figure 11. Current Gain

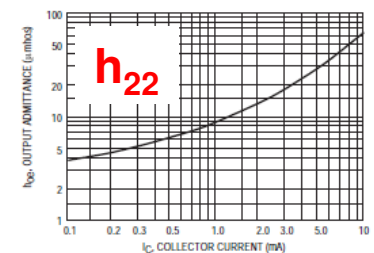


Figure 12. Output Admittance

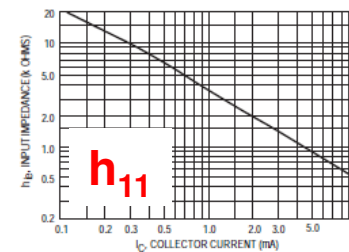


Figure 13. Input Impedance


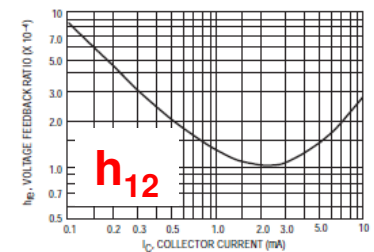


Figure 14. Voltage Feedback Ratio

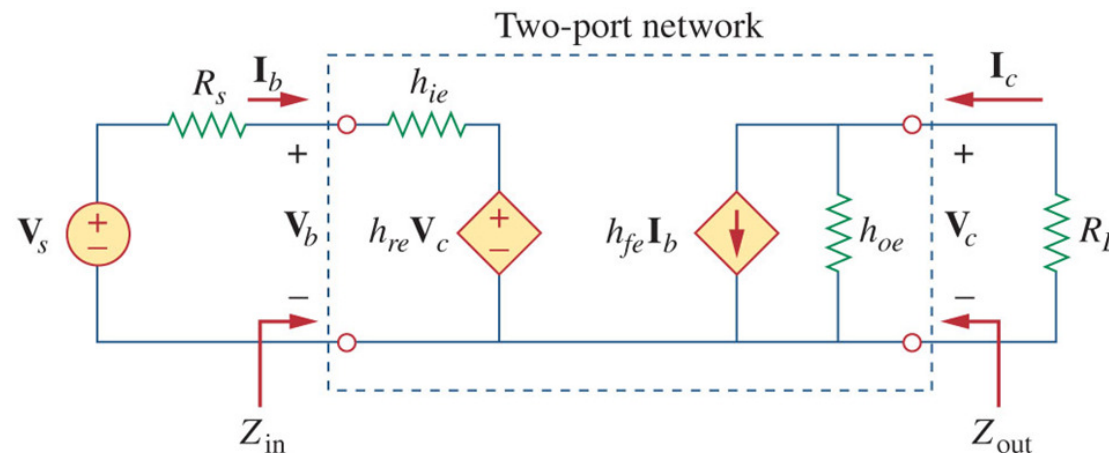19.9.1 Transistor Circuits (2)

Hybrid Parameters

- H parameters are often found in manufacturers spec sheets
- Provide ability to calculate the exact voltage gain, input impedance, and output impedance of the transistor.



Input Impedance

$$Z_{in} = \frac{V_b}{I_b} = h_{ie} - \frac{h_{re} h_{fe} R_L}{1 + h_{oe} R_L}$$

Current Gain

$$A_i = \frac{I_c}{I_b} = \frac{h_{fe}}{1 + h_{oe} R_L}$$


Output Impedance

$$Z_{out} = \frac{V_c}{I_c} \bigg|_{V_s=0} = \frac{R_s + h_{ie}}{(R_s + h_{ie})h_{oe} - h_{re} h_{fe}}$$

Voltage Gain

$$A_v = \frac{V_c}{V_b} = \frac{-h_{fe} R_L}{h_{ie} + (h_{ie} h_{oe} - h_{re} h_{fe}) R_L}$$

19.5 Transmission Parameters (1)

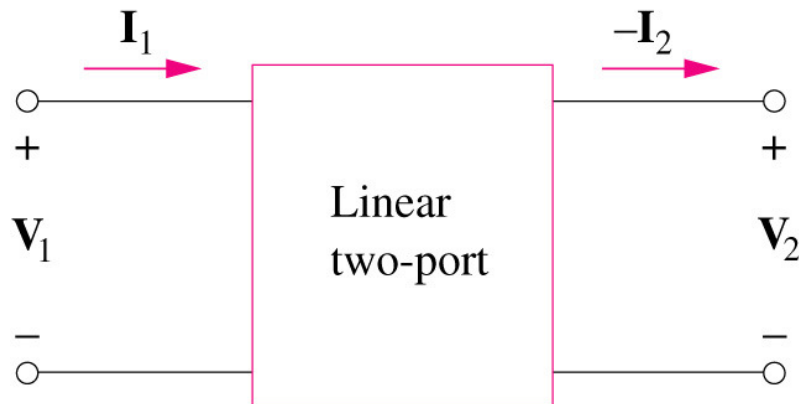

**Assume no
independent source
in the network**

$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = [T] \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

where the **T** terms are called the transmission parameters, or simply **T** or ABCD parameters.

•Note that $-I_2$ is used since the current is considered to be leaving the network. It is logical to think of I_2 as leaving the two-port; this is customary convention in the power industry.

19.5 Transmission Parameters (2)

- These two-port transmission parameters provide a measure of how a circuit transmits voltage and current from a source to a load.
- They are useful in the analysis of transmission lines and are therefore called transmission parameters.
- They are also known as ABCD parameters and are used in the design of telephone systems, microwave networks, and radars.

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

A=open-circuit
voltage ratio

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

C= open-circuit
transfer admittance
(S)

$$B = - \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

B= negative short-
circuit transfer
impedance (Ω)

$$D = - \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

D=negative short-
circuit current ratio

19.5 Transmission Parameters (3)

Solving for Transmission Parameters

- To find the transmission parameters, analyze the circuit as follows:
- Perform the analysis with the output Open Circuited ($I_2=0$)

$$\begin{array}{l} V_1 = AV_2 - \cancel{BI_2} \\ I_1 = CV_2 - \cancel{DI_2} \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} V_1 = AV_2 \\ I_1 = CV_2 \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} A = \frac{V_1}{V_2} \\ C = \frac{I_1}{V_2} \end{array}$$


- Perform the analysis with the output Short Circuited ($V_2=0$)

$$\begin{array}{l} V_1 = \cancel{AV_2} - BI_2 \\ I_1 = \cancel{CV_2} - DI_2 \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} V_1 = -BI_2 \\ I_1 = -DI_2 \end{array} \xrightarrow{\text{blue arrow}} \begin{array}{l} B = -\frac{V_1}{I_2} \\ D = -\frac{I_1}{I_2} \end{array}$$

19.5 Transmission Parameters (4)

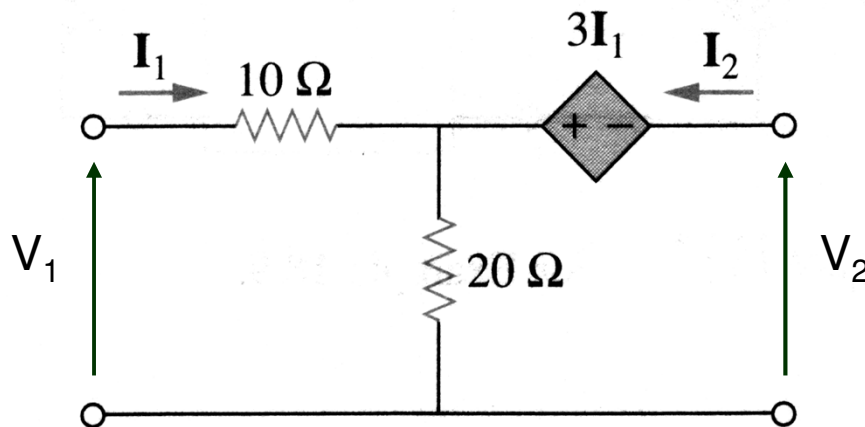Example 19.8

Determine the T-parameters of the following circuit.



Answer:

$$T = \begin{bmatrix} 1.765 & 15.294\Omega \\ 0.059S & 1.176 \end{bmatrix}$$

$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$

Apply KVL

$$\begin{aligned} V_1 &= 10I_1 + 20(I_1 + I_2) \\ V_2 &= -3I_1 + 20(I_1 + I_2) \end{aligned}$$



$$\begin{aligned} V_1 &= \frac{30}{17}V_2 - \frac{260}{17}I_2 \\ I_1 &= \frac{1}{17}V_2 - \frac{20}{17}I_2 \end{aligned}$$

19.5 Transmission Parameters (5)

Example 19.8

From KVL:

$$V_1 = 10I_1 + 20(I_1 + I_2) = 30I_1 + 20I_2$$

$$V_2 = -3I_1 + 20(I_1 + I_2) = 17I_1 + 20I_2$$


If we “open circuit” the output we get:

$$V_1 = 30I_1 + 20\overset{0}{I_2}$$

$$V_1 = 30I_1$$

$$V_2 = 17I_1 + 20\overset{0}{I_2}$$

$$V_2 = 17I_1$$

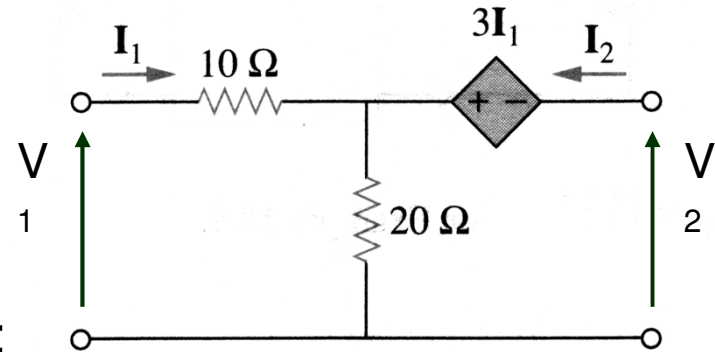

$$A = \frac{V_1}{V_2} = \frac{30I_1}{17I_1} = \frac{30}{17} = 1.765$$

$$C = \frac{1}{17} = 0.0588$$

If we “short circuit” the output we get:

$$V_1 = 30I_1 + 20I_2$$

$$\overset{0}{V_2} = 17I_1 + 20I_2$$

$$V_1 = 30I_1 + 20I_2$$

$$0 = 17I_1 + 20I_2$$

$$V_1 = 30\left(\frac{-20}{17}\right)I_2 + 20I_2$$


$$I_1 = \frac{-20}{17}I_2$$

$$B = -\frac{V_1}{I_2} = -\frac{(30\left(\frac{-20}{17}\right) + 20)I_2}{I_2} = 15.29$$

$$D = -\frac{I_1}{I_2} = \frac{20}{17} = 1.176$$

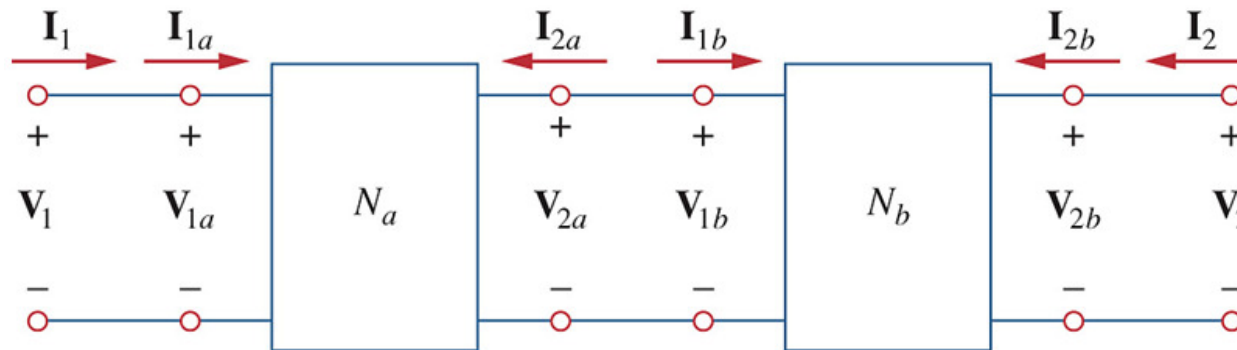19.5 Transmission Parameters (6)

- Transmission Parameters can be cascaded with the result found through simple matrix multiplication



$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$-I_{2a} = I_{1b}$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

19.5 Transmission Parameters (7)

Properties: Building Block Circuits

Consider the following
simple circuits

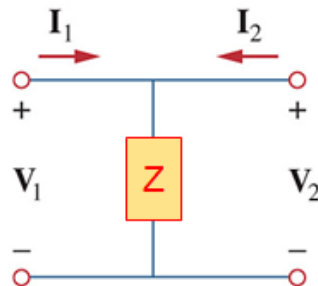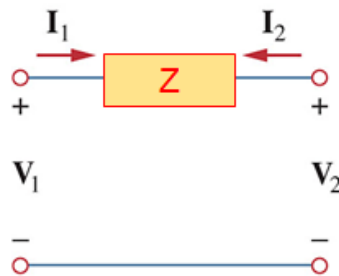


We can find their T
Parameters to be:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{Z} & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Note, following
is equivalent

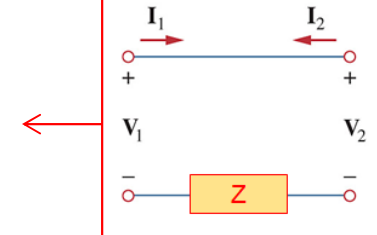

19.5 Transmission Parameters (8)

Properties: Building Block Circuits

- We can use this to construct the following “building block T parameters” to find the T parameters for any ladder type circuit.

$$\begin{bmatrix} 1 & R \\ 0 & 1 \end{bmatrix}$$




$$\begin{bmatrix} 1 & \frac{1}{sC} \\ 0 & 1 \end{bmatrix}$$




$$\begin{bmatrix} 1 & sL \\ 0 & 1 \end{bmatrix}$$



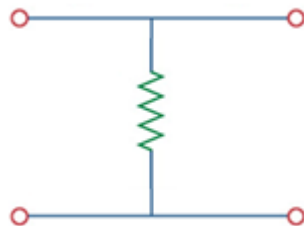
$$\begin{bmatrix} 1 & 0 \\ \frac{1}{R} & 1 \end{bmatrix}$$


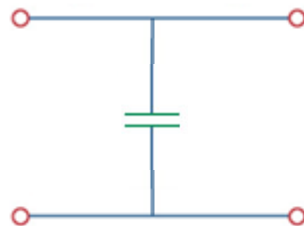
$$\begin{bmatrix} 1 & 0 \\ sC & 1 \end{bmatrix}$$


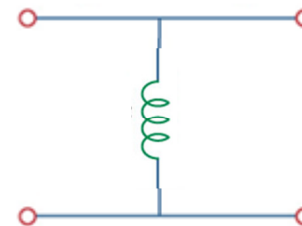
$$\begin{bmatrix} 1 & 0 \\ \frac{1}{sL} & 1 \end{bmatrix}$$



19.5 Transmission Parameters (9)

Properties: Transfer function / Thevenin Equivalent

- The “A” parameter can be used to provide the inverse of the voltage Transfer Function $H(s)$.

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

- Parameters “A” and “B” can be used to find a relationship between the Open Circuit Voltage (V_2) and the Short Circuit Current ($-I_2$).
- We can use this to find the parameters for the Thevenin Equivalent Circuit.


$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{V_1}{V_{oc}}$$

$$V_{Th} = V_{oc} = \frac{V_1}{A}$$


$$Z_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{B}{A}$$

$$B = - \left. \frac{V_1}{I_2} \right|_{V_2=0} = \frac{V_1}{I_{sc}}$$

$$I_N = I_{sc} = \frac{V_1}{B}$$

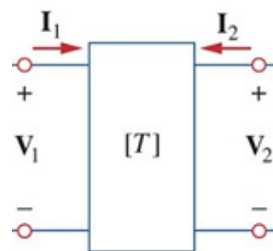

$$V_{Th} = \frac{V_1}{A}$$

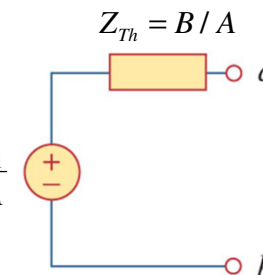


19.5 Transmission Parameters (10)

Transfer Function - Example

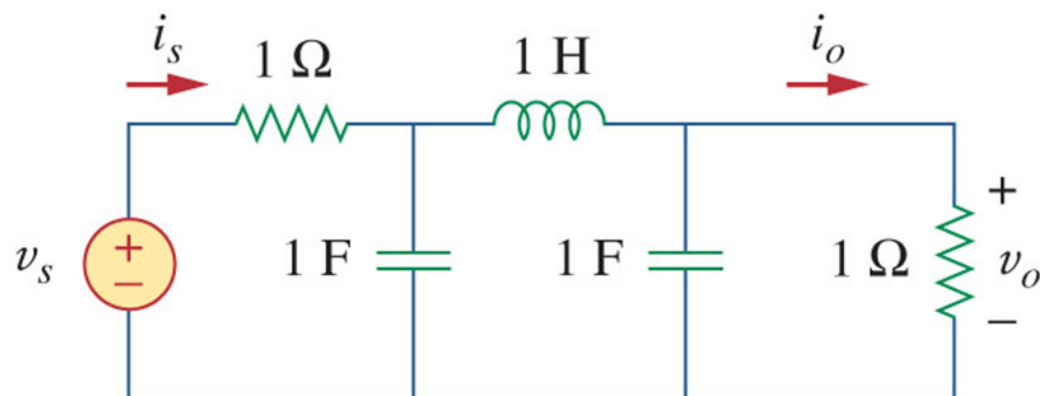Problem 16.80(a)

Find the transfer function $V_o(s)/V_s(s)$ for the following circuit



Answer:


$$H(s) = \frac{1}{s^3 + 2s^2 + 3s + 2}$$

19.5 Transmission Parameters (11)

Transfer Function - Example

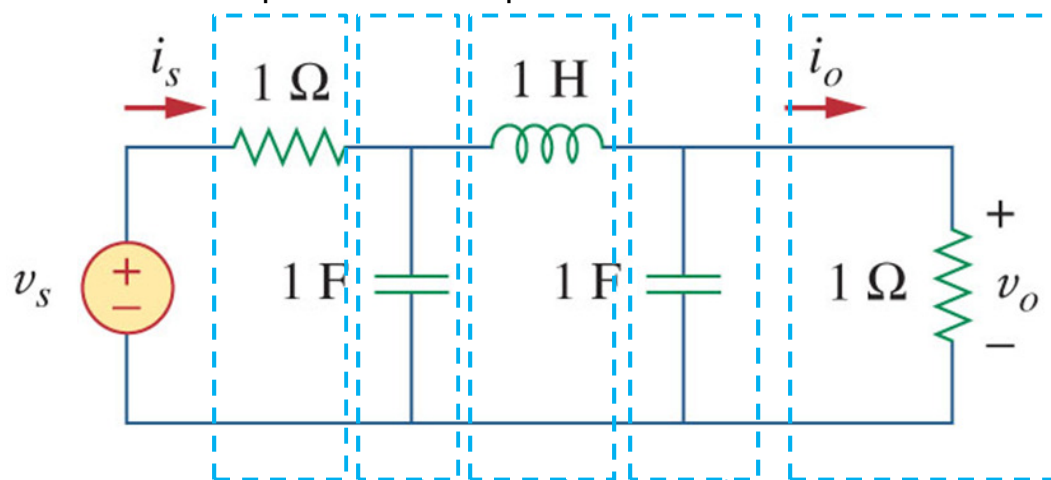Problem 16.80(a) Solution:

- Break up the circuit into a series of cascaded series and shunt components
- Find the composite "T" parameters for the circuit
- Use the relationship between the parameter "A" and the Transfer function



$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

19.5 Transmission Parameters (12)

Transfer Function - Example

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix}$$

Finding the
combined T-matrix

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ (s+1) & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1+s(s+1) & s \\ (s+1) & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1+s(s+1) & s \\ s+s^2(s+1)+(s+1) & s^2 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} s^2+s+1 & s \\ s^3+s^2+2s+1 & s^2 \end{bmatrix}$$

$$\begin{bmatrix} s^3+2s^2+3s+2 & s+s^2 \\ s^3+s^2+2s+1 & s^2 \end{bmatrix}$$

The transfer function can be found
directly from the Transmission
Parameter "A" !

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

$$H(s) = \frac{1}{s^3+2s^2+3s+2}$$


19.5 Transmission Parameters (13)

Example 19.9

The ABCD parameters of the two-port network at right are




$$\mathbf{T} = \begin{bmatrix} 4 & 20 \, \Omega \\ 0.1 \text{ S} & 2 \end{bmatrix}$$

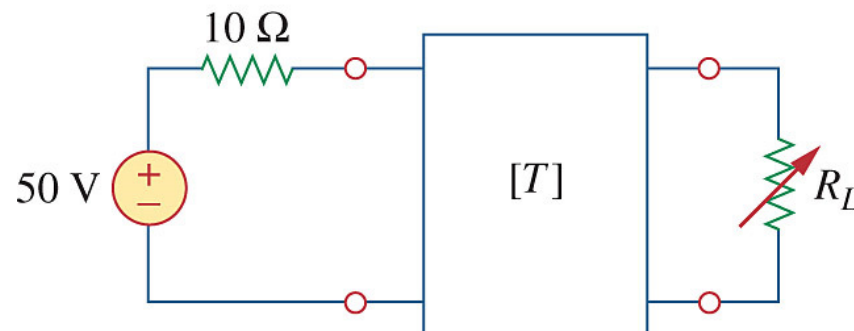Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



The output port is connected to a variable load for maximum power transfer. Find R_L and the maximum power transferred.

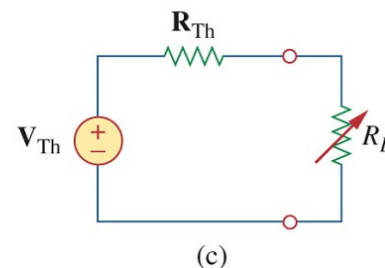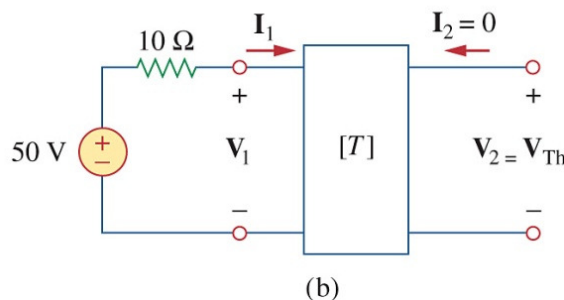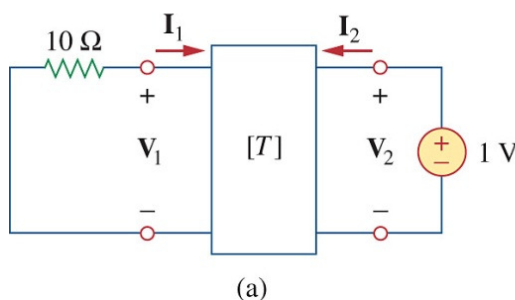Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Answer: $V_{TH} = 10 \text{ V}$; $R_L = 8 \Omega$; $P_m = 3.125 \text{ W}$.

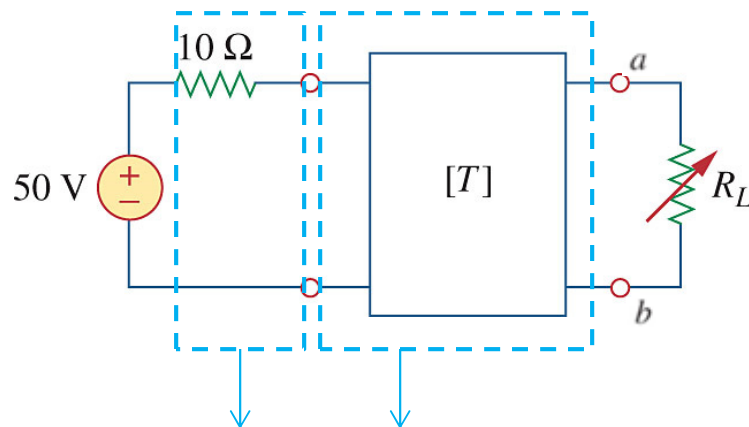19.5 Transmission Parameters (14)


Solution: Example 19.9

- Cascade the Series Resistor with the network
- Find the composite "T" parameters for the circuit
- Use the relationships to find V_{Th} and Z_{Th}



$$[T'] = \begin{bmatrix} 1 & 10 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 4 & 20 \\ 0.1 & 2 \end{bmatrix} = \begin{bmatrix} 5 & 40 \\ 0.1 & 2 \end{bmatrix}$$

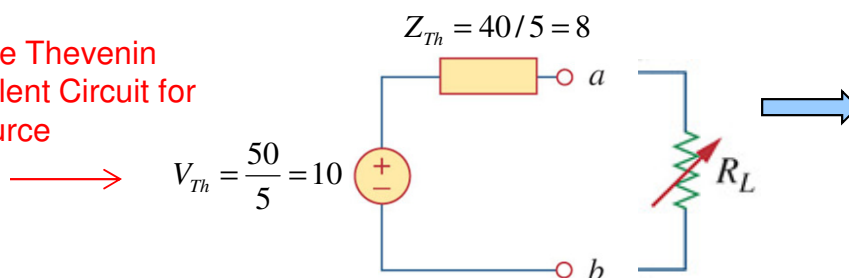Find the Thevenin
Equivalent Circuit for
the source



For Max Power Transfer

$$R_L = Z_{Th} = 8 \Omega$$

$$P_{\max} = I^2 R_L$$


$$P_{\max} = \left(\frac{V_{Th}}{R_L + Z_{Th}} \right)^2 R_L$$

$$P_{\max} = \left(\frac{10}{16} \right)^2 8 = 3.125 \text{ W}$$

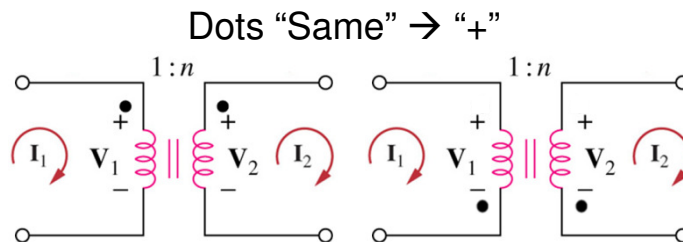19.5 Transmission Parameters (15)

Properties: Building Block Circuits – Ideal Transformer

- We can also use these “building blocks” to model ideal transformers. Remember from Chapter 13




$$V_2 = nV_1$$

$$I_2 = \frac{I_1}{n}$$


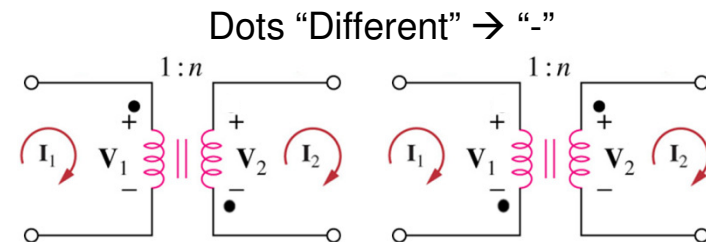
$$\begin{bmatrix} \frac{1}{n} & 0 \\ 0 & n \end{bmatrix}$$



$$V_2 = -nV_1$$

$$I_2 = -\frac{I_1}{n}$$



$$\begin{bmatrix} -\frac{1}{n} & 0 \\ 0 & -n \end{bmatrix}$$


T - parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

19.5 Transmission Parameters (16)

Example 13.8 Revisited

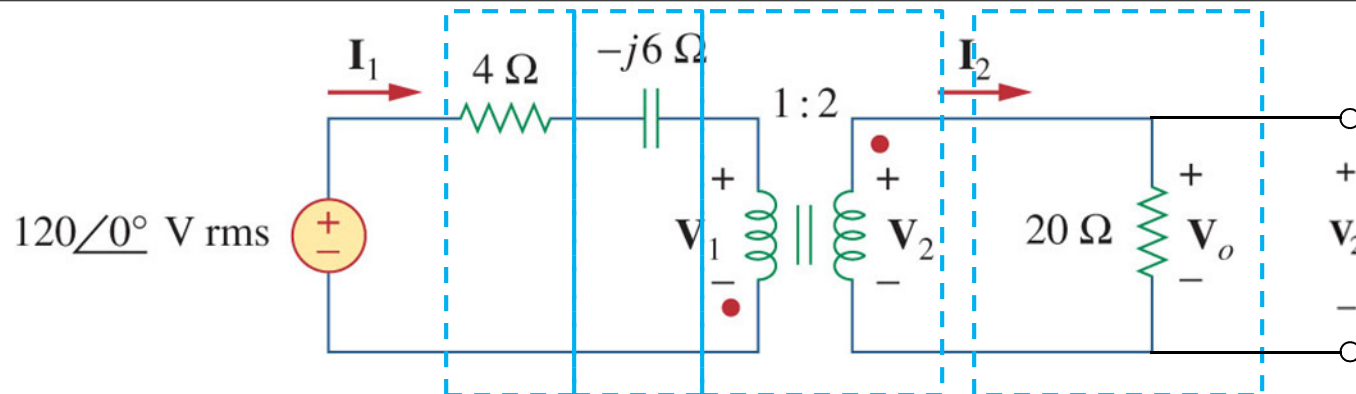

Cascaded T parameters →

$$\begin{bmatrix} 1 & 4 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & -j6 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} -\frac{1}{2} & 0 \\ 0 & -2 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0.05 & 1 \end{bmatrix}$$

a b c d

Using MATLAB: →

```
>> T=a*b*c*d


T =

-0.9000 + 0.6000i -8.0000 + 12.0000i
-0.1000 + 0.0000i -2.0000 + 0.0000i
```

$$V_0 = V_2 = \frac{1}{A} V_1 = \left(\frac{1}{-0.9 + 0.6j} \right) (120 \angle 0^\circ) = 110.94 \angle -146.31^\circ \text{ V}$$

19.5 Transmission Parameters (17)

Example 13.8 Revisited

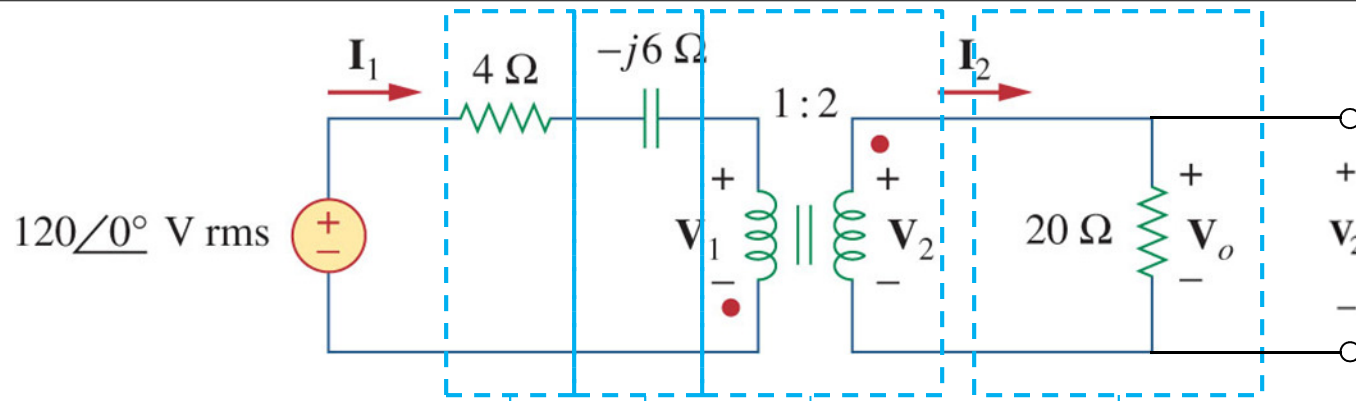

```
>> T=a*b*c*d
```

```
T =
```


```
-0.9000 + 0.6000i  -8.0000 +12.0000i  
-0.1000 + 0.0000i  -2.0000 + 0.0000i
```

$$I_1 = CV_2 = (-0.1)(110.94\angle -146.31^\circ) = 11.09\angle 33.69^\circ \text{ A}$$

$$I_2 = \frac{V_2}{20} = \frac{(110.94\angle -146.31^\circ)}{20} = 5.55\angle -146.31^\circ \text{ A}$$

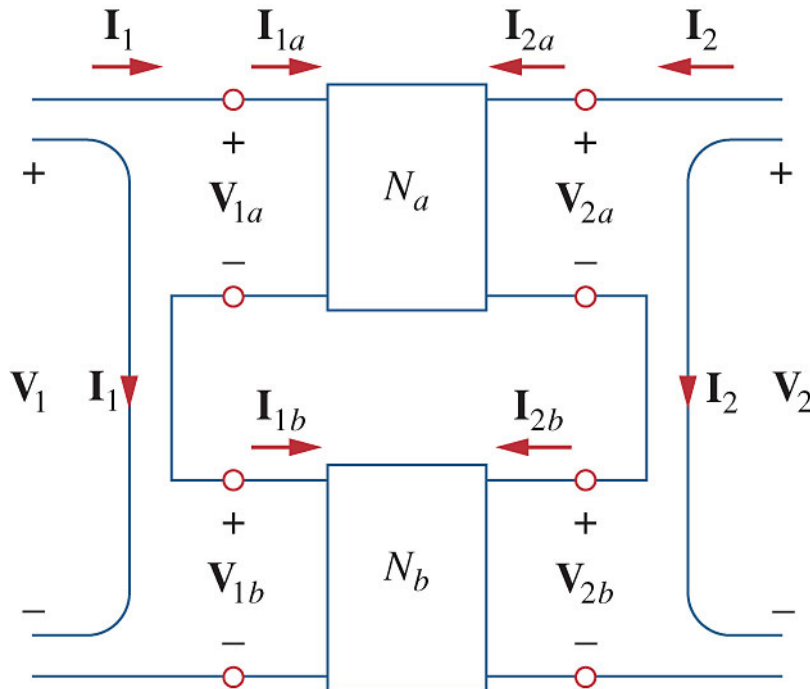19.7 Interconnection of Networks (1)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Series Connection of
two-port networks:

For Impedances; ADD
matrices.

$$Z = Z_a + Z_b$$

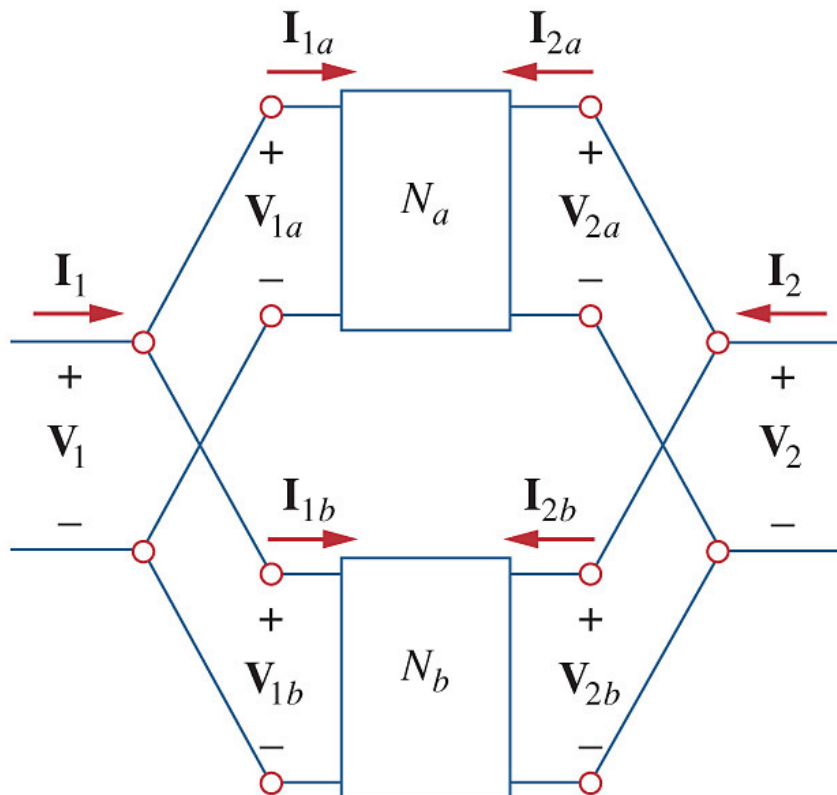19.7 Interconnection of Networks (2)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Parallel Connection of
two-port networks:

For Admittances; ADD
matrices.

$$Y = Y_a + Y_b$$

19.6 Relationships Between Networks

- Use this table to convert between two port parameters

	z		y		h		T	
z	z_{11}	z_{12}	$\frac{y_{22}}{\Delta_y}$	$-\frac{y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$
	z_{21}	z_{22}	$-\frac{y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{C}$	$\frac{D}{C}$
y	$\frac{z_{22}}{\Delta_z}$	$-\frac{z_{12}}{\Delta_z}$	y_{11}	y_{12}	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$	$\frac{D}{B}$	$-\frac{\Delta_T}{B}$
	$-\frac{z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	y_{21}	y_{22}	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$-\frac{1}{B}$	$\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	h_{11}	h_{12}	$\frac{B}{D}$	$\frac{\Delta_T}{D}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	h_{21}	h_{22}	$-\frac{1}{D}$	$\frac{C}{D}$
T	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$-\frac{h_{11}}{h_{21}}$	A	B
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta_y}{y_{21}}$	$-\frac{y_{11}}{y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$-\frac{1}{h_{21}}$	C	D

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21} \quad \Delta_z = z_{11}z_{22} - z_{12}z_{21} \quad \Delta_h = h_{11}h_{22} - h_{12}h_{21} \quad \Delta_T = AD - BC$$

Chapter 19 Review

Z-Parameters

- Parameters:
$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$


- Open circuit the **output** to find z_{11} and z_{21}

$$\begin{aligned} V_1 &= z_{11}I_1 + \cancel{z_{12}I_2}^0 \\ V_2 &= z_{21}I_1 + \cancel{z_{22}I_2}^0 \end{aligned}$$



$$\begin{aligned} V_1 &= z_{11}I_1 \\ V_2 &= z_{21}I_1 \end{aligned}$$

Set $I_1 = 1$ then solve for V_1 and V_2

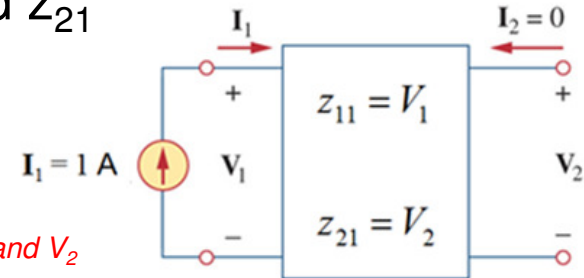


- Open circuit the **input** to find z_{21} and z_{22}

$$\begin{aligned} \cancel{V_1}^0 &= \cancel{z_{11}I_1}^0 + z_{12}I_2 \\ V_2 &= \cancel{z_{21}I_1}^0 + z_{22}I_2 \end{aligned}$$



$$\begin{aligned} V_1 &= z_{12}I_2 \\ V_2 &= z_{22}I_2 \end{aligned}$$


Set $I_2 = 1$ then solve for V_1 and V_2

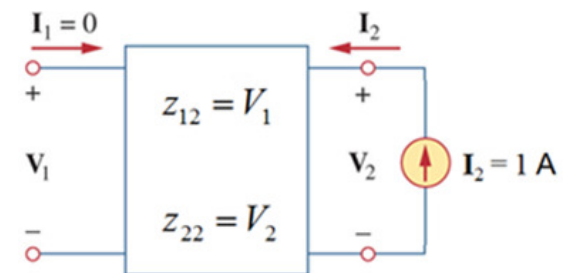

Chapter 19 Review

Z-Parameters (Given a circuit, find Z-parameters)

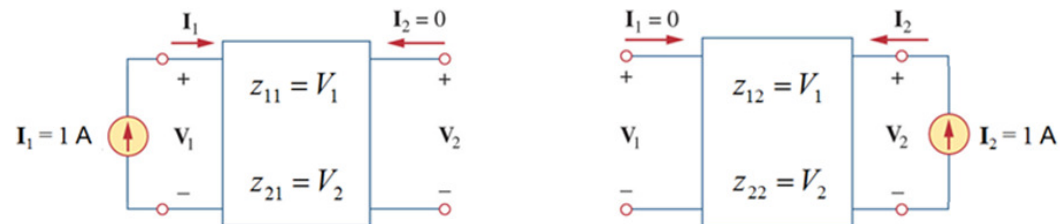
- Solving problems to find z-parameters:
 1. Refer to definition, apply 1 amp source at input and output with opposite port left open (see previous slide)



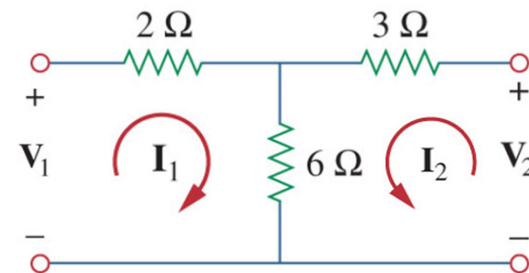2. Sometimes, KVL (mesh current equations) will cause z-parameters to fall right out! :

$$V_1 = 2I_1 + 6(I_1 + I_2) = 8I_1 + 6I_2$$
$$V_2 = 6(I_1 + I_2) + 3I_2 = 6I_1 + 9I_2$$

$$\mathbf{z} = \begin{bmatrix} 8 & 6 \\ 6 & 9 \end{bmatrix} \Omega$$




This mesh defined in counter clockwise direction for convenience

Chapter 19 Review


Z-Parameters (Given Z parameters, find circuit parameters)

- If given, z-parameters can use following techniques to find other circuit parameters (V_1 , V_2 , I_1 , I_2 , etc.):

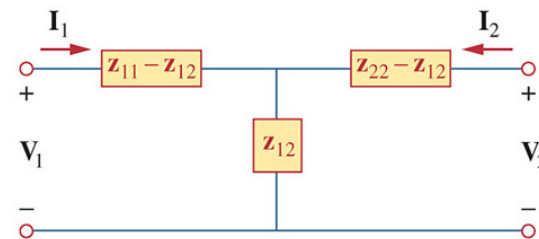1. Apply the model and solve the circuit:



Reciprocal
Network

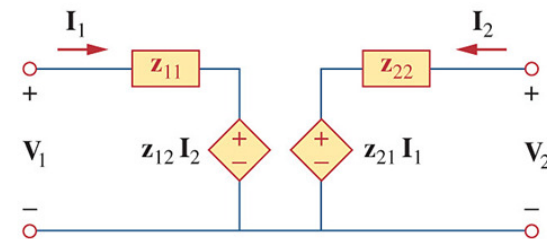

General
Network

2. Substitute the defining equations into your analysis:

Mesh Analysis


$$10 = 5I_1 + V_1 + 10(I_1 + I_2)$$

$$0 = V_2 + 10(I_1 + I_2) + 20I_2$$

Substitute for V_1 and V_2

$$10 = 5I_1 + (12I_1 + 8I_2) + 10(I_1 + I_2)$$
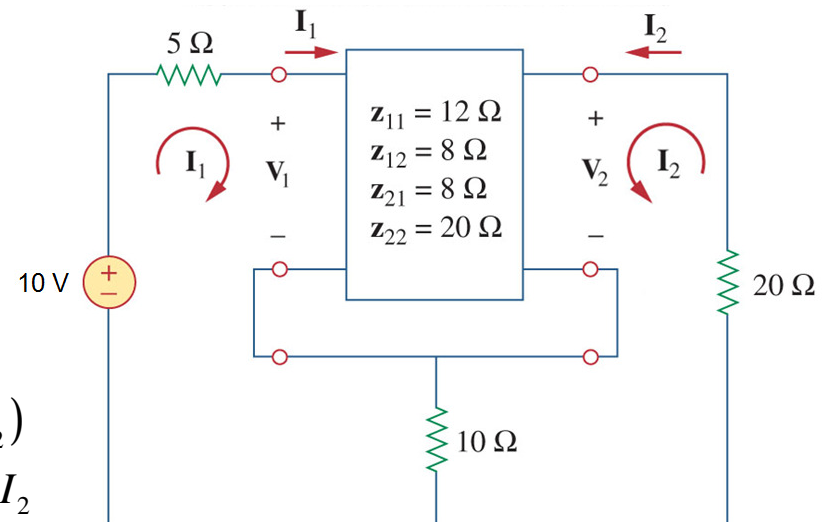
$$0 = (8I_1 + 20I_2) + 10(I_1 + I_2) + 20I_2$$



Chapter 19 Review

Y-Parameters

- Parameters:
$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$


- Short circuit the **output** to find y_{11} and y_{21}

$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} \cancel{V_2^0} \\ I_2 &= y_{21} V_1 + y_{22} \cancel{V_2^0} \end{aligned}$$



$$\begin{aligned} I_1 &= y_{11} V_1 \\ I_2 &= y_{21} V_1 \end{aligned}$$

Set $V_1 = 1$ then solve for I_1 and I_2

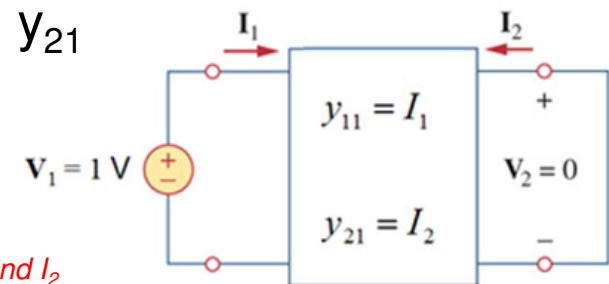


- Short circuit the **input** to find y_{21} and y_{22}

$$\begin{aligned} I_1 &= y_{11} \cancel{V_1^0} + y_{12} V_2 \\ I_2 &= y_{21} \cancel{V_1^0} + y_{22} V_2 \end{aligned}$$



$$\begin{aligned} I_1 &= y_{12} V_2 \\ I_2 &= y_{22} V_2 \end{aligned}$$

Set $V_2 = 1$ then solve for I_1 and I_2

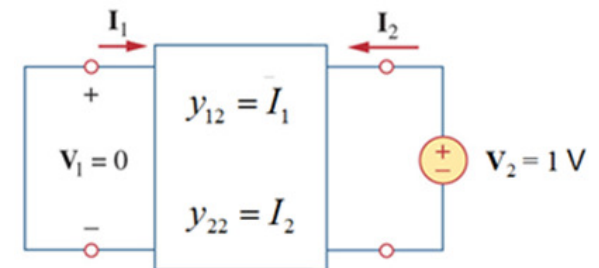


Chapter 19 Review


Y-Parameters (Solving Problems)

- To solve Y-parameter problems, can use these techniques

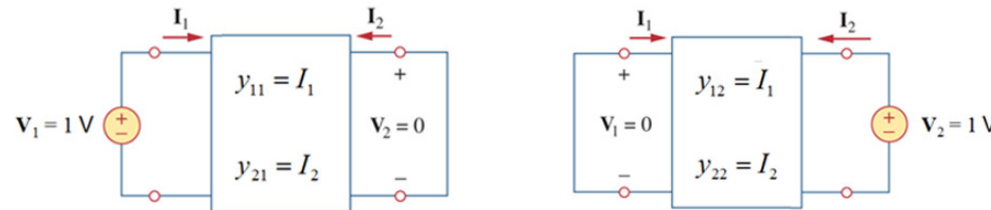1. Apply method from previous slide. Apply 1 Volt source at input and output while shorting opposite port



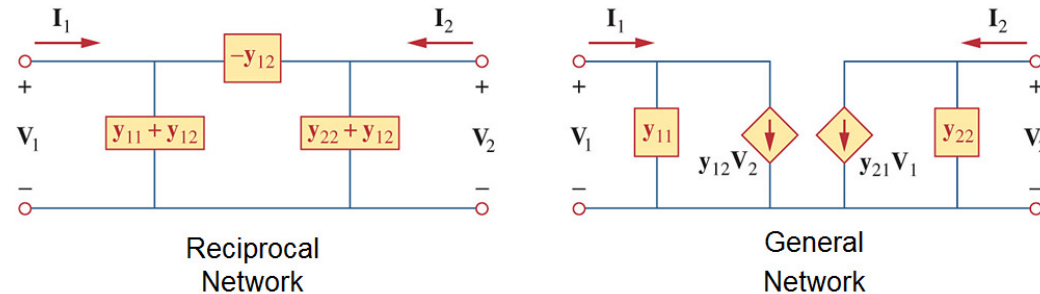2. If given Y parameters can apply the model and solve the circuit:



3. Make it easy on yourself! Use conversions from $Z \rightarrow Y$ or $Y \rightarrow Z$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \left(\frac{1}{\Delta_y} \right) \begin{bmatrix} y_{22} & -y_{12} \\ -y_{21} & y_{11} \end{bmatrix}$$

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21}$$

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \left(\frac{1}{\Delta_z} \right) \begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix}$$

$$\Delta_z = z_{11}z_{22} - z_{12}z_{21}$$

Chapter 19 Review

H-Parameters

- Parameters (hybrid of z and y):

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$


- Short circuit the **output** to find h_{11} and h_{21}

$$\begin{aligned} V_1 &= h_{11} I_1 + \cancel{h_{12} V_2}^0 \\ I_2 &= h_{21} I_1 + \cancel{h_{22} V_2}^0 \end{aligned}$$



$$\begin{aligned} V_1 &= h_{11} I_1 \\ I_2 &= h_{21} I_1 \end{aligned}$$

Set $I_1 = 1$ then solve for V_1 and I_2

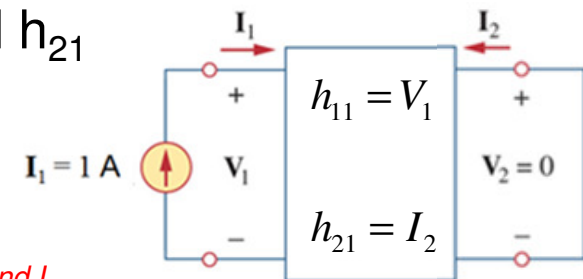


- Open circuit the **input** to find h_{21} and h_{22}

$$\begin{aligned} V_1 &= \cancel{h_{11} I_1}^0 + h_{12} V_2 \\ I_2 &= \cancel{h_{21} I_1}^0 + h_{22} V_2 \end{aligned}$$



$$\begin{aligned} V_1 &= h_{12} V_2 \\ I_2 &= h_{22} V_2 \end{aligned}$$

Set $V_2 = 1$ then solve for V_1 and I_2

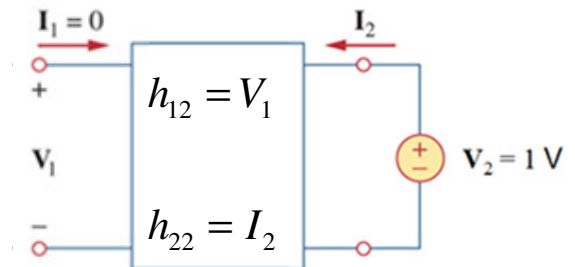


Chapter 19 Review

H-Parameters (Solving Problems)


- To solve H-parameter problems, can use these techniques

1. Apply methods from previous slide.

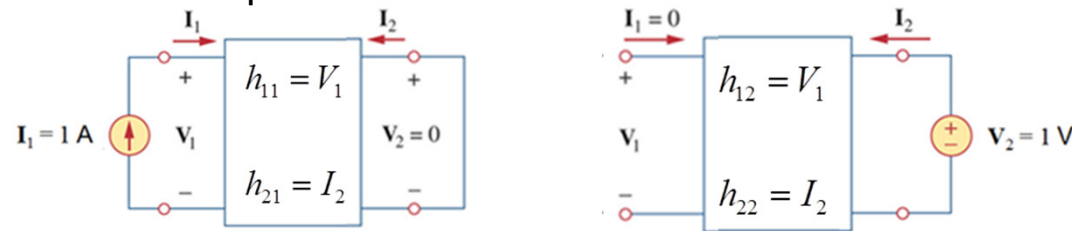

2. H parameters can be found by performing a set of tests on the device
 - a) Shorting the output and applying a current
 - b) Leaving the input open and applying a voltage across the output

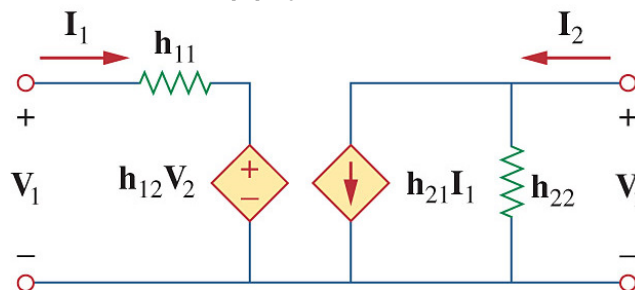3. If given H parameters can apply the model and solve the circuit:




4. If helpful, use conversion tables

Chapter 19 Review

H-Parameters (Transistor Model)

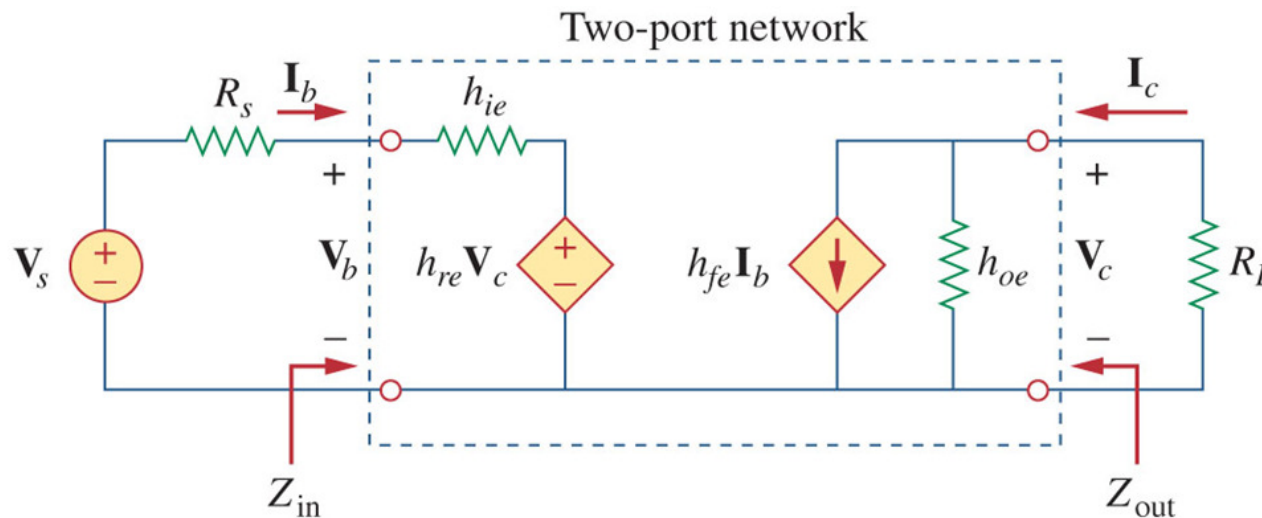
- H parameters are often used in modeling transistors
- Parameters vary depending on biasing conditions
- Spec sheets often use different subscripts:
 - $h_{11} \rightarrow h_{ie}$ = Base input impedance
 - $h_{12} \rightarrow h_{re}$ = Reverse voltage feedback ration
 - $h_{21} \rightarrow h_{fe}$ = Base-collector current gain
 - $h_{22} \rightarrow h_{oe}$ = Output admittance



Chapter 19 Review

H-Parameters (Transistor Model)

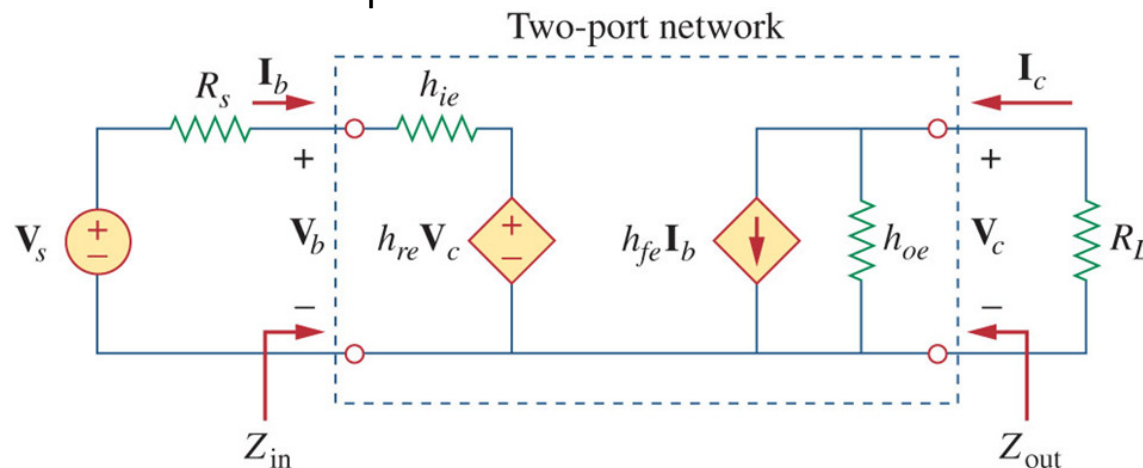- Equations for calculating input impedance, output impedance, voltage gain, and current gain for simple transistor circuit:
 - V_s and R_s can be the Thevenin equivalent source driving the input.
 - R_L can be the input impedance looking into the load of the circuit connected to the output



Input Impedance

$$Z_{in} = \frac{V_b}{I_b} = h_{ie} - \frac{h_{re} h_{fe} R_L}{1 + h_{oe} R_L}$$

Current Gain

$$A_i = \frac{I_c}{I_b} = \frac{h_{fe}}{1 + h_{oe} R_L}$$

Output Impedance

$$Z_{out} = \frac{V_c}{I_c} \bigg|_{V_s=0} = \frac{R_s + h_{ie}}{(R_s + h_{ie}) h_{oe} - h_{re} h_{fe}}$$

Voltage Gain

$$A_v = \frac{V_c}{V_b} = \frac{-h_{fe} R_L}{h_{ie} + (h_{ie} h_{oe} - h_{re} h_{fe}) R_L}$$

Chapter 19 Review

Transmission ("T") Parameters

- Parameters: $V_1 = AV_2 - BI_2$
 $I_1 = CV_2 - DI_2$

- Perform the analysis with the **output** Open Circuited ($I_2=0$)

$$\begin{array}{l} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{array} \xrightarrow{I_2=0} \begin{array}{l} V_1 = AV_2 \\ I_1 = CV_2 \end{array} \xrightarrow{} \begin{array}{l} A = \frac{V_1}{V_2} \\ C = \frac{I_1}{V_2} \end{array}$$


- Perform the analysis with the **output** Short Circuited ($V_2=0$)

$$\begin{array}{l} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{array} \xrightarrow{V_2=0} \begin{array}{l} V_1 = -BI_2 \\ I_1 = -DI_2 \end{array} \xrightarrow{} \begin{array}{l} B = -\frac{V_1}{I_2} \\ D = -\frac{I_1}{I_2} \end{array}$$

Chapter 19 Review

Transmission ("T") Parameters (Cascading)

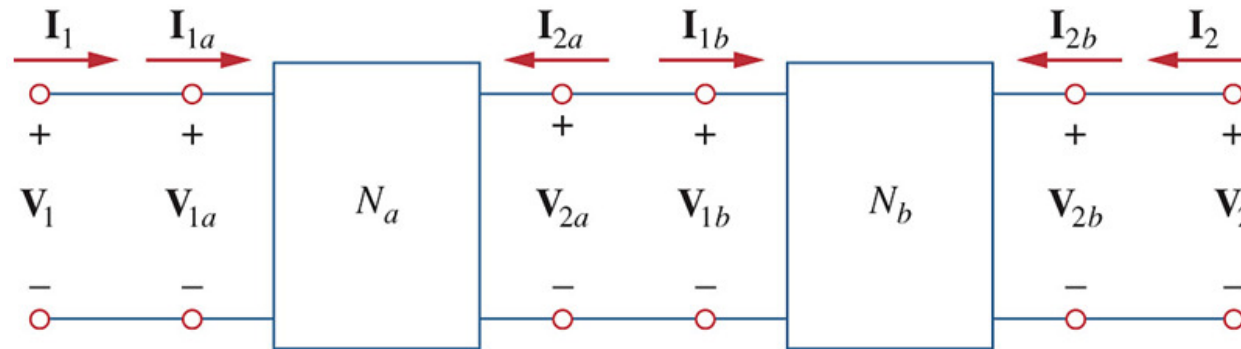- Primary benefit of "T"-Parameters is their ability to be cascaded.



$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$-I_{2a} = I_{1b}$$




$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Chapter 19 Review

T - Parameters (Building Block models)

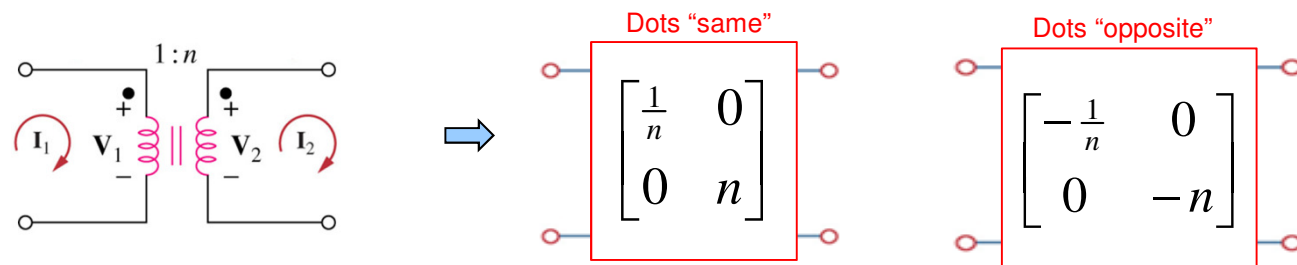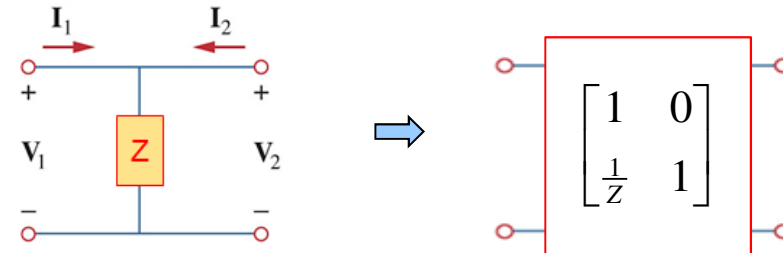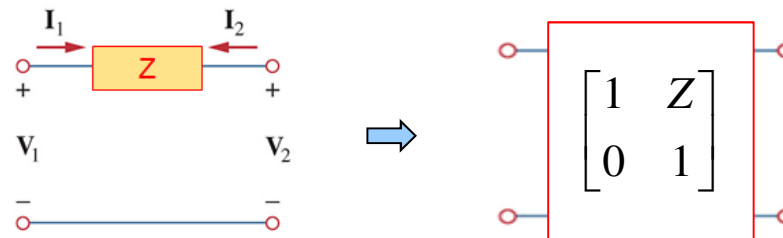
- We can create “building block” models of components by finding their T-parameters and use the cascading property to find the T-parameters for the complete circuit/system.



Chapter 19 Review

T - Parameters (Building Block models)

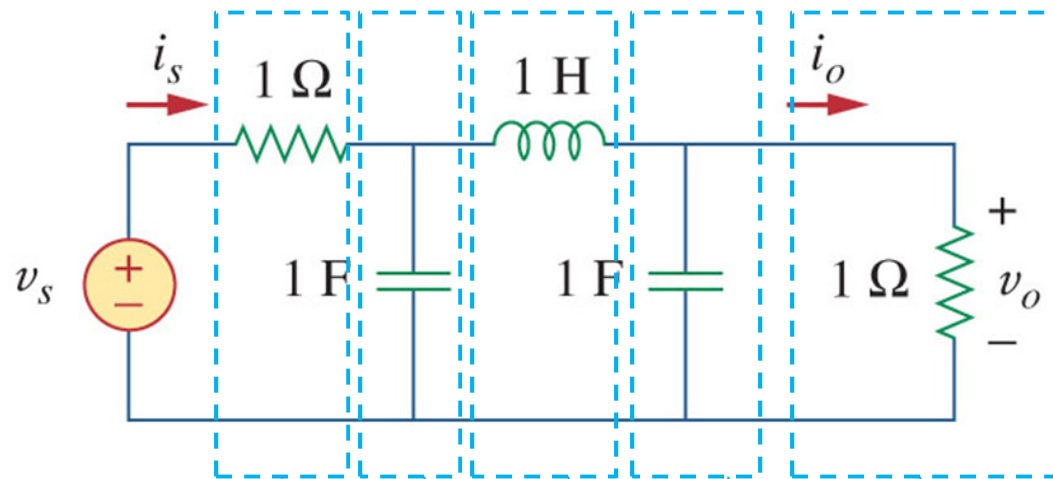- With “Building Block” approach, circuits can be broke up into discrete components and analyzed using T-parameters



$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)}$$

Chapter 19 Review


T - Parameters (Useful Properties)

- The T parameters give us useful properties in the analysis of circuits:

- Open Circuit Voltage Transfer Function:

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{H(s)} \quad H(s) = \frac{1}{A}$$

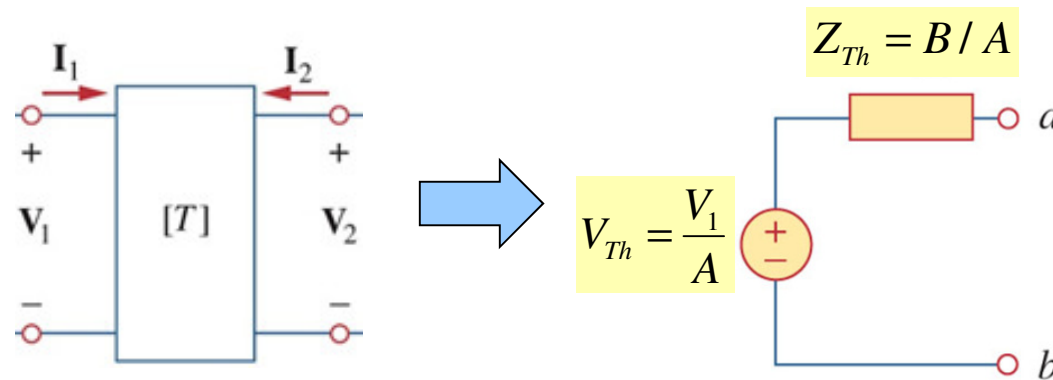- Thevenin Equivalent Circuit (Replace circuit as a source)



Chapter 19 Review

Conversion between Parameters

- Conversion tables exist to convert between parameters

	z		y		h		T	
z	z ₁₁	z ₁₂	$\frac{y_{22}}{\Delta_y}$	$-\frac{y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$
	z ₂₁	z ₂₂	$-\frac{y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{C}$	$\frac{D}{C}$
y	$\frac{z_{22}}{\Delta_z}$	$-\frac{z_{12}}{\Delta_z}$	y ₁₁	y ₁₂	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$	$\frac{D}{B}$	$-\frac{\Delta_T}{B}$
	$-\frac{z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	y ₂₁	y ₂₂	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$-\frac{1}{B}$	$\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	h ₁₁	h ₁₂	$\frac{B}{D}$	$\frac{\Delta_T}{D}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	h ₂₁	h ₂₂	$-\frac{1}{D}$	$\frac{C}{D}$
T	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$-\frac{h_{11}}{h_{21}}$	A	B
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta_y}{y_{21}}$	$-\frac{y_{11}}{y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$-\frac{1}{h_{21}}$	C	D

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21} \quad \Delta_z = z_{11}z_{22} - z_{12}z_{21} \quad \Delta_h = h_{11}h_{22} - h_{12}h_{21} \quad \Delta_T = AD - BC$$