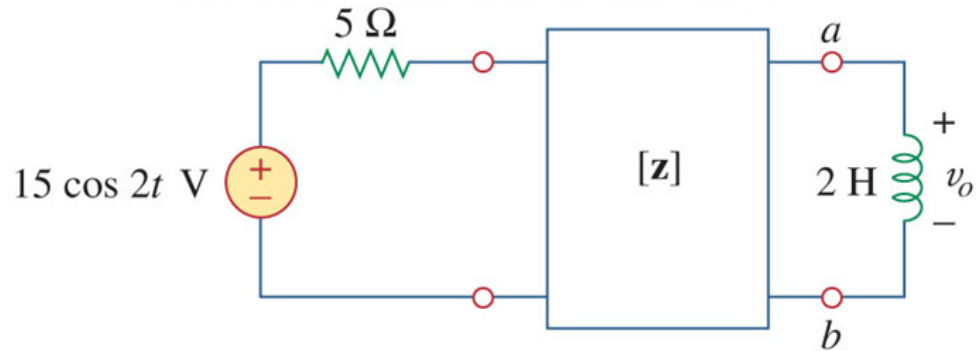


IUPUI ECE 202 Spring 2015:

Homework #11 (Due in class: April 20, 2015)      Name: \_\_\_\_\_

---


1. (Prob. 19.16 from Text) For the circuit shown, at  $\omega = 2 \text{ rad/s}$ ,  $\mathbf{z}_{11} = 10 \Omega$ ,  $\mathbf{z}_{12} = \mathbf{z}_{21} = j6 \text{ ohms}$ ,  $\mathbf{z}_{22} = 4 \Omega$ . Obtain the Thevenin equivalent circuit at terminals  $a - b$  and calculate  $v_o$ :



IUPUI ECE 202 Spring 2015:  
Homework #11 (Due in class: April 20, 2015) Name:

---

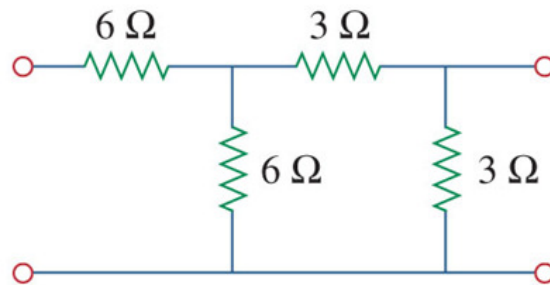
2. (Prob. 19.18 from Text) Calculate the y parameters for the circuit below:



IUPUI ECE 202 Spring 2015:  
Homework #11 (Due in class: April 20, 2015) Name: \_\_\_\_\_

---

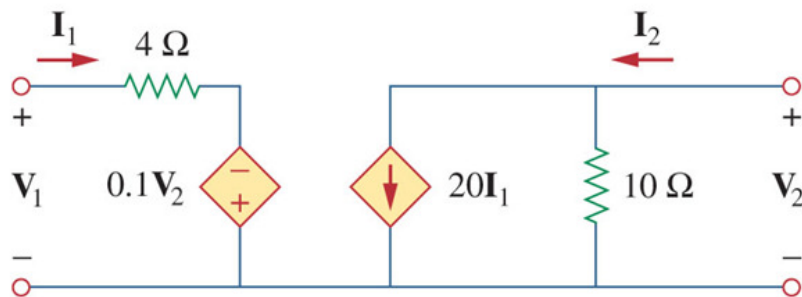3. (Prob. 19.27 from Text) Find the y parameters for the circuit below:




IUPUI ECE 202 Spring 2015:  
Homework #11 (Due in class: April 20, 2015) Name: \_\_\_\_\_

---

4. (Prob. 19.36 from Text) For the two-port shown below, find:

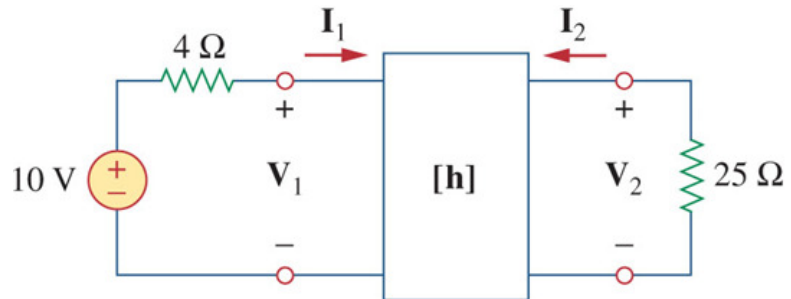- a)  $V_2/V_1$
- b)  $I_2/I_1$
- c)  $I_1/V_1$
- d)  $V_2/I_1$


$$[h] = \begin{bmatrix} 16 \, \Omega & 3 \\ -2 & 0.01 \, \Omega^{-1} \end{bmatrix}$$



IUPUI ECE 202 Spring 2015:  
Homework #11 (Due in class: April 20, 2015) Name:

---

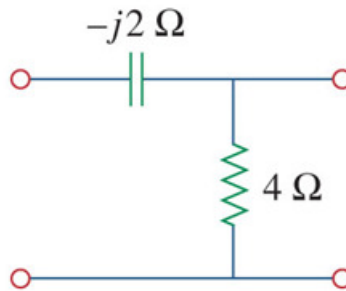
5. (Prob. 19.45 from Text) Find the **ABCD** parameters for the circuit below:



IUPUI ECE 202 Spring 2015:  
Homework #11 (Due in class: April 20, 2015) Name: \_\_\_\_\_

---

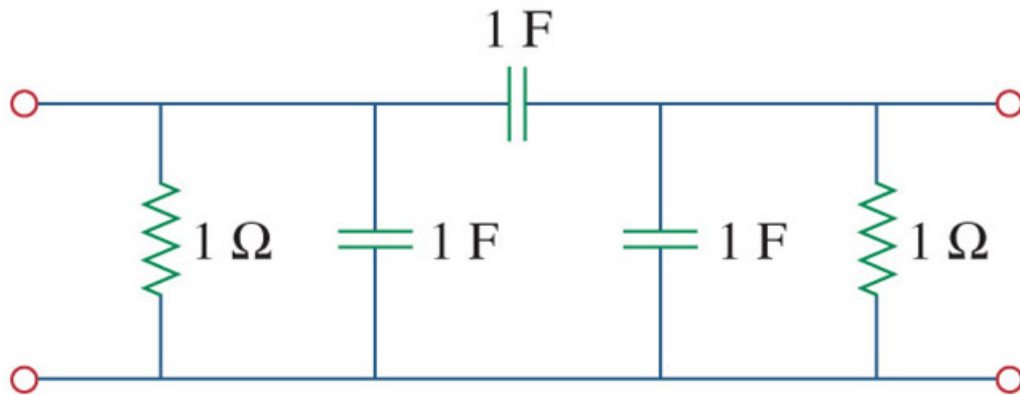6. (Prob. 19.49 from Text) Using impedances in the  $s$ -domain, obtain the transmission (**ABCD**) parameters for the circuit below:



IUPUI ECE 202 Spring 2015:

Homework #11 (**Due in class: April 20, 2015**)      Name: \_\_\_\_\_

---

7. (Prob. 19.94 from Text) A transistor in its common-emitter mode is specified by the following  $\mathbf{h}$  parameters:

$$[\mathbf{h}] = \begin{bmatrix} 200 \, \Omega & 0 \\ 100 & 10^{-6} \, \Omega^{-1} \end{bmatrix}$$

Two such identical transistors are connected in cascade to form a two-stage amplifier used at audio frequencies. If the amplifier is terminated by a  $4 \, \text{k}\Omega$  resistor, calculate the overall voltage gain  $A_v$  and input impedance  $Z_{in}$ .

*Hint: Use the equations in section 19.9.1 for  $A_v$  and  $Z_{in}$ .*