

# Chapter 13


## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers
- 13.9 Applications
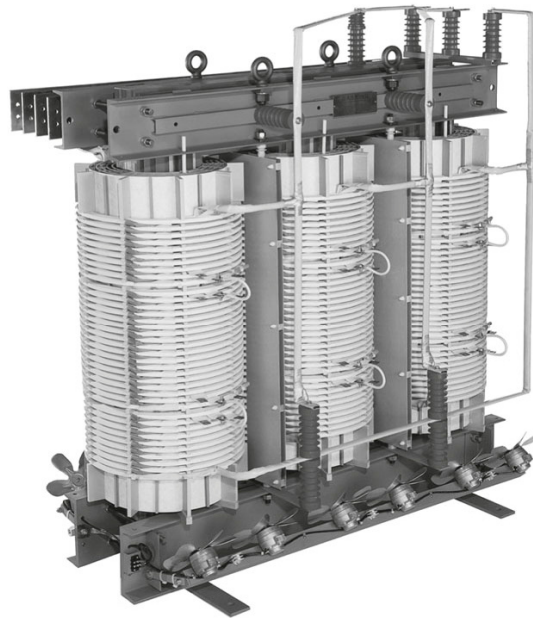
## 13.1 What is a transformer? (1)

- It is an electrical device designed on the basis of the concept of magnetic coupling
- It uses magnetically coupled coils to transfer energy from one circuit to another
- It is the key circuit elements for stepping up or stepping down ac voltages or currents, impedance matching, isolation, etc.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)



(b)


ECE 202 Ch 13

Courtesy of: (a) Electric Service Co., (b) Jensen Transformers
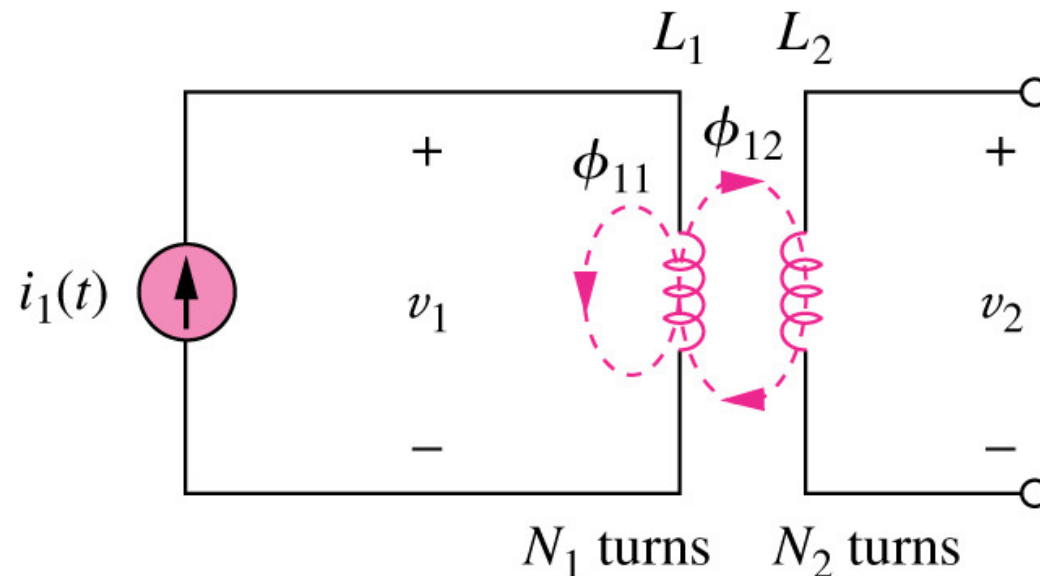
## 13.2 Mutual Inductance (1)


- Mutual Inductance

- When two inductors (or coils) are in close proximity of each other, the magnetic flux caused by current in one coil links with the other coil, thereby inducing voltage in the latter.


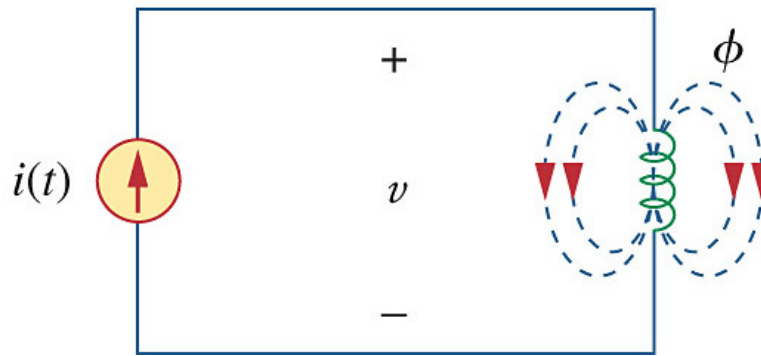
## 13.2 Mutual Inductance (2)

- First consider a single inductor, a coil with  $N$  turns:



When current  $i$  flows through the coil, a magnetic flux  $\Phi$  is produced around it.

- According to Faraday's law, the voltage  $v$  induced in the coil is proportional to the number of turns  $N$  and the time rate of change of magnetic flux  $\Phi$ :

$$v = N \frac{d \phi}{d t}$$

## 13.2 Mutual Inductance (3)

- Voltage induced in the coil given by:
- But the flux  $\Phi$  is produced by current  $i$  so that any change in  $\Phi$  is caused by a change in the current:
- Recall the voltage-current relationship for an inductor:
- The “Self” inductance  $L$  of the inductor is thus given by:
- Self-inductance  $L$  relates the voltage induced in a coil by a time-varying current in the same coil.

$$v = N \frac{d \phi}{d t}$$


$$v = N \frac{d \phi}{d i} \frac{d i}{d t}$$

$$v = L \frac{d i}{d t}$$

$$L = N \frac{d \phi}{d i}$$
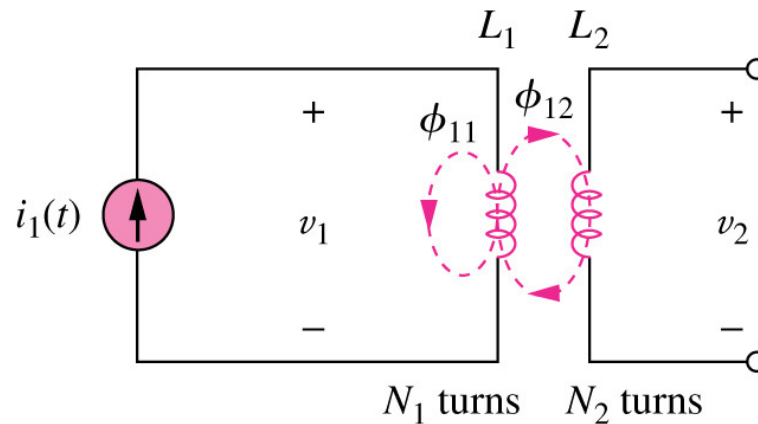
## 13.2 Mutual Inductance (4)

- Now consider two coils with self-inductances  $L_1$  and  $L_2$  that are in close proximity of each other:



Coil 1 has  $N_1$  turns

Coil 2 has  $N_2$  turns.


*Assume coil 2 carries no current.*

- The total magnetic flux  $\Phi_1$  emanating from coil 1 has two components:
  - $\Phi_{11}$  links only coil 1
  - $\Phi_{12}$  links both coils

$$\phi_1 = \phi_{11} + \phi_{12}$$

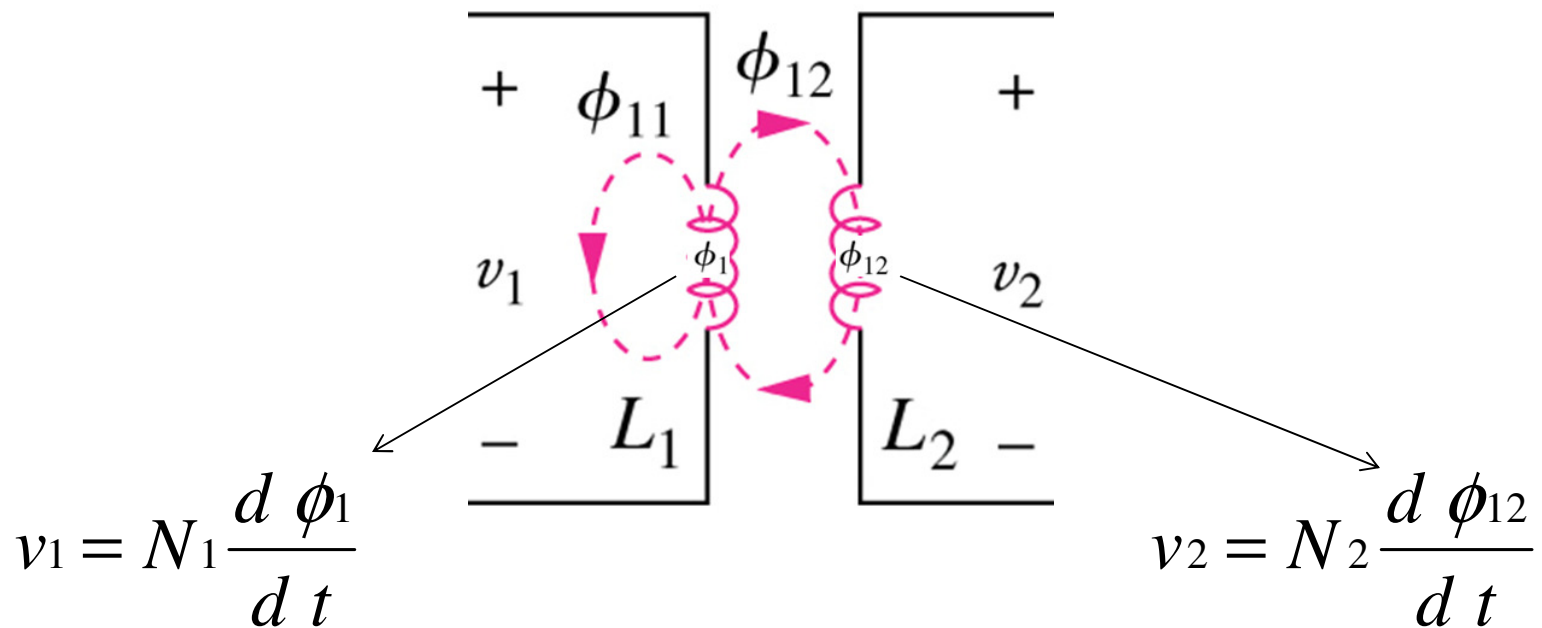
## 13.2 Mutual Inductance (5)

- Although the two coils are physically separated, they are magnetically coupled.
- The voltage induced in each coil is proportional to the flux in each coil.


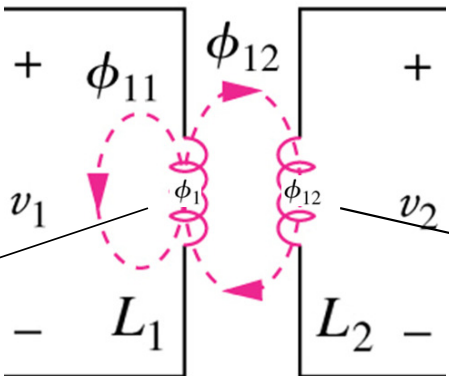
## 13.2 Mutual Inductance (6)

- The voltage equations can be rewritten as follows:



$v_1 = N_1 \frac{d \phi_1}{d t}$

$v_1 = N_1 \frac{d \phi_1}{d i_1} \frac{d i_1}{d t}$

$v_1 = L_1 \frac{d i_1}{d t}$

$v_2 = N_2 \frac{d \phi_{12}}{d t}$

$v_2 = N_2 \frac{d \phi_{12}}{d i_1} \frac{d i_1}{d t}$

$v_2 = M_{21} \frac{d i_1}{d t}$

$v_2$  is the open-circuit mutual voltage (or induced voltage) across coil 2


$L_1$  is the self-inductance of coil 1

$M_{21}$  is the mutual inductance of coil 2 with respect to coil 1


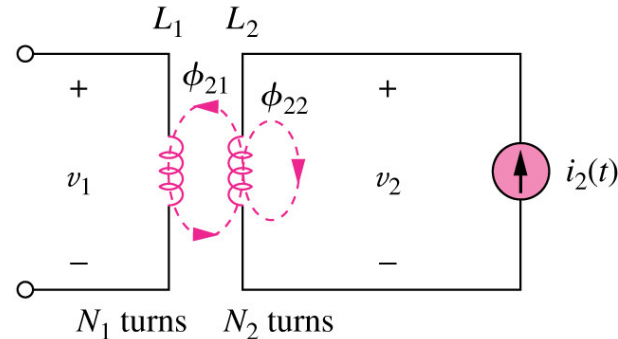
## 13.2 Mutual Inductance (7)

- Suppose now we let current  $i_2$  flow in coil 2 while coil 1 carries no current:



- The magnetic flux  $\Phi_2$  emanating from coil 2 comprises flux  $\Phi_{22}$  that links only coil 2 and flux  $\Phi_{21}$  that links both coils:

$$\phi_2 = \phi_{21} + \phi_{22}$$

- The resulting symmetry is true:


$$v_2 = L_2 \frac{d i_2}{d t} \quad v_1 = M_{12} \frac{d i_2}{d t} \quad M_{12} = N_1 \frac{d \phi_{21}}{d i_2}$$

## 13.2 Mutual Inductance (8)

- $M_{12} = M_{21} = M$  ; The “Mutual inductance” between the coils
- Mutual inductance  $M$  is measured in Henrys (just like inductors)
- Mutual inductance only exists when inductors or coils are in close proximity and the circuits are driven by time-varying sources
- Although mutual inductance  $M$  is always a positive quantity, the mutual voltage  $M \, di/dt$  may be negative or positive, just like the self-induced voltage  $L \, di/dt$  (determined by “Dot” convention)
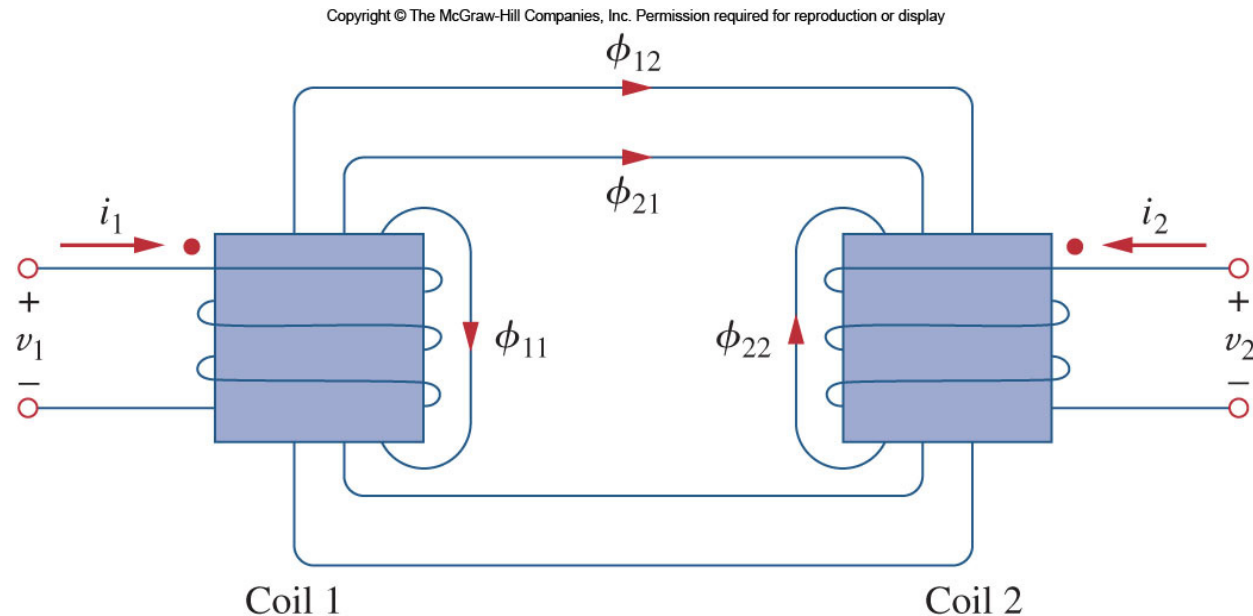
## 13.2 Mutual Inductance (9)

- Self-induced voltage polarity is determined by the reference direction of the current and the reference polarity of the voltage,
- The polarity of the mutual voltage is not as easy to determine (depends on winding direction of the coils).
- We use the dot convention to determine





## 13.2 Mutual Inductance (10)

### “Dot Convention”

- If a current **enters** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **positive** at the dotted terminal of the second coil.



Voltage is  
“Negative”

Enters the  
“Un-Dotted” side

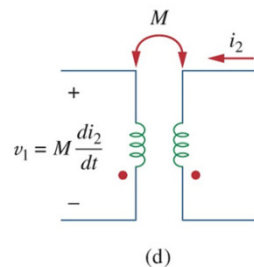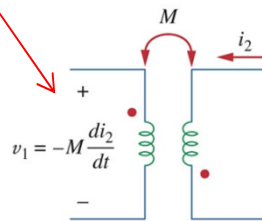

Enters the “Dot”

Voltage is  
“Positive”

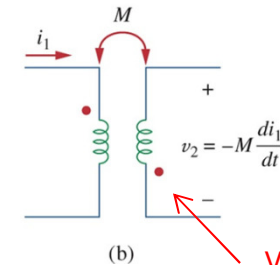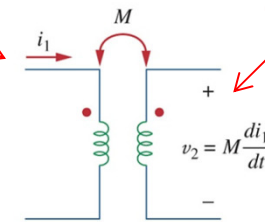

Voltage is  
“Positive”  
At “Dotted”  
Terminal


- Alternatively, if a current **leaves** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **negative** at the dotted terminal of the second coil.

## 13.2 Mutual Inductance (11)
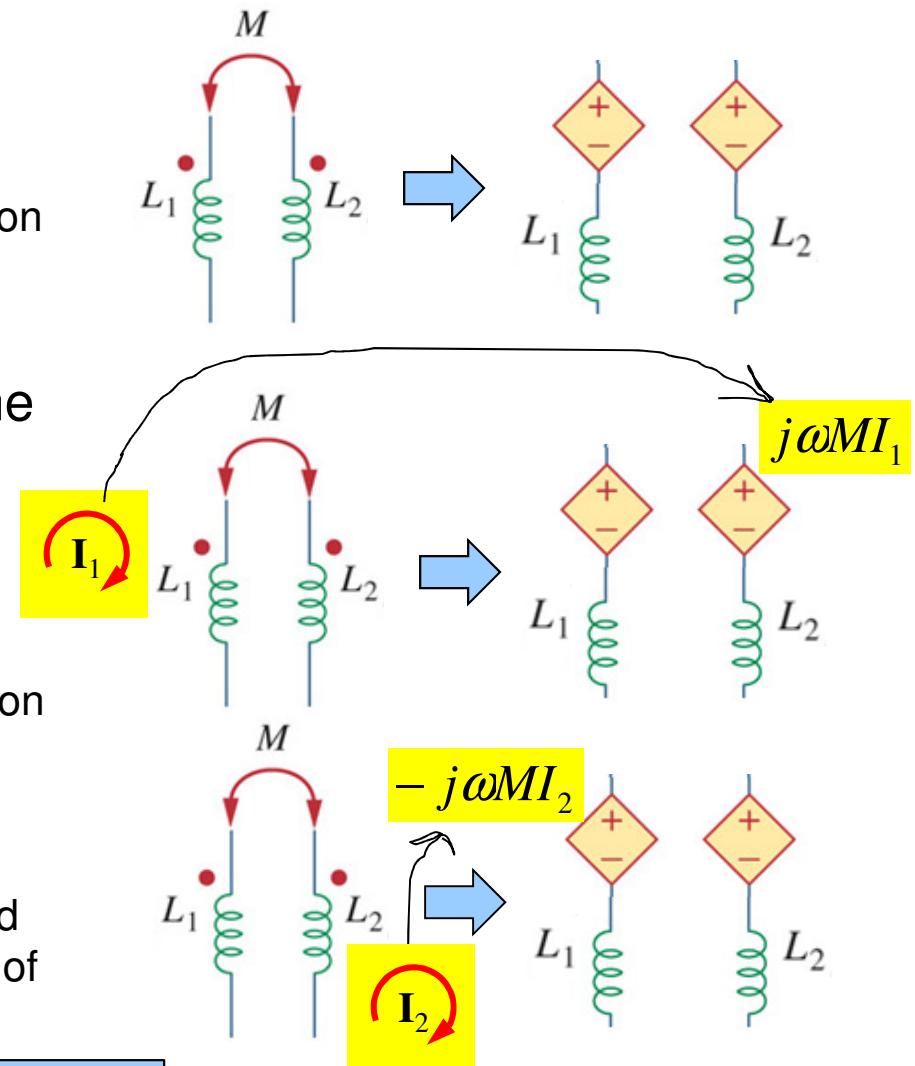
### “The Model” (Phasor domain)

- Replace the “Dot” with a controlled voltage source.
  - Place on same side as the Dot
  - Positive terminal in same direction as the Dot
- Now look at the current entering each dot to determine the magnitude of the voltage source
  - If the current enters the dotted terminal, it will induce a positive voltage in the controlled source on the opposite terminal of  $j\omega M(I)$
  - If the current enters the “un-dotted” terminal, it will induce a negative voltage in the controlled source on the opposite terminal of  $-j\omega M(I)$


Note: This method differs slightly from the text



KEY CONCEPT !

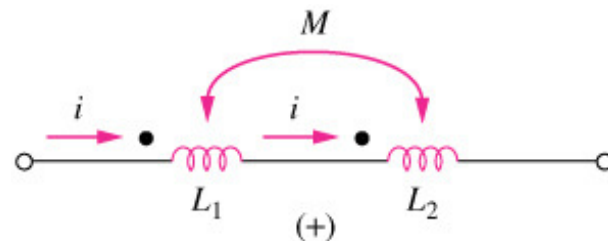
## 13.2 Mutual Inductance (12)

Dot convention for coils in series; the sign indicates the polarity of the mutual voltage



$$L = L_1 + L_2 + 2M$$

(series - aiding connection)

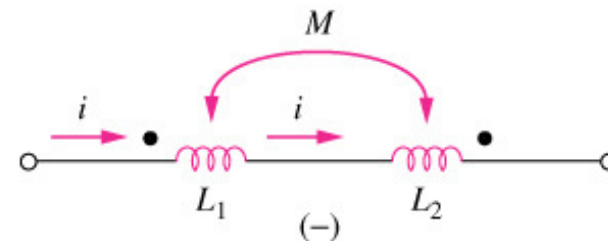

$$L = L_1 + L_2 - 2M$$

(series - opposing connection)


We can show this using the model!

## 13.2 Mutual Inductance (13)

### Example Problem 13.1
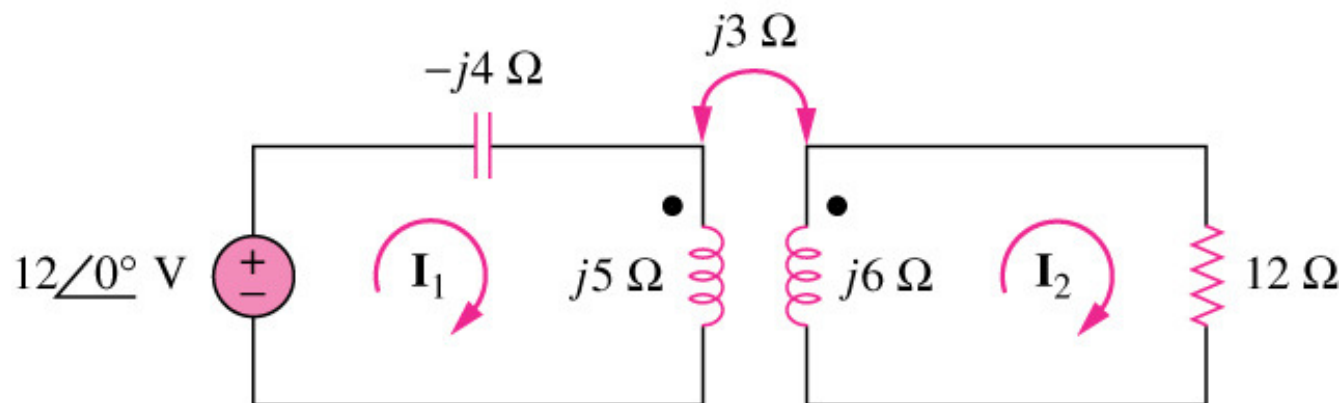
#### Example 13.1 (Textbook)

Calculate the phasor currents  $I_1$  and  $I_2$  in the circuit shown below.





Ans:  $I_1 = 13.02 \angle -49.40^\circ \text{ A}$ ;  $I_2 = 2.91 \angle 14.04^\circ \text{ A}$

## 13.2 Mutual Inductance (14)

### Example Problem 13.1

First, replace with the model:

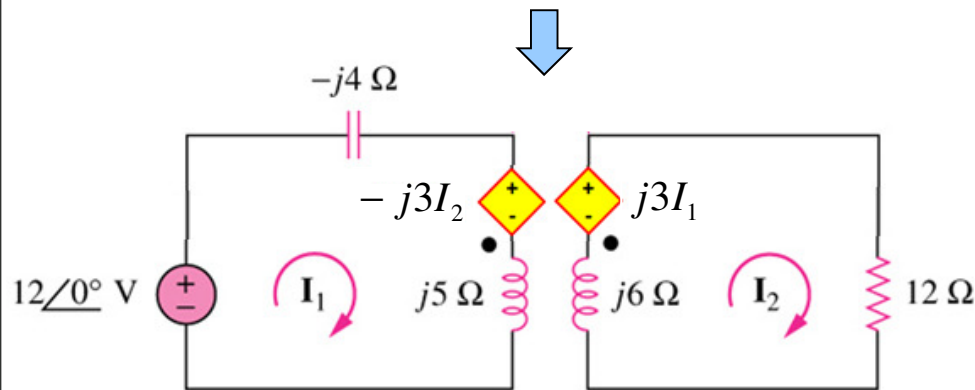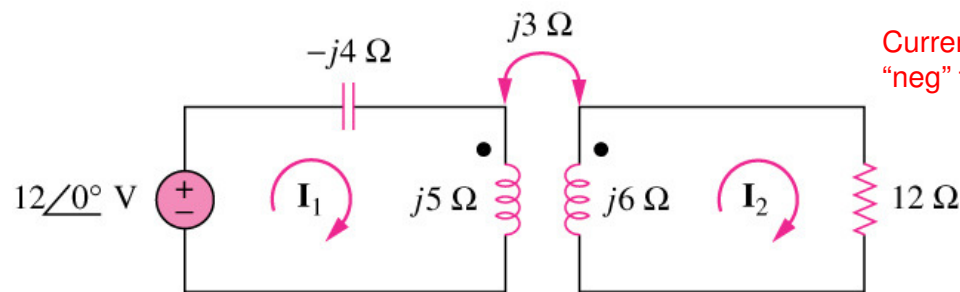

Then, solve Loop Equations:

**Loop  $I_1$**

$$-12 - j4I_1 + (-j3I_2) + j5I_1 = 0$$

$$jI_1 - j3I_2 = 12$$

Current enters  
"neg" terminal

**Loop  $I_2$**

$$j6I_2 - j3I_1 + 12I_2 = 0$$

$$-j3I_1 + (12 + j6)I_2 = 0$$

NOTE:

$I_1$  goes "into" the dot → Induced voltage on the second coil is "Positive"

$I_2$  goes "into" the un-dotted side → Induced voltage on the first coil is "Negative"

**Pay Attention to Sign Conventions !**



## 13.2 Mutual Inductance (15)

### Example Problem 13.1

Lastly, solve 2 equations, 2 unknowns (expected you know this):

$$\text{Loop } I_1 \longrightarrow jI_1 - j3I_2 = 12 \longrightarrow jI_1 = 12 + j3I_2 \Rightarrow I_1 = 3I_2 - j12$$

$$\text{Loop } I_2 \longrightarrow -j3I_1 + (12 + j6)I_2 = 0 \quad I_1 = 3(2.824 + j0.706) - j12$$

$$\text{Substitution: } -3(12 + j3I_2) + (12 + j6)I_2 = 0 \quad I_1 = 8.471 + j2.118 - j12$$

$$\div \text{ by } 3 \quad -12 - j3I_2 + (4 + j2)I_2 = 0 \quad I_1 = 8.471 - j9.882 = 13.02 \angle -49.40^\circ \text{ A}$$

$$\text{Collect Terms: } (4 - j)I_2 = 12$$

$$\text{Solve for } I_2 \quad I_2 = \frac{12}{(4 - j)} = 2.824 + j0.706 = 2.91 \angle 14.04^\circ \text{ A} \quad \text{Find } I_1 \text{ (Substitute back to Eq1)}$$

Think about where we could have made mistakes!

- Applying the model incorrectly (wrong sign convention)
- Incorrect Phasor notation ( Understand:  $j\omega M \leftrightarrow j3$  ;  $j\omega L \leftrightarrow j5$  ;  $1/j\omega C \leftrightarrow -j4$  )
- Incorrect sign convention for loop equations
  - Current entering negative terminal of a voltage source
- Understanding of complex numbers!
  - Familiarity with your calculators handling of complex numbers
  - Converting from rectangular to polar


Review / Understand these concepts to avoid these mistakes

## 13.2 Recommended Viewing:

- Watch these videos illustrating solving mutual inductance problems:
  - <http://www.youtube.com/watch?v=tD35a-uzd34>
  - <http://www.youtube.com/watch?v=hzU4XKQYTWw>
  - <http://www.youtube.com/watch?v=OqSvesTtnUo>
- Uses the model described previously to solve mutual inductance problems.

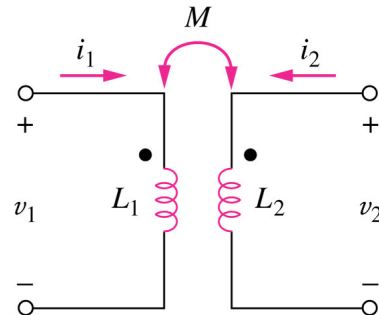
## 13.3 Energy in a Coupled Circuit (1)

- The instantaneous energy  $w$  stored in the circuit is:




$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

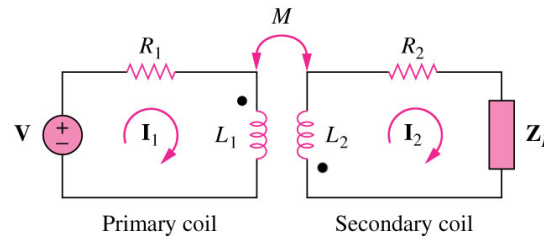- If **both** currents enter (or **both** leave) the dotted terminal the mutual term is (positive):



$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

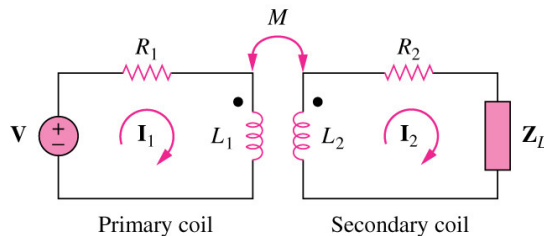- Otherwise the mutual term is (negative):



$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$

## 13.3 Energy in a Coupled Circuit (2)


- The coupling coefficient,  $k$ , is a measure of the magnetic coupling between two coils;  $0 \leq k \leq 1$ .

$$M = k\sqrt{L_1 L_2}$$


$K = 1$  coils perfectly coupled

$K < 0.5$  coils loosely coupled

$K > 0.5$  coils tightly coupled

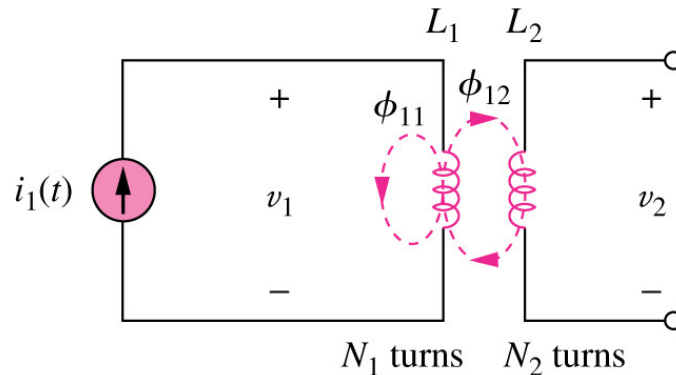
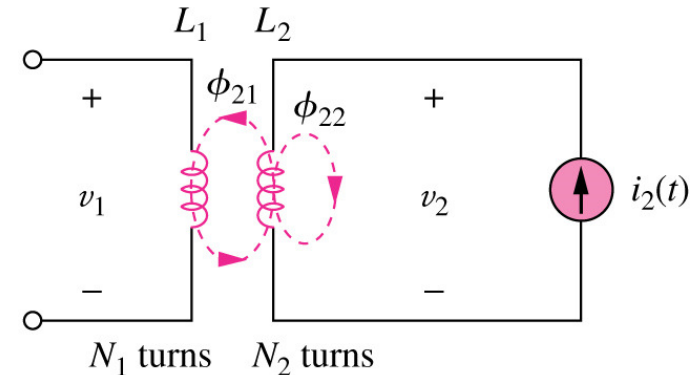
$$K = \frac{\phi_{12}}{\phi_{11} + \phi_{12}}$$




$$K = \frac{\phi_{21}}{\phi_{21} + \phi_{22}}$$

## 13.3 Energy in a Coupled Circuit (3)

### Example 13.3
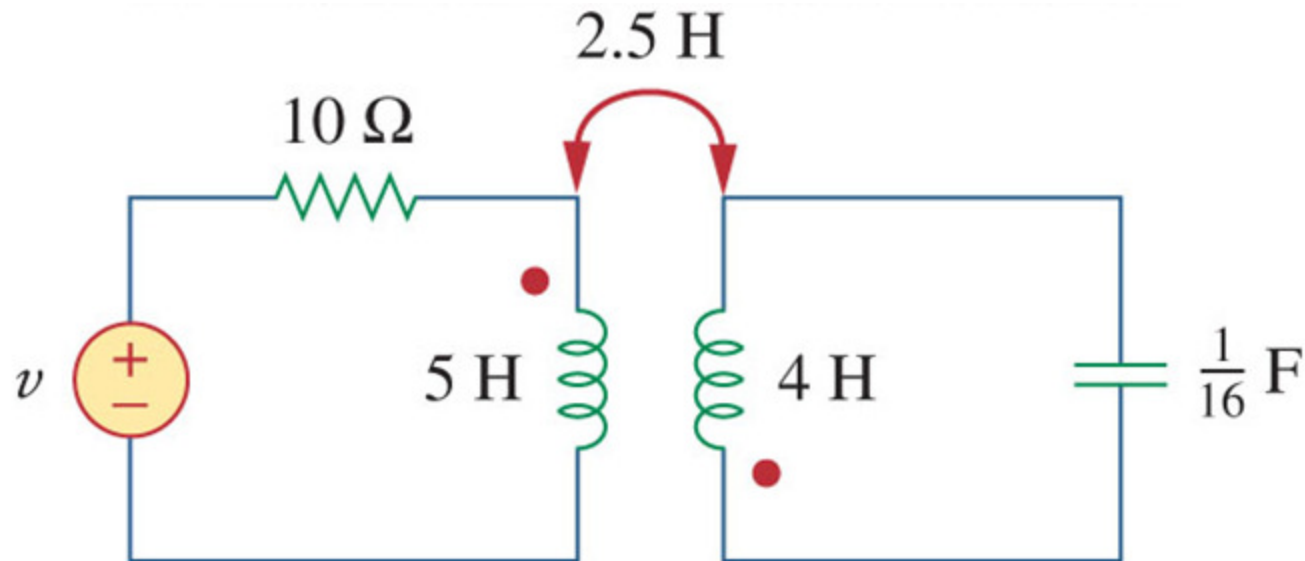
### Example 13.3 (Textbook)


Consider the circuit below. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time  $t = 1$  s if  $v = 60\cos(4t + 30^\circ)$  V.



Ans:  $k=0.56$ ;  $w(1)=20.73$  J

# 13.3 Energy in a Coupled Circuit (4)

## Example 13.3

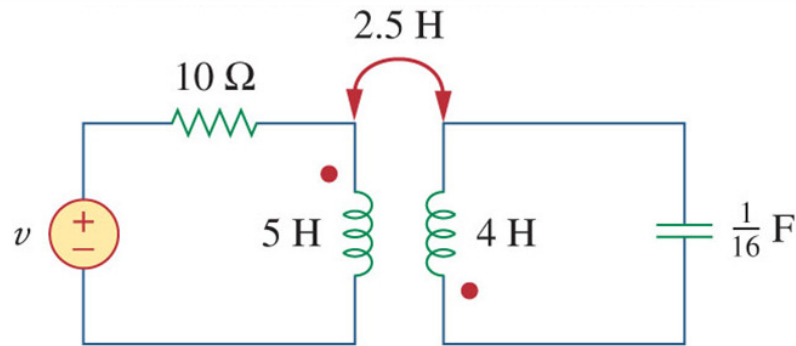


To find k, use the relation between  $L_1$ ,  $L_2$ , and  $M$ :

$$L_1 = 5 ; L_2 = 4 ; M = 2.5$$


$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2.5}{\sqrt{(5)(4)}} = 0.56$$

Apply the "Model"

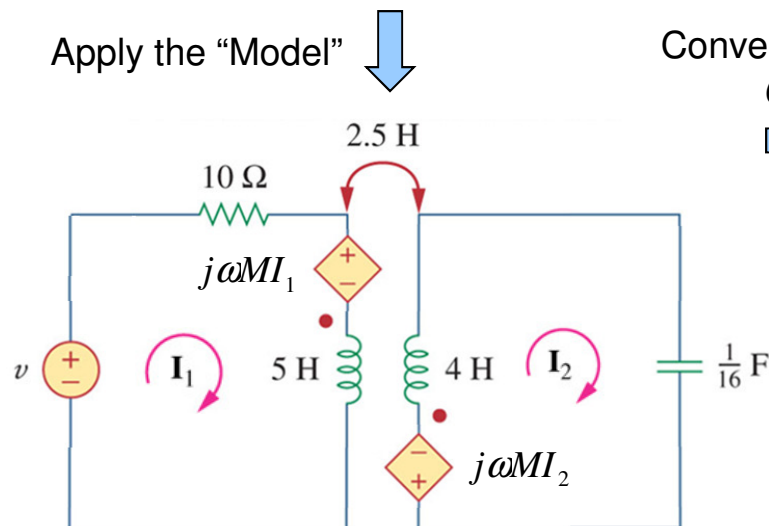

Convert to Phasor

$$\omega = 4$$

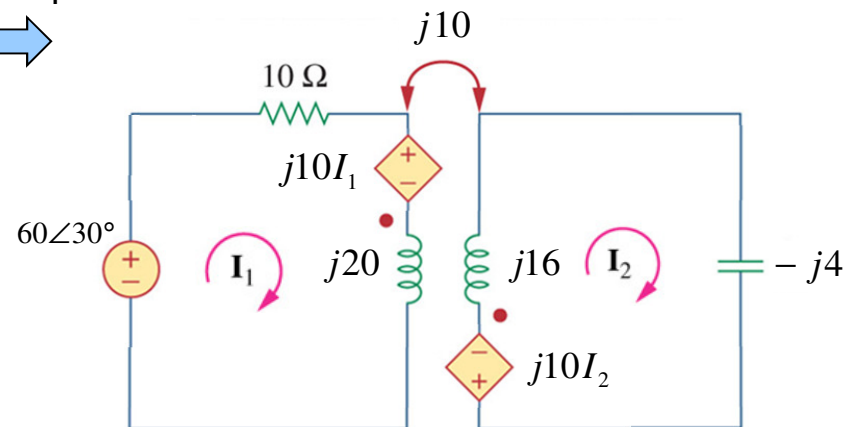

Solve Mesh equations for  $I_1$  and  $I_2$

## 13.3 Energy in a Coupled Circuit (5)

### Example 13.3

From Mesh analysis:

$$I_1 = 3.905 \angle -19.4^\circ \text{ A}$$

$$I_2 = 3.254 \angle 160.6^\circ \text{ A}$$

At  $t = 1$ , the value of  $\omega t = (4)(1) = 4$  radians =  $229.2^\circ$

To find the energy at  $t = 1$ :

$$i_1 = 3.905 \cos(\omega t - 19.4^\circ)$$

$$i_2 = 3.254 \cos(\omega t + 160.6^\circ)$$

$$i_1 = 3.905 \cos(229.2^\circ - 19.4^\circ) = -3.389$$

$$i_2 = 3.254 \cos(229.2^\circ + 160.6^\circ) = 2.824$$

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

Positive since current (as defined) enters **both** dots

$$w = \frac{1}{2} (5) (-3.389)^2 + \frac{1}{2} (4) (2.824)^2 + 2.5 (-3.389) (2.824) = 20.73 \text{ J}$$

# Homework #2

Due in class Monday, January 26, 2015

- 13.1
- 13.7
- 13.9
- 13.24




# Chapter 13

## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers**
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers
- 13.9 Applications
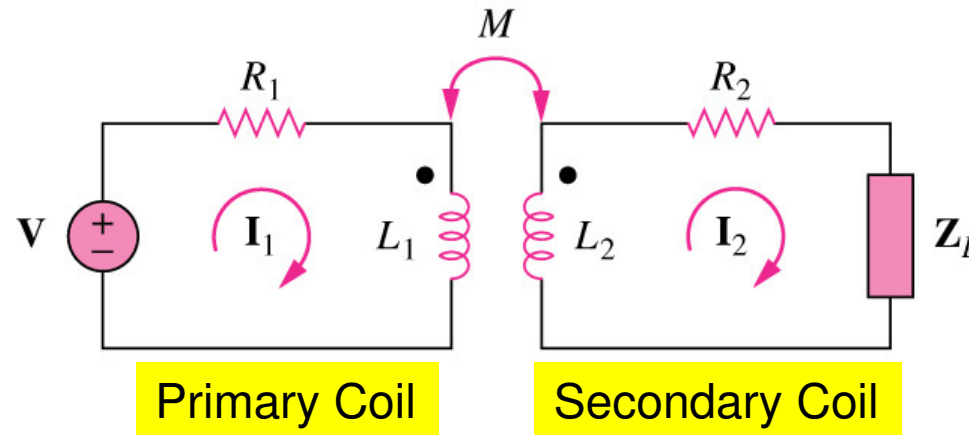
## 13.4 Linear Transformers (1)

- A transformer is generally a four-terminal device comprising two (or more) magnetically coupled coils. Below is a “simple” model:




- The coil connected to the voltage source is called the **primary winding**.
- The coil connected to the load is called the **secondary winding**.
- Resistances  $R_1$  and  $R_2$  are included to account for the losses in the coils.
- A transformer is said to be linear if the coils are wound on a magnetically linear material for which the permeability is constant.
  - Air, plastic, Bakelite, wood, etc.
  - Most materials are magnetically linear.

## 13.4 Linear Transformers (2)
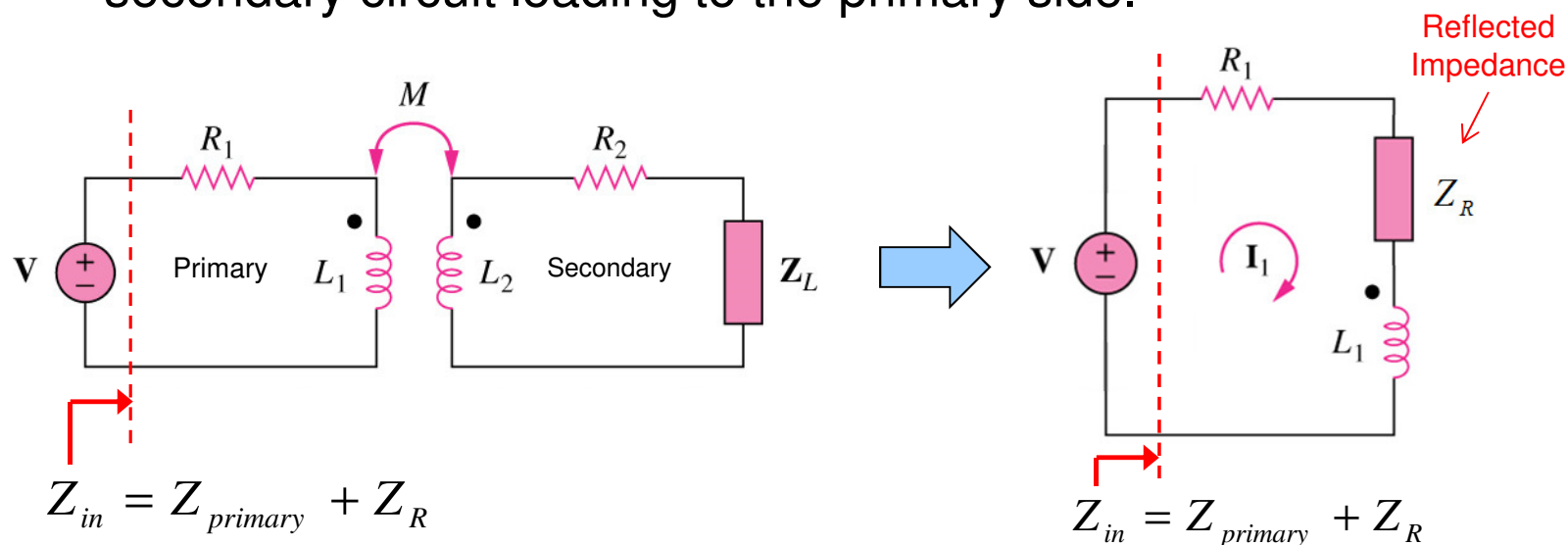
### Reflected Impedance


- Often we are interested in the input impedance  $Z_{in}$  seen by the source.
  - For example, may want to match  $Z_{in}$  to the source impedance for maximum power transfer!
- To simplify our analysis we can break  $Z_{in}$  up into:
  - $Z_{primary}$  -- The impedance of the “primary” circuit ( $Z_{primary} = R_1 + j\omega L_1$ )
  - $Z_R$  -- The “reflected” impedance back to the “primary”.
- The “reflected” impedance  $Z_R$  is the contribution of the secondary circuit loading to the primary side.



## 13.4 Linear Transformers (2)

### Reflected Impedance

To obtain the input impedance  $Z_{in}$  as seen from the source:

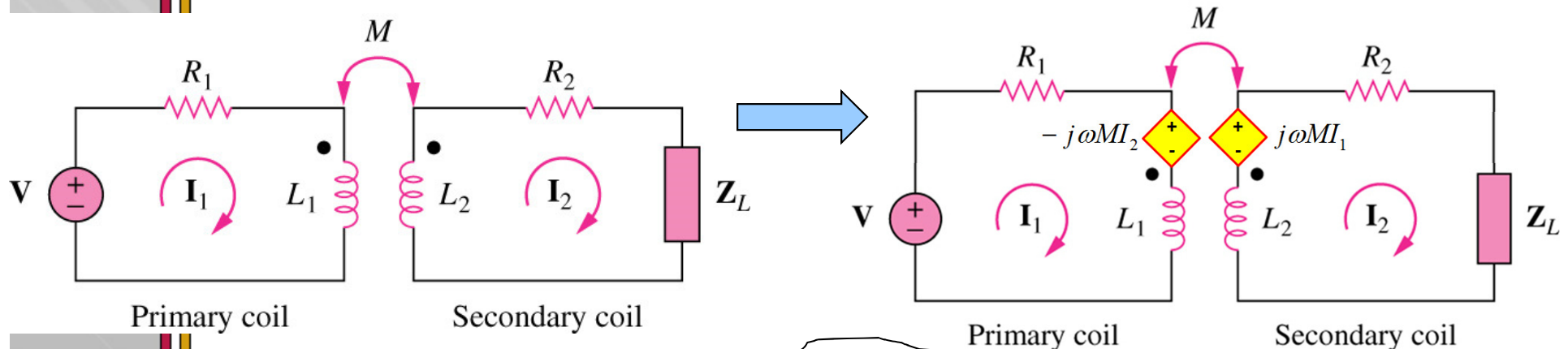

Mesh 1:  $V = (R_1 + j\omega L_1)I_1 - j\omega MI_2$  Current enters positive terminal so it is + ( $-j\omega MI_2$ )

Mesh 2:  $0 = -j\omega MI_1 + (R_2 + j\omega L_2 + Z_L)I_2$  Current enters negative terminal so it is - ( $j\omega MI_1$ )

From Mesh 2:

$$I_2 = \frac{j\omega M}{R_2 + j\omega L_2 + Z_L} I_1$$

Substituting into Mesh 1 gives:

$$V = (R_1 + j\omega L_1)I_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} I_1$$

**Reflected Impedance**


$$Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

$$V = Z_{primary} I_1 + Z_{reflected} I_1$$

# 13.4 Linear Transformers (3)

## Reflected Impedance (Another way of looking at it !)

Obtain input impedance  $Z_{in}$  as seen from the source:

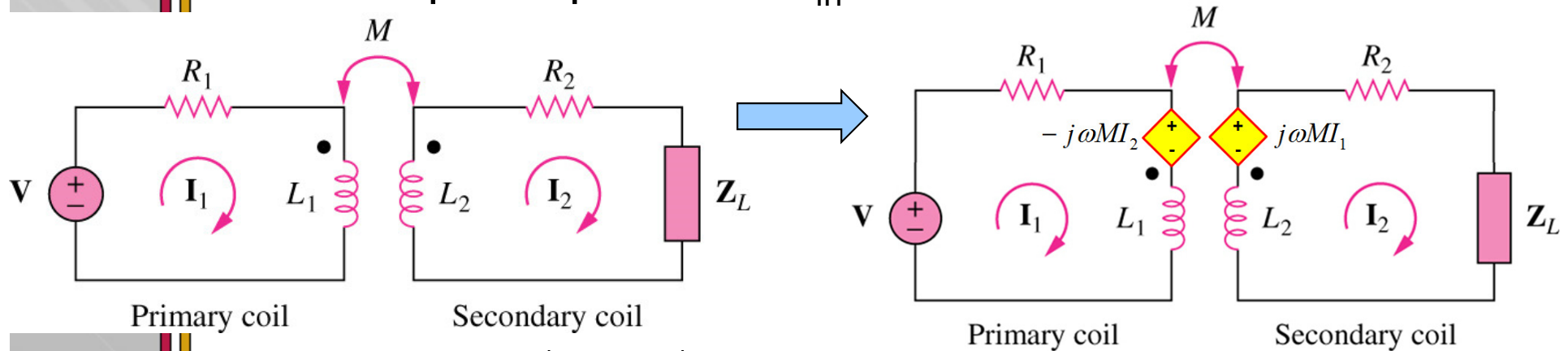

Mesh 1:  $V = (Z_{primary})I_1 - j\omega MI_2$

Mesh 2:  $0 = -j\omega MI_1 + (Z_{secondary})I_2$

$Z_{secondary}$  = the total series impedance in the secondary loop

From Mesh 2:

$$I_2 = \frac{j\omega M}{Z_{secondary}} I_1$$

**Reflected Impedance**

$$Z_R = \frac{\omega^2 M^2}{Z_{secondary}}$$

Substituting into Mesh 1 gives:


$$V = Z_{primary} I_1 + \frac{\omega^2 M^2}{Z_{secondary}} I_1$$

$$V = Z_{primary} I_1 + Z_{reflected} I_1$$

## 13.4 Linear Transformers (4)
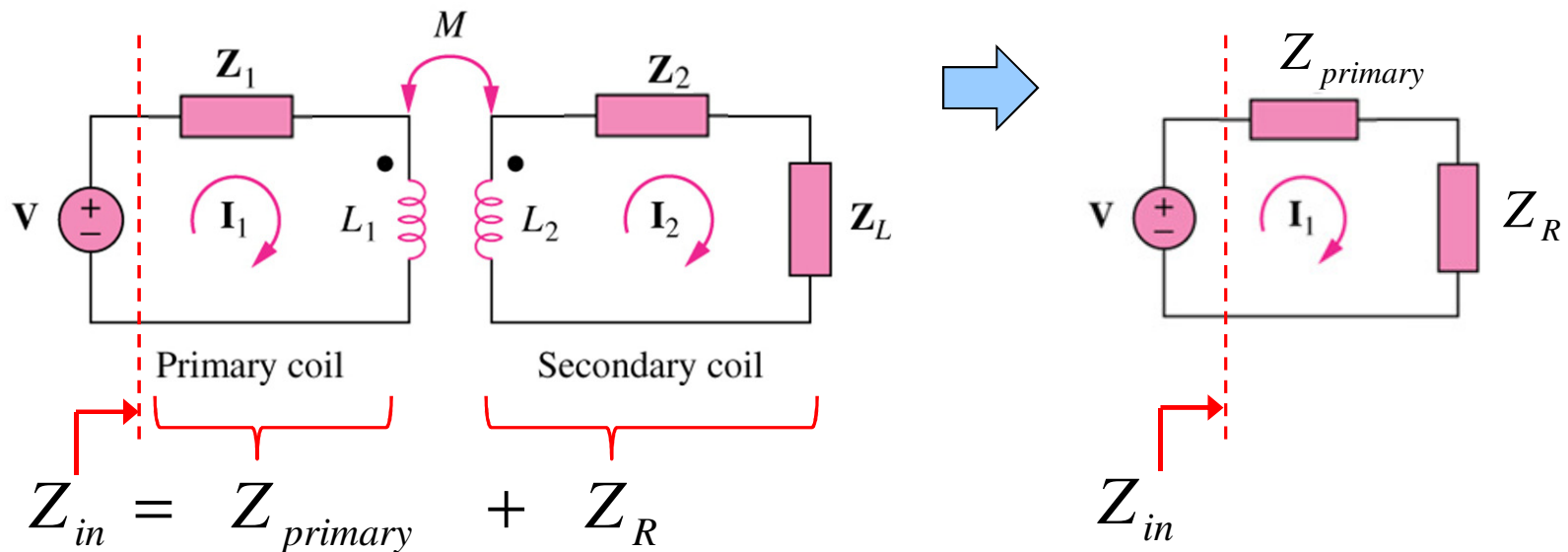
### Reflected Impedance

- The input impedance can be broken into two parts as follows:



- Series Impedance in Primary Coil:  $Z_{primary} = Z_1 + j\omega L_1$
- Series Impedance in Secondary Coil:  $Z_{secondary} = Z_2 + Z_L + j\omega L_2$
- Input Impedance:  $Z_{in} = Z_{primary} + \frac{\omega^2 M^2}{Z_{secondary}}$


*Note:  $Z_{in}$  will be the same if the dot on  $L_2$  is switched*

## 13.4 Linear Transformers (5)

### Example 13.4
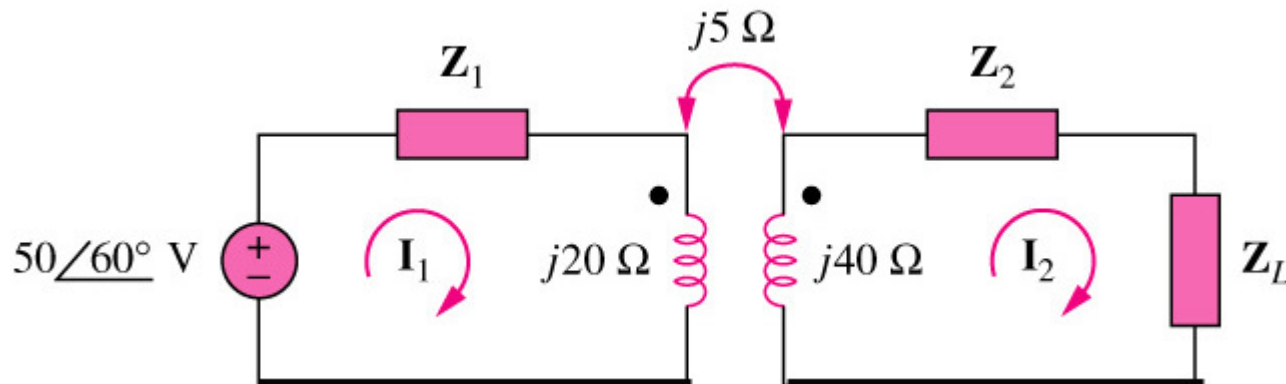
### Example 13.4 (textbook)


In the circuit below, calculate the input impedance and current  $I_1$ . Take  $Z_1 = 60 - j100\Omega$ ,  $Z_2 = 30 + j40\Omega$ , and  $Z_L = 80 + j60\Omega$ .



Ans:  $Z_{in} = 100.14\angle -53.1^\circ\Omega$ ;  $I_1 = 0.5\angle 113.1^\circ\text{A}$

## 13.4 Linear Transformers (5)

### Example 13.4

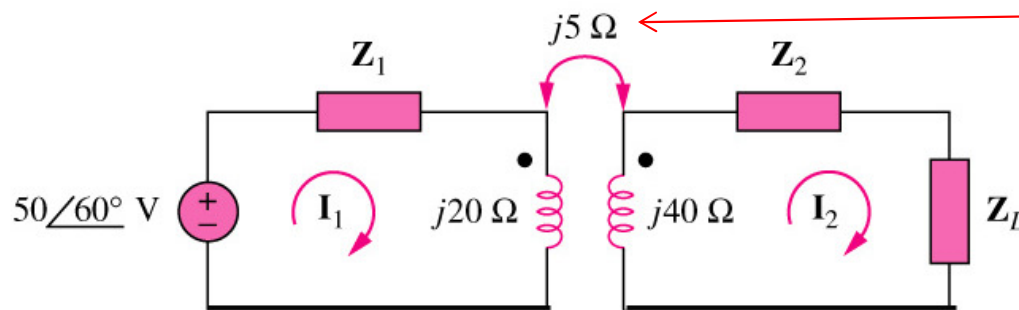

**Note:**

$$j\omega M = j5$$

$$\omega M = 5$$

$$(\omega M)^2 = 25$$

- The series impedance in the primary coil:

$$Z_{primary} = (60 - j100) + j20 = 60 - j80$$

- The series impedance in the secondary coil:

$$Z_{secondary} = (30 + j40) + (80 + j60) + j40 = 110 + j140$$

- Input Impedance given by:

$$Z_{in} = Z_{primary} + \frac{\omega^2 M^2}{Z_{secondary}} = (60 - 80j) + \frac{25}{(110 + j140)} = 60.09 - j80.11$$


- Current  $I_1$  given by: 
$$I_1 = \frac{V_s}{Z_{in}} = \frac{50 \angle 60^\circ}{60.09 - j80.11} = \frac{50 \angle 60^\circ}{100.14 \angle -53.1^\circ}$$




## 13.4 Linear Transformers (6)
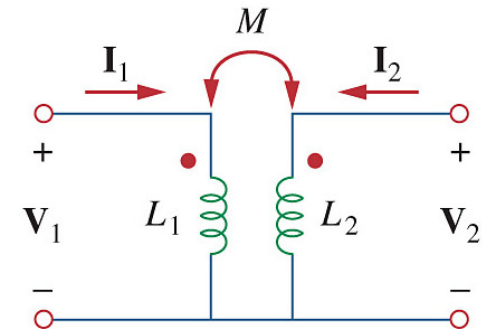
### Equivalent T and $\pi$ Circuits:


- It is sometimes convenient to replace a magnetically couple circuit with an equivalent circuit with no magnetic coupling.
- We can replace the linear transformer with an equivalent T or  $\pi$  circuit that has no mutual inductance.



T Circuit

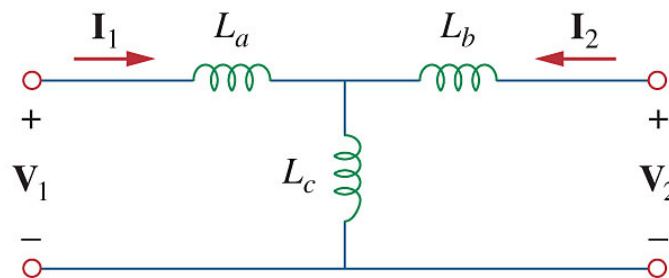


$\pi$  Circuit

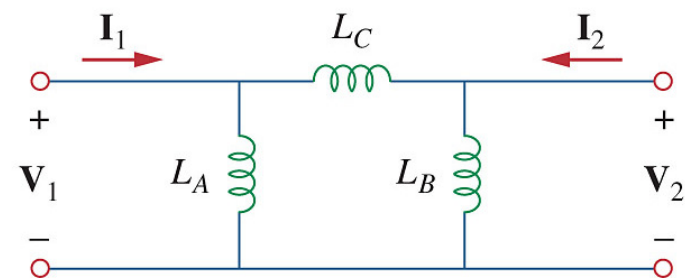

## 13.4 Linear Transformers (7)

### Equivalent T Circuit:


Linear Transformer Circuit

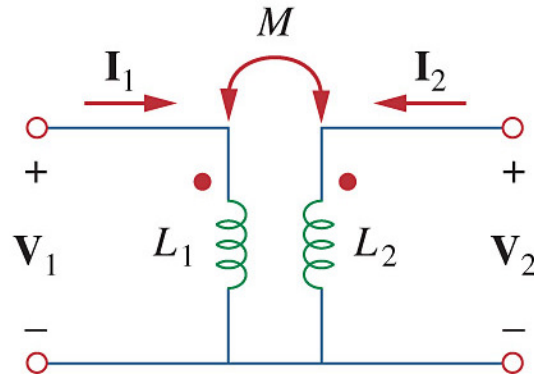

Mesh Analysis of this transformer circuit results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Equivalent T Network

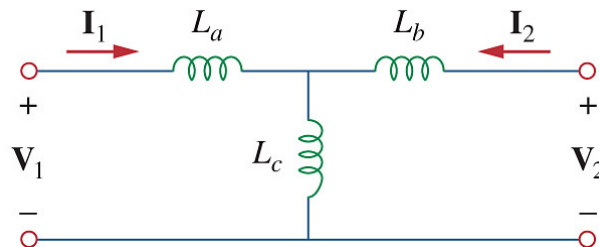

Mesh Analysis of the equivalent T network results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


Equating the terms gives the following relationships:

$$L_a = L_1 - M \quad L_b = L_2 - M \quad L_c = M$$

## 13.4 Linear Transformers (8)

### Equivalent T Circuits (Swapped Dots):


Linear Transformer Circuit

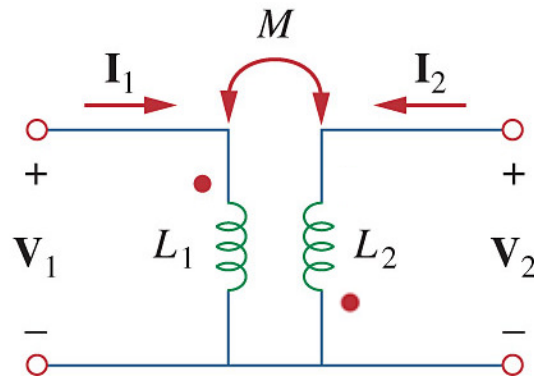

Mesh Analysis of this transformer circuit results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & -j\omega M \\ -j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Equivalent T Network

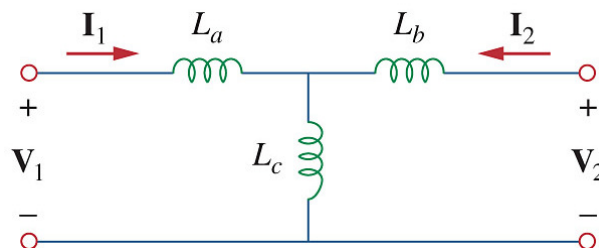

Mesh Analysis of the equivalent T network results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


Equating the terms gives the following relationships:

$$L_a = L_1 + M \quad L_b = L_2 + M \quad L_c = -M$$

# 13.4 Linear Transformers (9)

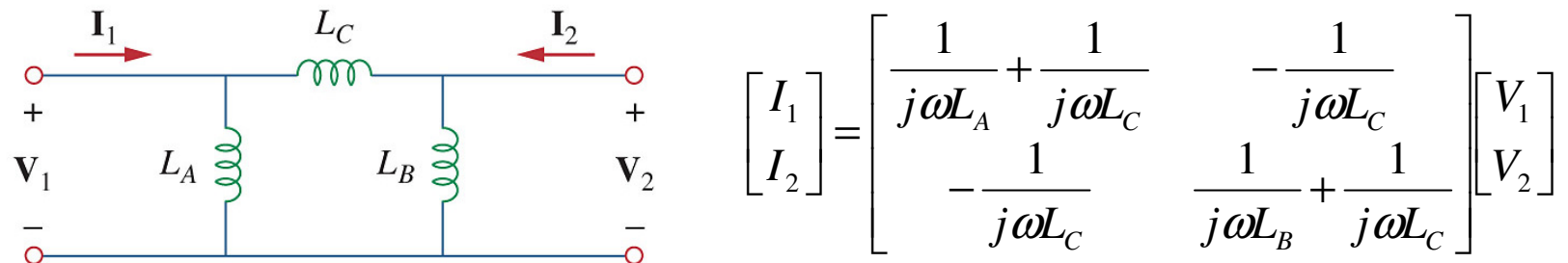
## Equivalent $\pi$ Circuit:

Similarly, for the  $\pi$  network nodal analysis provides:




Equivalent  $\pi$  Network

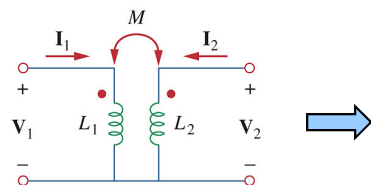By equating terms in admittance matrices, for the  $\pi$  equivalent network we obtain (note if dots are different, replace with  $-M$ ):



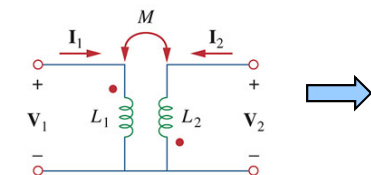
$$L_A = \frac{L_1 L_2 - M^2}{L_2 - M} ; L_B = \frac{L_1 L_2 - M^2}{L_1 - M} ; L_C = \frac{L_1 L_2 - M^2}{M}$$




$$L_A = \frac{L_1 L_2 - M^2}{L_2 + M} ; L_B = \frac{L_1 L_2 - M^2}{L_1 + M} ; L_C = \frac{L_1 L_2 - M^2}{-M}$$

# 13.4 Linear Transformers (10)


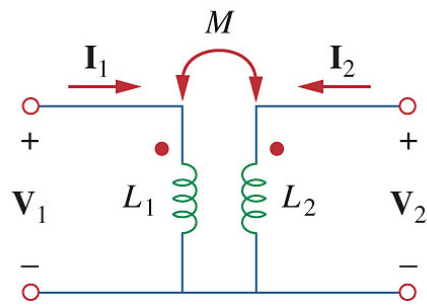
## Equivalent T or $\pi$ Circuits Summary




T Circuit

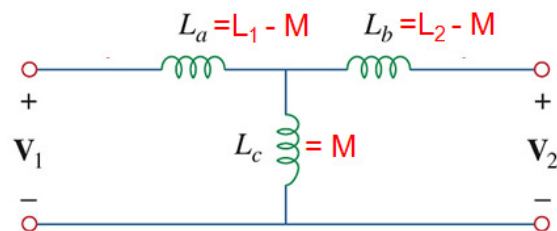


$\pi$  Circuit

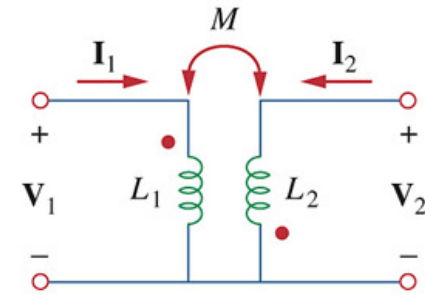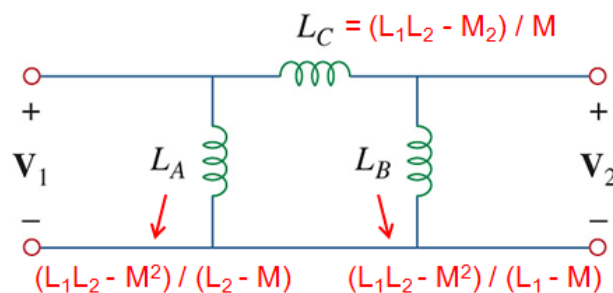

T Circuit

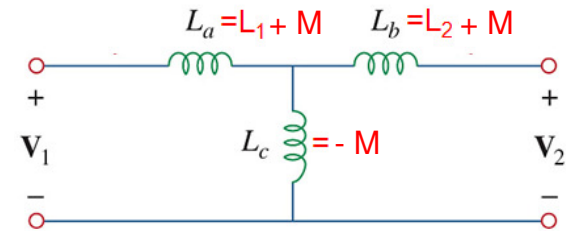



$\pi$  Circuit

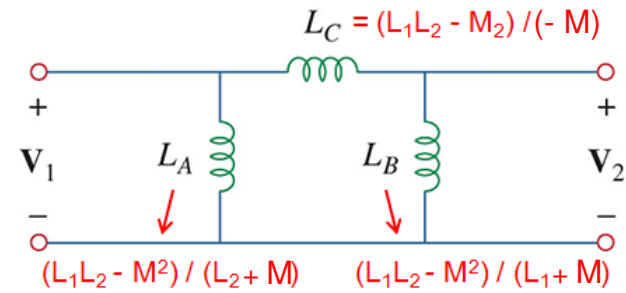

# 13.4 Linear Transformers (11)
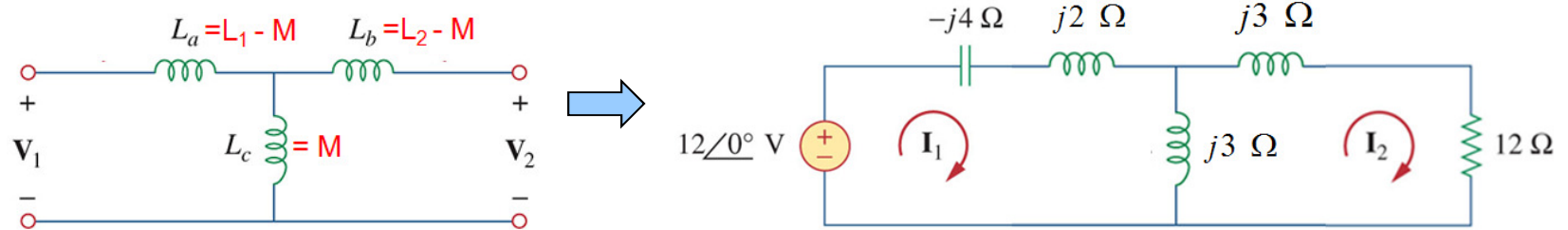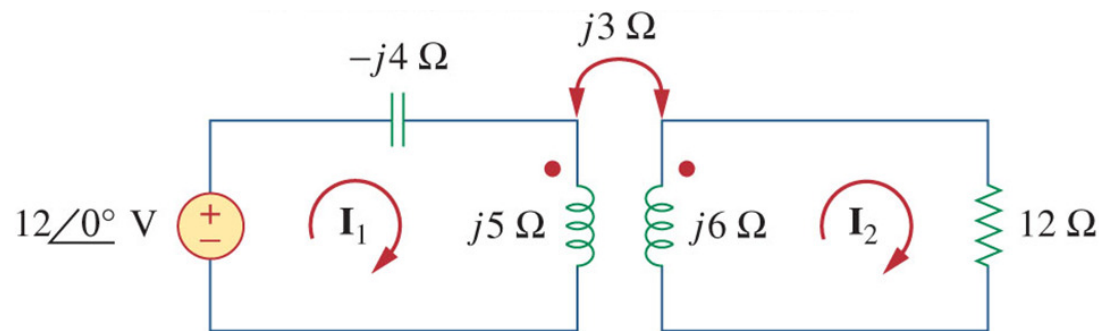
## Practice Problem 13.6

Find  $I_1$  and  $I_2$  using the T equivalent circuit



$$\text{Mesh } I_1: -12\angle 0^\circ - j4I_1 + j2I_1 + j3(I_1 - I_2) = 0 \quad jI_1 - j3I_2 = 12\angle 0^\circ$$

$$\text{Mesh } I_2: j3(I_2 - I_1) + j3I_2 + 12I_2 = 0 \quad -j3I_1 + (12 + j6)I_2 = 0$$



# Chapter 13

## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers**
- 13.6 Ideal Autotransformers
- 13.9 Applications
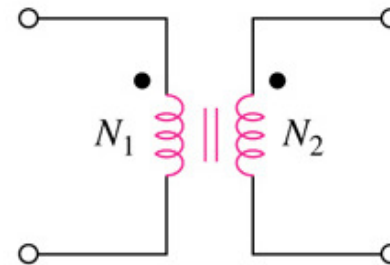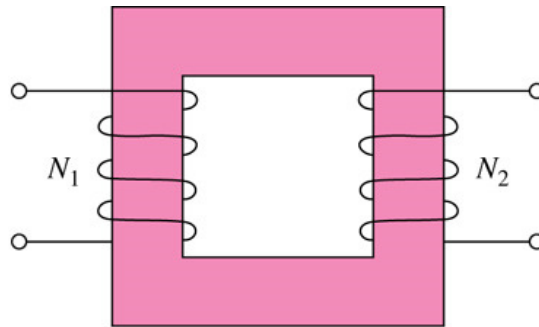
## 13.5 Ideal Transformers (1)

- An ideal transformer has perfect coupling ( $k=1$ ).
- It consists of two or more coils with a large number of turns wound on a common core of high permeability.



- Because of the high permeability of the core, the flux links all the turns of both coils, thereby resulting in a perfect coupling.



## 13.5 Ideal Transformers (2)

“Dot’s the same polarity”

Recall the coupled circuit:

$$V_1 = j\omega L_1 I_1 + j\omega M I_2 \quad (1)$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2 \quad (2)$$


Solving for  $I_1$  in (1):  $I_1 = \frac{V_1 - j\omega M I_2}{j\omega L_1} \quad (3)$

Substituting (3) into (2):  $V_2 = j\omega L_2 I_2 + \frac{M V_1}{L_1} - \frac{j\omega M^2 I_2}{L_1}$

$M = \sqrt{L_1 L_2}$  For perfect coupling ( $k=1$ ):

$$V_2 = j\omega L_2 I_2 + \frac{\sqrt{L_1 L_2} V_1}{L_1} - \frac{j\omega L_1 L_2 I_2}{L_1} = \sqrt{\frac{L_2}{L_1}} V_1 = n V_1$$

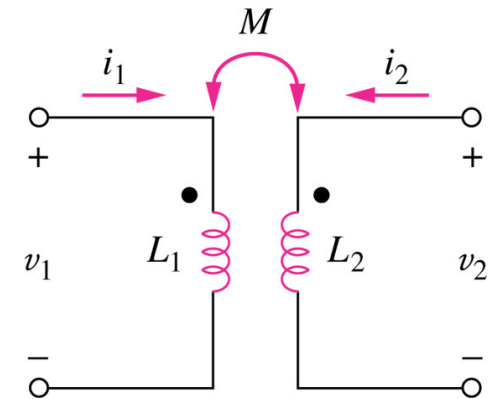Therefore:  $V_2 = n V_1$  where  $n = \sqrt{L_2 / L_1}$  = turns ratio



## 13.5 Ideal Transformers (3)

“Dot’s opposite each other”

Mesh Equations give the following:

$$V_1 = j\omega L_1 I_1 - j\omega M I_2 \quad (1)$$

$$V_2 = -j\omega M I_1 + j\omega L_2 I_2 \quad (2)$$


Solving for  $I_1$  in (1):  $I_1 = \frac{V_1 + j\omega M I_2}{j\omega L_1} \quad (3)$

Substituting (3) into (2):  $V_2 = j\omega L_2 I_2 - \frac{M V_1}{L_1} - \frac{j\omega M^2 I_2}{L_1}$

$M = \sqrt{L_1 L_2}$  For perfect coupling ( $k=1$ ):

$$V_2 = j\omega L_2 I_2 - \frac{\sqrt{L_1 L_2} V_1}{L_1} - \frac{j\omega L_1 L_2 I_2}{L_1} = -\sqrt{\frac{L_2}{L_1}} V_1 = -n V_1$$

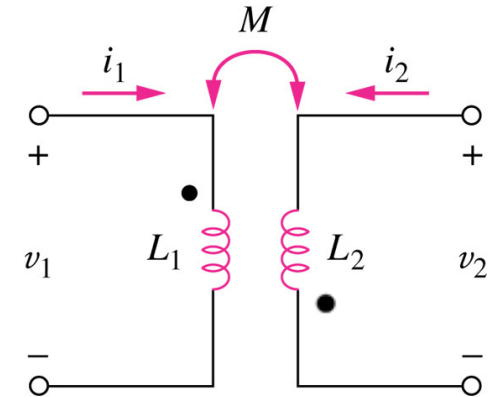Therefore:  $V_2 = -n V_1$  If dot is swapped at output




## 13.5 Ideal Transformers (4)

### Properties

- A transformer is said to be **ideal** if it has the following properties:
  1. Coils have very large reactances ( $L_1, L_2, M \rightarrow \infty$ )
  2. Coupling coefficient is equal to unity ( $k=1$ )
  3. Primary and secondary coils are lossless ( $R_1 = R_2 = 0$ )
- An ideal transformer is a unity-coupled ( $k=1$ ) lossless transformer in which the primary and secondary coils have infinite self-inductances ( $L_1 \& L_2 \rightarrow \infty$ ).
- Iron core transformers are close approximations to ideal transformers and are used in power systems and electronics.
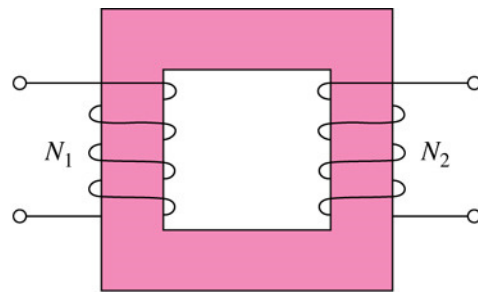
## 13.5 Ideal Transformers (5)

- When a sinusoidal voltage is applied to the primary winding, the same magnetic flux  $\Phi$  goes through both windings.



$$v_1 = N_1 \frac{d\phi}{dt} \quad ; \quad v_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = n = \text{Turns ratio or transformation ratio}$$


- Using the phasor voltages rather than the instantaneous voltages:

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$
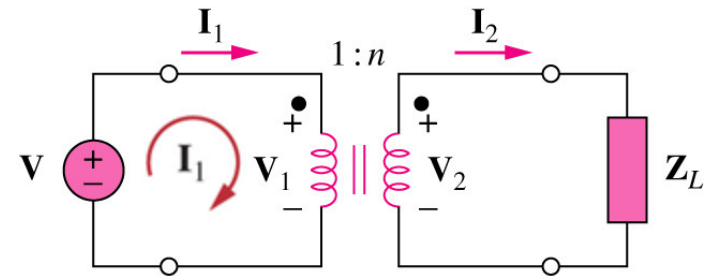
## 13.5 Ideal Transformers (6)

- Power conservation:  $v_1 i_1 = v_2 i_2$
- The energy supplied to the primary must equal the energy absorbed by the secondary, since there are no losses in an ideal transformer.

- In phasor form:  $\frac{I_1}{I_2} = \frac{V_2}{V_1} = n$



- $n=1 \rightarrow$  isolation transformer ( $V_2 = V_1$ )
- $n>1 \rightarrow$  step-up transformer ( $V_2 > V_1$ )
- $n<1 \rightarrow$  step-down transformer ( $V_2 < V_1$ )


## 13.5 Ideal Transformers (7)

- Transformer ratings are usually specified as  $V_1 / V_2$
- Power companies often generate at some convenient voltage and use the step-up transformer to increase the voltage so that the power can be transmitted at very high voltage and low current over transmission lines, resulting in significant cost savings. Near residential consumers, step-down transformers are used to bring the voltage down to 120 V.
- It is important to get the proper polarity of the voltages and the direction of the currents for the transformer.
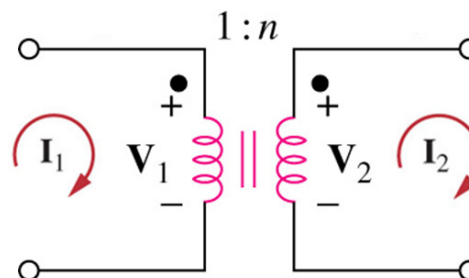
# 13.5 Ideal transformers (8)


V and I relationships (simpler way to remember)

Given this standard  
definition for Voltages  
and currents



**Note:** This definition  
of  $I_2$  differs from the  
text.

Dots "Same"  $\rightarrow$  "+"

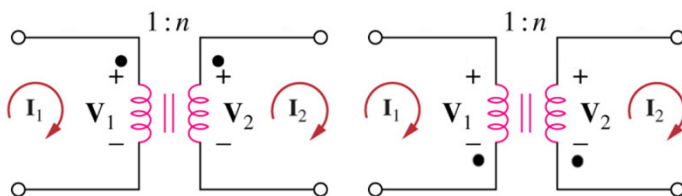

$$V_2 = nV_1$$

$$I_2 = \frac{I_1}{n}$$

$$Z_{in} = \frac{Z_L}{n^2}$$


Reflected  
Impedance  $\rightarrow$

*Note: The larger the turns ratio  
The larger "n"  
The larger " $N_2$ "  
The larger  $V_2$*

**Turns Ratio**

$$n = \frac{N_2}{N_1}$$

Dots "Different"  $\rightarrow$  "-"

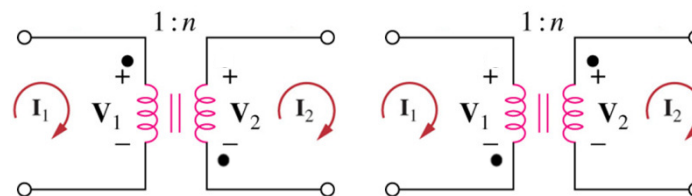

$$V_2 = -nV_1$$


$$I_2 = -\frac{I_1}{n}$$

$$Z_{in} = \frac{Z_L}{n^2}$$

## 13.5 Ideal Transformers (9)
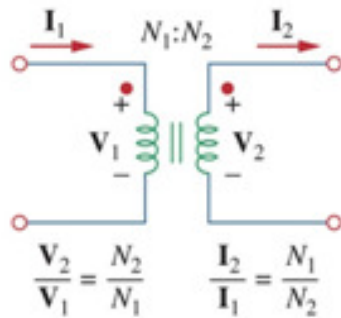
### V and I relationships

- Expressing  $V_1$  in terms of  $V_2$  and  $I_1$  in terms of  $I_2$  or vice versa:



$$V_1 = \frac{V_2}{n} \quad V_2 = nV_1$$

$$I_2 = \frac{I_1}{n} \quad I_1 = nI_2$$

Positive, if Voltage “**same**” polarity at dot

Positive, if current “**different**” polarity at dot

- Complex Power is:

$$S_1 = V_1 I_1^* = \frac{V_2}{n} (nI_2)^* = V_2 I_2^* = S_2$$

Complex Conjugate of  $I_2$


- Complex power supplied to the primary is delivered to the secondary without loss.
- The ideal transformer is **lossless** and absorbs **no power**.



## 13.5 Ideal Transformers (10)
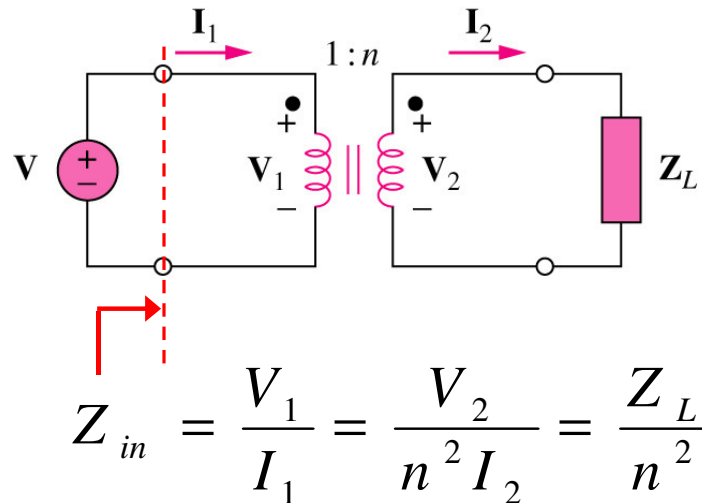
### Reflected impedance

- The input impedance as seen by the source is:




- The input impedance is also called the reflected impedance since it appears as if the load impedance is reflected to the primary side.
- The ability of the transformer to transform a given impedance to another allows impedance matching to ensure maximum power transfer.

## 13.5 Ideal Transformers (11)
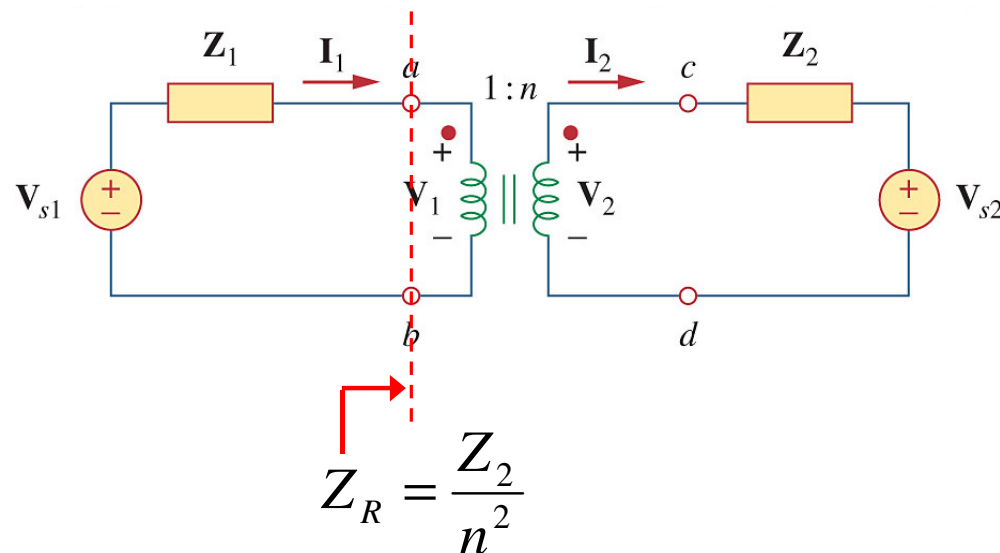
### Equivalent circuit analysis


- In analyzing a circuit containing an ideal transformer, it is common practice to eliminate the transformer by reflecting impedances and sources from one side of the transformer to the other.
- Suppose we want to reflect the secondary side of the circuit to the primary side:



# 13.5 Ideal Transformers (12)
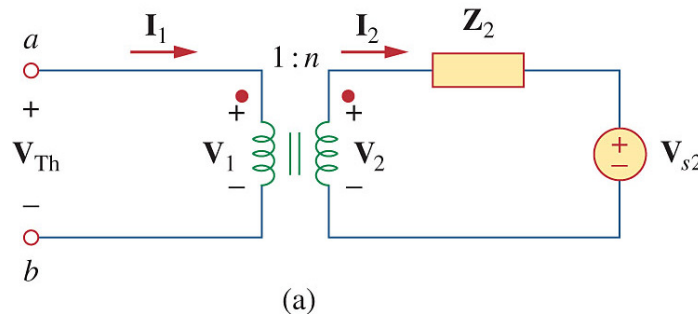
## Equivalent circuit analysis

- We find the Thevenin equivalent of the circuit to the right of a-b:
- Obtaining  $V_{th}$  from “open circuit voltage”:





$$I_1 = 0 = I_2 \quad \text{Since a-b is open}$$

$$V_2 = V_{s2}$$


$$V_{Th} = V_1 = \frac{V_2}{n} = \frac{V_{s2}}{n}$$

- Obtaining  $Z_{Th}$  (remove the voltage source in the secondary and insert a unit source at a-b terminals.)
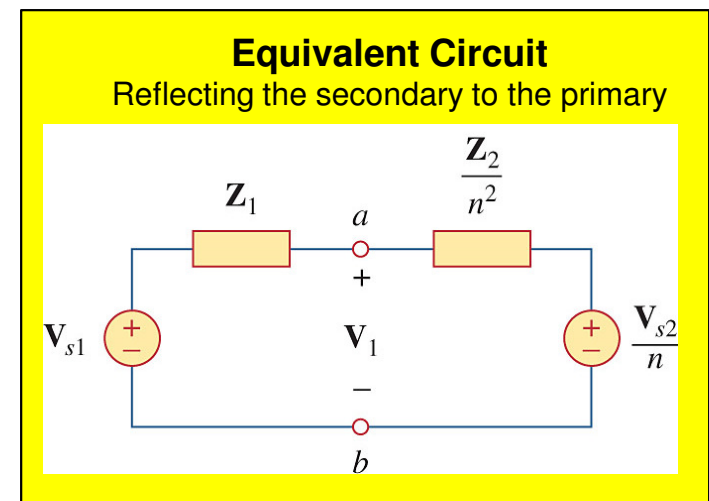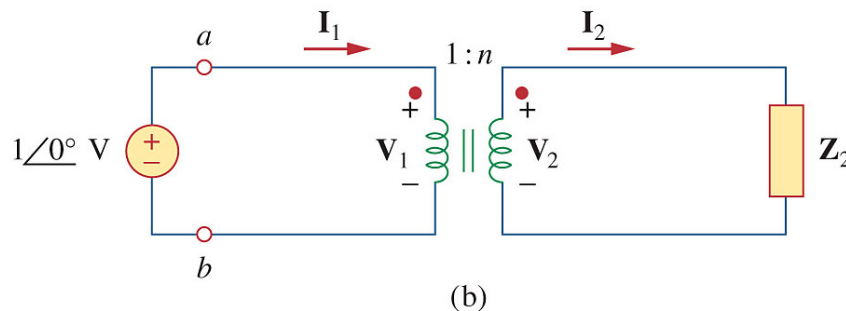
$$Z_{Th} = \frac{V_1}{I_1} = \frac{V_2}{n^2 I_2} = \frac{Z_2}{n^2}$$




## 13.5 Ideal Transformers (13)

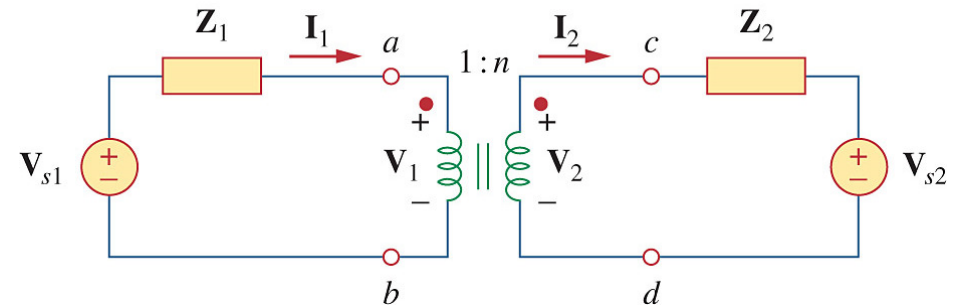


- The general rule for eliminating the transformer and reflecting the secondary circuit to the primary side:

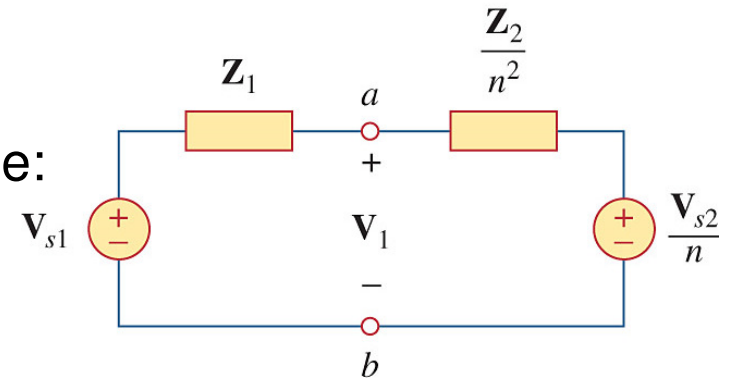- Divide the secondary impedance by  $n^2$
- Divide the secondary voltage by  $n$
- Multiply the secondary current by  $n$



- The general rule for eliminating the transformer and reflecting the secondary circuit to the primary side:

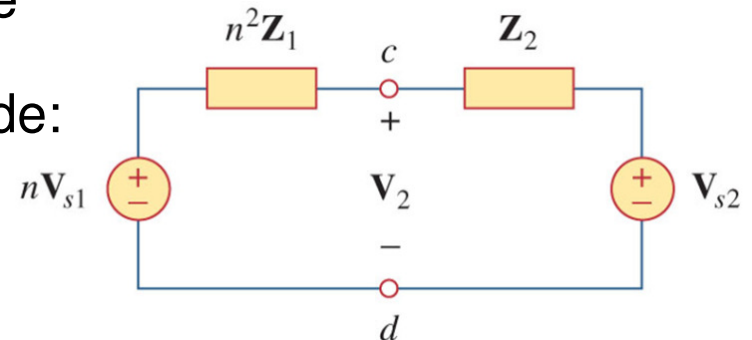
- Multiply the primary impedance by  $n^2$
- Multiply the primary voltage by  $n$
- Divide the primary current by  $n$




## 13.5 Ideal Transformer (14)
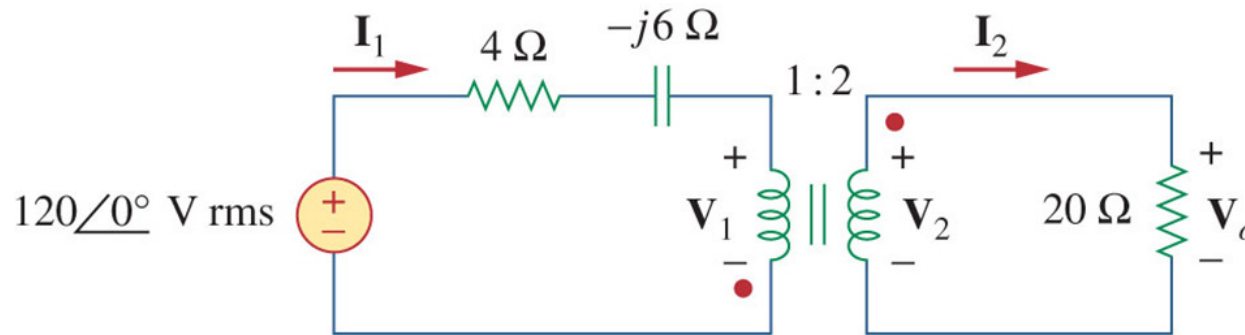
### Example 13.8 (Textbook)

For the ideal transformer, find: (a) the source current  $I_1$ , (b) the output voltage  $V_o$ , and (c) the complex power supplied by the source



## 13.5 Ideal Transformer (14)

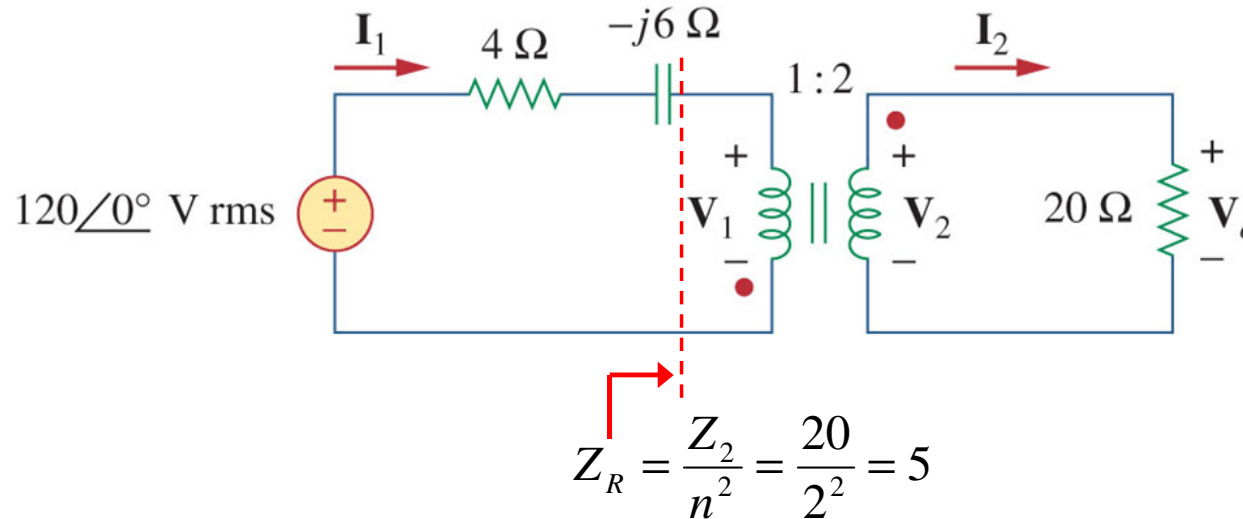

Impedance seen by the Voltage source is:

$$Z_{in} = (4 - j6) + 5 = 9 - j6 = 10.82 \angle -33.69^\circ \Omega$$

Input current  $I_1$  is:

$$I_1 = \frac{V_s}{Z_{in}} = \frac{120 \angle 0^\circ}{10.82 \angle -33.69^\circ} = 11.09 \angle 33.69^\circ \text{ A}$$

$$I_2 = -\frac{I_1}{n} = \frac{-11.09 \angle 33.69^\circ}{2} = 5.55 \angle -146.31^\circ \text{ A}$$

$$V_o = 20I_2 = 20(5.55 \angle -146.31^\circ) = 110.9 \angle -146.31^\circ \text{ V}$$


# Chapter 13

## Magnetically Coupled Circuits


- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers**
- 13.9 Applications**
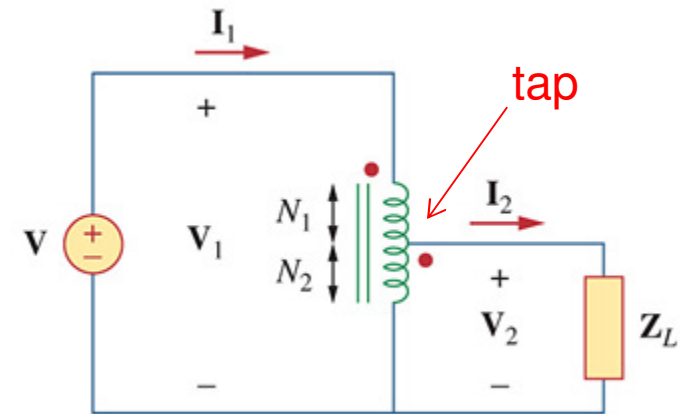
## 13.6 Ideal Auto-Transformers (1)

- An **autotransformer** is a transformer in which both the primary and the secondary are in a single winding
- A connection point called a *tap* separates the primary and secondary.
- The tap is often adjustable to provide a desired turns ratio.
- An adjustable tap provides a variable voltage to the load
- A disadvantage of the autotransformer is it provides *no electrical isolation*



Step Down Auto-Transformer

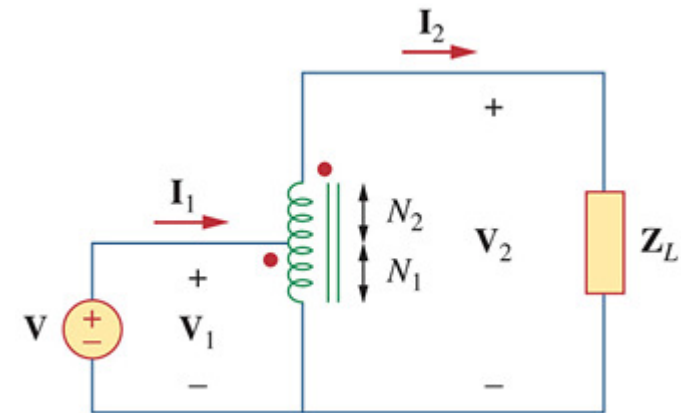


Step Up Auto-Transformer


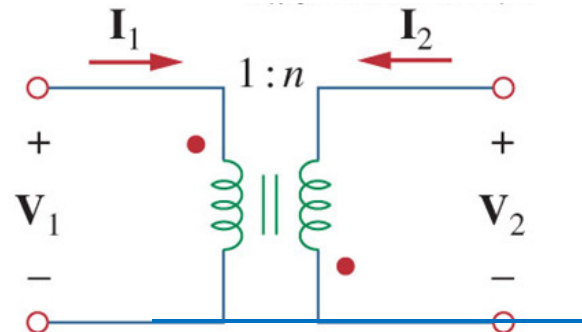
## 13.6 Ideal Auto-Transformers (2)


- In analyzing the autotransformer, consider the following circuit:



From earlier we know the following relationship

$$V_2 = -nV_1$$

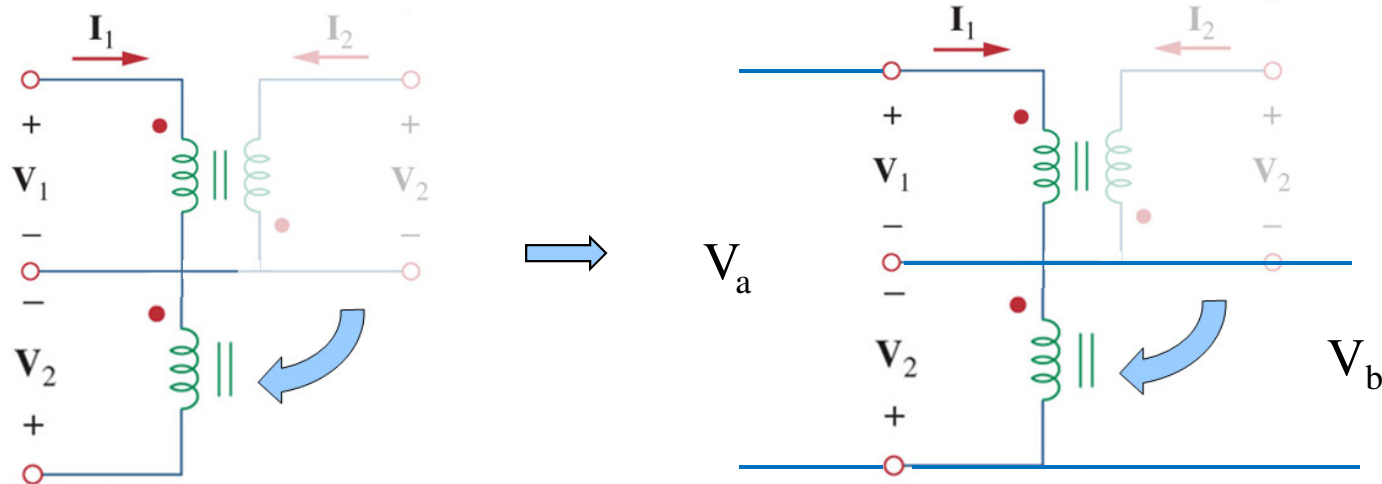- If we flip the secondary side underneath the primary, we can create an autotransformer as shown



## 13.6 Ideal Auto-Transformers (3)


- Analysis of this circuit provides the following results:

Primary Side

$$V_a = V_1 - V_2$$

$$V_a = V_1 + nV_1$$

$$V_a = (1+n)V_1$$

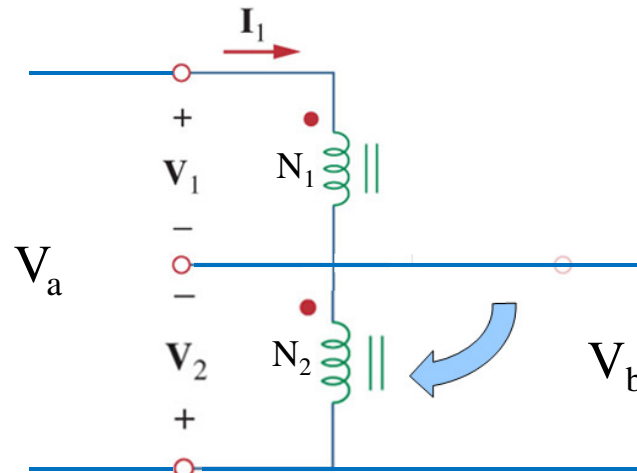

Secondary Side

$$V_b = -V_2 = nV_1$$

Ratio Primary/Secondary


$$\frac{V_a}{V_b} = \frac{1+n}{n} = \frac{N_1 + N_2}{N_2} \quad \Rightarrow$$

Notice, this looks like  
a Voltage Divider !


$$V_b = \left( \frac{N_2}{N_1 + N_2} \right) V_a$$
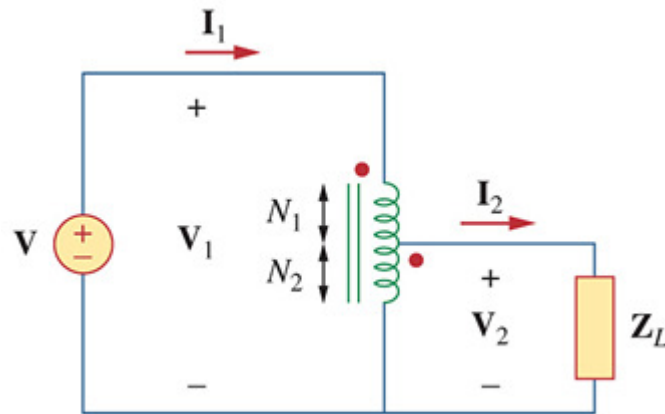
## 13.6 Ideal Auto-Transformers (4)

- The voltage / current relationships for the lossless ideal autotransformer are as follows:



Step Down Auto-Transformer

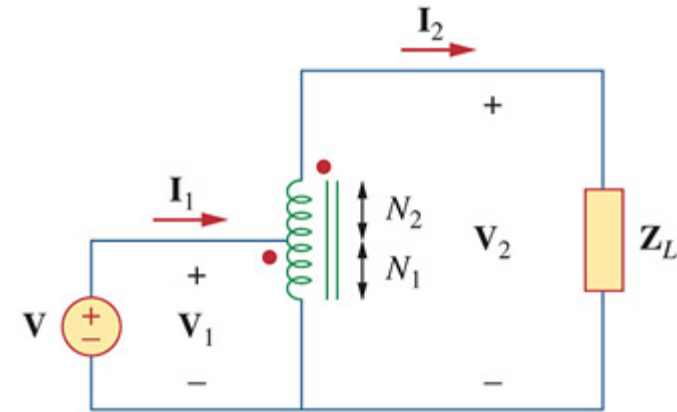

Step Up Auto-Transformer

$$V_2 = \frac{N_2}{N_1 + N_2} V_1$$

Similar to  
Voltage Divider  
equation

$$V_2 = \frac{N_1 + N_2}{N_1} V_1$$

$$I_2 = \frac{N_1 + N_2}{N_2} I_1$$

Inverse Relation

$$I_2 = \frac{N_1}{N_1 + N_2} I_1$$

$$Z_{in} = \left( \frac{N_1 + N_2}{N_2} \right)^2 Z_L$$


Derive from V/I

$$Z_{in} = \left( \frac{N_1}{N_1 + N_2} \right)^2 Z_L$$

## 13.6 Ideal Auto-Transformers (5)



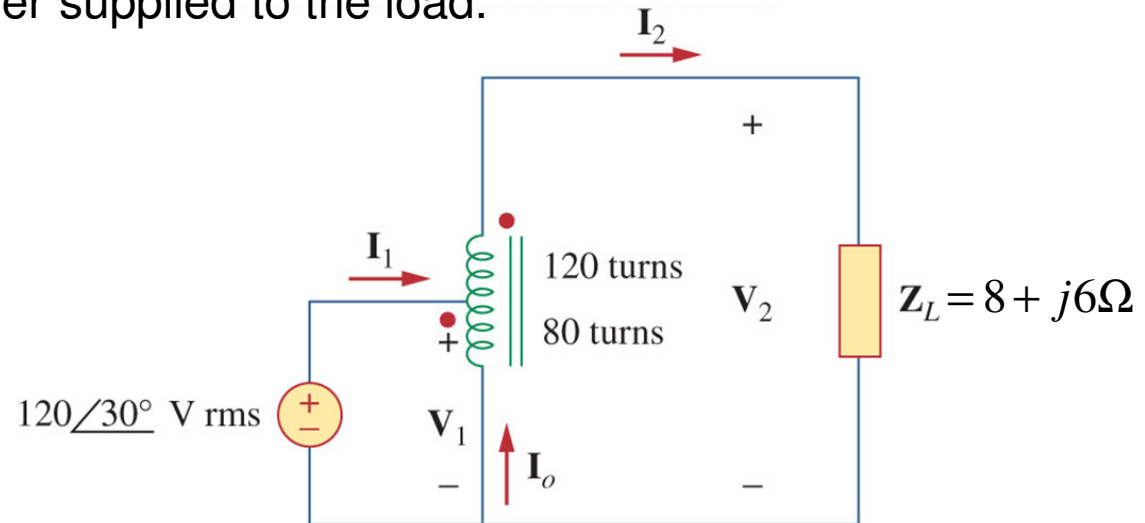
### Example 13.11 (Textbook)

For the autotransformer below, find: (a) the currents  $I_1$ ,  $I_2$ ,  $I_o$ , (b) the complex power supplied to the load.



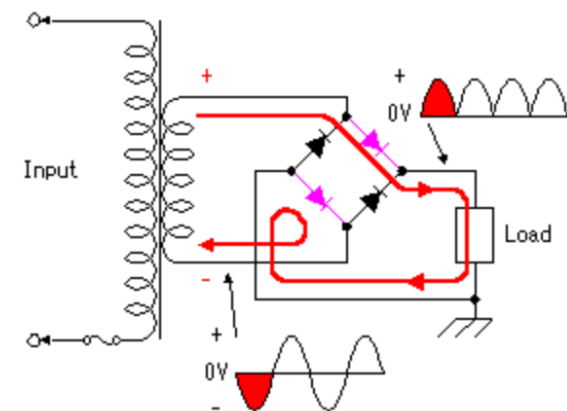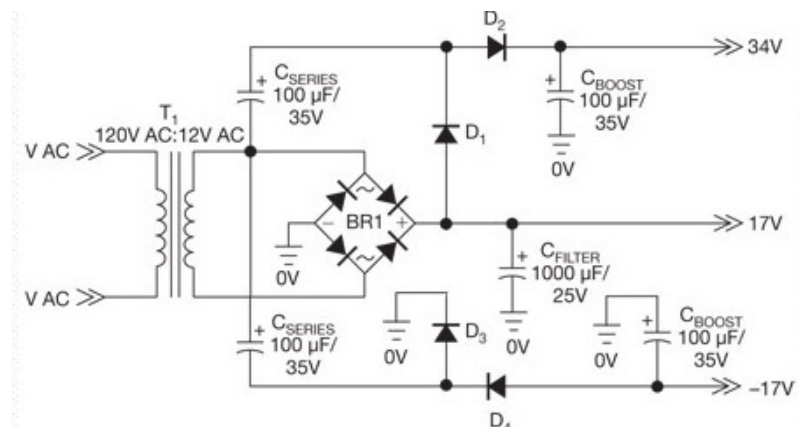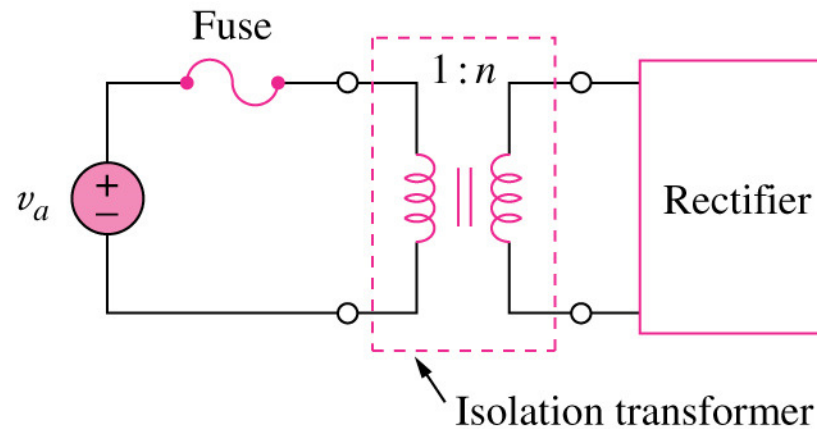
## 13.9 Applications (1)

- Transformer as an Isolation Device to isolate ac supply from a rectifier


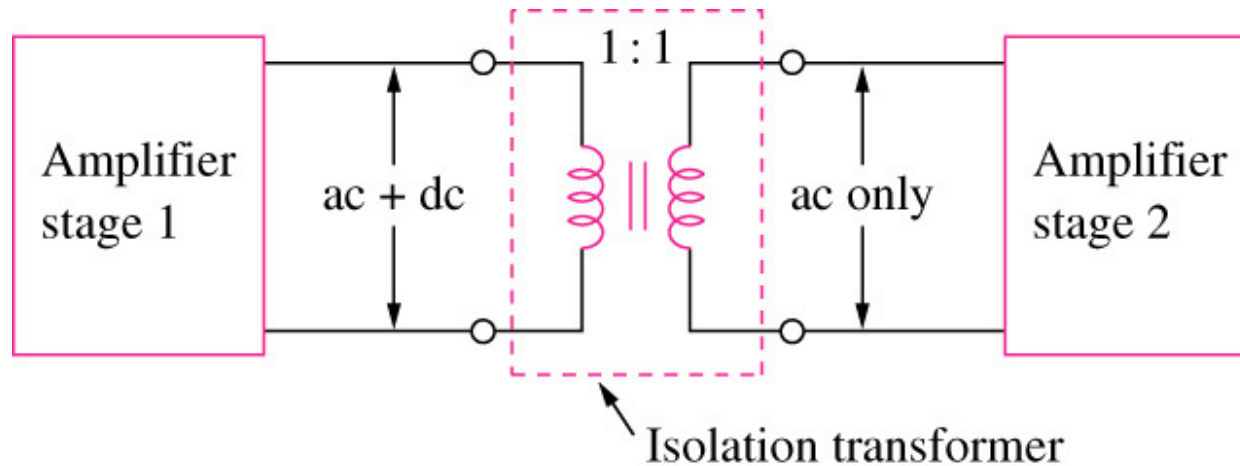
## 13.9 Applications (2)


- Transformer as an Isolation Device to isolate dc between two amplifier stages.



- Biasing is the application of a DC voltage to a transistor amplifier to produce a desired mode of operation.
- Each amplifier stage can be biased separately to operate in a particular mode.


## 13.9 Applications (3)

- Transformer as a Matching Device

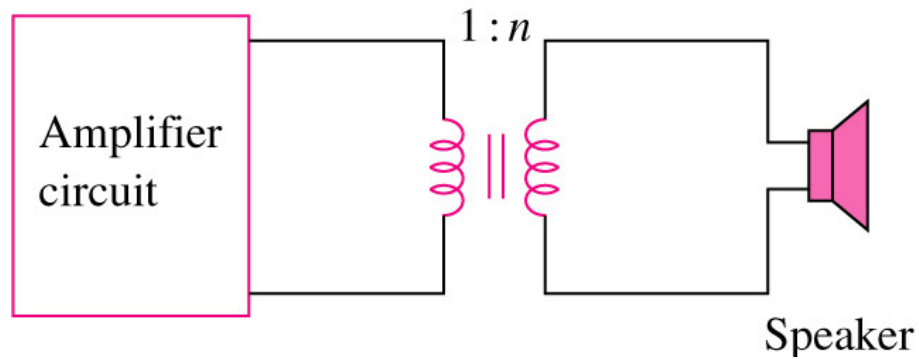

**Equivalent circuit**

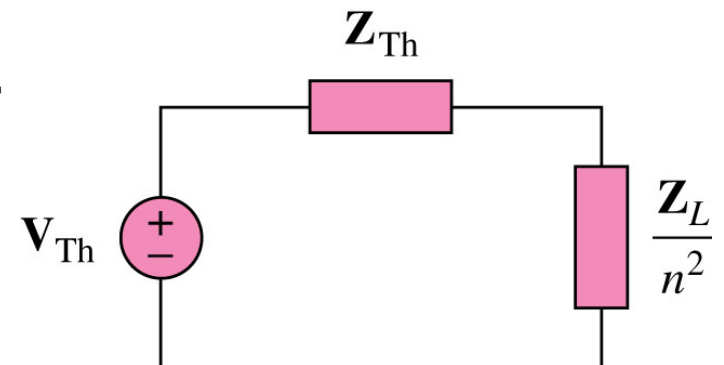**Using an ideal transformer to match the speaker to the amplifier**



## 13.9 Applications (4)

### Practice Problem 13.16 (Textbook)


Calculate the turns ratio of an ideal transformer required to match a  $400\Omega$  load to a source with internal impedance of  $2.5k\Omega$ . Find the load voltage when the source voltage is  $30V$ .

Ans:  $n = 0.4$ ;  $V_L = 6V$



## 13.9 Applications (5)

- A typical power distribution system

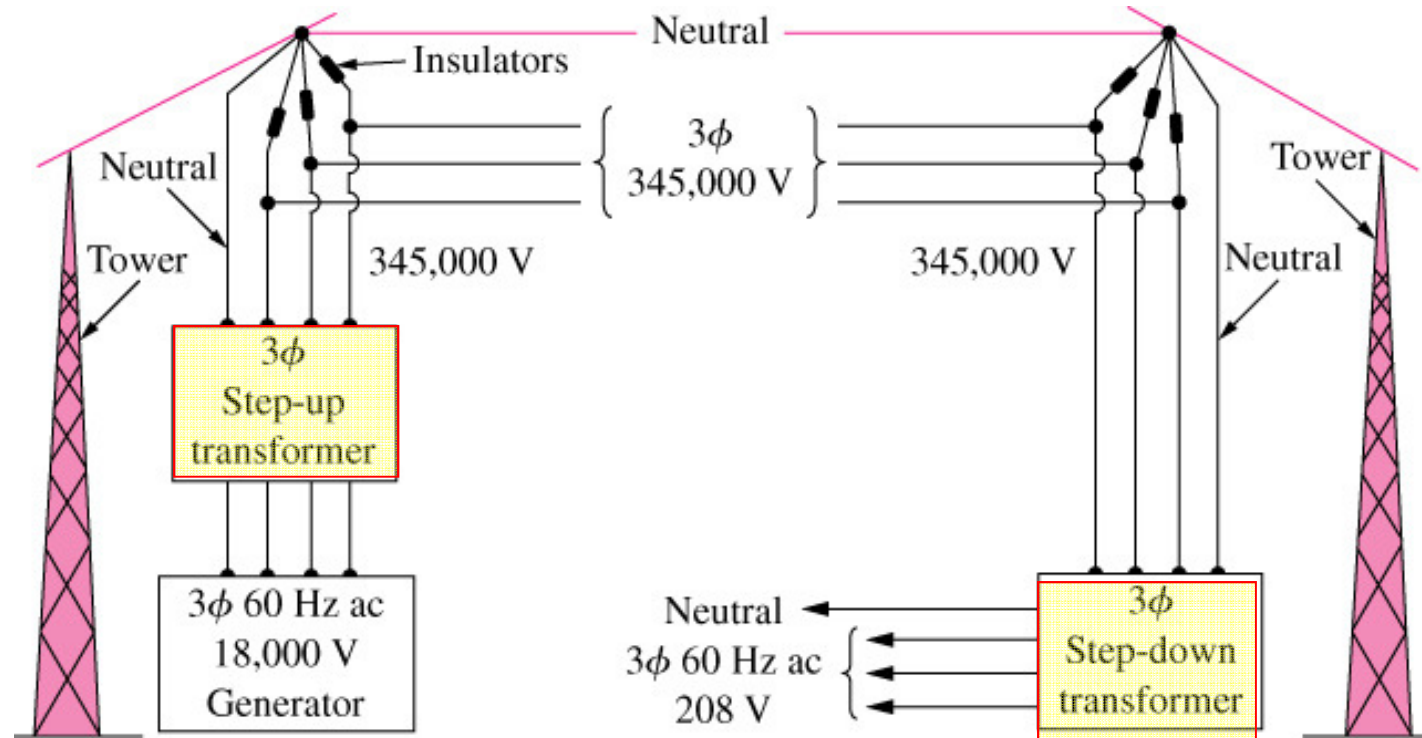

## Homework #3

**Due beginning of class Wednesday Feb 4, 2015**

- 13.30
- 13.35
- 13.42
- 13.50
- 13.53 (modified)
- Autotransformer (See handout)

**Exam over Chapter 13 on Monday Feb 9**

# Chapter 13

## Equation / Analysis Summary

- Series Aiding  $L = L_1 + L_2 + 2M$  / Opposing  $L = L_1 + L_2 - 2M$

- Dot Convention Model

- Coupling coefficient "k"  $M = k\sqrt{L_1 L_2}$

- Linear Transformer


- Input Impedance:

$$Z_{in} = Z_{primary} + \frac{\omega^2 M^2}{Z_{secondary}}$$

- Reflected Impedance:

$$Z_{reflected} = \frac{\omega^2 M^2}{Z_{secondary}}$$

- Equivalent T or  $\pi$  Circuits:

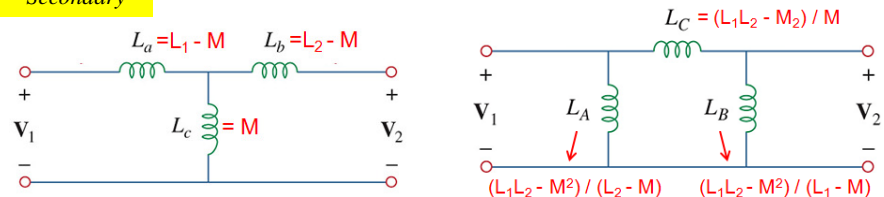

- Ideal Transformer

- $K = 1, L_1, L_2 \rightarrow \infty$

- Lossless ( $S_1 = S_2$ )


- Voltage / Current Relationship:

- Dots "same" = +n, Dots "diff" = -n

- Complex Power:  $S_1 = V_1 I_1^* = V_2 I_2^* = S_2$

- Autotransformer

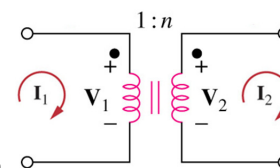- Adjustable "tap"
- No electrical Isolation
- Voltage Divider like relationship




$$V_2 = nV_1$$

$$I_2 = \frac{I_1}{n}$$

$$Z_{in} = \frac{Z_L}{n^2}$$

$$P_{ave} = |I_2|^2 R_L$$

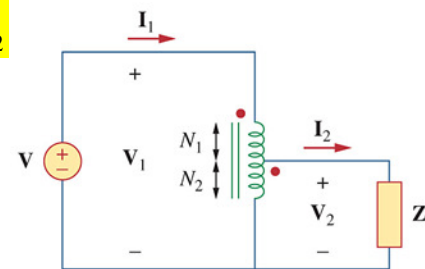

$$V_2 = \frac{N_2}{N_1 + N_2} V_1$$

$$I_2 = \frac{N_1 + N_2}{N_2} I_1$$

# Chapter 13


## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers
- 13.9 Applications
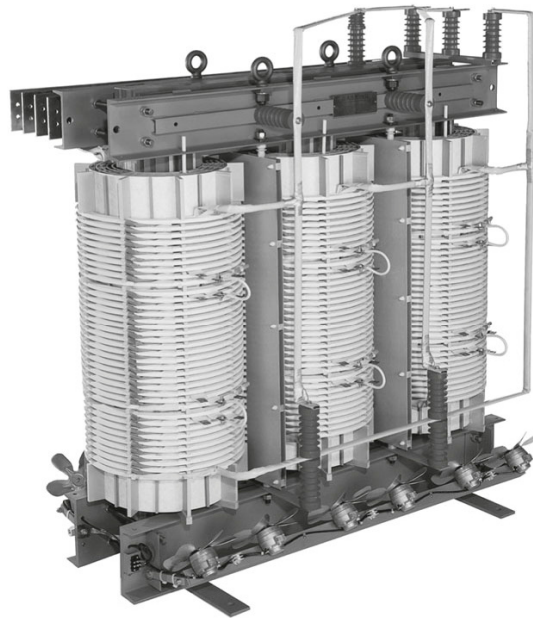
## 13.1 What is a transformer? (1)

- It is an electrical device designed on the basis of the concept of magnetic coupling
- It uses magnetically coupled coils to transfer energy from one circuit to another
- It is the key circuit elements for stepping up or stepping down ac voltages or currents, impedance matching, isolation, etc.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)



(b)


ECE 202 Ch 13

Courtesy of: (a) Electric Service Co., (b) Jensen Transformers
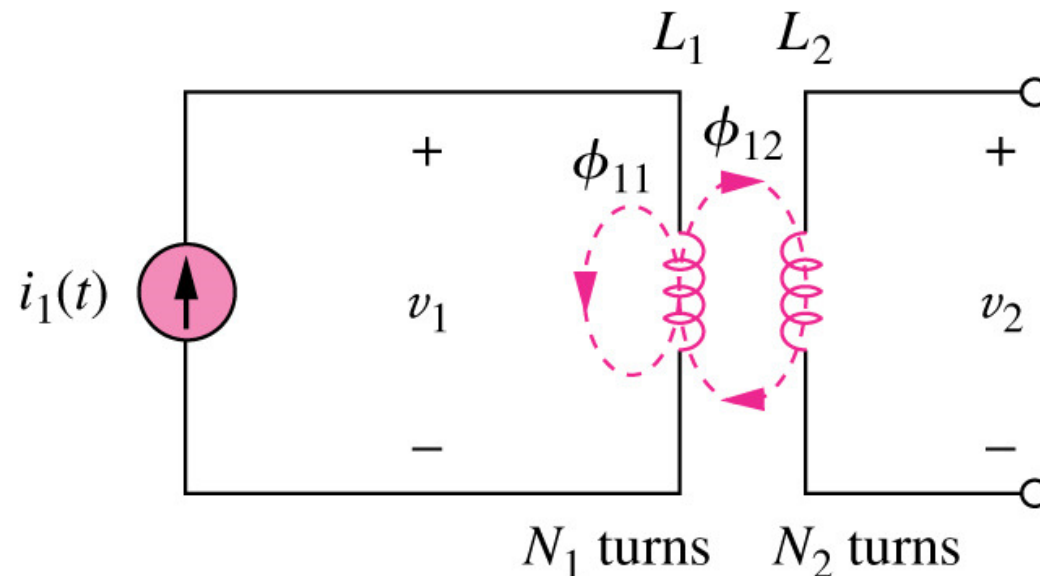
## 13.2 Mutual Inductance (1)


- Mutual Inductance

- When two inductors (or coils) are in close proximity of each other, the magnetic flux caused by current in one coil links with the other coil, thereby inducing voltage in the latter.


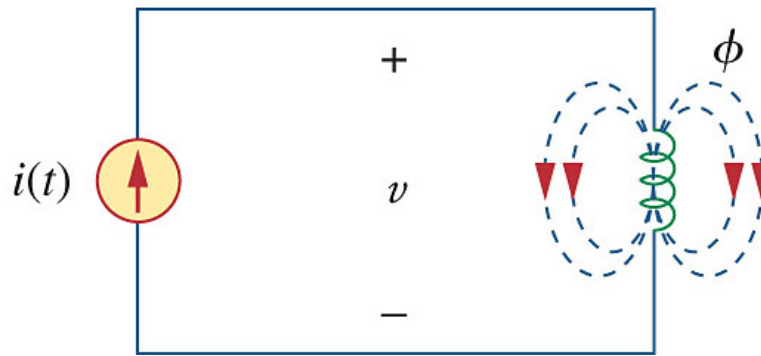
## 13.2 Mutual Inductance (2)

- First consider a single inductor, a coil with  $N$  turns:



When current  $i$  flows through the coil, a magnetic flux  $\Phi$  is produced around it.

- According to Faraday's law, the voltage  $v$  induced in the coil is proportional to the number of turns  $N$  and the time rate of change of magnetic flux  $\Phi$ :

$$v = N \frac{d \phi}{d t}$$

## 13.2 Mutual Inductance (3)

- Voltage induced in the coil given by:
- But the flux  $\Phi$  is produced by current  $i$  so that any change in  $\Phi$  is caused by a change in the current:
- Recall the voltage-current relationship for an inductor:
- The “Self” inductance  $L$  of the inductor is thus given by:
- Self-inductance  $L$  relates the voltage induced in a coil by a time-varying current in the same coil.

$$v = N \frac{d \phi}{d t}$$

$$v = N \frac{d \phi}{d i} \frac{d i}{d t}$$


$$v = L \frac{d i}{d t}$$

$$L = N \frac{d \phi}{d i}$$


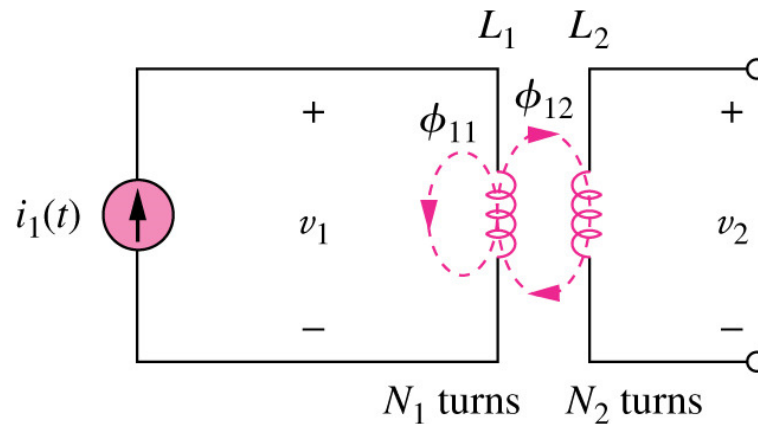
## 13.2 Mutual Inductance (4)

- Now consider two coils with self-inductances  $L_1$  and  $L_2$  that are in close proximity of each other:



Coil 1 has  $N_1$  turns

Coil 2 has  $N_2$  turns.


*Assume coil 2 carries no current.*

- The total magnetic flux  $\Phi_1$  emanating from coil 1 has two components:
  - $\Phi_{11}$  links only coil 1
  - $\Phi_{12}$  links both coils

$$\phi_1 = \phi_{11} + \phi_{12}$$

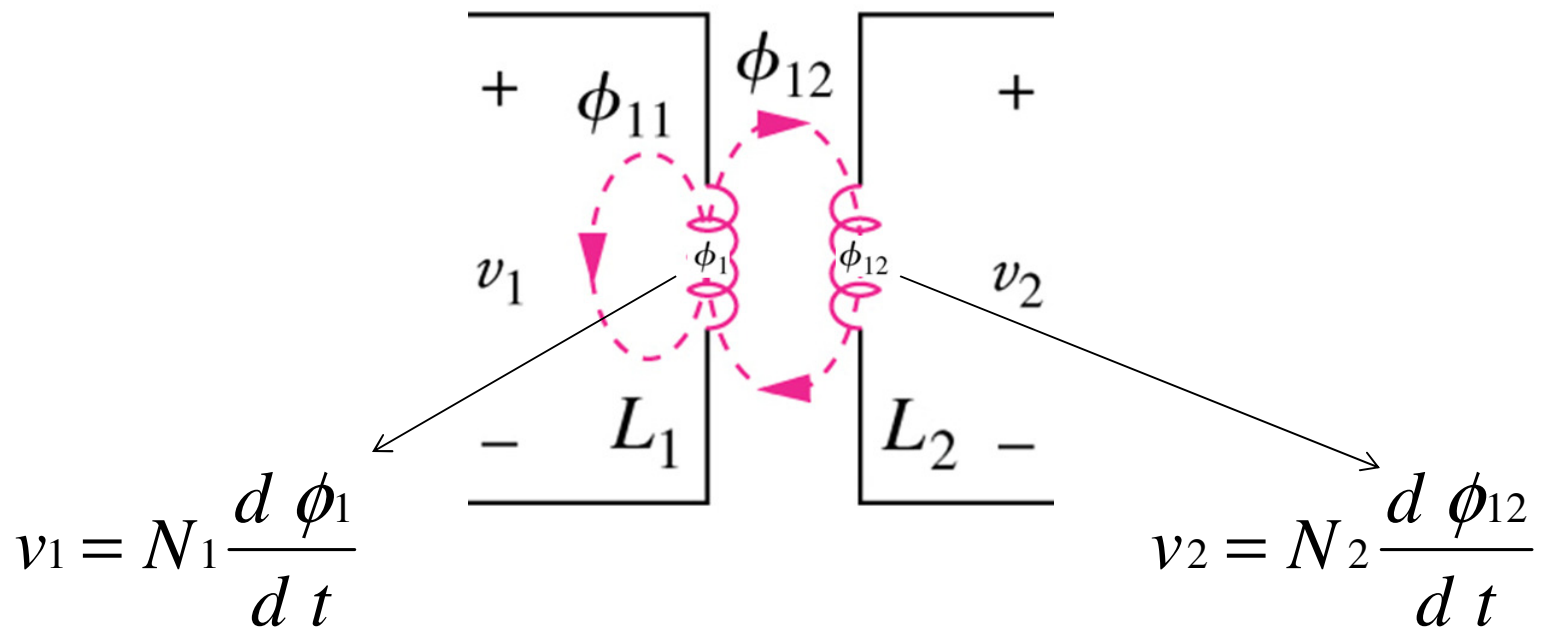
## 13.2 Mutual Inductance (5)

- Although the two coils are physically separated, they are magnetically coupled.
- The voltage induced in each coil is proportional to the flux in each coil.


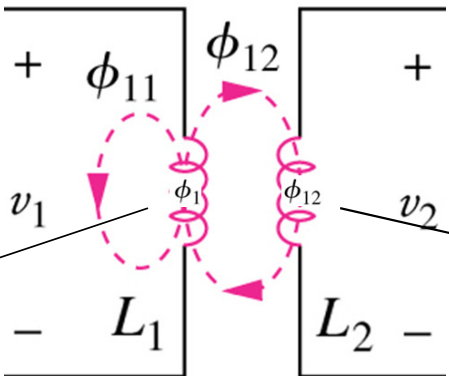
## 13.2 Mutual Inductance (6)

- The voltage equations can be rewritten as follows:



$v_2$  is the open-circuit mutual voltage (or induced voltage) across coil 2

$$v_1 = N_1 \frac{d \phi_1}{d t}$$

$$v_2 = N_2 \frac{d \phi_{12}}{d t}$$

$$v_1 = N_1 \frac{d \phi_1}{d i_1} \frac{d i_1}{d t}$$

$$v_2 = N_2 \frac{d \phi_{12}}{d i_1} \frac{d i_1}{d t}$$

$$v_1 = L_1 \frac{d i_1}{d t}$$


$$v_2 = M_{21} \frac{d i_1}{d t}$$

$L_1$  is the self-inductance of coil 1

$M_{21}$  is the mutual inductance of coil 2 with respect to coil 1
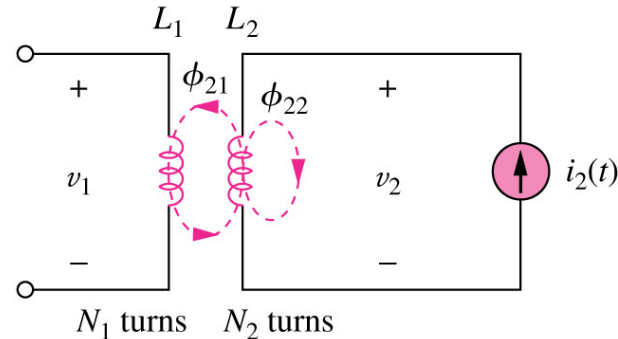
## 13.2 Mutual Inductance (7)

- Suppose now we let current  $i_2$  flow in coil 2 while coil 1 carries no current:



- The magnetic flux  $\Phi_2$  emanating from coil 2 comprises flux  $\Phi_{22}$  that links only coil 2 and flux  $\Phi_{21}$  that links both coils:

$$\phi_2 = \phi_{21} + \phi_{22}$$

- The resulting symmetry is true:


$$v_2 = L_2 \frac{d i_2}{d t} \quad v_1 = M_{12} \frac{d i_2}{d t} \quad M_{12} = N_1 \frac{d \phi_{21}}{d i_2}$$

## 13.2 Mutual Inductance (8)

- $M_{12} = M_{21} = M$  ; The “Mutual inductance” between the coils
- Mutual inductance  $M$  is measured in Henrys (just like inductors)
- Mutual inductance only exists when inductors or coils are in close proximity and the circuits are driven by time-varying sources
- Although mutual inductance  $M$  is always a positive quantity, the mutual voltage  $M \, di/dt$  may be negative or positive, just like the self-induced voltage  $L \, di/dt$  (determined by “Dot” convention)
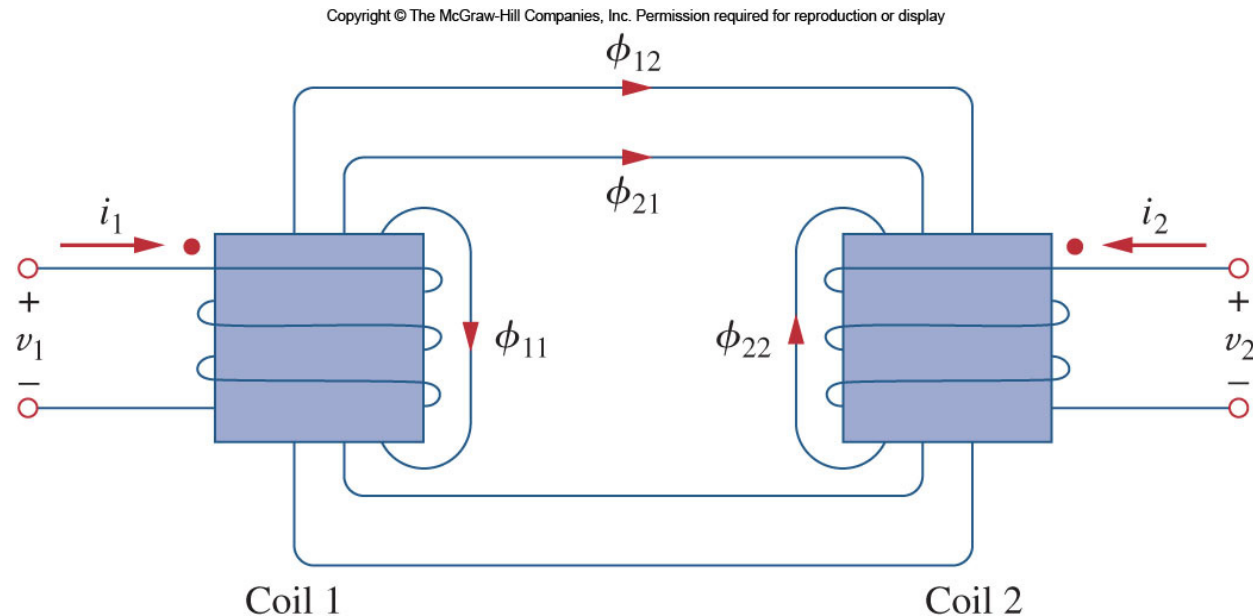
## 13.2 Mutual Inductance (9)

- Self-induced voltage polarity is determined by the reference direction of the current and the reference polarity of the voltage,
- The polarity of the mutual voltage is not as easy to determine (depends on winding direction of the coils).
- We use the dot convention to determine





## 13.2 Mutual Inductance (10)

### “Dot Convention”

- If a current **enters** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **positive** at the dotted terminal of the second coil.



Voltage is  
“Negative”

Enters the  
“Un-Dotted” side

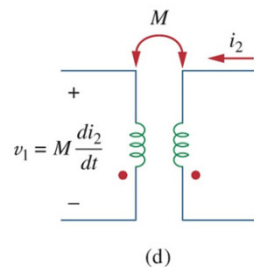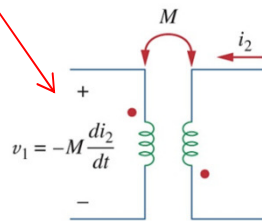

Enters the “Dot”

Voltage is  
“Positive”

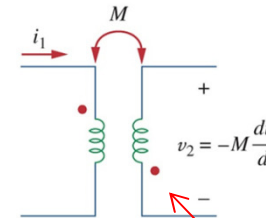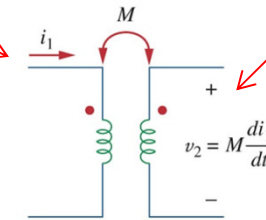


Voltage is  
“Positive”  
At “Dotted”  
Terminal

- Alternatively, if a current **leaves** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **negative** at the dotted terminal of the second coil.

## 13.2 Mutual Inductance (11)
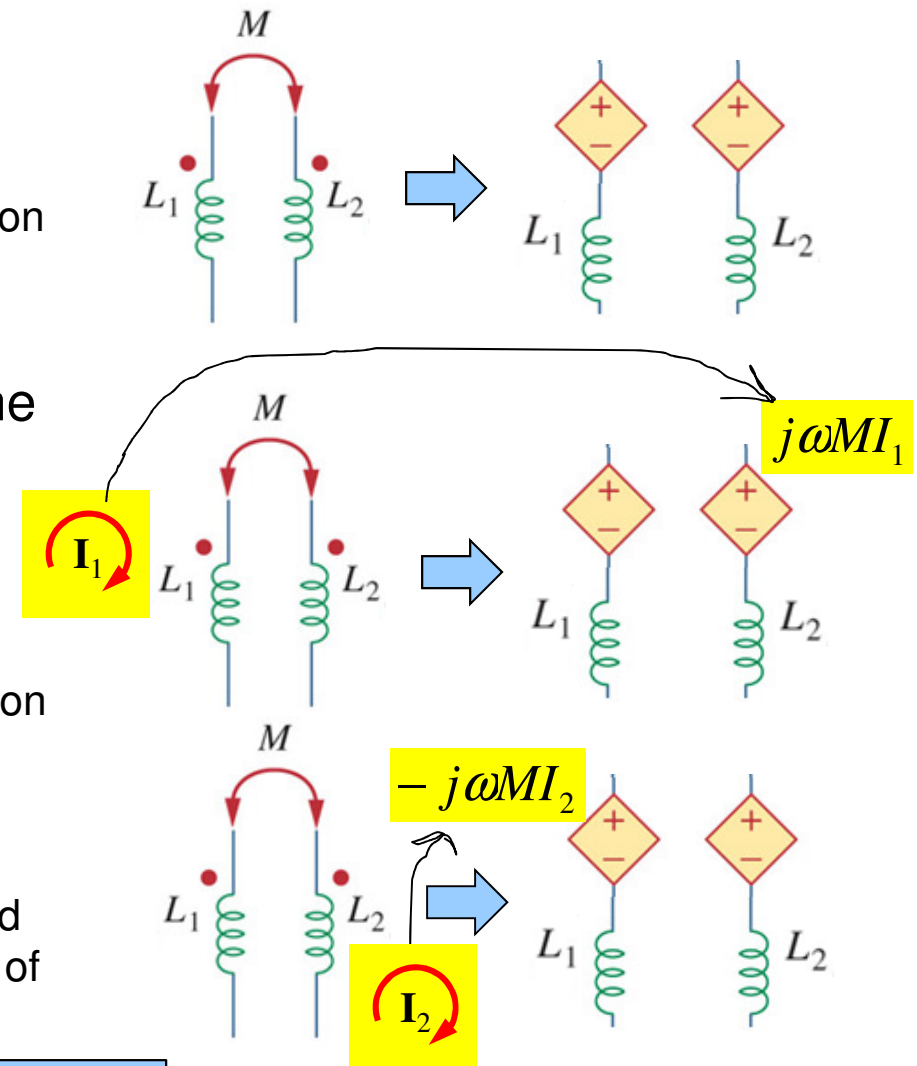
### “The Model” (Phasor domain)

- Replace the “Dot” with a controlled voltage source.
  - Place on same side as the Dot
  - Positive terminal in same direction as the Dot
- Now look at the current entering each dot to determine the magnitude of the voltage source
  - If the current enters the dotted terminal, it will induce a positive voltage in the controlled source on the opposite terminal of  $j\omega M(I)$
  - If the current enters the “un-dotted” terminal, it will induce a negative voltage in the controlled source on the opposite terminal of  $-j\omega M(I)$




Note: This method differs slightly from the text



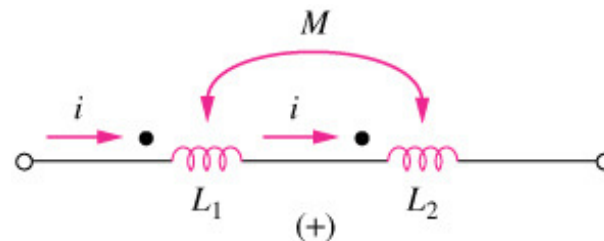
## 13.2 Mutual Inductance (12)

Dot convention for coils in series; the sign indicates the polarity of the mutual voltage



$$L = L_1 + L_2 + 2M$$

(series - aiding connection)

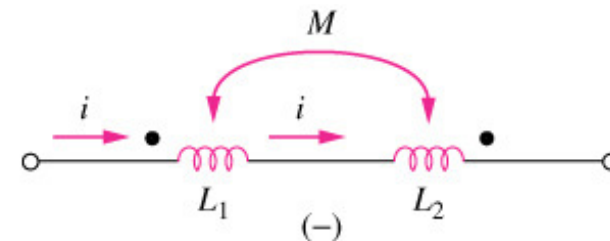

$$L = L_1 + L_2 - 2M$$

(series - opposing connection)


We can show this using the model!

## 13.2 Mutual Inductance (13)

### Example Problem 13.1
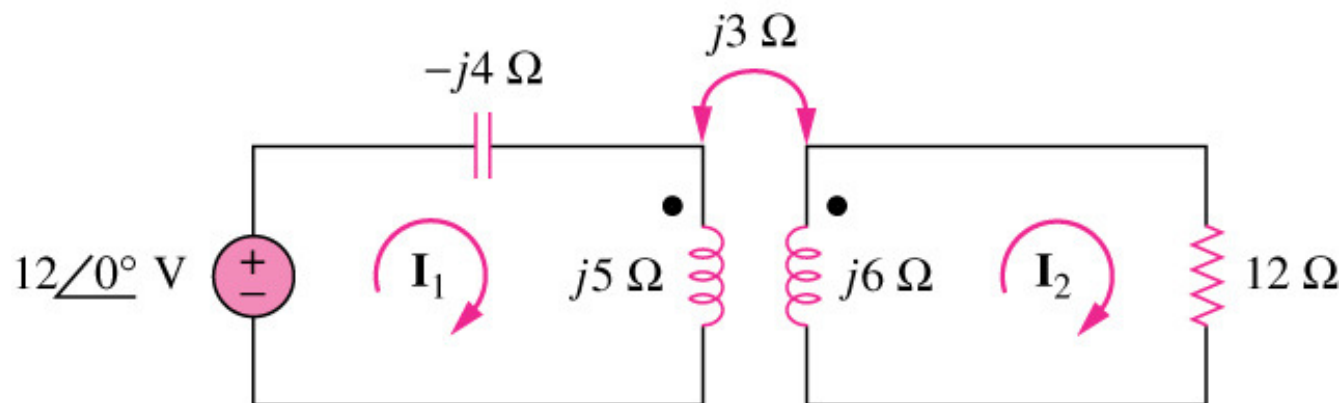
#### Example 13.1 (Textbook)

Calculate the phasor currents  $I_1$  and  $I_2$  in the circuit shown below.




Ans:  $I_1 = 13.02 \angle -49.40^\circ \text{ A}$ ;  $I_2 = 2.91 \angle 14.04^\circ \text{ A}$

## 13.2 Mutual Inductance (14)

### Example Problem 13.1

First, replace with the model:

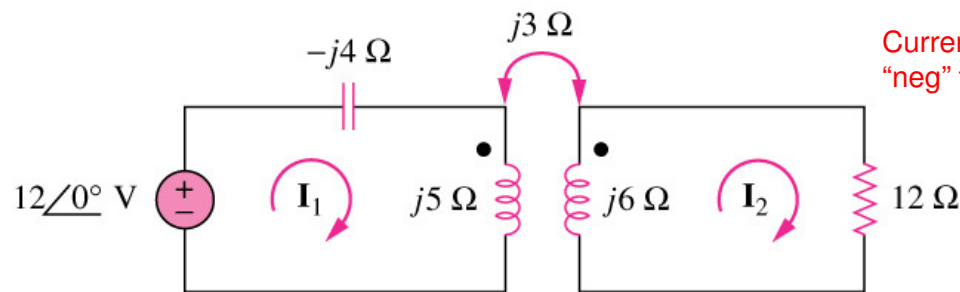

Then, solve Loop Equations:


**Loop  $I_1$**

Current enters "neg" terminal

Current enters "+" terminal but value is  $-j3I_2$

$$-12 - j4I_1 + (-j3I_2) + j5I_1 = 0$$

$$jI_1 - j3I_2 = 12$$

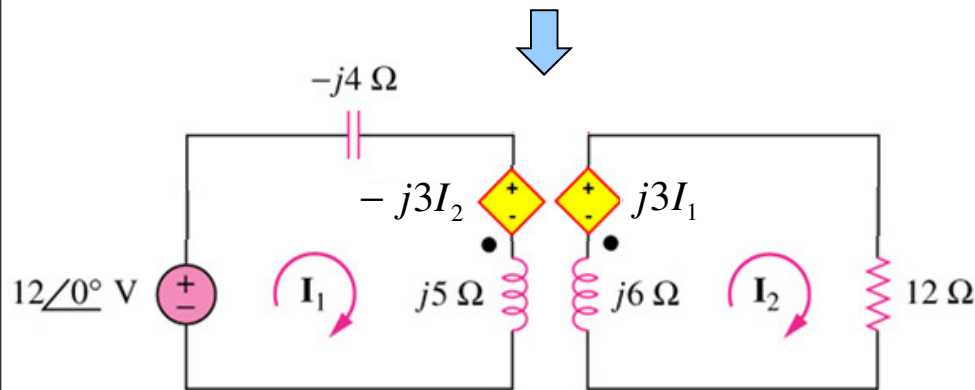

**Loop  $I_2$**

Current enters "neg" terminal

$$j6I_2 - j3I_1 + 12I_2 = 0$$

$$-j3I_1 + (12 + j6)I_2 = 0$$

NOTE:

$I_1$  goes "into" the dot  $\rightarrow$  Induced voltage on the second coil is "Positive"

$I_2$  goes "into" the un-dotted side  $\rightarrow$  Induced voltage on the first coil is "Negative"

**Pay Attention to Sign Conventions !**

## 13.2 Mutual Inductance (15)

### Example Problem 13.1

Lastly, solve 2 equations, 2 unknowns (expected you know this):

$$\text{Loop } I_1 \longrightarrow jI_1 - j3I_2 = 12 \longrightarrow jI_1 = 12 + j3I_2 \Rightarrow I_1 = 3I_2 - j12$$

$$\text{Loop } I_2 \longrightarrow -j3I_1 + (12 + j6)I_2 = 0 \quad I_1 = 3(2.824 + j0.706) - j12$$

$$\text{Substitution: } -3(12 + j3I_2) + (12 + j6)I_2 = 0$$

$$\div \text{ by } 3 \quad -12 - j3I_2 + (4 + j2)I_2 = 0$$

$$\text{Collect Terms: } (4 - j)I_2 = 12$$

$$\text{Solve for } I_2 \quad I_2 = \frac{12}{(4 - j)} = 2.824 + j0.706 = 2.91 \angle 14.04^\circ \text{ A}$$

Find  $I_1$  (Substitute back to Eq1)



$$I_1 = 8.471 + j2.118 - j12$$

$$I_1 = 8.471 - j9.882 = 13.02 \angle -49.40^\circ \text{ A}$$

Think about where we could have made mistakes!

- Applying the model incorrectly (wrong sign convention)
- Incorrect Phasor notation ( Understand:  $j\omega M \leftrightarrow j3$  ;  $j\omega L \leftrightarrow j5$  ;  $1/j\omega C \leftrightarrow -j4$  )
- Incorrect sign convention for loop equations
  - Current entering negative terminal of a voltage source
- Understanding of complex numbers!
  - Familiarity with your calculators handling of complex numbers
  - Converting from rectangular to polar


Review / Understand these concepts to avoid these mistakes

## 13.2 Recommended Viewing:

- Watch these videos illustrating solving mutual inductance problems:
  - <http://www.youtube.com/watch?v=tD35a-uzd34>
  - <http://www.youtube.com/watch?v=hzU4XKQYTWw>
  - <http://www.youtube.com/watch?v=OqSvesTtnUo>
- Uses the model described previously to solve mutual inductance problems.

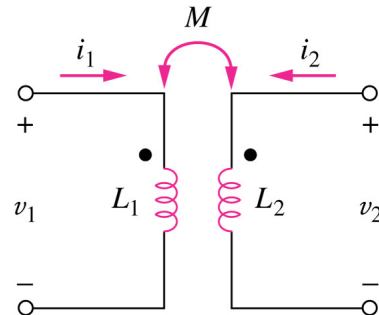
## 13.3 Energy in a Coupled Circuit (1)

- The instantaneous energy  $w$  stored in the circuit is:




$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

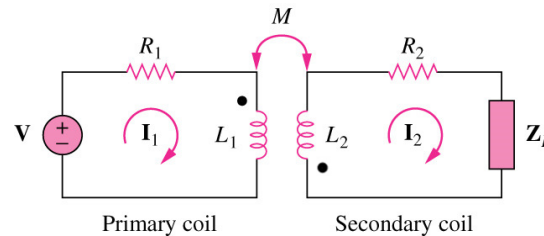- If **both** currents enter (or **both** leave) the dotted terminal the mutual term is (positive):



$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

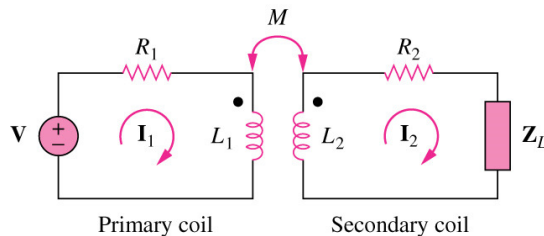- Otherwise the mutual term is (negative):



$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$

## 13.3 Energy in a Coupled Circuit (2)


- The coupling coefficient,  $k$ , is a measure of the magnetic coupling between two coils;  $0 \leq k \leq 1$ .

$$M = k\sqrt{L_1 L_2}$$


$K = 1$  coils perfectly coupled

$K < 0.5$  coils loosely coupled

$K > 0.5$  coils tightly coupled

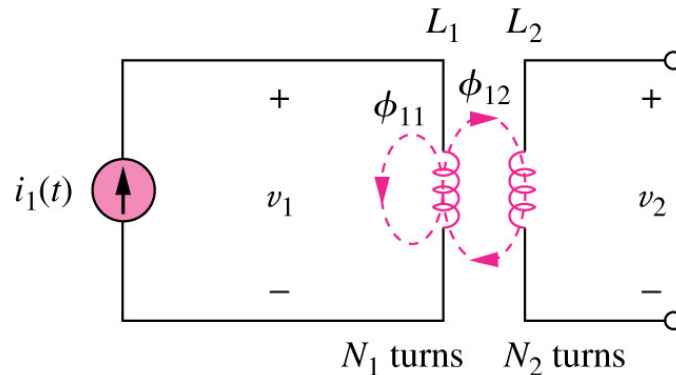
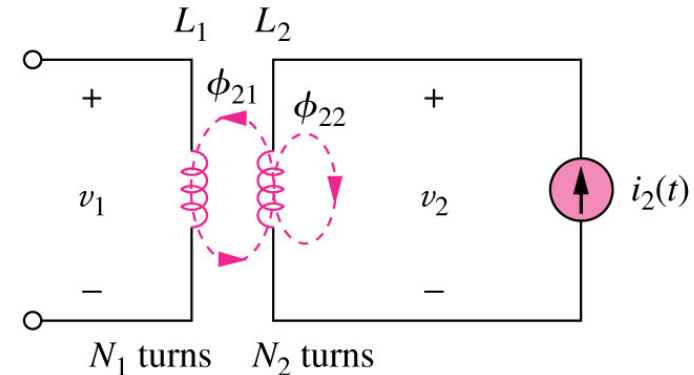
$$K = \frac{\phi_{12}}{\phi_{11} + \phi_{12}}$$




$$K = \frac{\phi_{21}}{\phi_{21} + \phi_{22}}$$

## 13.3 Energy in a Coupled Circuit (3)

### Example 13.3
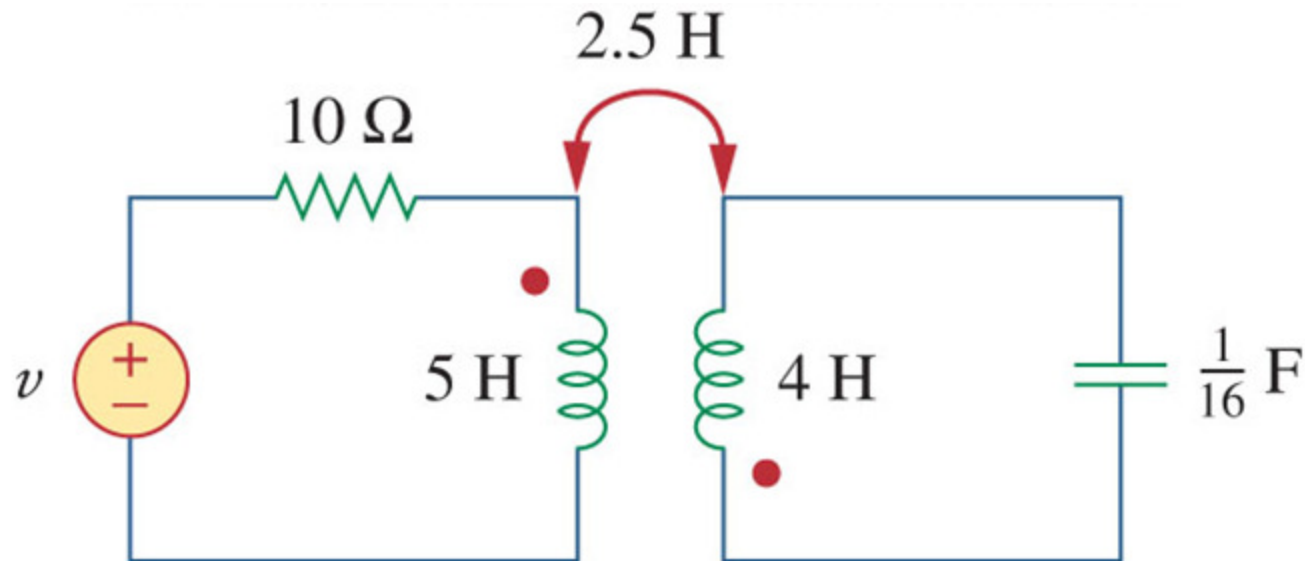
### Example 13.3 (Textbook)

Consider the circuit below. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time  $t = 1\text{ s}$  if  $v = 60\cos(4t + 30^\circ)\text{ V}$ .




Ans:  $k=0.56$ ;  $w(1)=20.73\text{ J}$



# 13.3 Energy in a Coupled Circuit (4)

## Example 13.3

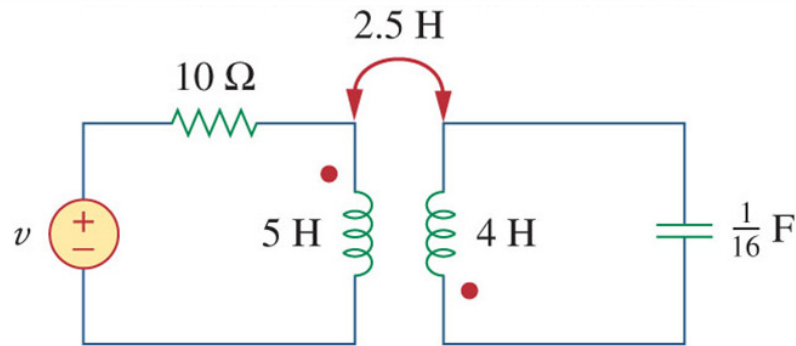


To find k, use the relation between  $L_1$ ,  $L_2$ , and  $M$ :

$$L_1 = 5 ; L_2 = 4 ; M = 2.5$$


$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2.5}{\sqrt{(5)(4)}} = 0.56$$

Apply the "Model" ↓

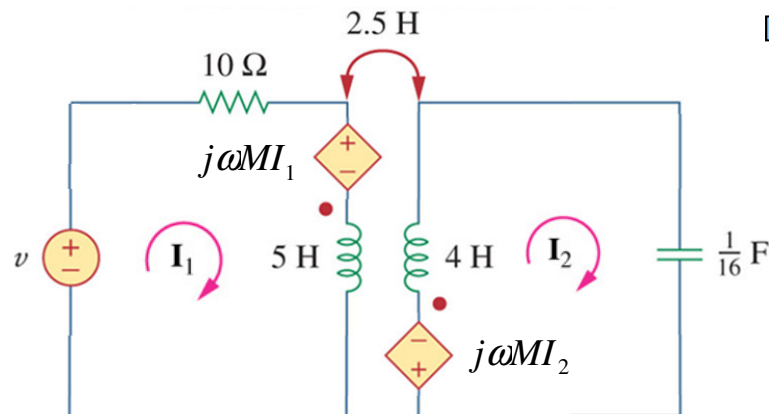

Convert to Phasor

$$\omega = 4$$

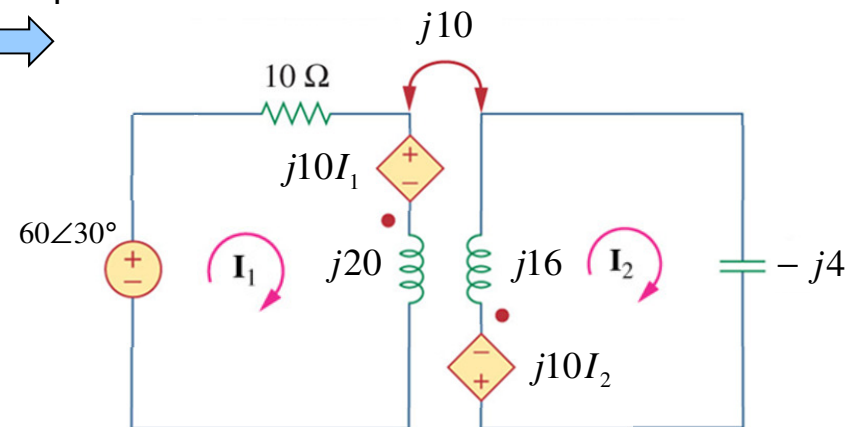

Solve Mesh equations for  $I_1$  and  $I_2$

## 13.3 Energy in a Coupled Circuit (5)

### Example 13.3

From Mesh analysis:

$$I_1 = 3.905 \angle -19.4^\circ \text{ A}$$

$$I_2 = 3.254 \angle 160.6^\circ \text{ A}$$

At  $t = 1$ , the value of  $\omega t = (4)(1) = 4$  radians =  $229.2^\circ$

To find the energy at  $t = 1$ :

$$i_1 = 3.905 \cos(\omega t - 19.4^\circ)$$

$$i_2 = 3.254 \cos(\omega t + 160.6^\circ)$$

$$i_1 = 3.905 \cos(229.2^\circ - 19.4^\circ) = -3.389$$

$$i_2 = 3.254 \cos(229.2^\circ + 160.6^\circ) = 2.824$$

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

Positive since current (as defined) enters **both** dots

$$w = \frac{1}{2} (5)(-3.389)^2 + \frac{1}{2} (4)(2.824)^2 + 2.5(-3.389)(2.824) = 20.73 \text{ J}$$

# Homework #2

Due in class Monday, January 26, 2015

- 13.1
- 13.7
- 13.9
- 13.24


# Chapter 13

## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers**
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers
- 13.9 Applications
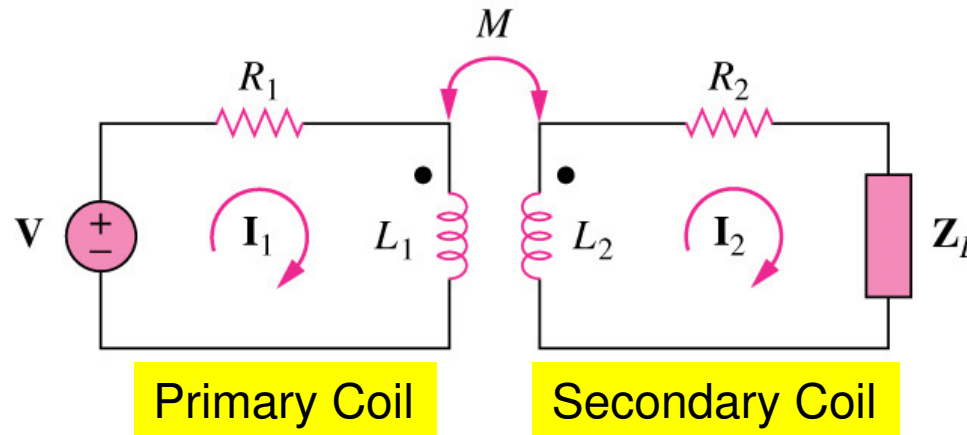
## 13.4 Linear Transformers (1)

- A transformer is generally a four-terminal device comprising two (or more) magnetically coupled coils. Below is a “simple” model:




- The coil connected to the voltage source is called the **primary winding**.
- The coil connected to the load is called the **secondary winding**.
- Resistances  $R_1$  and  $R_2$  are included to account for the losses in the coils.
- A transformer is said to be linear if the coils are wound on a magnetically linear material for which the permeability is constant.
  - Air, plastic, Bakelite, wood, etc.
  - Most materials are magnetically linear.

## 13.4 Linear Transformers (2)
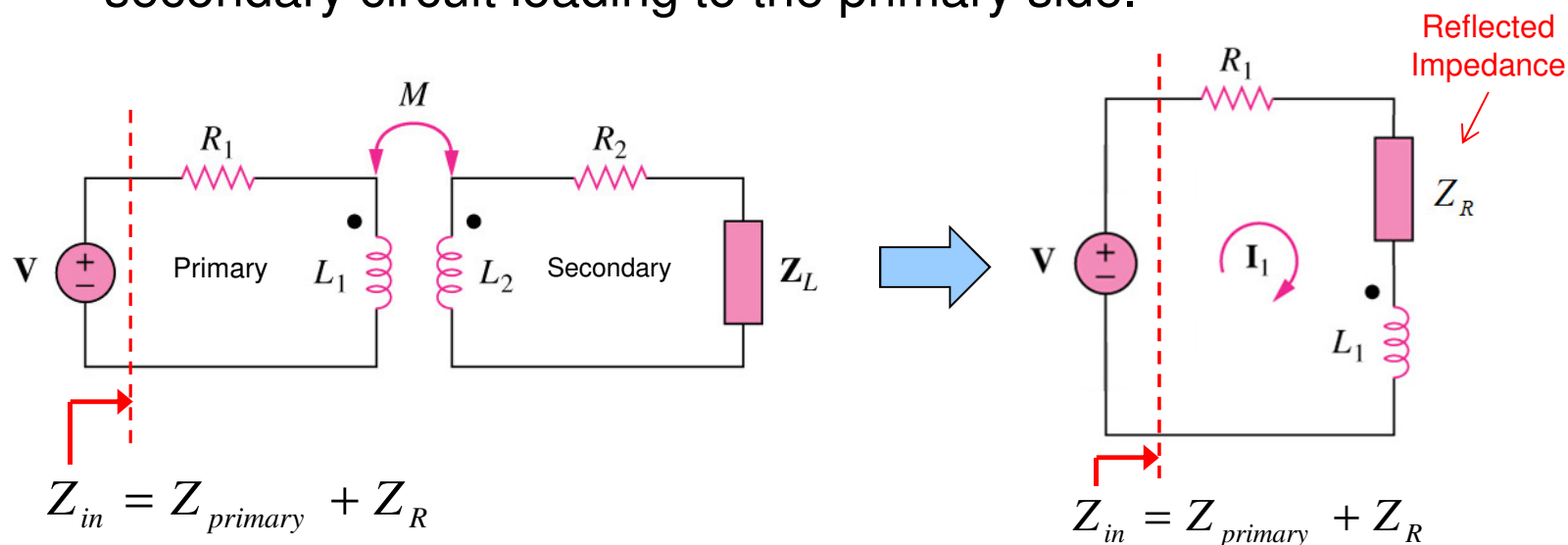
### Reflected Impedance


- Often we are interested in the input impedance  $Z_{in}$  seen by the source.
  - For example, may want to match  $Z_{in}$  to the source impedance for maximum power transfer!
- To simplify our analysis we can break  $Z_{in}$  up into:
  - $Z_{primary}$  -- The impedance of the “primary” circuit ( $Z_{primary} = R_1 + j\omega L_1$ )
  - $Z_R$  -- The “reflected” impedance back to the “primary”.
- The “reflected” impedance  $Z_R$  is the contribution of the secondary circuit loading to the primary side.



# 13.4 Linear Transformers (2)

## Reflected Impedance

To obtain the input impedance  $Z_{in}$  as seen from the source:

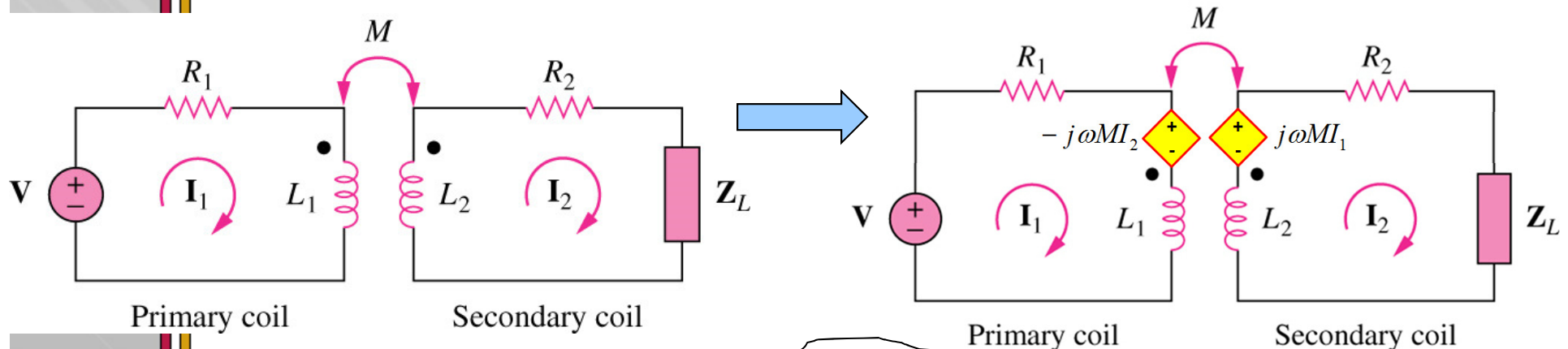

Mesh 1:  $V = (R_1 + j\omega L_1)I_1 - j\omega MI_2$  → Current enters positive terminal so it is  $+$  ( $-j\omega MI_2$ )

Mesh 2:  $0 = -j\omega MI_1 + (R_2 + j\omega L_2 + Z_L)I_2$  → Current enters negative terminal so it is  $-$  ( $j\omega MI_1$ )

From Mesh 2:

$$I_2 = \frac{j\omega M}{R_2 + j\omega L_2 + Z_L} I_1$$

Substituting into Mesh 1 gives:

$$V = (R_1 + j\omega L_1)I_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} I_1$$

**Reflected Impedance**


$$Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

$$V = Z_{primary} I_1 + Z_{reflected} I_1$$

# 13.4 Linear Transformers (3)

## Reflected Impedance (Another way of looking at it !)

Obtain input impedance  $Z_{in}$  as seen from the source:

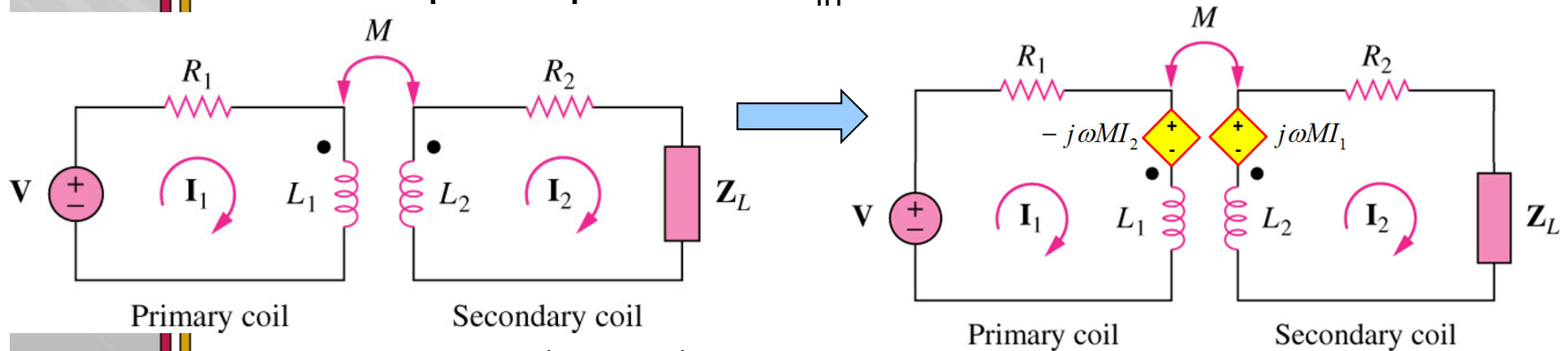

Mesh 1:  $V = (Z_{primary})I_1 - j\omega M I_2$

Mesh 2:  $0 = -j\omega M I_1 + (Z_{Secondary})I_2$

$Z_{Secondary}$  = the total series impedance in the secondary loop

From Mesh 2:

$$I_2 = \frac{j\omega M}{Z_{Secondary}} I_1$$

**Reflected Impedance**

$$Z_R = \frac{\omega^2 M^2}{Z_{Secondary}}$$

Substituting into Mesh 1 gives:

$$V = Z_{primary} I_1 + \frac{\omega^2 M^2}{Z_{Secondary}} I_1$$


$$V = Z_{primary} I_1 + Z_{reflected} I_1$$



## 13.4 Linear Transformers (4)
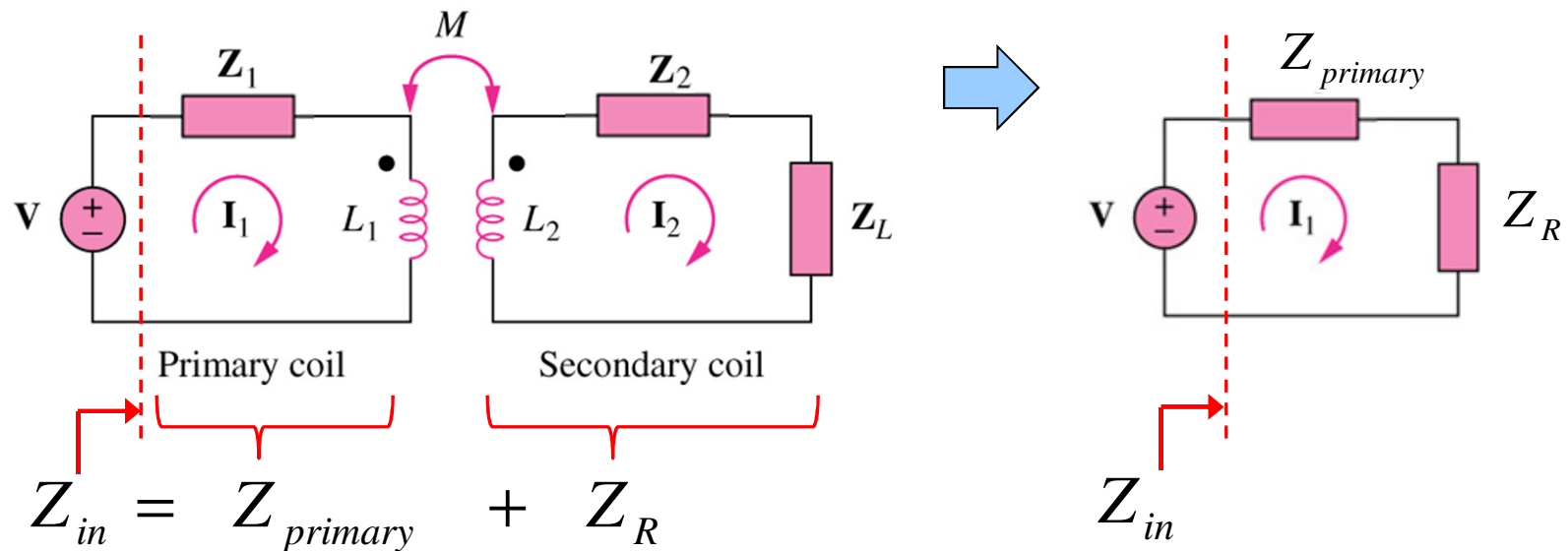
### Reflected Impedance

- The input impedance can be broken into two parts as follows:



- Series Impedance in Primary Coil:  $Z_{primary} = Z_1 + j\omega L_1$
- Series Impedance in Secondary Coil:  $Z_{secondary} = Z_2 + Z_L + j\omega L_2$
- Input Impedance:  $Z_{in} = Z_{primary} + \frac{\omega^2 M^2}{Z_{secondary}}$


*Note:  $Z_{in}$  will be the same if the dot on  $L_2$  is switched*

## 13.4 Linear Transformers (5)

### Example 13.4
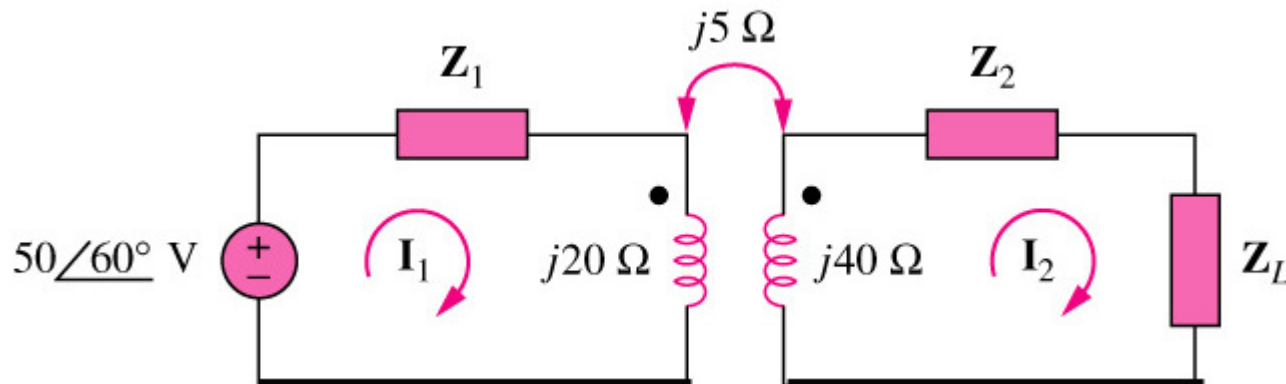
### Example 13.4 (textbook)


In the circuit below, calculate the input impedance and current  $I_1$ . Take  $Z_1=60-j100\Omega$ ,  $Z_2=30+j40\Omega$ , and  $Z_L=80+j60\Omega$ .



Ans:  $Z_{in} = 100.14\angle -53.1^\circ\Omega$ ;  $I_1 = 0.5\angle 113.1^\circ\text{A}$

## 13.4 Linear Transformers (5)

### Example 13.4

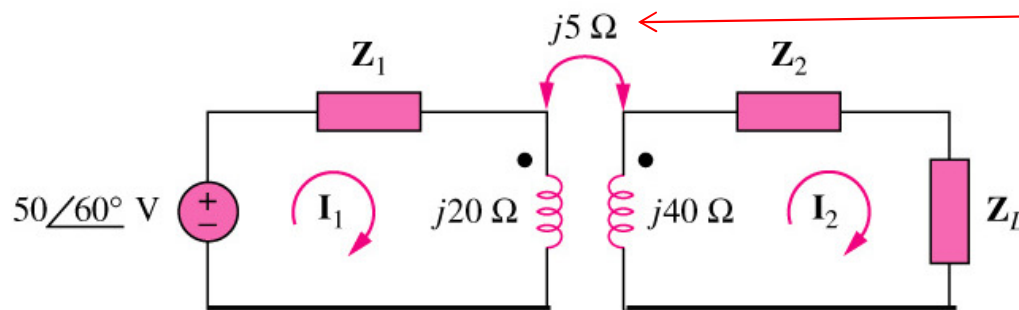

**Note:**

$$j\omega M = j5$$

$$\omega M = 5$$

$$(\omega M)^2 = 25$$

- The series impedance in the primary coil:

$$Z_{primary} = (60 - j100) + j20 = 60 - j80$$

- The series impedance in the secondary coil:

$$Z_{secondary} = (30 + j40) + (80 + j60) + j40 = 110 + j140$$

- Input Impedance given by:


$$Z_{in} = Z_{primary} + \frac{\omega^2 M^2}{Z_{Secondary}} = (60 - 80j) + \frac{25}{(110 + j140)} = 60.09 - j80.11$$

- Current  $I_1$  given by: 
$$I_1 = \frac{V_s}{Z_{in}} = \frac{50 \angle 60^\circ}{60.09 - j80.11} = \frac{50 \angle 60^\circ}{100.14 \angle -53.1^\circ}$$


## 13.4 Linear Transformers (6)
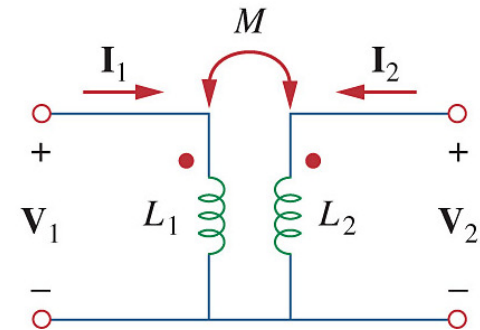
### Equivalent T and $\pi$ Circuits:


- It is sometimes convenient to replace a magnetically couple circuit with an equivalent circuit with no magnetic coupling.
- We can replace the linear transformer with an equivalent T or  $\pi$  circuit that has no mutual inductance.



T Circuit

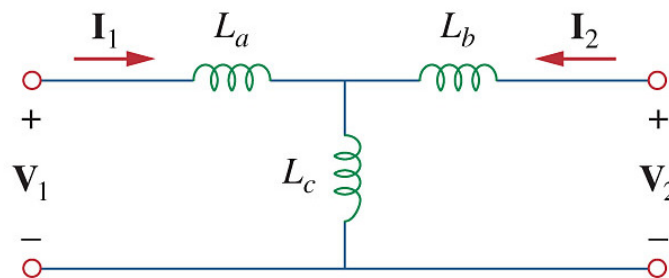


$\pi$  Circuit

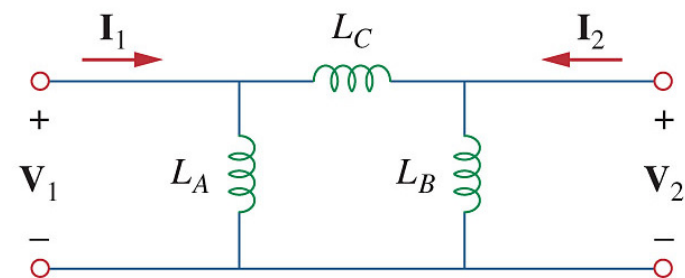

## 13.4 Linear Transformers (7)

### Equivalent T Circuit:


#### Linear Transformer Circuit

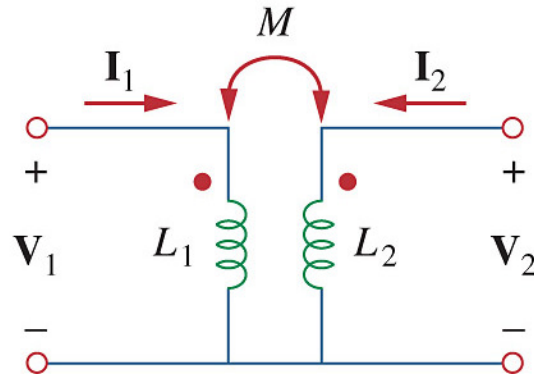

Mesh Analysis of this transformer circuit results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

#### Equivalent T Network

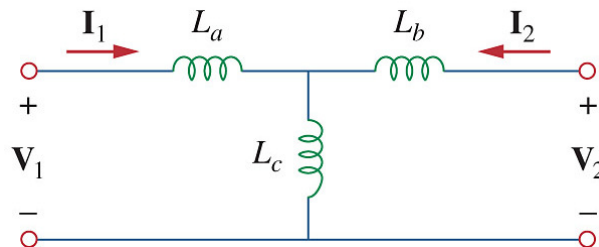

Mesh Analysis of the equivalent T network results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


Equating the terms gives the following relationships:

$$L_a = L_1 - M \quad L_b = L_2 - M \quad L_c = M$$

## 13.4 Linear Transformers (8)

### Equivalent T Circuits (Swapped Dots):


Linear Transformer Circuit

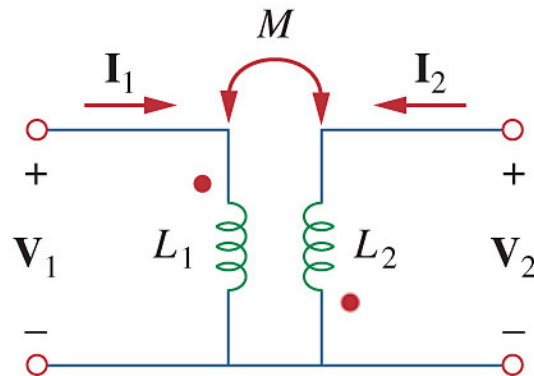

Mesh Analysis of this transformer circuit results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & -j\omega M \\ -j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Equivalent T Network

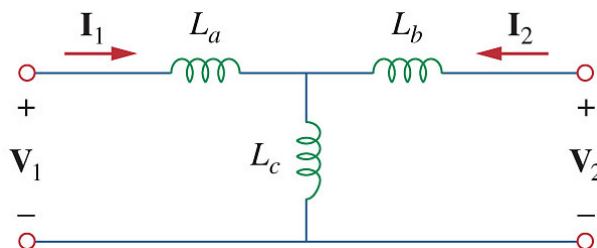

Mesh Analysis of the equivalent T network results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


Equating the terms gives the following relationships:

$$L_a = L_1 + M \quad L_b = L_2 + M \quad L_c = -M$$

## 13.4 Linear Transformers (9)

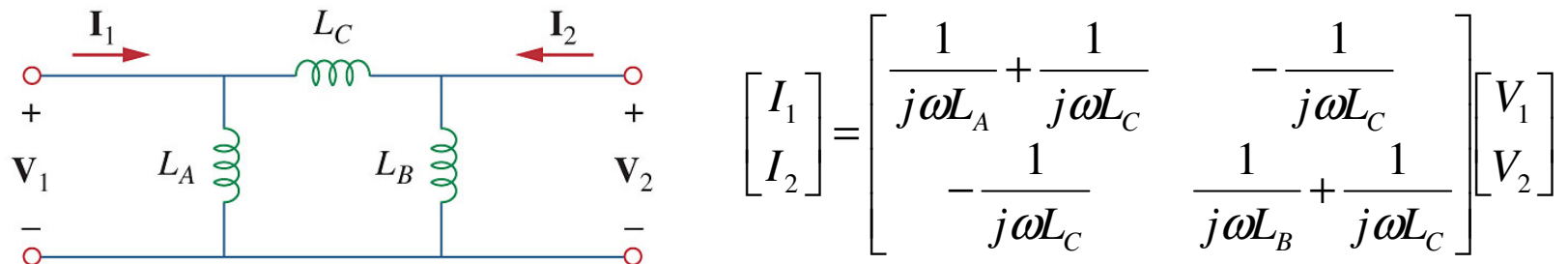
### Equivalent $\pi$ Circuit:

Similarly, for the  $\pi$  network nodal analysis provides:




Equivalent  $\pi$  Network

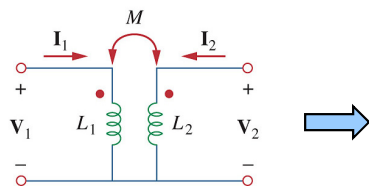By equating terms in admittance matrices, for the  $\pi$  equivalent network we obtain (note if dots are different, replace with  $-M$ ):



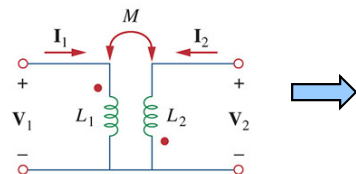
$$L_A = \frac{L_1 L_2 - M^2}{L_2 - M} ; L_B = \frac{L_1 L_2 - M^2}{L_1 - M} ; L_C = \frac{L_1 L_2 - M^2}{M}$$




$$L_A = \frac{L_1 L_2 - M^2}{L_2 + M} ; L_B = \frac{L_1 L_2 - M^2}{L_1 + M} ; L_C = \frac{L_1 L_2 - M^2}{-M}$$

# 13.4 Linear Transformers (10)


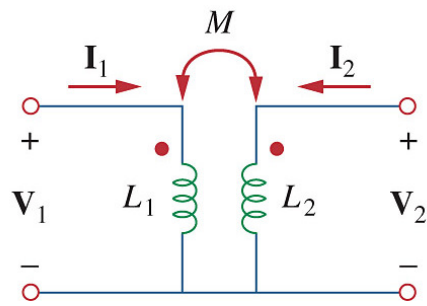
## Equivalent T or $\pi$ Circuits Summary




T Circuit

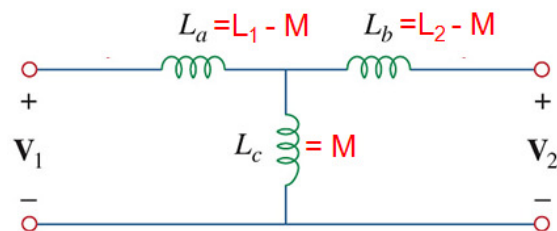


$\pi$  Circuit

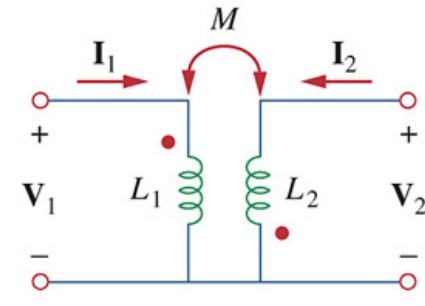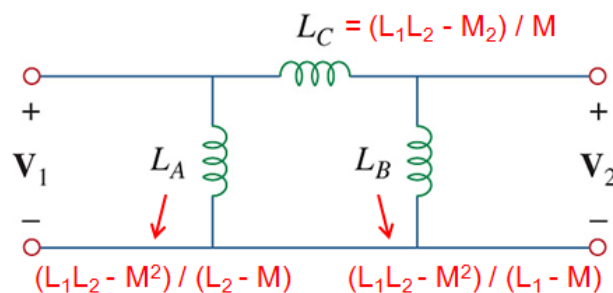

T Circuit

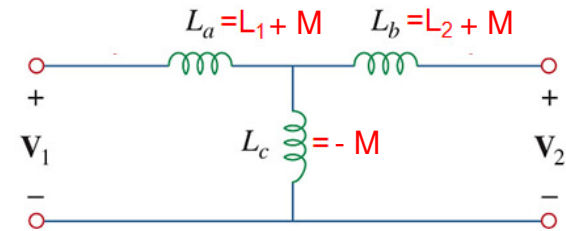

$\pi$  Circuit


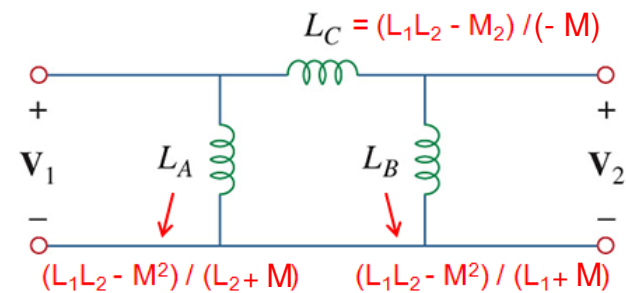




# 13.4 Linear Transformers (11)
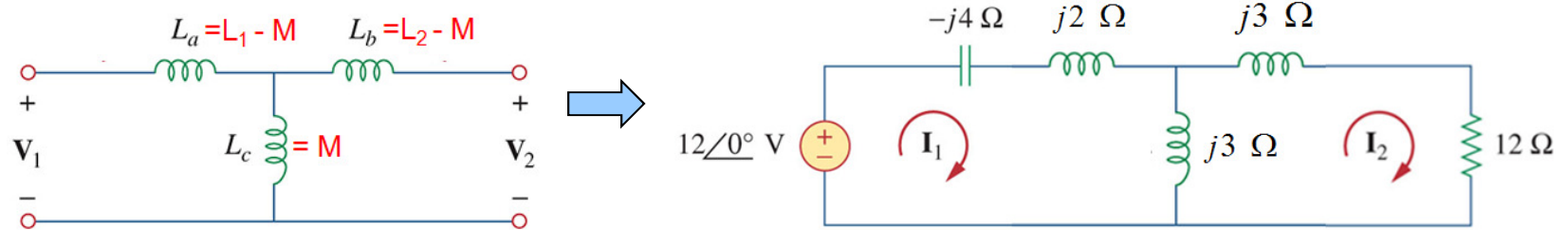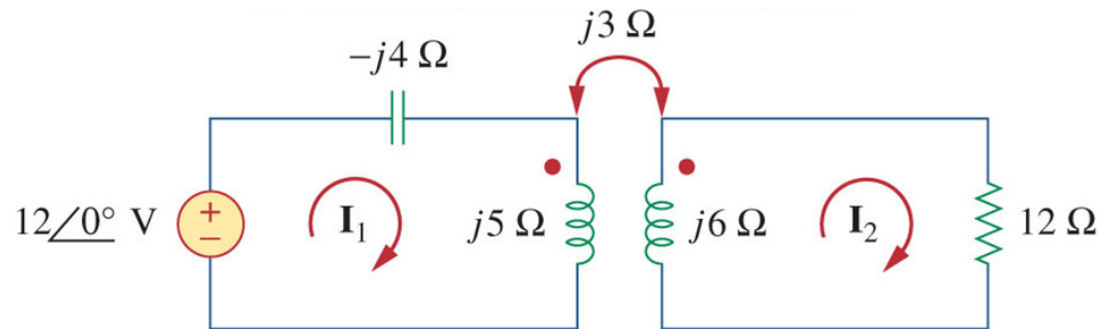
## Practice Problem 13.6

Find  $I_1$  and  $I_2$  using the T equivalent circuit



$$\text{Mesh } I_1: -12\angle 0^\circ - j4I_1 + j2I_1 + j3(I_1 - I_2) = 0 \qquad jI_1 - j3I_2 = 12\angle 0^\circ$$

$$\text{Mesh } I_2: j3(I_2 - I_1) + j3I_2 + 12I_2 = 0 \qquad -j3I_1 + (12 + j6)I_2 = 0$$



# Chapter 13

## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers**
- 13.6 Ideal Autotransformers
- 13.9 Applications
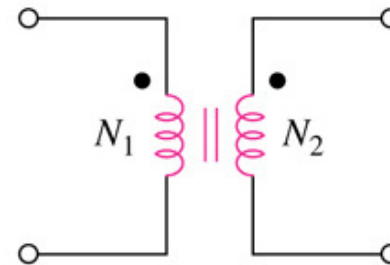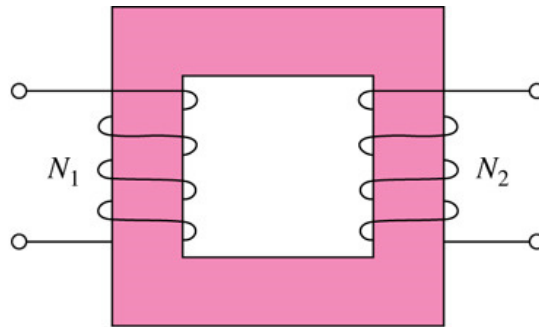
## 13.5 Ideal Transformers (1)

- An ideal transformer has perfect coupling ( $k=1$ ).
- It consists of two or more coils with a large number of turns wound on a common core of high permeability.



- Because of the high permeability of the core, the flux links all the turns of both coils, thereby resulting in a perfect coupling.

## 13.5 Ideal Transformers (2)

“Dot’s the same polarity”

Recall the coupled circuit:

$$V_1 = j\omega L_1 I_1 + j\omega M I_2 \quad (1)$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2 \quad (2)$$


Solving for  $I_1$  in (1):  $I_1 = \frac{V_1 - j\omega M I_2}{j\omega L_1} \quad (3)$

Substituting (3) into (2):  $V_2 = j\omega L_2 I_2 + \frac{M V_1}{L_1} - \frac{j\omega M^2 I_2}{L_1}$

$M = \sqrt{L_1 L_2}$  For perfect coupling ( $k=1$ ):

$$V_2 = j\omega L_2 I_2 + \frac{\sqrt{L_1 L_2} V_1}{L_1} - \frac{j\omega L_1 L_2 I_2}{L_1} = \sqrt{\frac{L_2}{L_1}} V_1 = n V_1$$

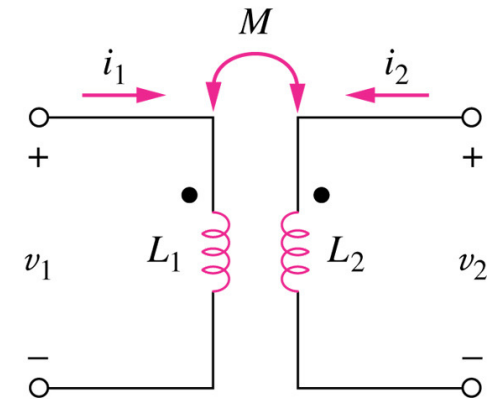Therefore:  $V_2 = n V_1$  where  $n = \sqrt{L_2 / L_1}$  = turns ratio



## 13.5 Ideal Transformers (3)

“Dot’s opposite each other”

Mesh Equations give the following:

$$V_1 = j\omega L_1 I_1 - j\omega M I_2 \quad (1)$$

$$V_2 = -j\omega M I_1 + j\omega L_2 I_2 \quad (2)$$


Solving for  $I_1$  in (1):  $I_1 = \frac{V_1 + j\omega M I_2}{j\omega L_1} \quad (3)$

Substituting (3) into (2):  $V_2 = j\omega L_2 I_2 - \frac{M V_1}{L_1} - \frac{j\omega M^2 I_2}{L_1}$

$M = \sqrt{L_1 L_2}$  For perfect coupling ( $k=1$ ):

$$V_2 = j\omega L_2 I_2 - \frac{\sqrt{L_1 L_2} V_1}{L_1} - \frac{j\omega L_1 L_2 I_2}{L_1} = -\sqrt{\frac{L_2}{L_1}} V_1 = -n V_1$$

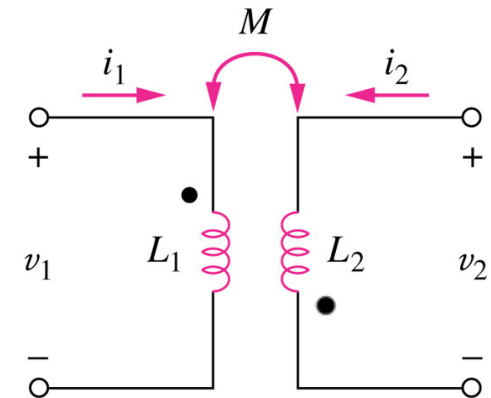Therefore:  $V_2 = -n V_1$  If dot is swapped at output




## 13.5 Ideal Transformers (4)

### Properties

- A transformer is said to be **ideal** if it has the following properties:
  1. Coils have very large reactances ( $L_1, L_2, M \rightarrow \infty$ )
  2. Coupling coefficient is equal to unity ( $k=1$ )
  3. Primary and secondary coils are lossless ( $R_1 = R_2 = 0$ )
- An ideal transformer is a unity-coupled ( $k=1$ ) lossless transformer in which the primary and secondary coils have infinite self-inductances ( $L_1 \& L_2 \rightarrow \infty$ ).
- Iron core transformers are close approximations to ideal transformers and are used in power systems and electronics.
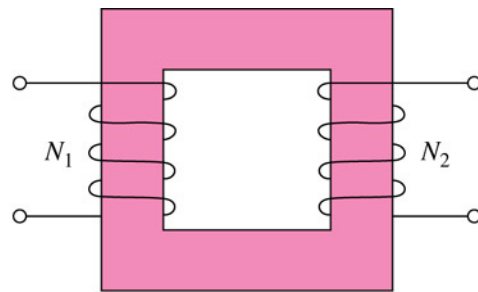
## 13.5 Ideal Transformers (5)

- When a sinusoidal voltage is applied to the primary winding, the same magnetic flux  $\Phi$  goes through both windings.



$$v_1 = N_1 \frac{d\phi}{dt} \quad ; \quad v_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = n = \text{Turns ratio or transformation ratio}$$

- Using the phasor voltages rather than the instantaneous voltages:


$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$

## 13.5 Ideal Transformers (6)

- Power conservation:  $v_1 i_1 = v_2 i_2$
- The energy supplied to the primary must equal the energy absorbed by the secondary, since there are no losses in an ideal transformer.

- In phasor form:
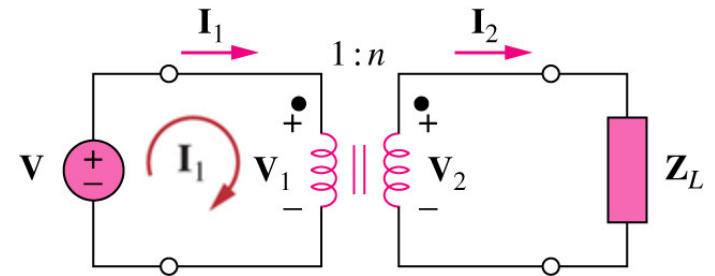
$$\frac{I_1}{I_2} = \frac{V_2}{V_1} = n$$



- $n=1 \rightarrow$  isolation transformer ( $V_2 = V_1$ )
- $n>1 \rightarrow$  step-up transformer ( $V_2 > V_1$ )
- $n<1 \rightarrow$  step-down transformer ( $V_2 < V_1$ )




## 13.5 Ideal Transformers (7)

- Transformer ratings are usually specified as  $V_1 / V_2$
- Power companies often generate at some convenient voltage and use the step-up transformer to increase the voltage so that the power can be transmitted at very high voltage and low current over transmission lines, resulting in significant cost savings. Near residential consumers, step-down transformers are used to bring the voltage down to 120 V.
- It is important to get the proper polarity of the voltages and the direction of the currents for the transformer.
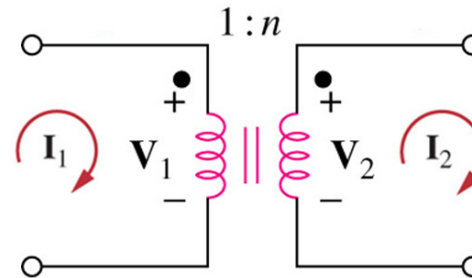
# 13.5 Ideal transformers (8)


V and I relationships (simpler way to remember)

Given this standard  
definition for Voltages  
and currents




**Note:** This definition  
of  $I_2$  differs from the  
text.

Dots "Same"  $\rightarrow$  "+"

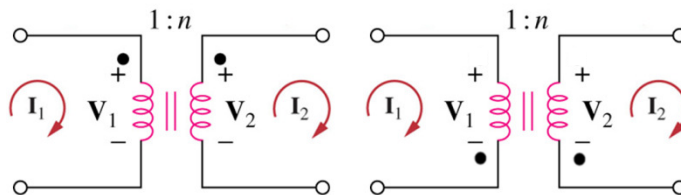

Dots "Different"  $\rightarrow$  "-"

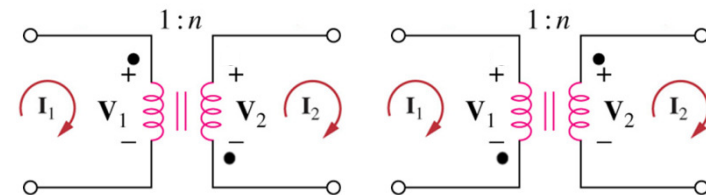

$$V_2 = nV_1$$

$$I_2 = \frac{I_1}{n}$$

$$Z_{in} = \frac{Z_L}{n^2}$$

Reflected  
Impedance  $\rightarrow$

*Note: The larger the turns ratio  
The larger "n"  
The larger " $N_2$ "  
The larger  $V_2$*

**Turns Ratio**

$$n = \frac{N_2}{N_1}$$

$$V_2 = -nV_1$$


$$I_2 = -\frac{I_1}{n}$$

$$Z_{in} = \frac{Z_L}{n^2}$$

## 13.5 Ideal Transformers (9)
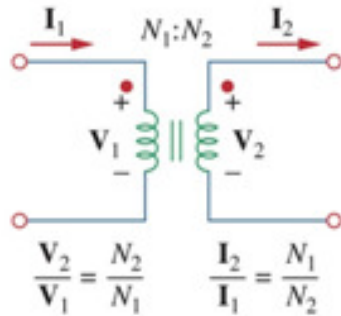
### V and I relationships

- Expressing  $V_1$  in terms of  $V_2$  and  $I_1$  in terms of  $I_2$  or vice versa:



$$V_1 = \frac{V_2}{n} \quad V_2 = nV_1$$

$$I_2 = \frac{I_1}{n} \quad I_1 = nI_2$$

Positive, if Voltage “**same**” polarity at dot

Positive, if current “**different**” polarity at dot

- Complex Power is:

$$S_1 = V_1 I_1^* = \frac{V_2}{n} (nI_2)^* = V_2 I_2^* = S_2$$


Complex Conjugate of  $I_2$

- Complex power supplied to the primary is delivered to the secondary without loss.
- The ideal transformer is **lossless** and absorbs **no power**.

## 13.5 Ideal Transformers (10)
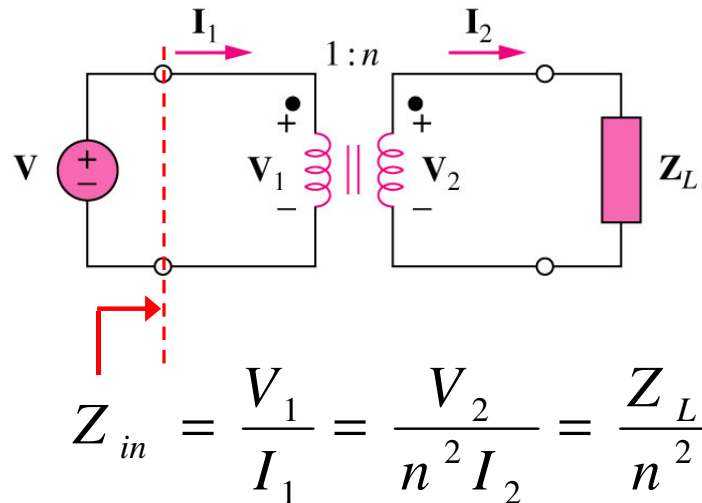
### Reflected impedance

- The input impedance as seen by the source is:




- The input impedance is also called the reflected impedance since it appears as if the load impedance is reflected to the primary side.
- The ability of the transformer to transform a given impedance to another allows impedance matching to ensure maximum power transfer.

## 13.5 Ideal Transformers (11)
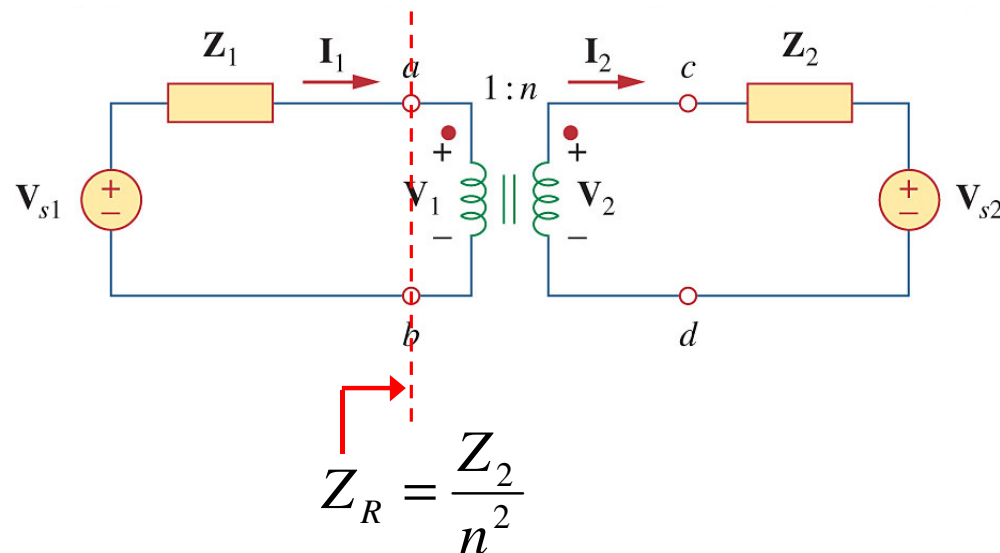
### Equivalent circuit analysis


- In analyzing a circuit containing an ideal transformer, it is common practice to eliminate the transformer by reflecting impedances and sources from one side of the transformer to the other.
- Suppose we want to reflect the secondary side of the circuit to the primary side:



# 13.5 Ideal Transformers (12)
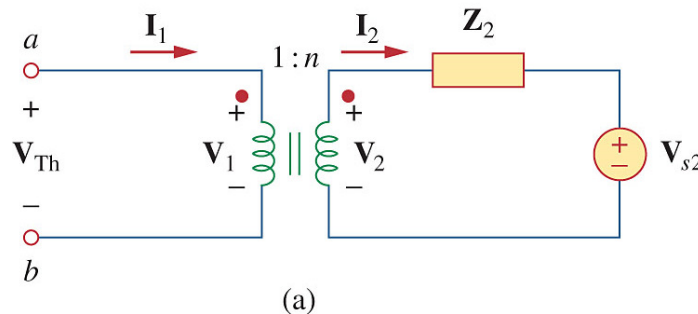
## Equivalent circuit analysis

- We find the Thevenin equivalent of the circuit to the right of a-b:
- Obtaining  $V_{th}$  from “open circuit voltage”:





$$I_1 = 0 = I_2 \quad \text{Since a-b is open}$$

$$V_2 = V_{s2}$$


$$V_{Th} = V_1 = \frac{V_2}{n} = \frac{V_{s2}}{n}$$

- Obtaining  $Z_{Th}$  (remove the voltage source in the secondary and insert a unit source at a-b terminals.)
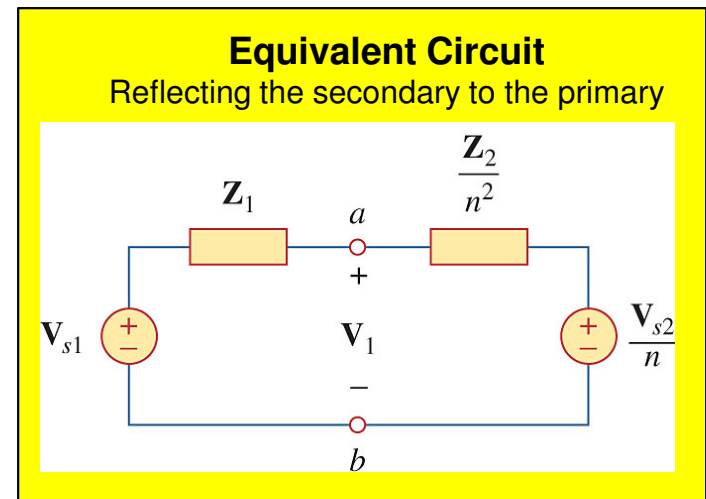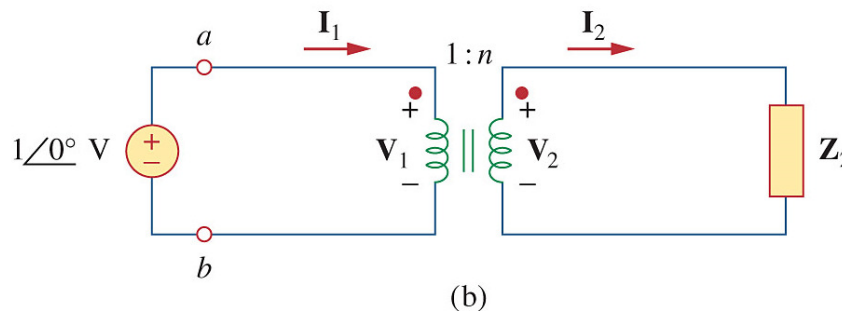
$$Z_{Th} = \frac{V_1}{I_1} = \frac{V_2}{n^2 I_2} = \frac{Z_2}{n^2}$$




## 13.5 Ideal Transformers (13)

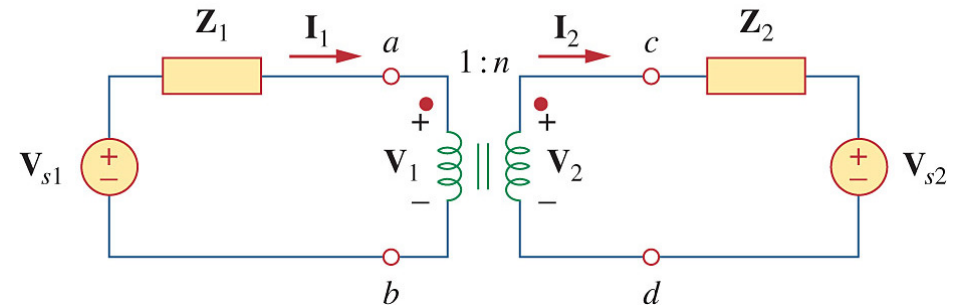


- The general rule for eliminating the transformer and reflecting the secondary circuit to the primary side:

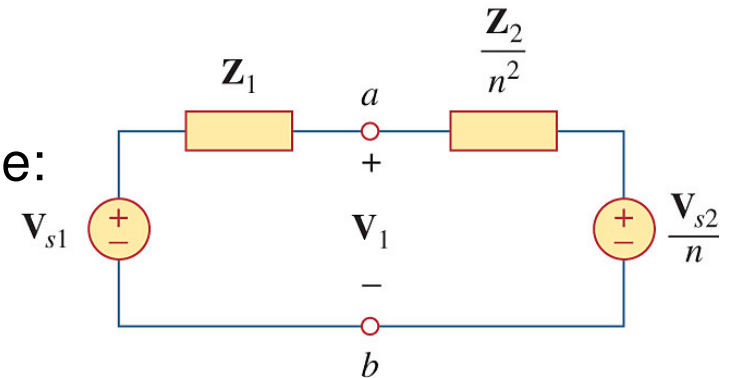- Divide the secondary impedance by  $n^2$
- Divide the secondary voltage by  $n$
- Multiply the secondary current by  $n$



- The general rule for eliminating the transformer and reflecting the secondary circuit to the primary side:

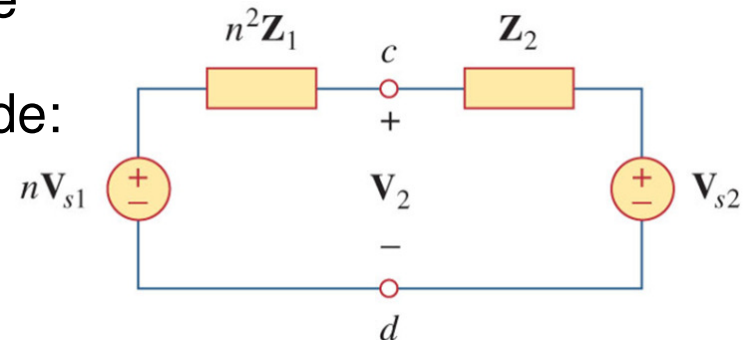
- Multiply the primary impedance by  $n^2$
- Multiply the primary voltage by  $n$
- Divide the primary current by  $n$



## 13.5 Ideal Transformer (14)

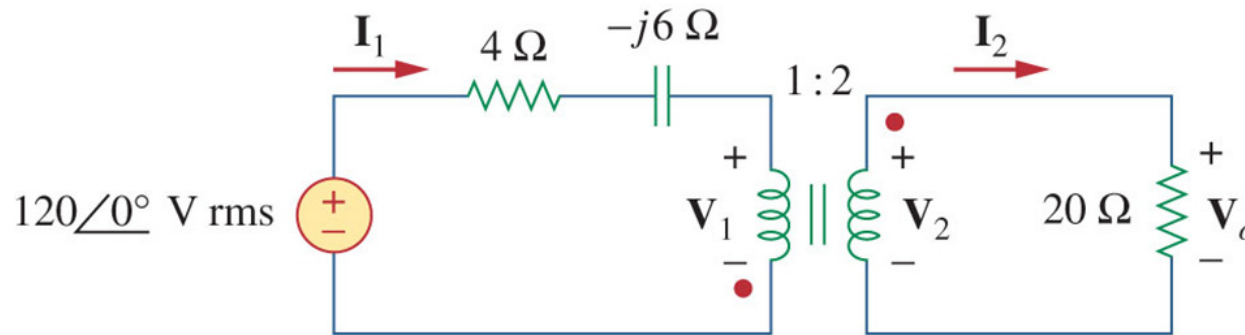
### Example 13.8 (Textbook)

For the ideal transformer, find: (a) the source current  $I_1$ , (b) the output voltage  $V_o$ , and (c) the complex power supplied by the source





## 13.5 Ideal Transformer (14)

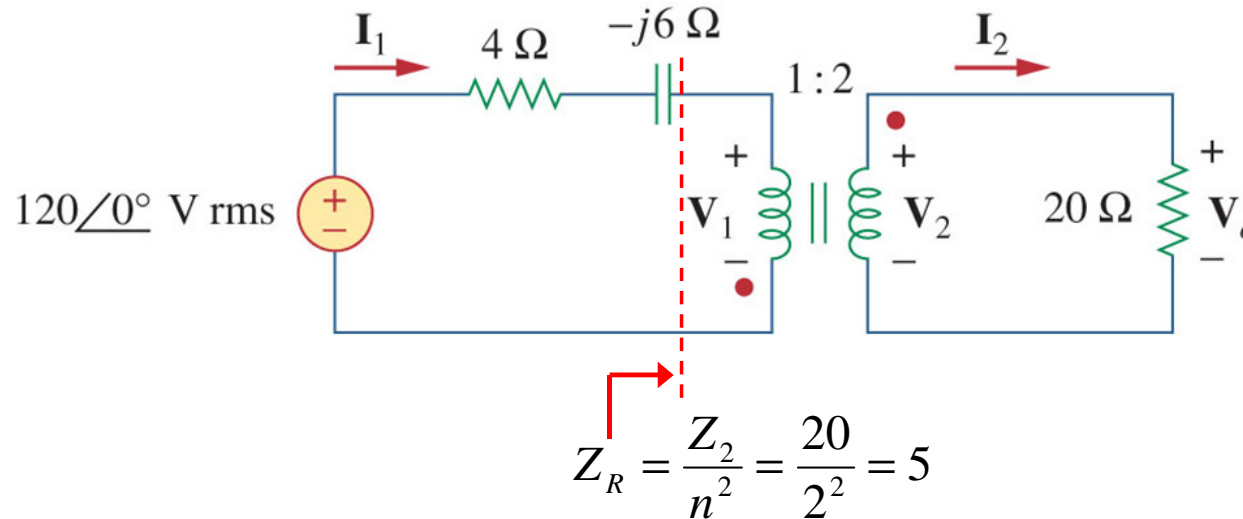

Impedance seen by the Voltage source is:

$$Z_{in} = (4 - j6) + 5 = 9 - j6 = 10.82 \angle -33.69^\circ \Omega$$

Input current  $I_1$  is:

$$I_1 = \frac{V_s}{Z_{in}} = \frac{120 \angle 0^\circ}{10.82 \angle -33.69^\circ} = 11.09 \angle 33.69^\circ \text{ A}$$

$$I_2 = -\frac{I_1}{n} = \frac{-11.09 \angle 33.69^\circ}{2} = 5.55 \angle -146.31^\circ \text{ A}$$

$$V_o = 20I_2 = 20(5.55 \angle -146.31^\circ) = 110.9 \angle -146.31^\circ \text{ V}$$


# Chapter 13

## Magnetically Coupled Circuits


- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers**
- 13.9 Applications**
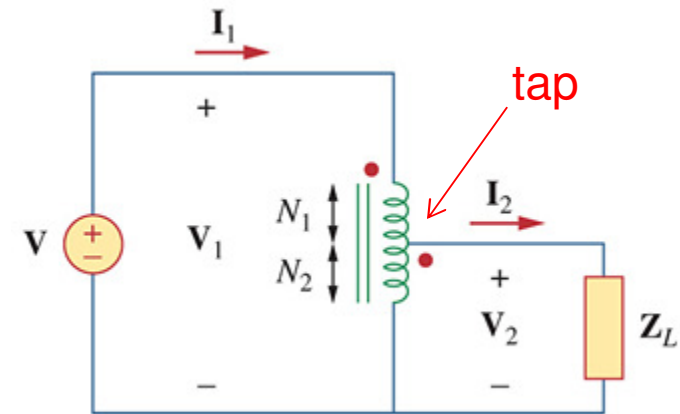
## 13.6 Ideal Auto-Transformers (1)

- An **autotransformer** is a transformer in which both the primary and the secondary are in a single winding
- A connection point called a *tap* separates the primary and secondary.
- The tap is often adjustable to provide a desired turns ratio.
- An adjustable tap provides a variable voltage to the load
- A disadvantage of the autotransformer is it provides *no electrical isolation*




Step Down Auto-Transformer

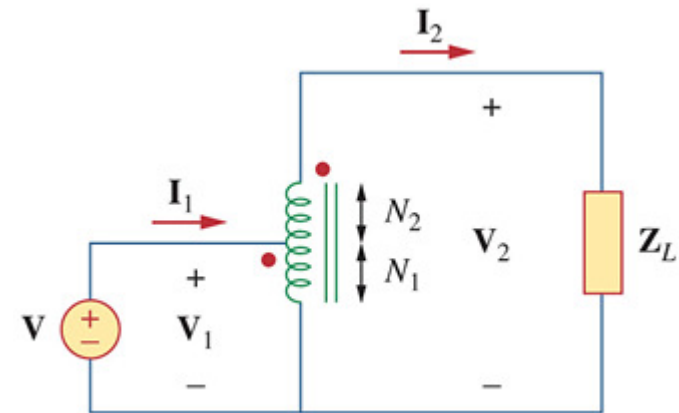

Step Up Auto-Transformer
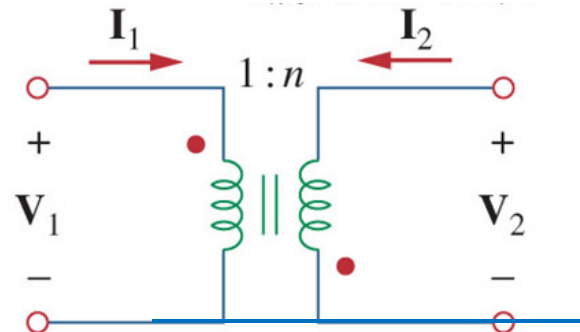
## 13.6 Ideal Auto-Transformers (2)


- In analyzing the autotransformer, consider the following circuit:



From earlier we know the following relationship

$$V_2 = -nV_1$$

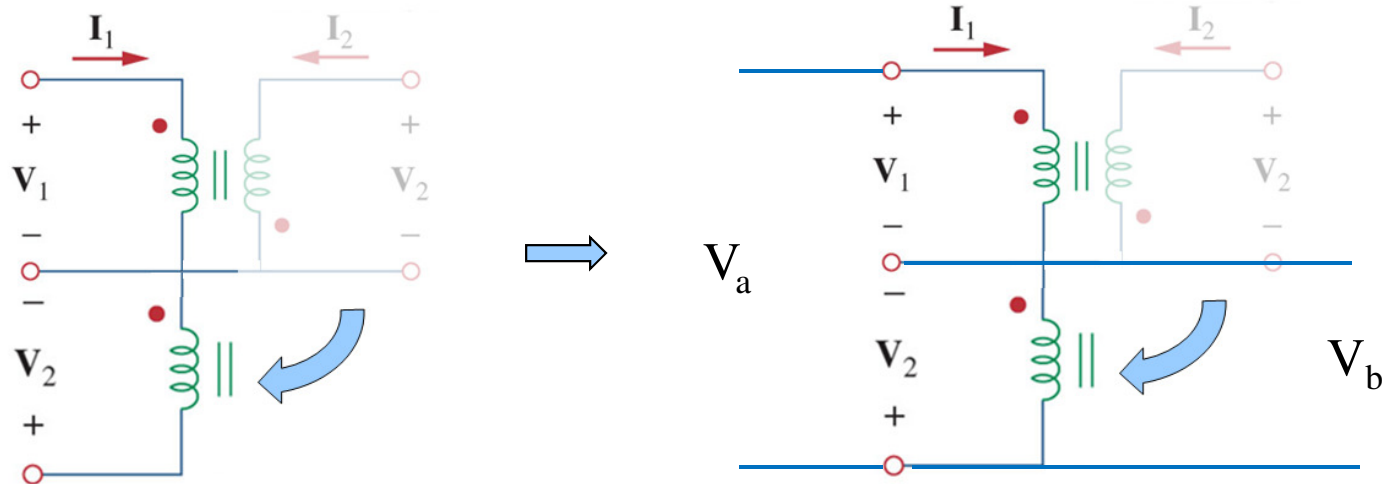- If we flip the secondary side underneath the primary, we can create an autotransformer as shown



## 13.6 Ideal Auto-Transformers (3)


- Analysis of this circuit provides the following results:

Primary Side

$$V_a = V_1 - V_2$$

$$V_a = V_1 + nV_1$$

$$V_a = (1+n)V_1$$

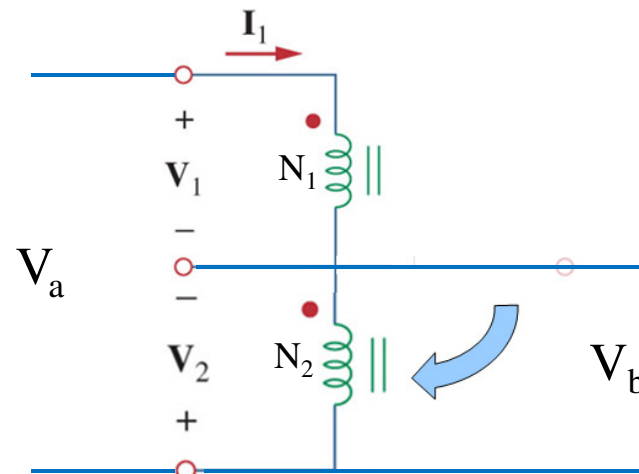

Secondary Side

$$V_b = -V_2 = nV_1$$

Ratio Primary/Secondary


$$\frac{V_a}{V_b} = \frac{1+n}{n} = \frac{N_1 + N_2}{N_2} \quad \Rightarrow$$

Notice, this looks like  
a Voltage Divider !


$$V_b = \left( \frac{N_2}{N_1 + N_2} \right) V_a$$
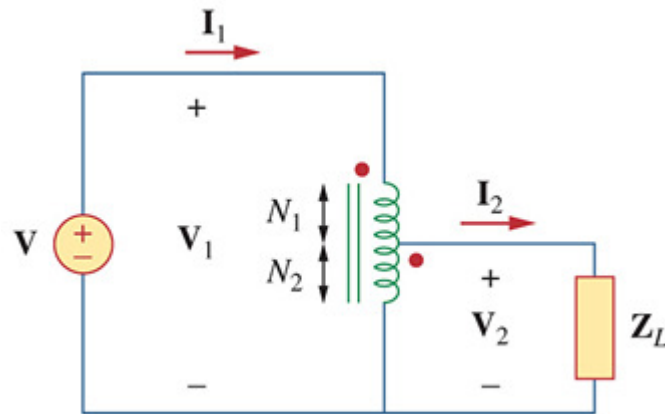
## 13.6 Ideal Auto-Transformers (4)

- The voltage / current relationships for the lossless ideal autotransformer are as follows:



Step Down Auto-Transformer

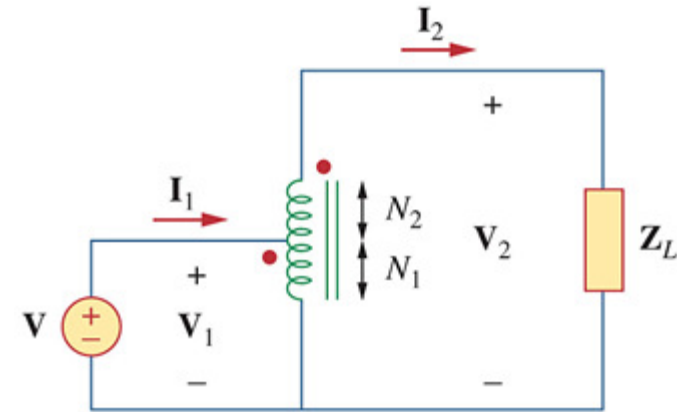

Step Up Auto-Transformer

$$V_2 = \frac{N_2}{N_1 + N_2} V_1$$

Similar to  
Voltage Divider  
equation

$$V_2 = \frac{N_1 + N_2}{N_1} V_1$$

$$I_2 = \frac{N_1 + N_2}{N_2} I_1$$

Inverse Relation

$$I_2 = \frac{N_1}{N_1 + N_2} I_1$$

$$Z_{in} = \left( \frac{N_1 + N_2}{N_2} \right)^2 Z_L$$


Derive from V/I

$$Z_{in} = \left( \frac{N_1}{N_1 + N_2} \right)^2 Z_L$$

## 13.6 Ideal Auto-Transformers (5)



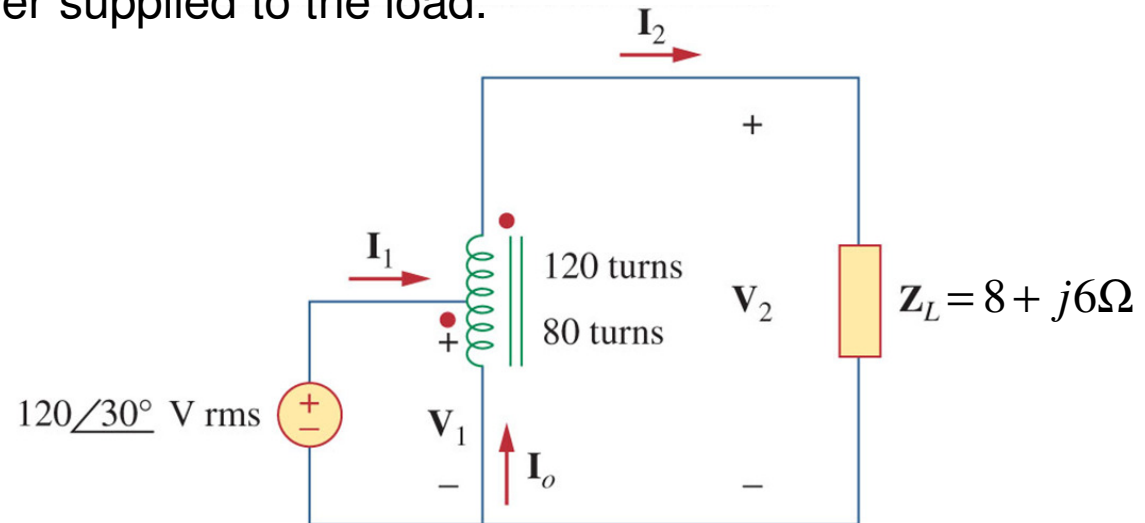
### Example 13.11 (Textbook)

For the autotransformer below, find: (a) the currents  $I_1$ ,  $I_2$ ,  $I_o$ , (b) the complex power supplied to the load.


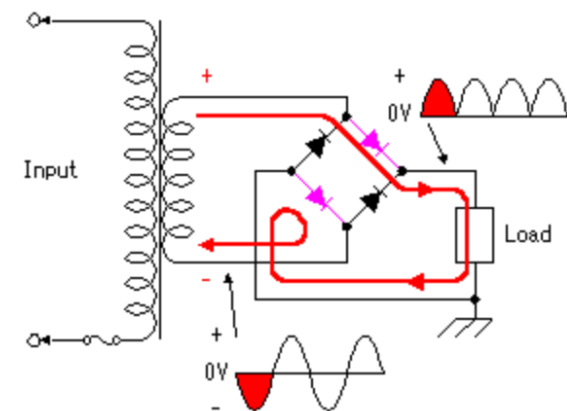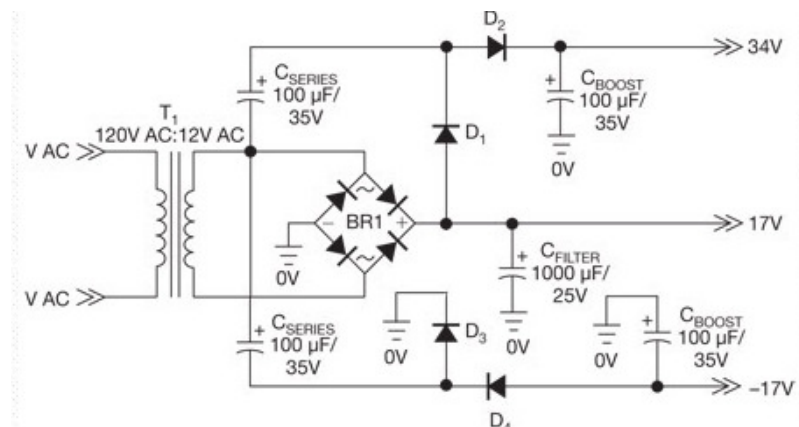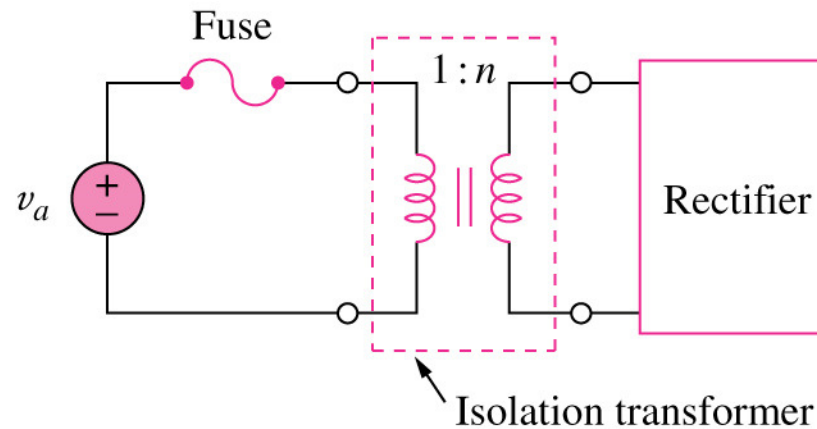
## 13.9 Applications (1)


- Transformer as an Isolation Device to isolate ac supply from a rectifier




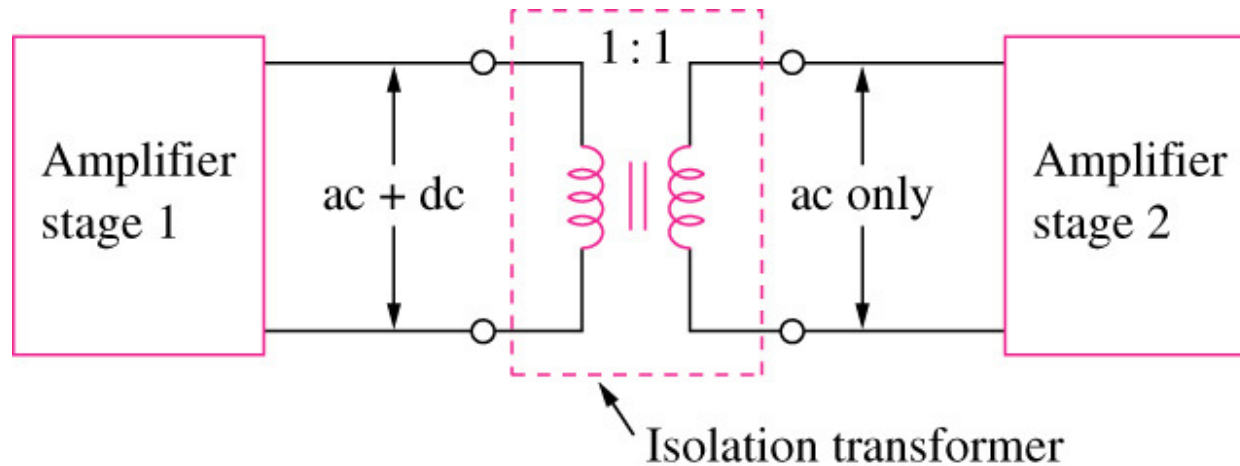
## 13.9 Applications (2)


- Transformer as an Isolation Device to isolate dc between two amplifier stages.



- Biasing is the application of a DC voltage to a transistor amplifier to produce a desired mode of operation.
- Each amplifier stage can be biased separately to operate in a particular mode.


## 13.9 Applications (3)

- Transformer as a Matching Device

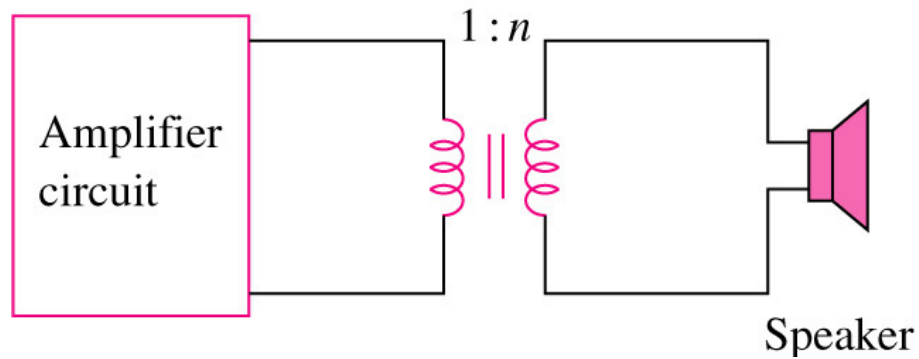

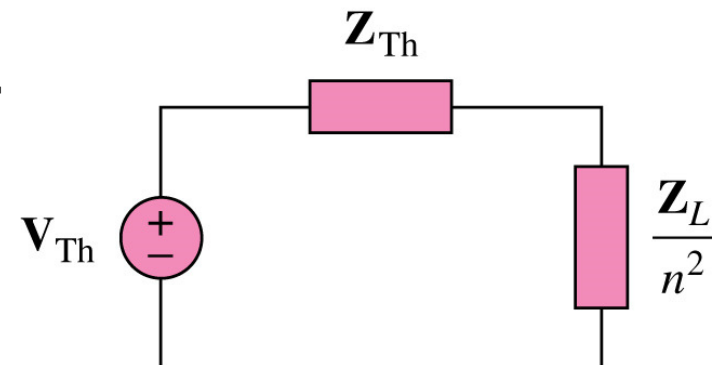**Equivalent circuit**

**Using an ideal transformer to  
match the speaker to the amplifier**



## 13.9 Applications (4)


### Practice Problem 13.16 (Textbook)

Calculate the turns ratio of an ideal transformer required to match a  $400\Omega$  load to a source with internal impedance of  $2.5k\Omega$ . Find the load voltage when the source voltage is  $30V$ .

Ans:  $n = 0.4$ ;  $V_L = 6V$

## 13.9 Applications (5)

- A typical power distribution system

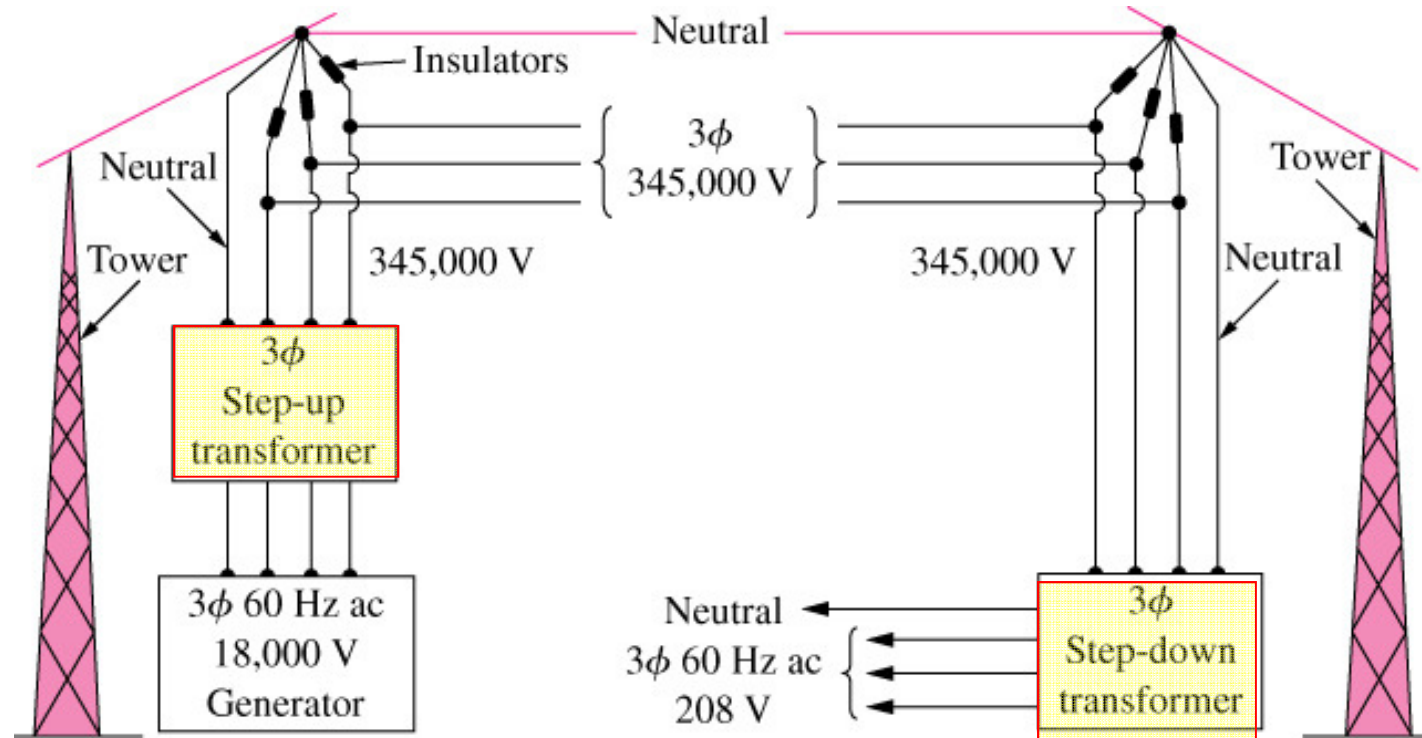

## Homework #3

**Due beginning of class Wednesday Feb 4, 2015**

- 13.30
- 13.35
- 13.42
- 13.50
- 13.53 (modified)
- Autotransformer (See handout)

**Exam over Chapter 13 on Monday Feb 9**

# Chapter 13

## Equation / Analysis Summary

- Series Aiding  $L = L_1 + L_2 + 2M$  / Opposing  $L = L_1 + L_2 - 2M$

- Dot Convention Model

- Coupling coefficient "k"  $M = k\sqrt{L_1 L_2}$

- Linear Transformer


- Input Impedance:

$$Z_{in} = Z_{primary} + \frac{\omega^2 M^2}{Z_{secondary}}$$

- Reflected Impedance:

$$Z_{reflected} = \frac{\omega^2 M^2}{Z_{secondary}}$$

- Equivalent T or  $\pi$  Circuits:

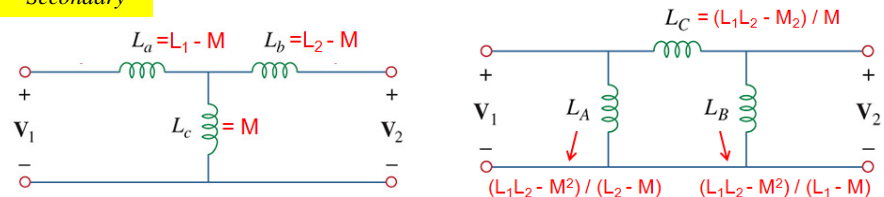

- Ideal Transformer

- $K = 1, L_1, L_2 \rightarrow \infty$

- Lossless ( $S_1 = S_2$ )


- Voltage / Current Relationship:

- Dots "same" = +n, Dots "diff" = -n

- Complex Power:  $S_1 = V_1 I_1^* = V_2 I_2^* = S_2$

- Autotransformer

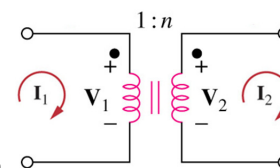- Adjustable "tap"
- No electrical Isolation
- Voltage Divider like relationship




$$V_2 = nV_1$$

$$I_2 = \frac{I_1}{n}$$

$$Z_{in} = \frac{Z_L}{n^2}$$

$$P_{ave} = |I_2|^2 R_L$$

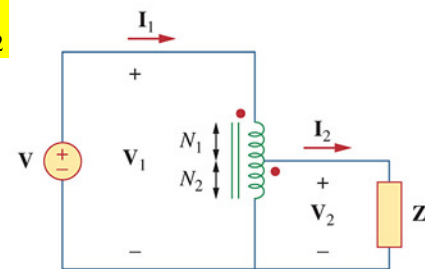

$$V_2 = \frac{N_2}{N_1 + N_2} V_1$$

$$I_2 = \frac{N_1 + N_2}{N_2} I_1$$

# Chapter 13


## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers
- 13.9 Applications
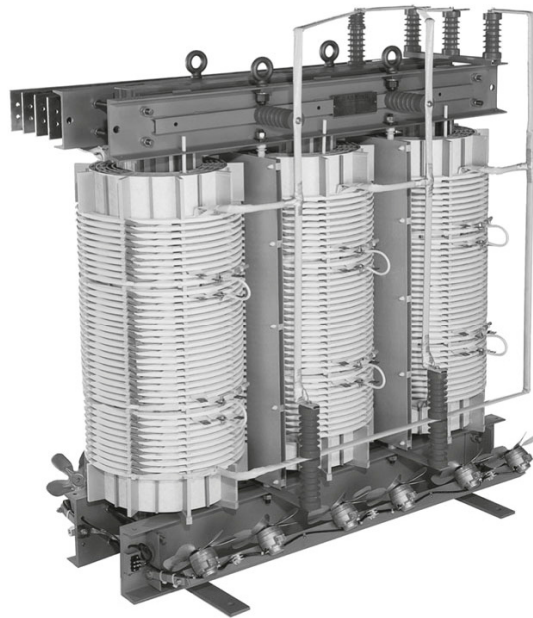
## 13.1 What is a transformer? (1)

- It is an electrical device designed on the basis of the concept of magnetic coupling
- It uses magnetically coupled coils to transfer energy from one circuit to another
- It is the key circuit elements for stepping up or stepping down ac voltages or currents, impedance matching, isolation, etc.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)



(b)

ECE 202 Ch 13


Courtesy of: (a) Electric Service Co., (b) Jensen Transformers


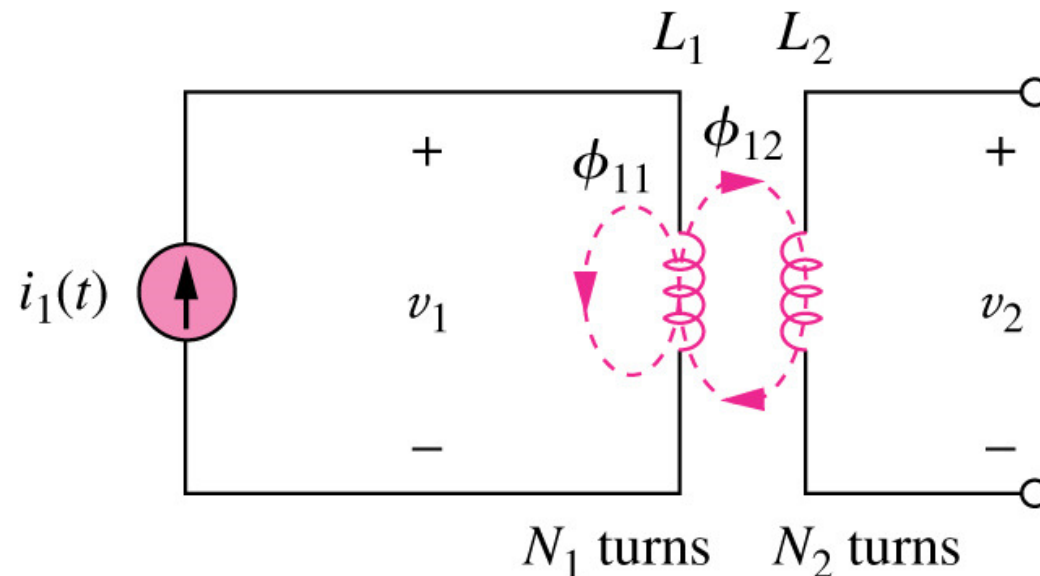
## 13.2 Mutual Inductance (1)


- Mutual Inductance

- When two inductors (or coils) are in close proximity of each other, the magnetic flux caused by current in one coil links with the other coil, thereby inducing voltage in the latter.


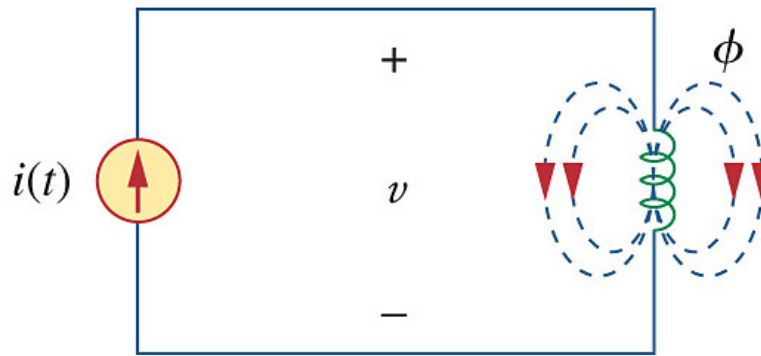
## 13.2 Mutual Inductance (2)

- First consider a single inductor, a coil with  $N$  turns:



When current  $i$  flows through the coil, a magnetic flux  $\Phi$  is produced around it.

- According to Faraday's law, the voltage  $v$  induced in the coil is proportional to the number of turns  $N$  and the time rate of change of magnetic flux  $\Phi$ :

$$v = N \frac{d \phi}{d t}$$

## 13.2 Mutual Inductance (3)

- Voltage induced in the coil given by:
- But the flux  $\Phi$  is produced by current  $i$  so that any change in  $\Phi$  is caused by a change in the current:
- Recall the voltage-current relationship for an inductor:
- The “Self” inductance  $L$  of the inductor is thus given by:
- Self-inductance  $L$  relates the voltage induced in a coil by a time-varying current in the same coil.

$$v = N \frac{d \phi}{d t}$$


$$v = N \frac{d \phi}{d i} \frac{d i}{d t}$$

$$v = L \frac{d i}{d t}$$

$$L = N \frac{d \phi}{d i}$$
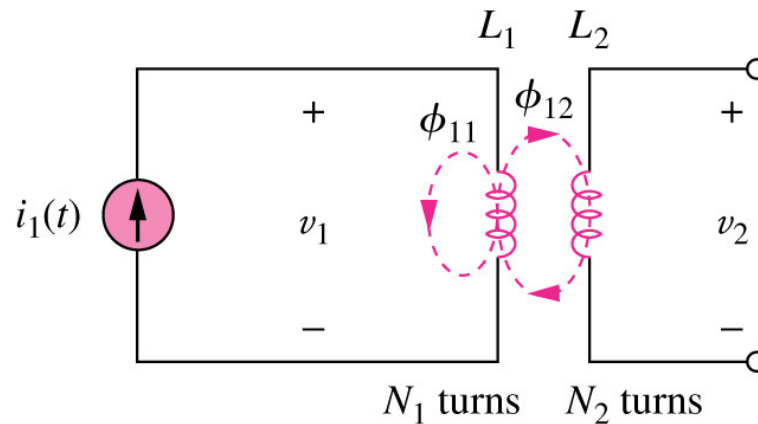
## 13.2 Mutual Inductance (4)

- Now consider two coils with self-inductances  $L_1$  and  $L_2$  that are in close proximity of each other:



Coil 1 has  $N_1$  turns

Coil 2 has  $N_2$  turns.


*Assume coil 2 carries no current.*

- The total magnetic flux  $\Phi_1$  emanating from coil 1 has two components:
  - $\Phi_{11}$  links only coil 1
  - $\Phi_{12}$  links both coils

$$\phi_1 = \phi_{11} + \phi_{12}$$

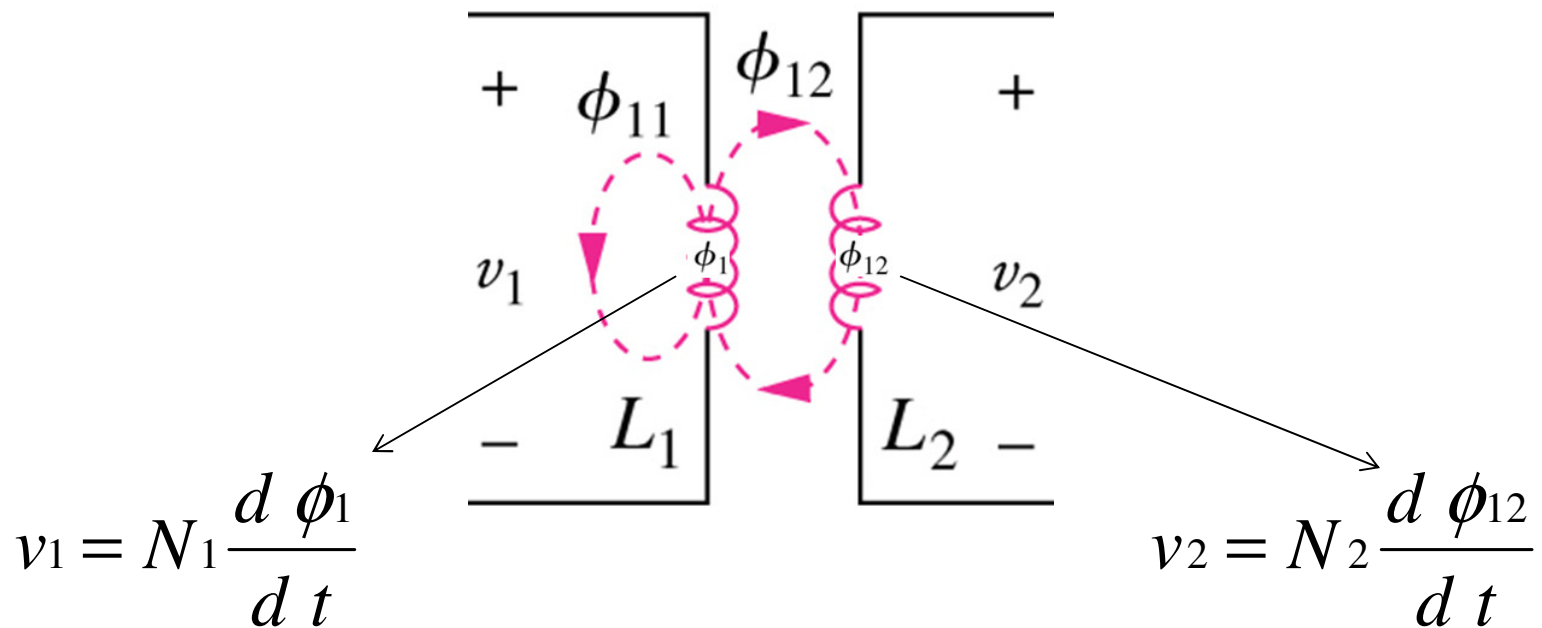
## 13.2 Mutual Inductance (5)

- Although the two coils are physically separated, they are magnetically coupled.
- The voltage induced in each coil is proportional to the flux in each coil.


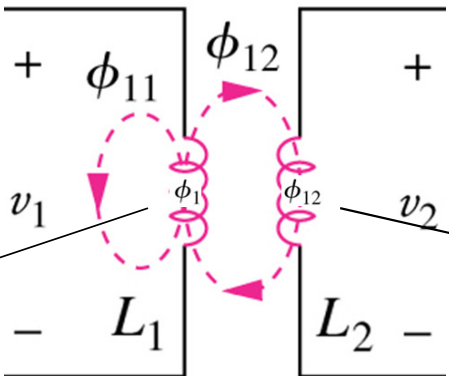
## 13.2 Mutual Inductance (6)

- The voltage equations can be rewritten as follows:



$v_1 = N_1 \frac{d \phi_1}{d t}$

$v_1 = N_1 \frac{d \phi_1}{d i_1} \frac{d i_1}{d t}$

$v_1 = L_1 \frac{d i_1}{d t}$

$v_2 = N_2 \frac{d \phi_{12}}{d t}$

$v_2 = N_2 \frac{d \phi_{12}}{d i_1} \frac{d i_1}{d t}$

$v_2 = M_{21} \frac{d i_1}{d t}$


$v_2$  is the open-circuit mutual voltage (or induced voltage) across coil 2

$L_1$  is the self-inductance of coil 1

$M_{21}$  is the mutual inductance of coil 2 with respect to coil 1
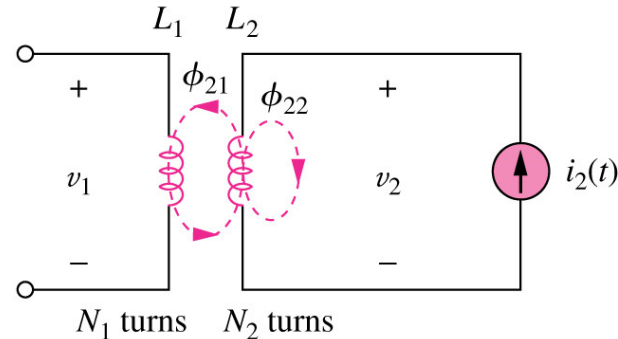
## 13.2 Mutual Inductance (7)

- Suppose now we let current  $i_2$  flow in coil 2 while coil 1 carries no current:



- The magnetic flux  $\Phi_2$  emanating from coil 2 comprises flux  $\Phi_{22}$  that links only coil 2 and flux  $\Phi_{21}$  that links both coils:

$$\phi_2 = \phi_{21} + \phi_{22}$$

- The resulting symmetry is true:

$$v_2 = L_2 \frac{d i_2}{d t} \quad v_1 = M_{12} \frac{d i_2}{d t} \quad M_{12} = N_1 \frac{d \phi_{21}}{d i_2}$$


## 13.2 Mutual Inductance (8)

- $M_{12} = M_{21} = M$  ; The “Mutual inductance” between the coils
- Mutual inductance  $M$  is measured in Henrys (just like inductors)
- Mutual inductance only exists when inductors or coils are in close proximity and the circuits are driven by time-varying sources
- Although mutual inductance  $M$  is always a positive quantity, the mutual voltage  $M \, di/dt$  may be negative or positive, just like the self-induced voltage  $L \, di/dt$  (determined by “Dot” convention)


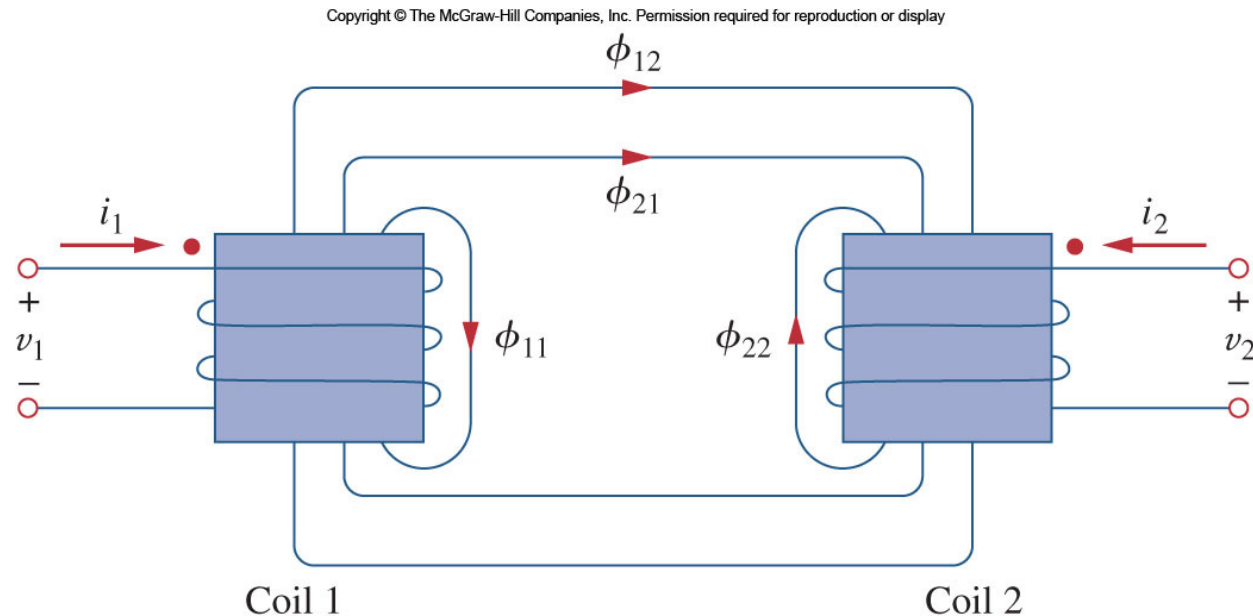
## 13.2 Mutual Inductance (9)

- Self-induced voltage polarity is determined by the reference direction of the current and the reference polarity of the voltage,
- The polarity of the mutual voltage is not as easy to determine (depends on winding direction of the coils).
- We use the dot convention to determine





## 13.2 Mutual Inductance (10)

### “Dot Convention”

- If a current **enters** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **positive** at the dotted terminal of the second coil.



Voltage is  
“Negative”

Enters the  
“Un-Dotted” side

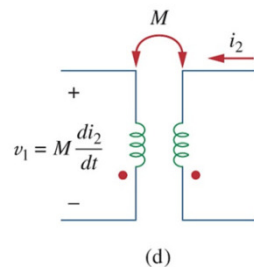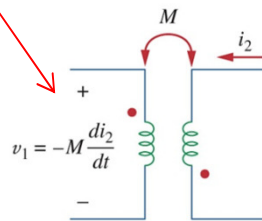

Enters the “Dot”

Voltage is  
“Positive”

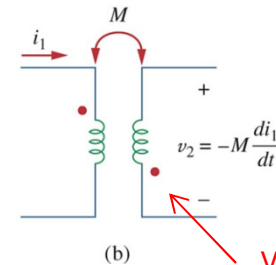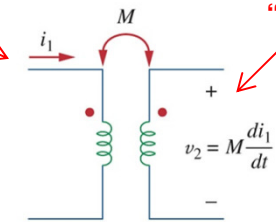

Voltage is  
“Positive”  
At “Dotted”  
Terminal


- Alternatively, if a current **leaves** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **negative** at the dotted terminal of the second coil.

## 13.2 Mutual Inductance (11)
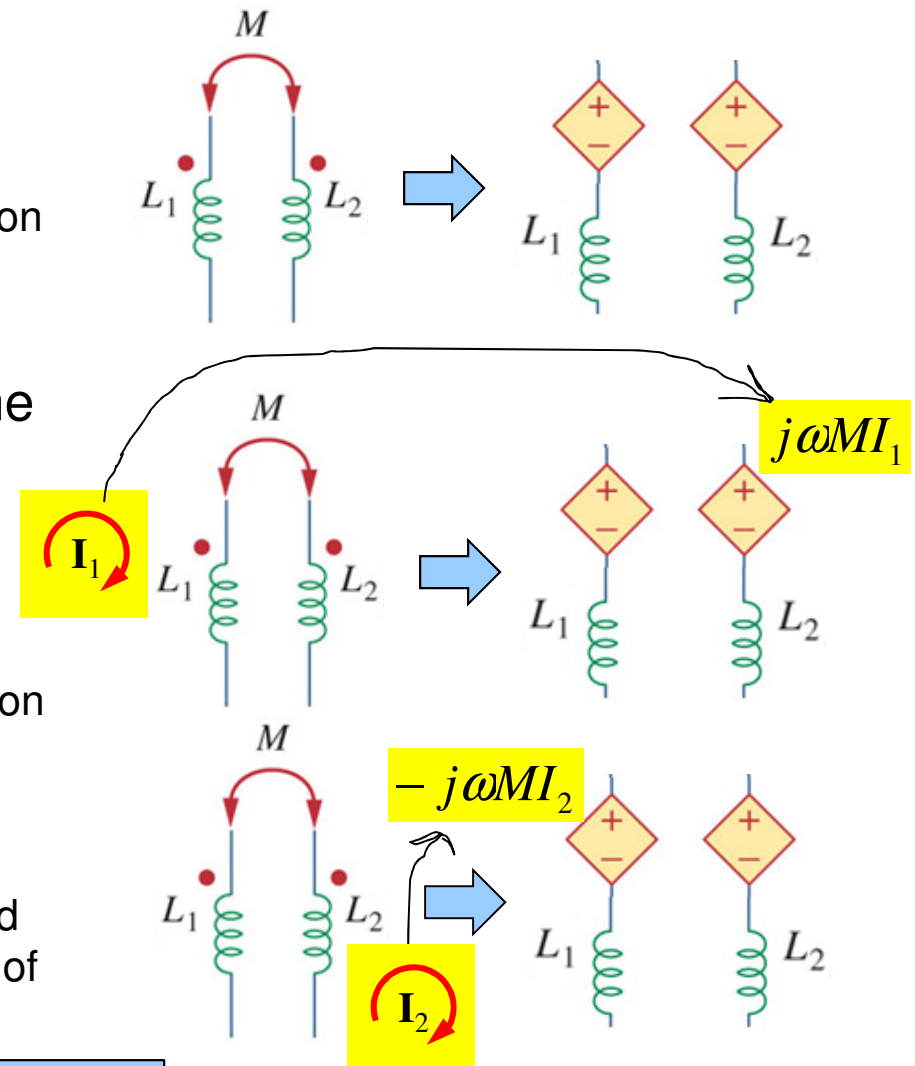
### “The Model” (Phasor domain)

- Replace the “Dot” with a controlled voltage source.
  - Place on same side as the Dot
  - Positive terminal in same direction as the Dot
- Now look at the current entering each dot to determine the magnitude of the voltage source
  - If the current enters the dotted terminal, it will induce a positive voltage in the controlled source on the opposite terminal of  $j\omega M(I)$
  - If the current enters the “un-dotted” terminal, it will induce a negative voltage in the controlled source on the opposite terminal of  $-j\omega M(I)$


Note: This method differs slightly from the text



KEY CONCEPT !

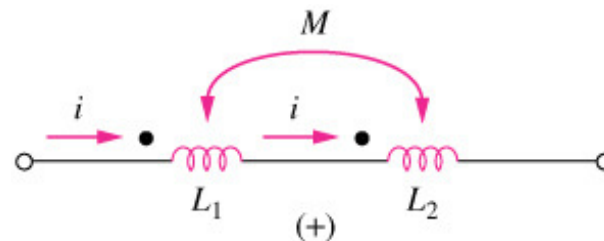
## 13.2 Mutual Inductance (12)

Dot convention for coils in series; the sign indicates the polarity of the mutual voltage



$$L = L_1 + L_2 + 2M$$

(series - aiding connection)

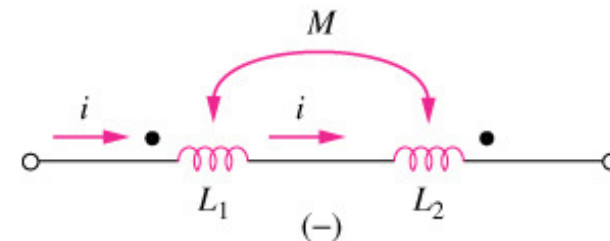

$$L = L_1 + L_2 - 2M$$

(series - opposing connection)


We can show this using the model!

## 13.2 Mutual Inductance (13)

### Example Problem 13.1
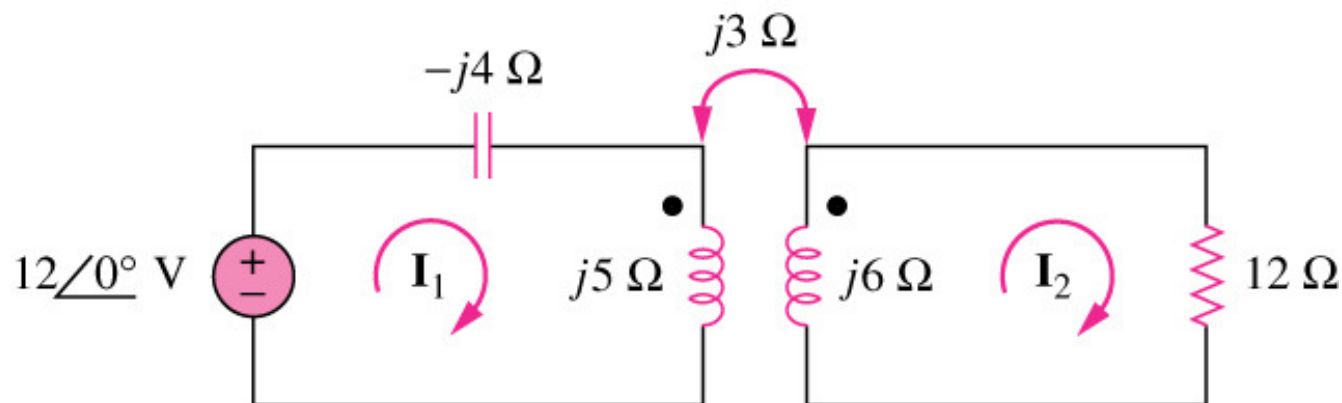
#### Example 13.1 (Textbook)

Calculate the phasor currents  $I_1$  and  $I_2$  in the circuit shown below.





Ans:  $I_1 = 13.02 \angle -49.40^\circ \text{ A}$ ;  $I_2 = 2.91 \angle 14.04^\circ \text{ A}$

## 13.2 Mutual Inductance (14)

### Example Problem 13.1

First, replace with the model:

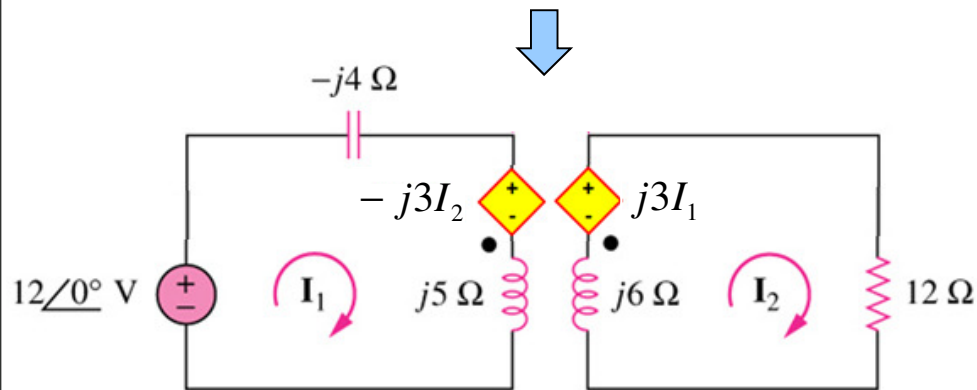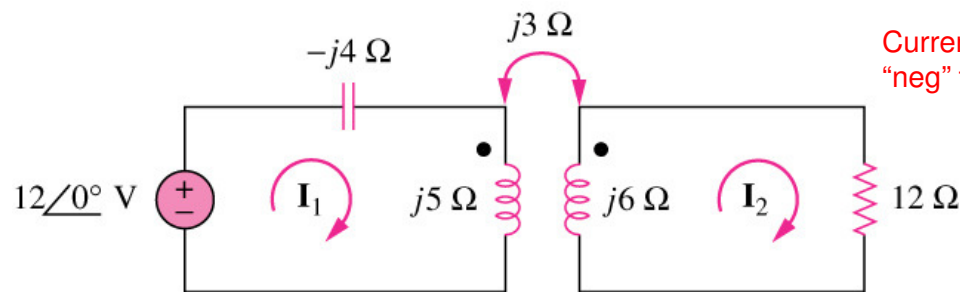

Then, solve Loop Equations:

**Loop  $I_1$**

Current enters "neg" terminal

Current enters "+" terminal but value is  $-j3I_2$

$$-12 - j4I_1 + (-j3I_2) + j5I_1 = 0$$

$$jI_1 - j3I_2 = 12$$

**Loop  $I_2$**

Current enters "neg" terminal

$$j6I_2 - j3I_1 + 12I_2 = 0$$

$$-j3I_1 + (12 + j6)I_2 = 0$$

NOTE:

$I_1$  goes "into" the dot  $\rightarrow$  Induced voltage on the second coil is "Positive"

$I_2$  goes "into" the un-dotted side  $\rightarrow$  Induced voltage on the first coil is "Negative"

**Pay Attention to Sign Conventions !**

## 13.2 Mutual Inductance (15)

### Example Problem 13.1

Lastly, solve 2 equations, 2 unknowns (expected you know this):

$$\text{Loop } I_1 \longrightarrow jI_1 - j3I_2 = 12 \longrightarrow jI_1 = 12 + j3I_2 \Rightarrow I_1 = 3I_2 - j12$$

$$\text{Loop } I_2 \longrightarrow -j3I_1 + (12 + j6)I_2 = 0 \quad I_1 = 3(2.824 + j0.706) - j12$$

$$\text{Substitution: } -3(12 + j3I_2) + (12 + j6)I_2 = 0$$

$$\div \text{ by } 3 \quad -12 - j3I_2 + (4 + j2)I_2 = 0$$

$$\text{Collect Terms: } (4 - j)I_2 = 12$$

$$\text{Solve for } I_2 \quad I_2 = \frac{12}{(4 - j)} = 2.824 + j0.706 = 2.91 \angle 14.04^\circ \text{ A}$$

Find  $I_1$  (Substitute back to Eq1)



$$I_1 = 8.471 + j2.118 - j12$$

$$I_1 = 8.471 - j9.882 = 13.02 \angle -49.40^\circ \text{ A}$$

Think about where we could have made mistakes!

- Applying the model incorrectly (wrong sign convention)
- Incorrect Phasor notation ( Understand:  $j\omega M \leftrightarrow j3$  ;  $j\omega L \leftrightarrow j5$  ;  $1/j\omega C \leftrightarrow -j4$  )
- Incorrect sign convention for loop equations
  - Current entering negative terminal of a voltage source
- Understanding of complex numbers!
  - Familiarity with your calculators handling of complex numbers
  - Converting from rectangular to polar

Review / Understand these concepts to avoid these mistakes


## 13.2 Recommended Viewing:

- Watch these videos illustrating solving mutual inductance problems:
  - <http://www.youtube.com/watch?v=tD35a-uzd34>
  - <http://www.youtube.com/watch?v=hzU4XKQYTWw>
  - <http://www.youtube.com/watch?v=OqSvesTtnUo>
- Uses the model described previously to solve mutual inductance problems.



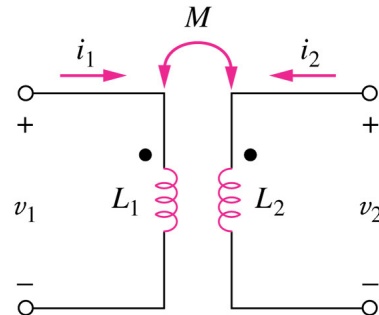
## 13.3 Energy in a Coupled Circuit (1)

- The instantaneous energy  $w$  stored in the circuit is:




$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

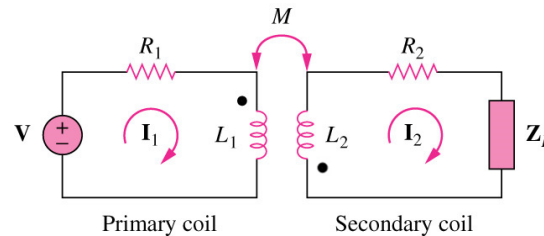- If **both** currents enter (or **both** leave) the dotted terminal the mutual term is (positive):



$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

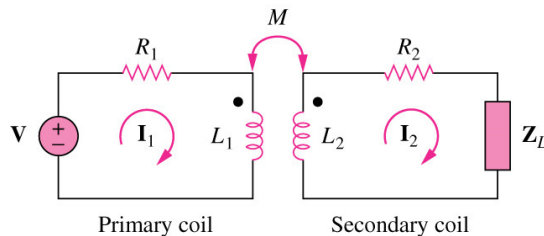- Otherwise the mutual term is (negative):



$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$

## 13.3 Energy in a Coupled Circuit (2)


- The coupling coefficient,  $k$ , is a measure of the magnetic coupling between two coils;  $0 \leq k \leq 1$ .

$$M = k\sqrt{L_1 L_2}$$


$K = 1$  coils perfectly coupled

$K < 0.5$  coils loosely coupled

$K > 0.5$  coils tightly coupled

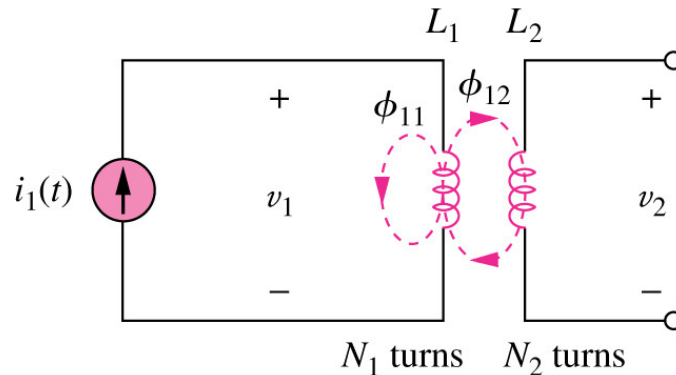
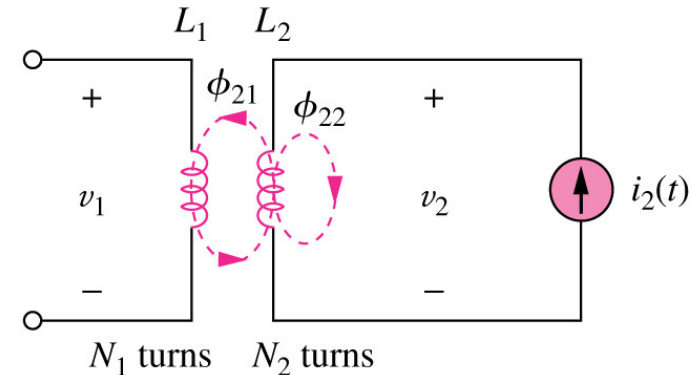
$$K = \frac{\phi_{12}}{\phi_{11} + \phi_{12}}$$




$$K = \frac{\phi_{21}}{\phi_{21} + \phi_{22}}$$

## 13.3 Energy in a Coupled Circuit (3)

### Example 13.3
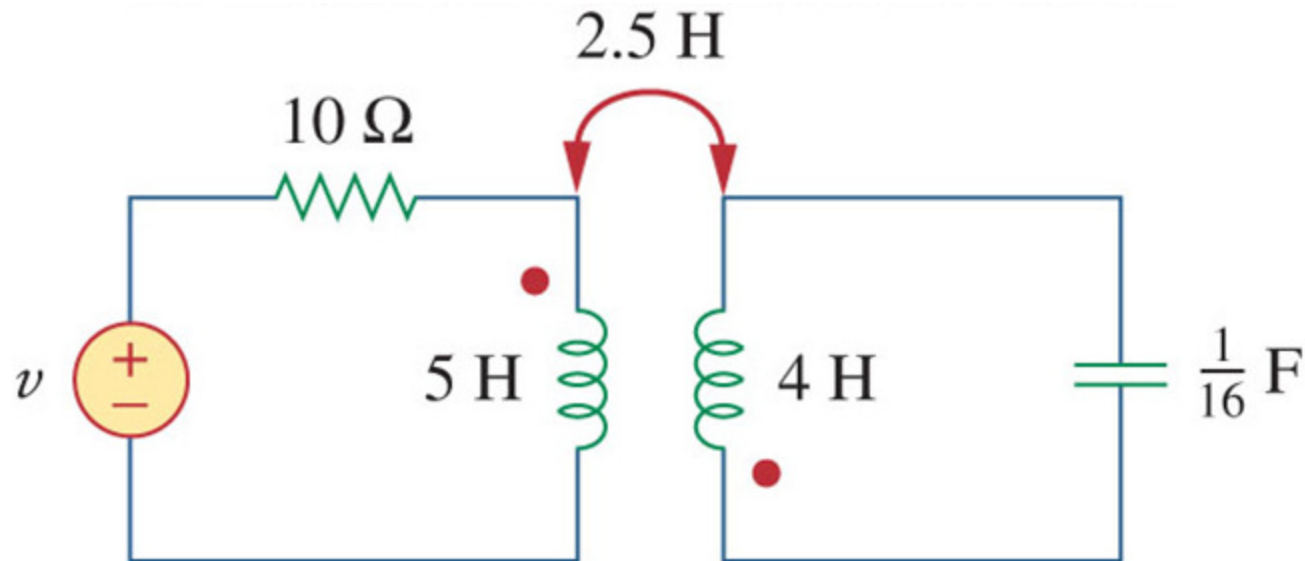
### Example 13.3 (Textbook)


Consider the circuit below. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time  $t = 1\text{ s}$  if  $v = 60\cos(4t + 30^\circ)\text{ V}$ .



Ans:  $k=0.56$ ;  $w(1)=20.73\text{ J}$

# 13.3 Energy in a Coupled Circuit (4)

## Example 13.3

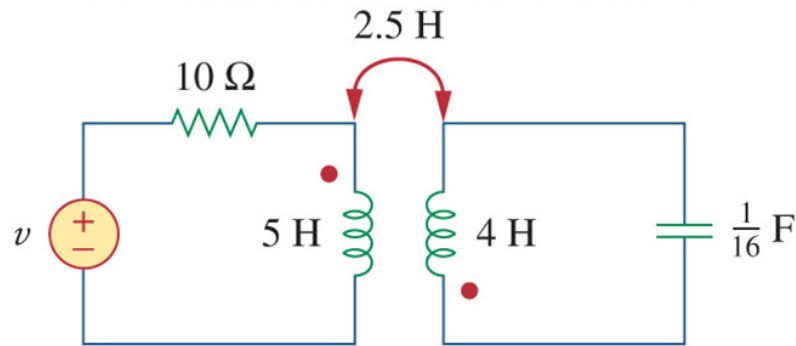


To find k, use the relation between  $L_1$ ,  $L_2$ , and  $M$ :

$$L_1 = 5 ; L_2 = 4 ; M = 2.5$$


$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2.5}{\sqrt{(5)(4)}} = 0.56$$

Apply the "Model"

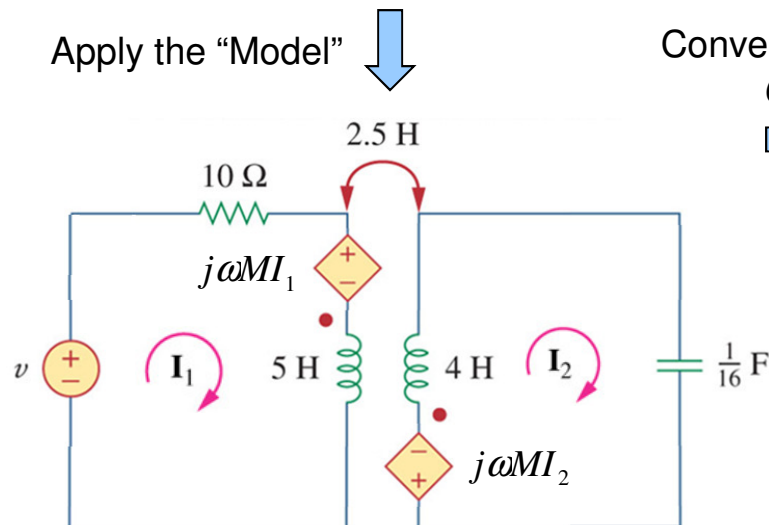

Convert to Phasor

$$\omega = 4$$

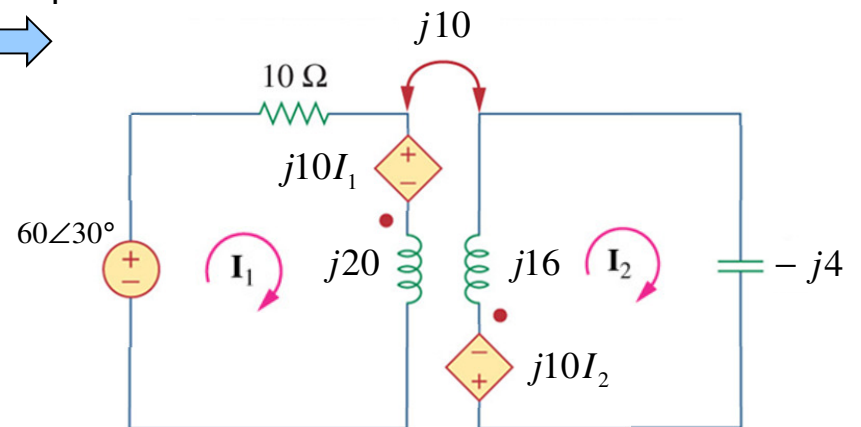

Solve Mesh equations for  $I_1$  and  $I_2$

## 13.3 Energy in a Coupled Circuit (5)

### Example 13.3

From Mesh analysis:

$$I_1 = 3.905 \angle -19.4^\circ \text{ A}$$

$$I_2 = 3.254 \angle 160.6^\circ \text{ A}$$

At  $t = 1$ , the value of  $\omega t = (4)(1) = 4$  radians =  $229.2^\circ$

To find the energy at  $t = 1$ :

$$i_1 = 3.905 \cos(\omega t - 19.4^\circ)$$

$$i_2 = 3.254 \cos(\omega t + 160.6^\circ)$$

$$i_1 = 3.905 \cos(229.2^\circ - 19.4^\circ) = -3.389$$

$$i_2 = 3.254 \cos(229.2^\circ + 160.6^\circ) = 2.824$$

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

Positive since current (as defined) enters **both** dots

$$w = \frac{1}{2} (5)(-3.389)^2 + \frac{1}{2} (4)(2.824)^2 + 2.5(-3.389)(2.824) = 20.73 \text{ J}$$

# Homework #2

Due in class Monday, January 26, 2015

- 13.1
- 13.7
- 13.9
- 13.24


# Chapter 13

## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers**
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers
- 13.9 Applications
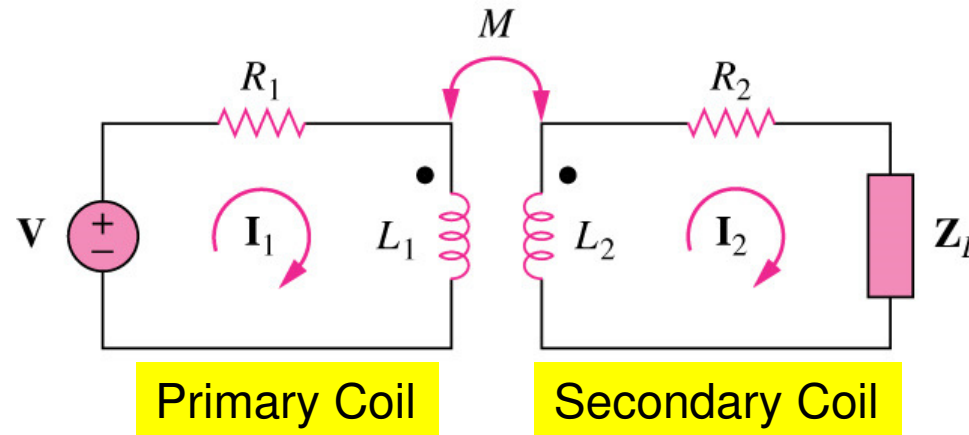
## 13.4 Linear Transformers (1)

- A transformer is generally a four-terminal device comprising two (or more) magnetically coupled coils. Below is a “simple” model:




- The coil connected to the voltage source is called the **primary winding**.
- The coil connected to the load is called the **secondary winding**.
- Resistances  $R_1$  and  $R_2$  are included to account for the losses in the coils.
- A transformer is said to be linear if the coils are wound on a magnetically linear material for which the permeability is constant.
  - Air, plastic, Bakelite, wood, etc.
  - Most materials are magnetically linear.



## 13.4 Linear Transformers (2)
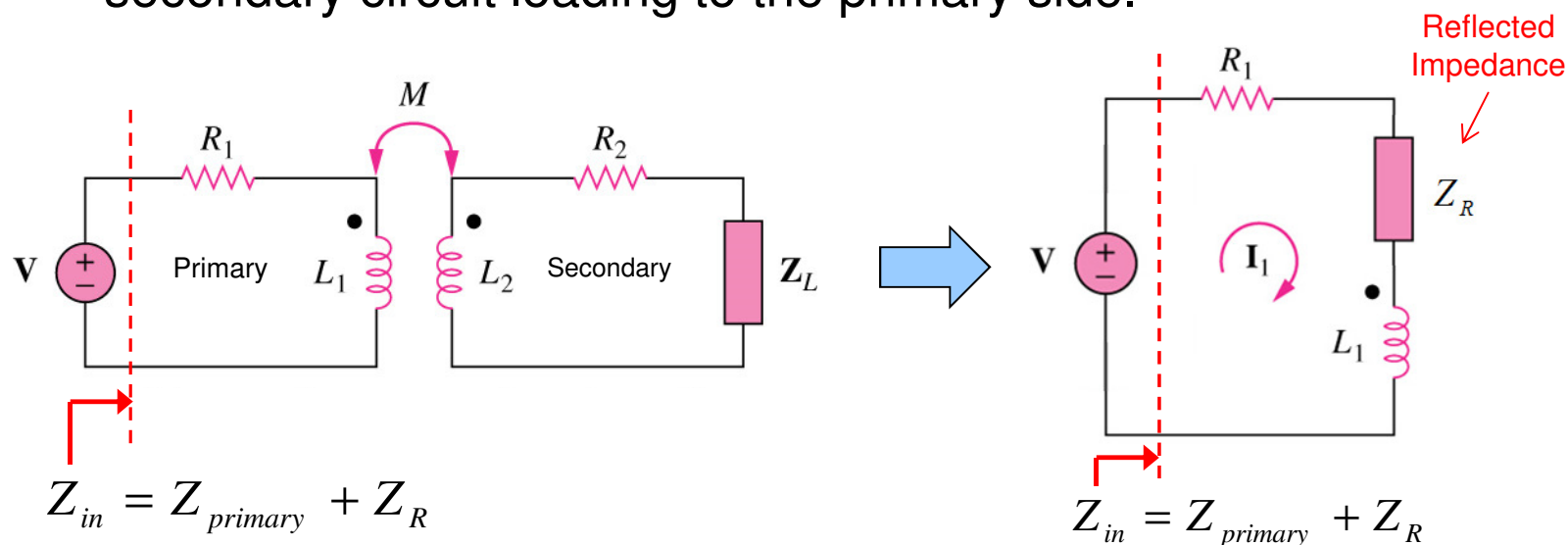
### Reflected Impedance


- Often we are interested in the input impedance  $Z_{in}$  seen by the source.
  - For example, may want to match  $Z_{in}$  to the source impedance for maximum power transfer!
- To simplify our analysis we can break  $Z_{in}$  up into:
  - $Z_{primary}$  -- The impedance of the “primary” circuit ( $Z_{primary} = R_1 + j\omega L_1$ )
  - $Z_R$  -- The “reflected” impedance back to the “primary”.
- The “reflected” impedance  $Z_R$  is the contribution of the secondary circuit loading to the primary side.



# 13.4 Linear Transformers (2)

## Reflected Impedance

To obtain the input impedance  $Z_{in}$  as seen from the source:

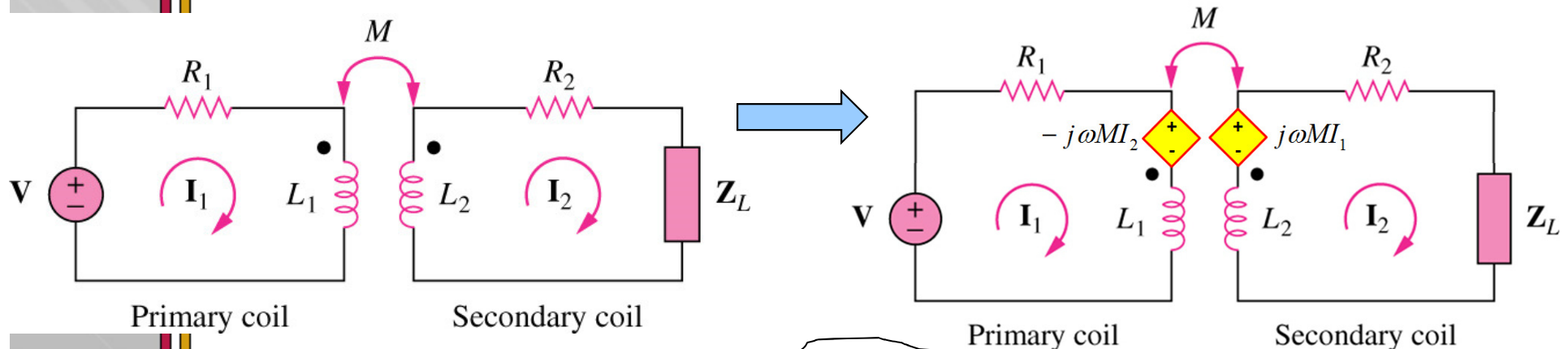

Mesh 1:  $V = (R_1 + j\omega L_1)I_1 - j\omega MI_2$  → Current enters positive terminal so it is + ( $-j\omega MI_2$ )

Mesh 2:  $0 = -j\omega MI_1 + (R_2 + j\omega L_2 + Z_L)I_2$  → Current enters negative terminal so it is - ( $j\omega MI_2$ )

From Mesh 2:

$$I_2 = \frac{j\omega M}{R_2 + j\omega L_2 + Z_L} I_1$$

Substituting into Mesh 1 gives:

$$V = (R_1 + j\omega L_1)I_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} I_1$$

**Reflected Impedance**


$$Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

$$V = Z_{primary} I_1 + Z_{reflected} I_1$$

# 13.4 Linear Transformers (3)

## Reflected Impedance (Another way of looking at it !)

Obtain input impedance  $Z_{in}$  as seen from the source:

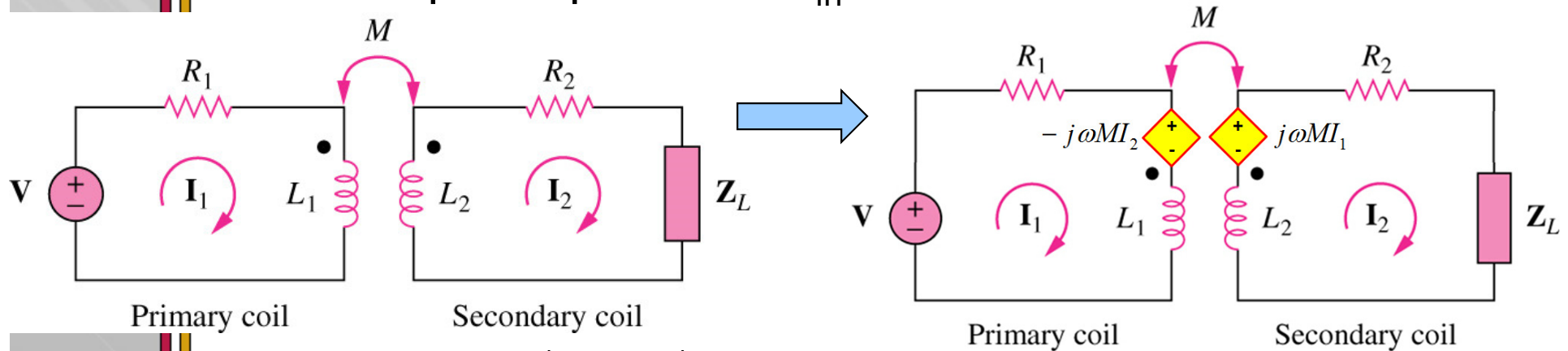

Mesh 1:  $V = (Z_{primary})I_1 - j\omega MI_2$

Mesh 2:  $0 = -j\omega MI_1 + (Z_{Secondary})I_2$

$Z_{Secondary}$  = the total series impedance in the secondary loop

From Mesh 2:

$$I_2 = \frac{j\omega M}{Z_{Secondary}} I_1$$

**Reflected Impedance**

$$Z_R = \frac{\omega^2 M^2}{Z_{Secondary}}$$

Substituting into Mesh 1 gives:


$$V = Z_{primary} I_1 + \frac{\omega^2 M^2}{Z_{Secondary}} I_1$$

$$V = Z_{primary} I_1 + Z_{reflected} I_1$$

## 13.4 Linear Transformers (4)
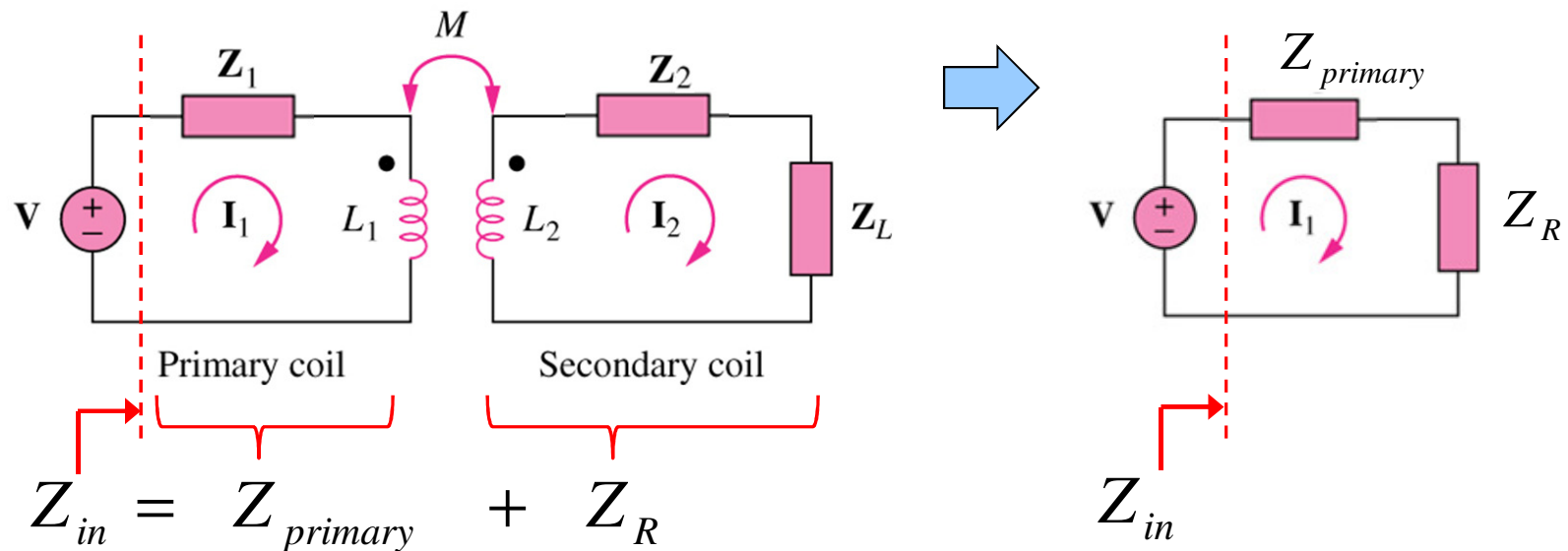
### Reflected Impedance

- The input impedance can be broken into two parts as follows:



- Series Impedance in Primary Coil:  $Z_{primary} = Z_1 + j\omega L_1$
- Series Impedance in Secondary Coil:  $Z_{secondary} = Z_2 + Z_L + j\omega L_2$
- Input Impedance:  $Z_{in} = Z_{primary} + \frac{\omega^2 M^2}{Z_{secondary}}$


*Note:  $Z_{in}$  will be the same if the dot on  $L_2$  is switched*

## 13.4 Linear Transformers (5)

### Example 13.4
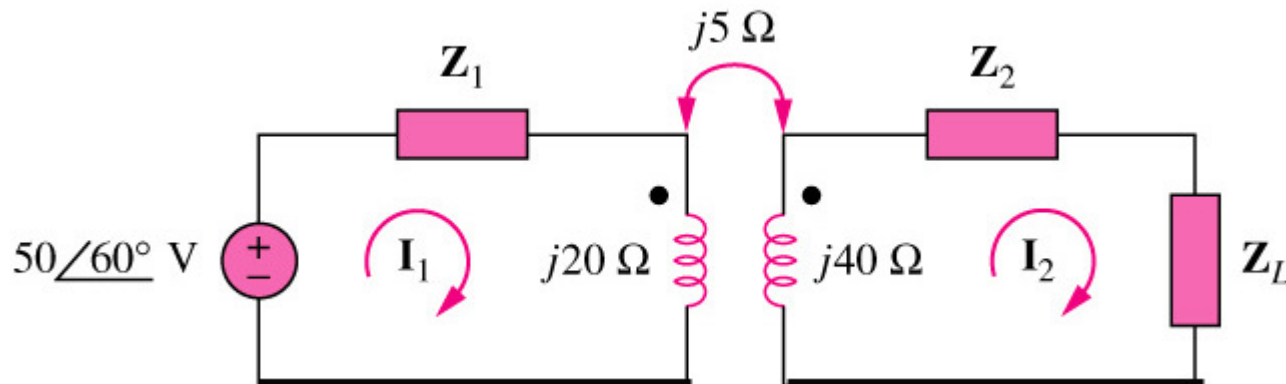
### Example 13.4 (textbook)


In the circuit below, calculate the input impedance and current  $I_1$ . Take  $Z_1=60-j100\Omega$ ,  $Z_2=30+j40\Omega$ , and  $Z_L=80+j60\Omega$ .



Ans:  $Z_{in} = 100.14\angle -53.1^\circ\Omega$ ;  $I_1 = 0.5\angle 113.1^\circ\text{A}$

## 13.4 Linear Transformers (5)

### Example 13.4

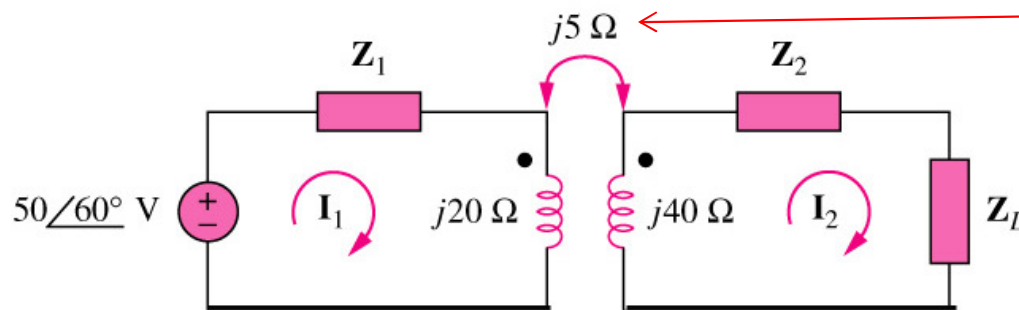

**Note:**

$$j\omega M = j5$$

$$\omega M = 5$$

$$(\omega M)^2 = 25$$

- The series impedance in the primary coil:

$$Z_{primary} = (60 - j100) + j20 = 60 - j80$$

- The series impedance in the secondary coil:

$$Z_{secondary} = (30 + j40) + (80 + j60) + j40 = 110 + j140$$

- Input Impedance given by:


$$Z_{in} = Z_{primary} + \frac{\omega^2 M^2}{Z_{Secondary}} = (60 - 80j) + \frac{25}{(110 + j140)} = 60.09 - j80.11$$

- Current  $I_1$  given by: 
$$I_1 = \frac{V_s}{Z_{in}} = \frac{50 \angle 60^\circ}{60.09 - j80.11} = \frac{50 \angle 60^\circ}{100.14 \angle -53.1^\circ}$$


## 13.4 Linear Transformers (6)
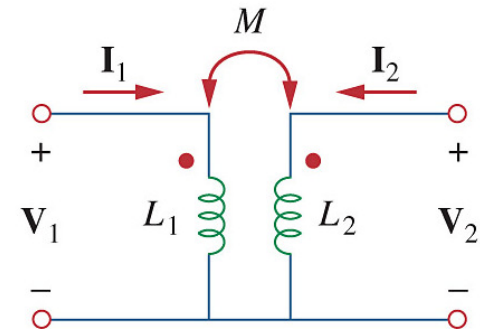
### Equivalent T and $\pi$ Circuits:


- It is sometimes convenient to replace a magnetically couple circuit with an equivalent circuit with no magnetic coupling.
- We can replace the linear transformer with an equivalent T or  $\pi$  circuit that has no mutual inductance.



T Circuit

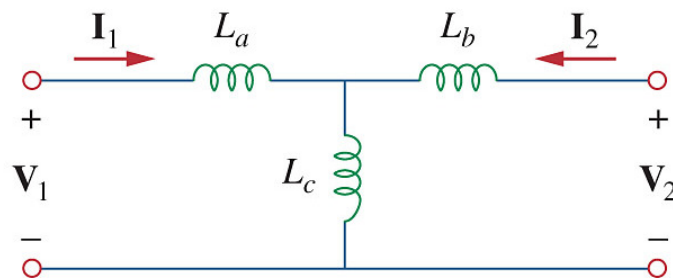


$\pi$  Circuit

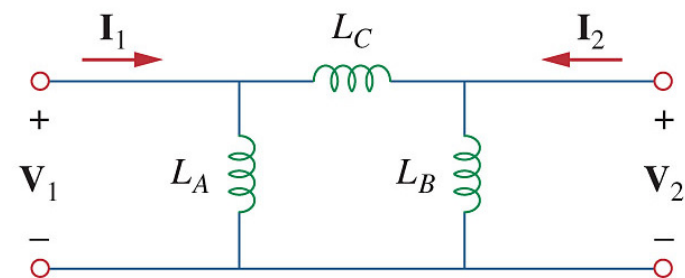

## 13.4 Linear Transformers (7)

### Equivalent T Circuit:


#### Linear Transformer Circuit

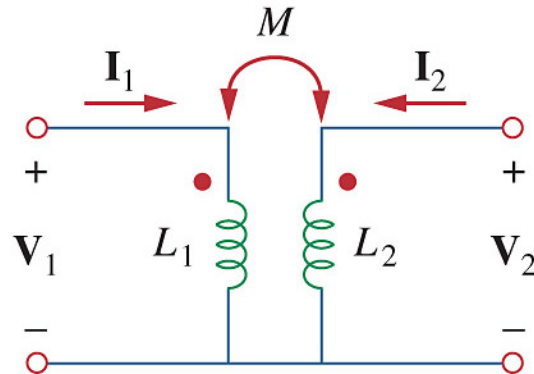

Mesh Analysis of this transformer circuit results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

#### Equivalent T Network

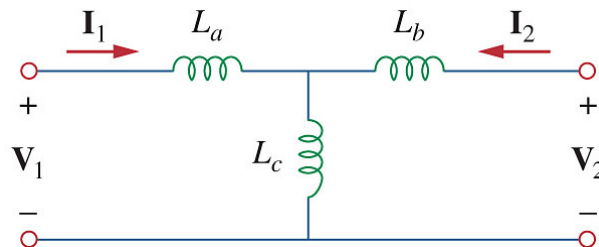

Mesh Analysis of the equivalent T network results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Equating the terms gives the following relationships:


$$L_a = L_1 - M \quad L_b = L_2 - M \quad L_c = M$$



## 13.4 Linear Transformers (8)

### Equivalent T Circuits (Swapped Dots):


Linear Transformer Circuit

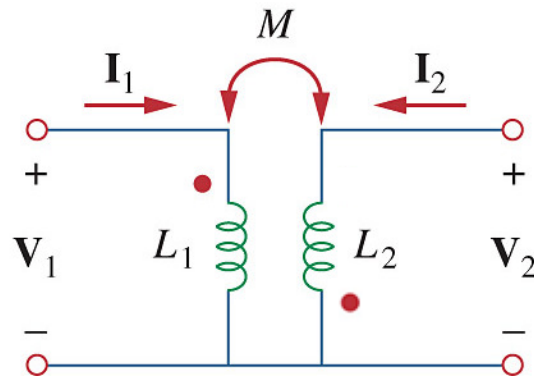

Mesh Analysis of this transformer circuit results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & -j\omega M \\ -j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Equivalent T Network

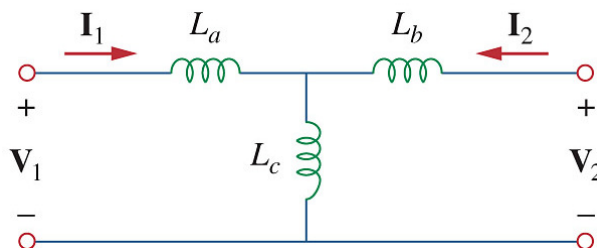

Mesh Analysis of the equivalent T network results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


Equating the terms gives the following relationships:

$$L_a = L_1 + M \quad L_b = L_2 + M \quad L_c = -M$$

## 13.4 Linear Transformers (9)

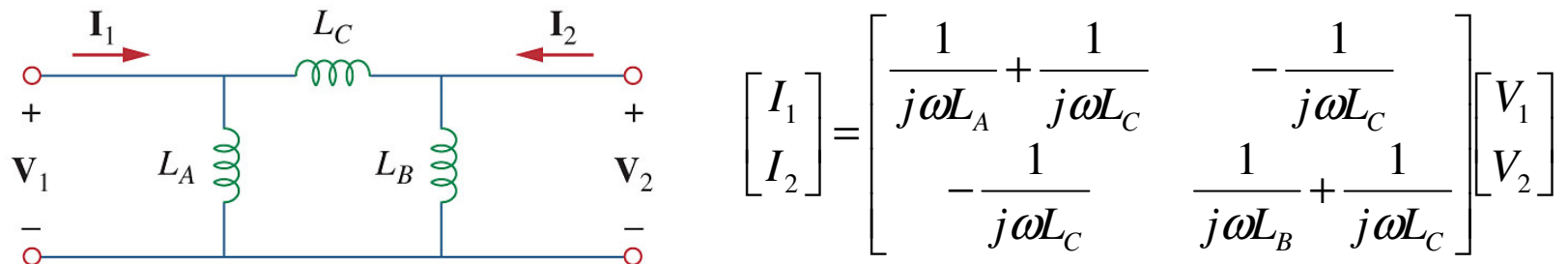
### Equivalent $\pi$ Circuit:

Similarly, for the  $\pi$  network nodal analysis provides:




Equivalent  $\pi$  Network

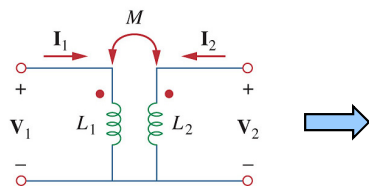By equating terms in admittance matrices, for the  $\pi$  equivalent network we obtain (note if dots are different, replace with  $-M$ ):



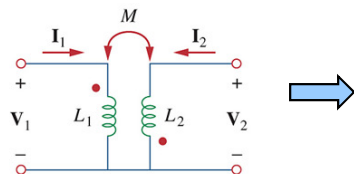
$$L_A = \frac{L_1 L_2 - M^2}{L_2 - M} ; L_B = \frac{L_1 L_2 - M^2}{L_1 - M} ; L_C = \frac{L_1 L_2 - M^2}{M}$$




$$L_A = \frac{L_1 L_2 - M^2}{L_2 + M} ; L_B = \frac{L_1 L_2 - M^2}{L_1 + M} ; L_C = \frac{L_1 L_2 - M^2}{-M}$$

# 13.4 Linear Transformers (10)


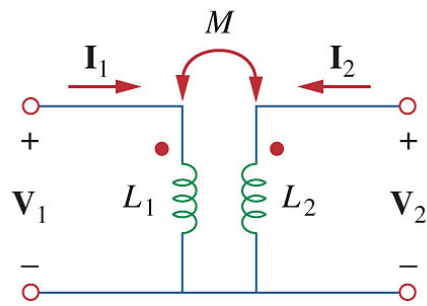
## Equivalent T or $\pi$ Circuits Summary




T Circuit

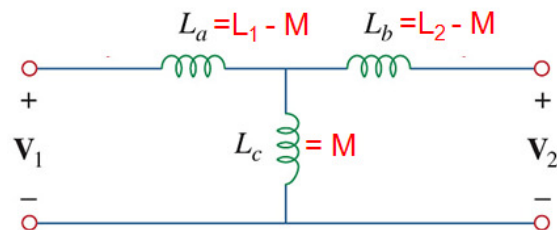


$\pi$  Circuit

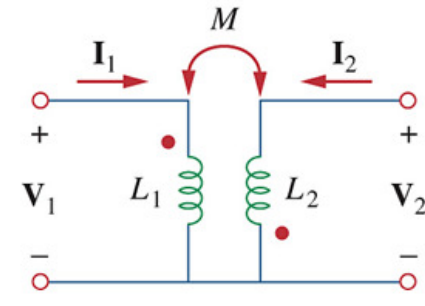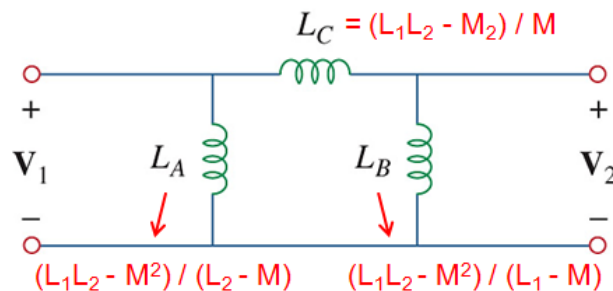

T Circuit

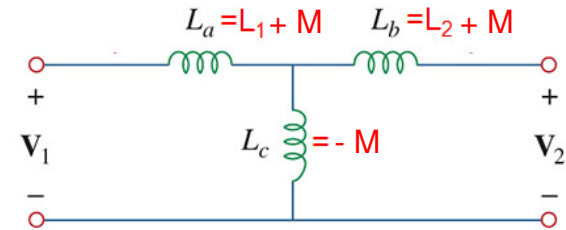



$\pi$  Circuit

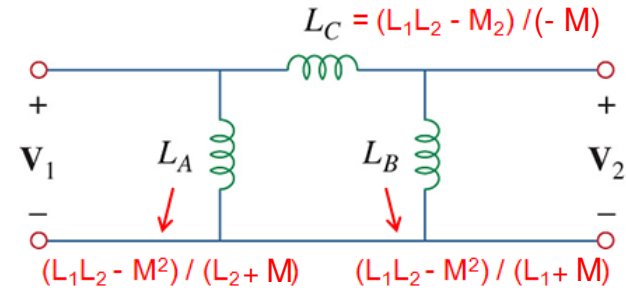

# 13.4 Linear Transformers (11)
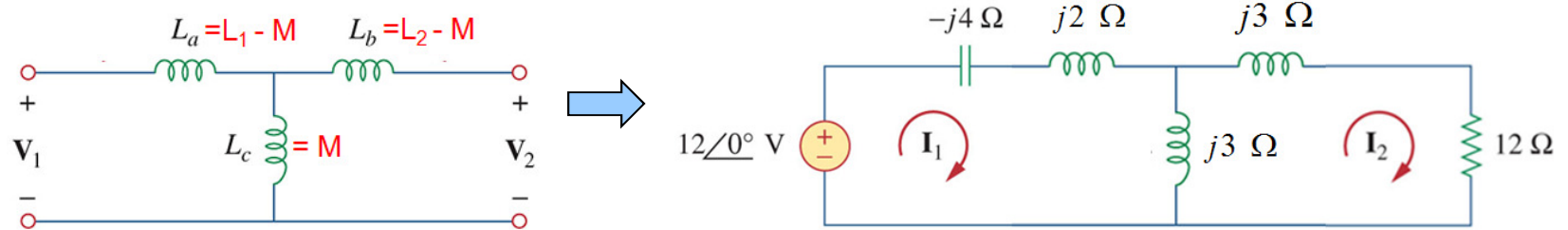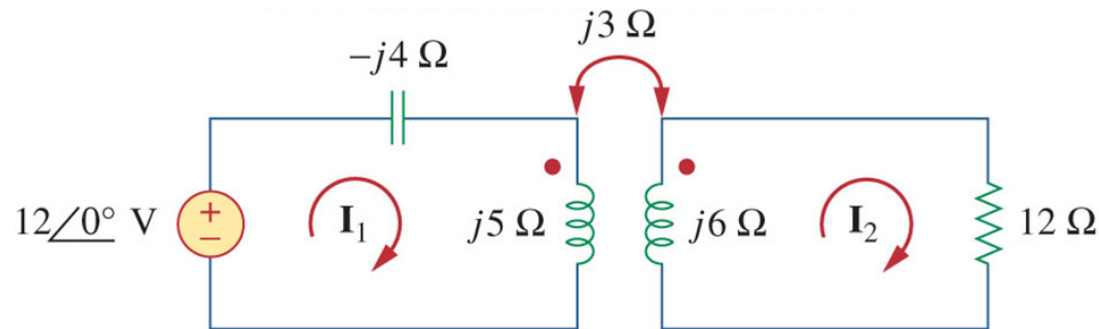
## Practice Problem 13.6

Find  $I_1$  and  $I_2$  using the T equivalent circuit



$$\text{Mesh } I_1: -12\angle 0^\circ - j4I_1 + j2I_1 + j3(I_1 - I_2) = 0 \quad jI_1 - j3I_2 = 12\angle 0^\circ$$

$$\text{Mesh } I_2: j3(I_2 - I_1) + j3I_2 + 12I_2 = 0 \quad -j3I_1 + (12 + j6)I_2 = 0$$



# Chapter 13

## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers**
- 13.6 Ideal Autotransformers
- 13.9 Applications
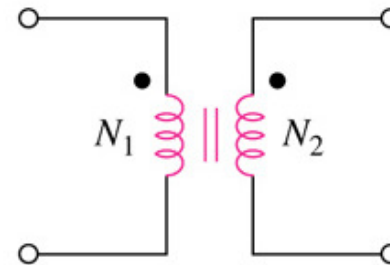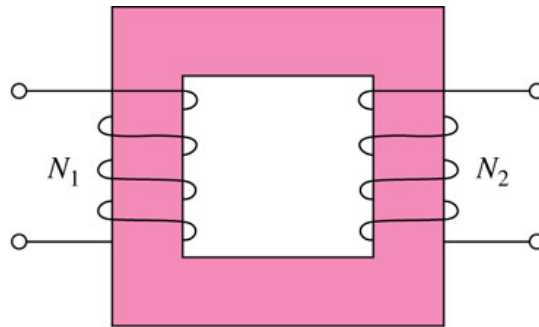
## 13.5 Ideal Transformers (1)

- An ideal transformer has perfect coupling ( $k=1$ ).
- It consists of two or more coils with a large number of turns wound on a common core of high permeability.



- Because of the high permeability of the core, the flux links all the turns of both coils, thereby resulting in a perfect coupling.

## 13.5 Ideal Transformers (2)

“Dot’s the same polarity”

Recall the coupled circuit:

$$V_1 = j\omega L_1 I_1 + j\omega M I_2 \quad (1)$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2 \quad (2)$$


Solving for  $I_1$  in (1):  $I_1 = \frac{V_1 - j\omega M I_2}{j\omega L_1} \quad (3)$

Substituting (3) into (2):  $V_2 = j\omega L_2 I_2 + \frac{M V_1}{L_1} - \frac{j\omega M^2 I_2}{L_1}$

$M = \sqrt{L_1 L_2}$  For perfect coupling ( $k=1$ ):

$$V_2 = j\omega L_2 I_2 + \frac{\sqrt{L_1 L_2} V_1}{L_1} - \frac{j\omega L_1 L_2 I_2}{L_1} = \sqrt{\frac{L_2}{L_1}} V_1 = n V_1$$

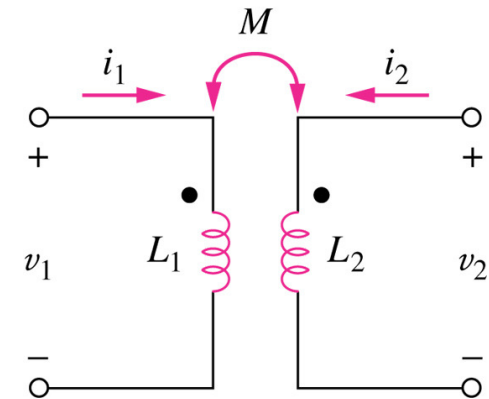Therefore:  $V_2 = n V_1$  where  $n = \sqrt{L_2 / L_1}$  = turns ratio



## 13.5 Ideal Transformers (3)

“Dot’s opposite each other”

Mesh Equations give the following:

$$V_1 = j\omega L_1 I_1 - j\omega M I_2 \quad (1)$$

$$V_2 = -j\omega M I_1 + j\omega L_2 I_2 \quad (2)$$


Solving for  $I_1$  in (1):  $I_1 = \frac{V_1 + j\omega M I_2}{j\omega L_1} \quad (3)$

Substituting (3) into (2):  $V_2 = j\omega L_2 I_2 - \frac{M V_1}{L_1} - \frac{j\omega M^2 I_2}{L_1}$

$M = \sqrt{L_1 L_2}$  For perfect coupling ( $k=1$ ):

$$V_2 = j\omega L_2 I_2 - \frac{\sqrt{L_1 L_2} V_1}{L_1} - \frac{j\omega L_1 L_2 I_2}{L_1} = -\sqrt{\frac{L_2}{L_1}} V_1 = -n V_1$$

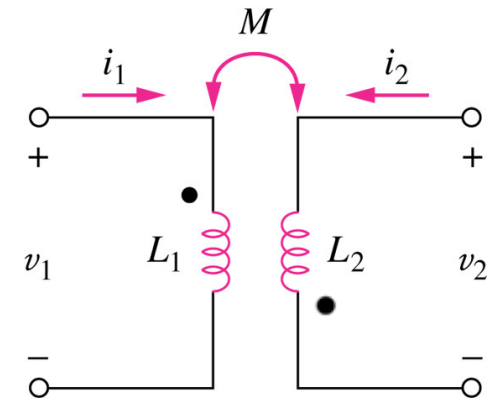Therefore:  $V_2 = -n V_1$  If dot is swapped at output






## 13.5 Ideal Transformers (4)

### Properties

- A transformer is said to be **ideal** if it has the following properties:
  1. Coils have very large reactances ( $L_1, L_2, M \rightarrow \infty$ )
  2. Coupling coefficient is equal to unity ( $k=1$ )
  3. Primary and secondary coils are lossless ( $R_1 = R_2 = 0$ )
- An ideal transformer is a unity-coupled ( $k=1$ ) lossless transformer in which the primary and secondary coils have infinite self-inductances ( $L_1 \& L_2 \rightarrow \infty$ ).
- Iron core transformers are close approximations to ideal transformers and are used in power systems and electronics.
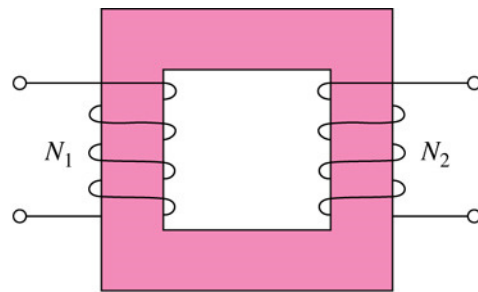
## 13.5 Ideal Transformers (5)

- When a sinusoidal voltage is applied to the primary winding, the same magnetic flux  $\Phi$  goes through both windings.



$$v_1 = N_1 \frac{d\phi}{dt} \quad ; \quad v_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = n = \text{Turns ratio or transformation ratio}$$

- Using the phasor voltages rather than the instantaneous voltages:


$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$

## 13.5 Ideal Transformers (6)

- Power conservation:  $v_1 i_1 = v_2 i_2$
- The energy supplied to the primary must equal the energy absorbed by the secondary, since there are no losses in an ideal transformer.

- In phasor form:
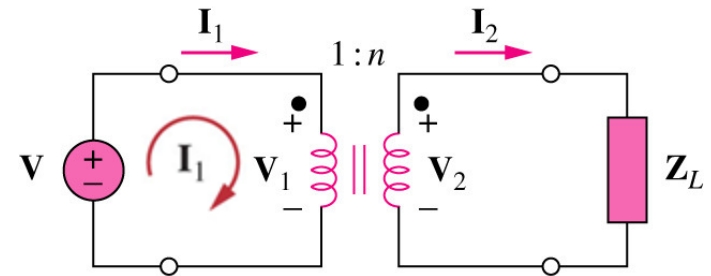
$$\frac{I_1}{I_2} = \frac{V_2}{V_1} = n$$



- $n=1 \rightarrow$  isolation transformer ( $V_2 = V_1$ )
- $n>1 \rightarrow$  step-up transformer ( $V_2 > V_1$ )
- $n<1 \rightarrow$  step-down transformer ( $V_2 < V_1$ )


## 13.5 Ideal Transformers (7)

- Transformer ratings are usually specified as  $V_1 / V_2$
- Power companies often generate at some convenient voltage and use the step-up transformer to increase the voltage so that the power can be transmitted at very high voltage and low current over transmission lines, resulting in significant cost savings. Near residential consumers, step-down transformers are used to bring the voltage down to 120 V.
- It is important to get the proper polarity of the voltages and the direction of the currents for the transformer.
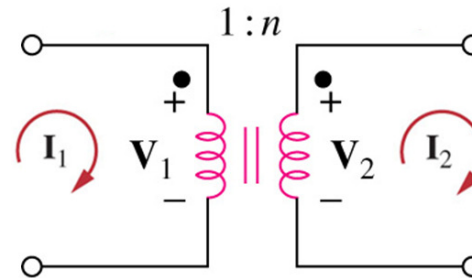
# 13.5 Ideal transformers (8)


V and I relationships (simpler way to remember)

Given this standard  
definition for Voltages  
and currents




**Note:** This definition  
of  $I_2$  differs from the  
text.

Dots "Same"  $\rightarrow$  "+"

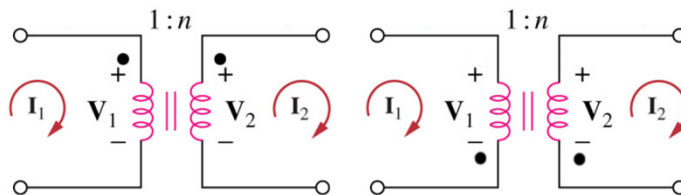

Dots "Different"  $\rightarrow$  "-"

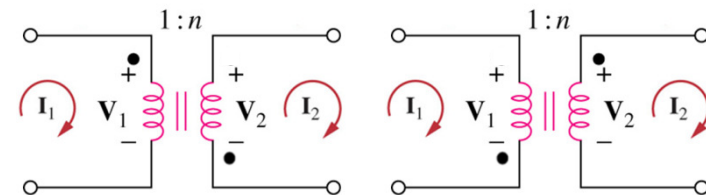

$$V_2 = nV_1$$

$$I_2 = \frac{I_1}{n}$$

$$Z_{in} = \frac{Z_L}{n^2}$$

Reflected  
Impedance  $\rightarrow$

*Note: The larger the turns ratio  
The larger "n"  
The larger " $N_2$ "  
The larger  $V_2$*

**Turns Ratio**

$$n = \frac{N_2}{N_1}$$

$$V_2 = -nV_1$$


$$I_2 = -\frac{I_1}{n}$$

$$Z_{in} = \frac{Z_L}{n^2}$$

## 13.5 Ideal Transformers (9)
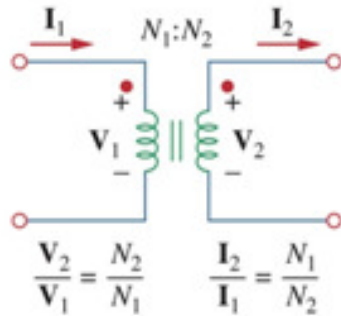
### V and I relationships

- Expressing  $V_1$  in terms of  $V_2$  and  $I_1$  in terms of  $I_2$  or vice versa:



$$V_1 = \frac{V_2}{n} \quad V_2 = nV_1$$

$$I_2 = \frac{I_1}{n} \quad I_1 = nI_2$$

Positive, if Voltage “**same**” polarity at dot

Positive, if current “**different**” polarity at dot

- Complex Power is:

$$S_1 = V_1 I_1^* = \frac{V_2}{n} (nI_2)^* = V_2 I_2^* = S_2$$


Complex Conjugate of  $I_2$

- Complex power supplied to the primary is delivered to the secondary without loss.
- The ideal transformer is **lossless** and absorbs **no power**.

## 13.5 Ideal Transformers (10)
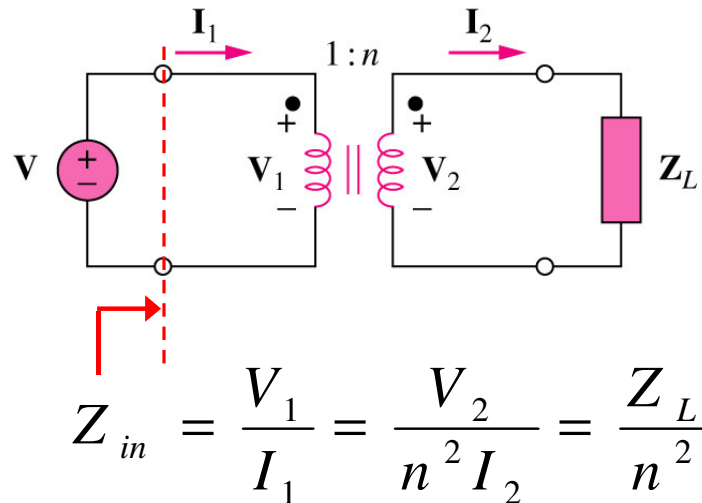
### Reflected impedance

- The input impedance as seen by the source is:




- The input impedance is also called the reflected impedance since it appears as if the load impedance is reflected to the primary side.
- The ability of the transformer to transform a given impedance to another allows impedance matching to ensure maximum power transfer.

## 13.5 Ideal Transformers (11)
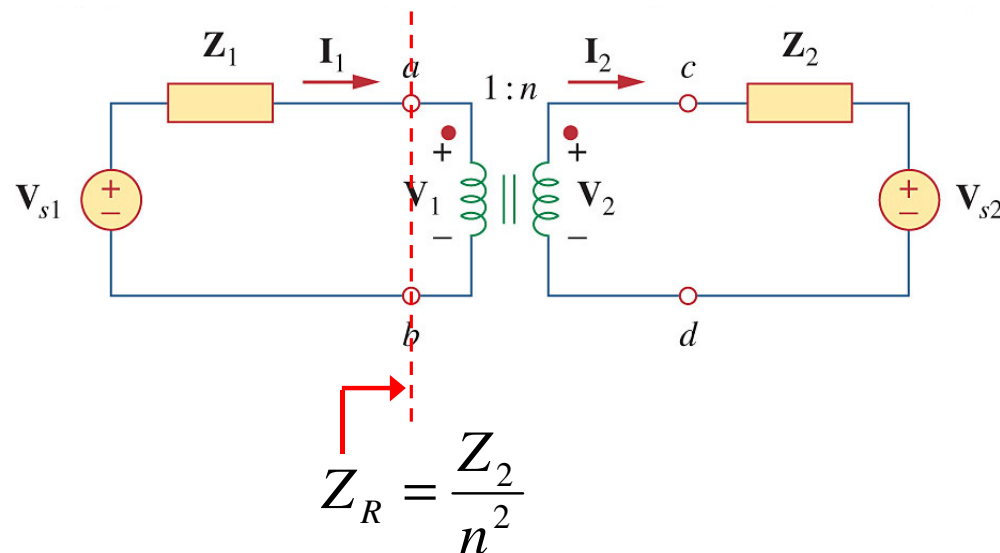
### Equivalent circuit analysis

- In analyzing a circuit containing an ideal transformer, it is common practice to eliminate the transformer by reflecting impedances and sources from one side of the transformer to the other.
- Suppose we want to reflect the secondary side of the circuit to the primary side:






# 13.5 Ideal Transformers (12)
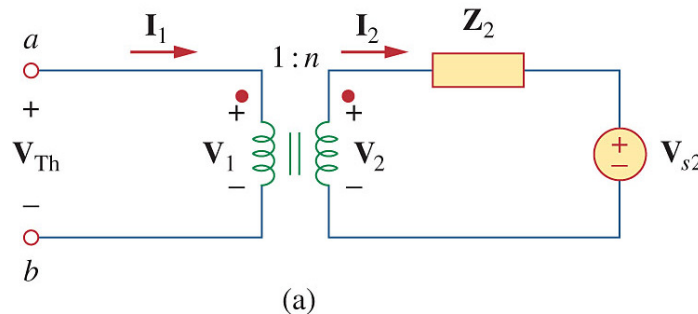
## Equivalent circuit analysis

- We find the Thevenin equivalent of the circuit to the right of a-b:
- Obtaining  $V_{th}$  from “open circuit voltage”:





$$I_1 = 0 = I_2 \quad \text{Since a-b is open}$$

$$V_2 = V_{s2}$$


$$V_{Th} = V_1 = \frac{V_2}{n} = \frac{V_{s2}}{n}$$

- Obtaining  $Z_{Th}$  (remove the voltage source in the secondary and insert a unit source at a-b terminals.)
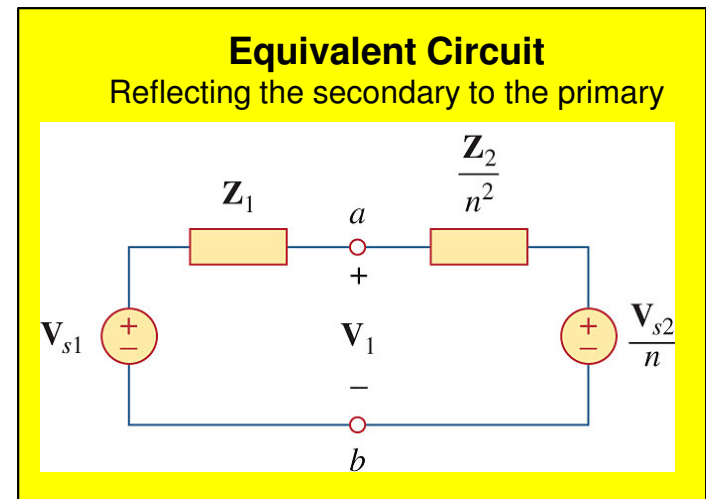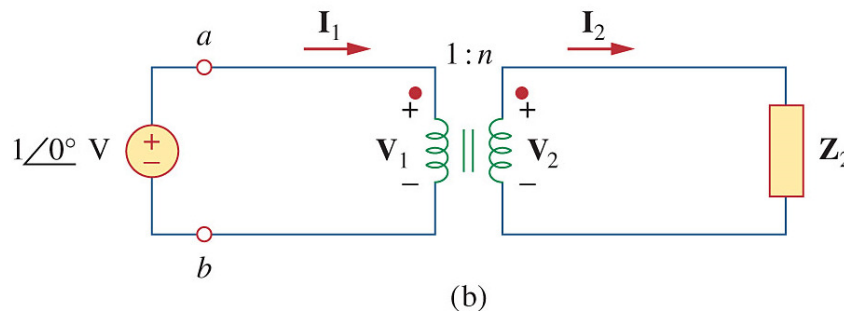
$$Z_{Th} = \frac{V_1}{I_1} = \frac{V_2}{n^2 I_2} = \frac{Z_2}{n^2}$$




## 13.5 Ideal Transformers (13)

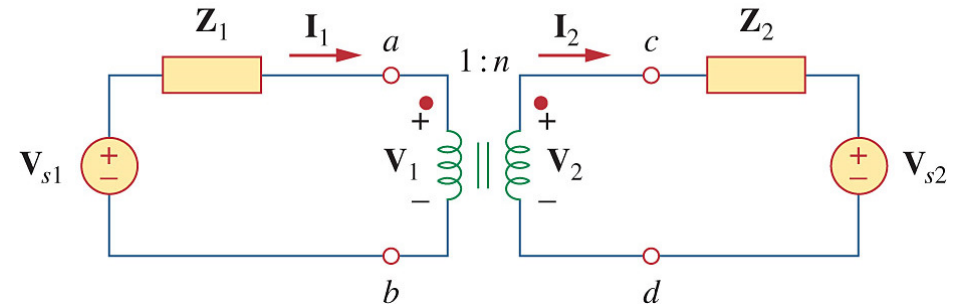


- The general rule for eliminating the transformer and reflecting the secondary circuit to the primary side:

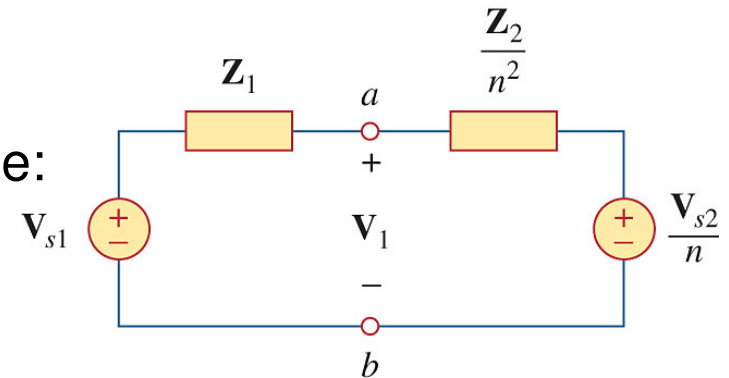- Divide the secondary impedance by  $n^2$
- Divide the secondary voltage by  $n$
- Multiply the secondary current by  $n$



- The general rule for eliminating the transformer and reflecting the secondary circuit to the primary side:

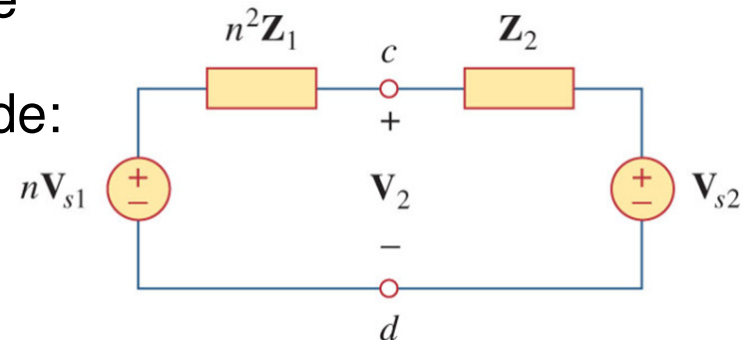
- Multiply the primary impedance by  $n^2$
- Multiply the primary voltage by  $n$
- Divide the primary current by  $n$




## 13.5 Ideal Transformer (14)
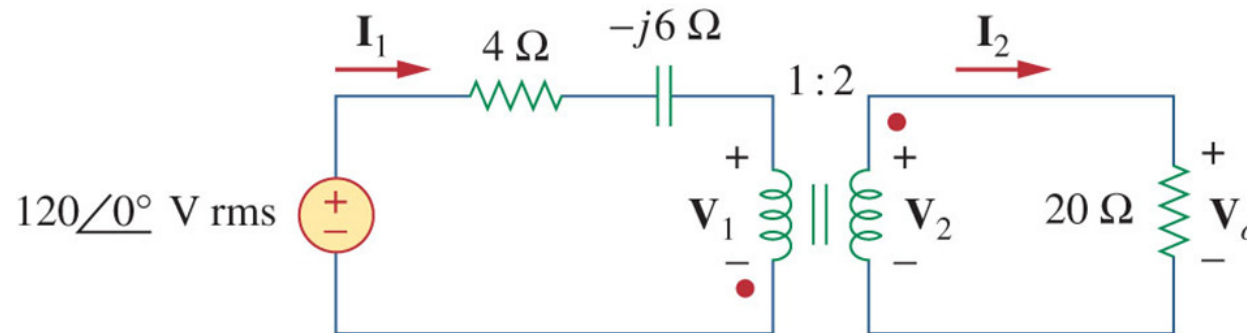
### Example 13.8 (Textbook)

For the ideal transformer, find: (a) the source current  $I_1$ , (b) the output voltage  $V_o$ , and (c) the complex power supplied by the source



## 13.5 Ideal Transformer (14)

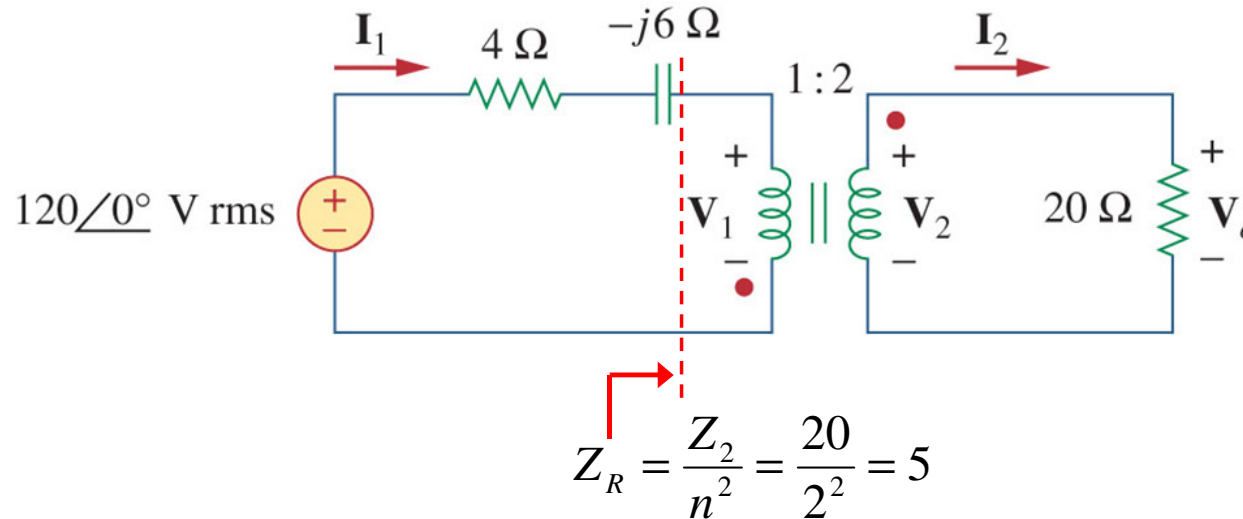

Impedance seen by the Voltage source is:

$$Z_{in} = (4 - j6) + 5 = 9 - j6 = 10.82 \angle -33.69^\circ \Omega$$

Input current  $I_1$  is:

$$I_1 = \frac{V_s}{Z_{in}} = \frac{120 \angle 0^\circ}{10.82 \angle -33.69^\circ} = 11.09 \angle 33.69^\circ \text{ A}$$

$$I_2 = -\frac{I_1}{n} = \frac{-11.09 \angle 33.69^\circ}{2} = 5.55 \angle -146.31^\circ \text{ A}$$

$$V_o = 20I_2 = 20(5.55 \angle -146.31^\circ) = 110.9 \angle -146.31^\circ \text{ V}$$


# Chapter 13

## Magnetically Coupled Circuits


- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers**
- 13.9 Applications**
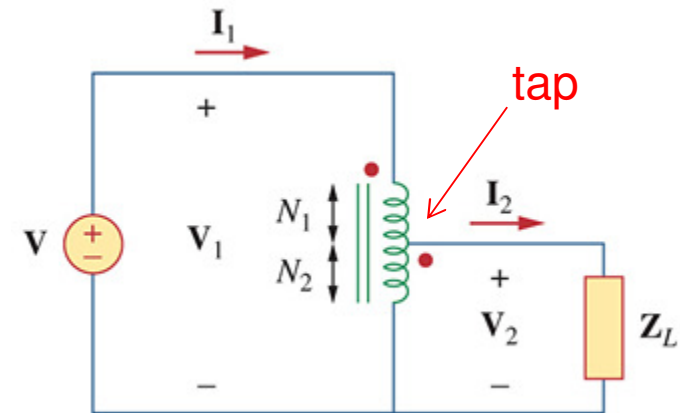
## 13.6 Ideal Auto-Transformers (1)

- An **autotransformer** is a transformer in which both the primary and the secondary are in a single winding
- A connection point called a *tap* separates the primary and secondary.
- The tap is often adjustable to provide a desired turns ratio.
- An adjustable tap provides a variable voltage to the load
- A disadvantage of the autotransformer is it provides *no electrical isolation*




Step Down Auto-Transformer

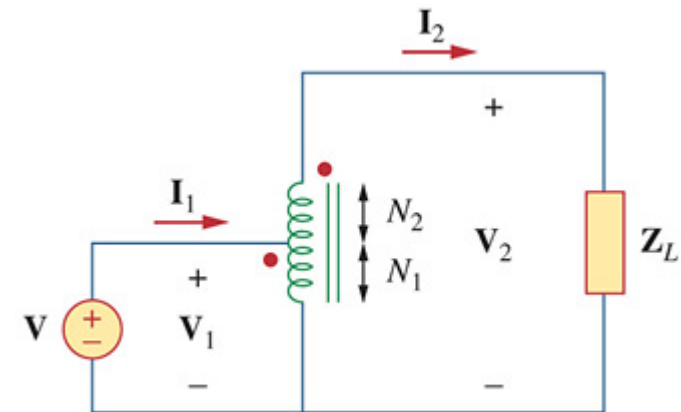

Step Up Auto-Transformer
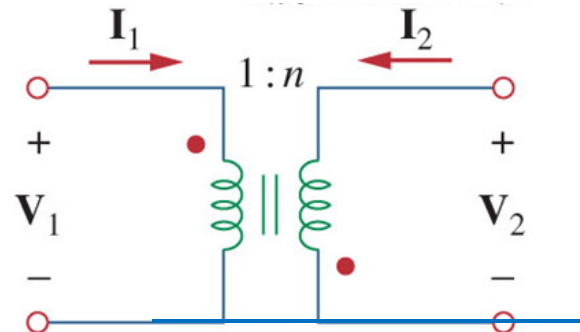
## 13.6 Ideal Auto-Transformers (2)


- In analyzing the autotransformer, consider the following circuit:



From earlier we know the following relationship

$$V_2 = -nV_1$$

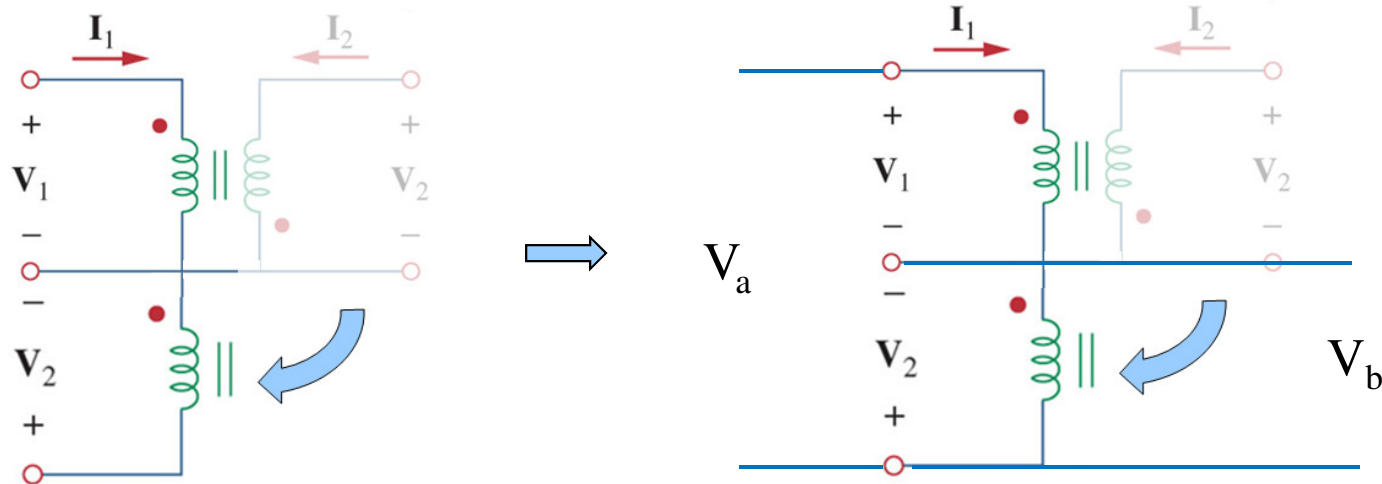- If we flip the secondary side underneath the primary, we can create an autotransformer as shown



## 13.6 Ideal Auto-Transformers (3)


- Analysis of this circuit provides the following results:

Primary Side

$$V_a = V_1 - V_2$$

$$V_a = V_1 + nV_1$$

$$V_a = (1+n)V_1$$

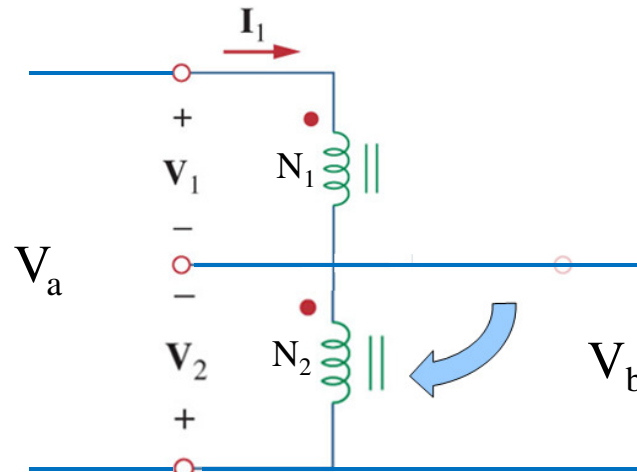

Secondary Side

$$V_b = -V_2 = nV_1$$

Ratio Primary/Secondary

$$\frac{V_a}{V_b} = \frac{1+n}{n} = \frac{N_1 + N_2}{N_2} \quad \Rightarrow$$


Notice, this looks like  
a Voltage Divider !

$$V_b = \left( \frac{N_2}{N_1 + N_2} \right) V_a$$



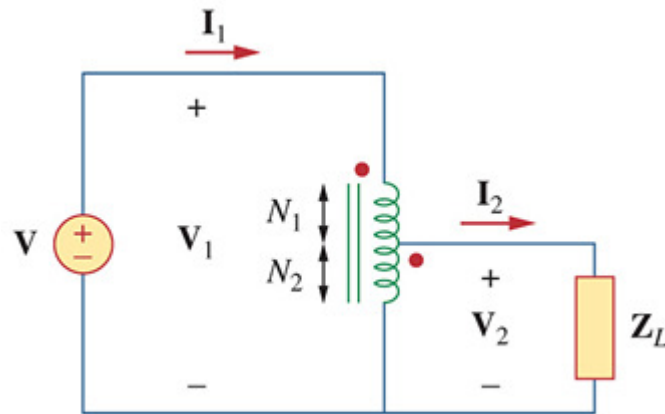
## 13.6 Ideal Auto-Transformers (4)

- The voltage / current relationships for the lossless ideal autotransformer are as follows:



Step Down Auto-Transformer

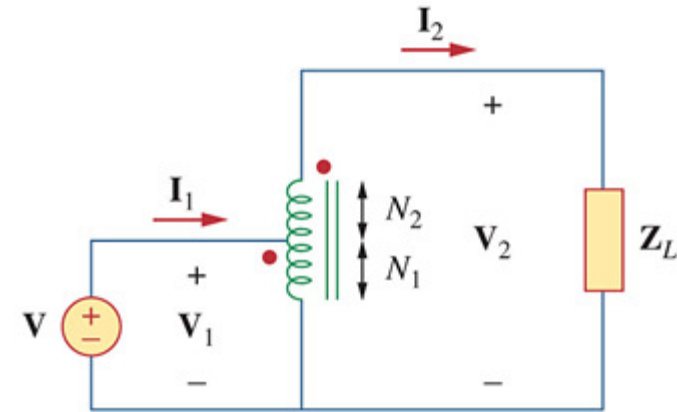

Step Up Auto-Transformer

$$V_2 = \frac{N_2}{N_1 + N_2} V_1$$

Similar to  
Voltage Divider  
equation

$$V_2 = \frac{N_1 + N_2}{N_1} V_1$$

$$I_2 = \frac{N_1 + N_2}{N_2} I_1$$

Inverse Relation

$$I_2 = \frac{N_1}{N_1 + N_2} I_1$$

$$Z_{in} = \left( \frac{N_1 + N_2}{N_2} \right)^2 Z_L$$


Derive from V/I

$$Z_{in} = \left( \frac{N_1}{N_1 + N_2} \right)^2 Z_L$$

## 13.6 Ideal Auto-Transformers (5)



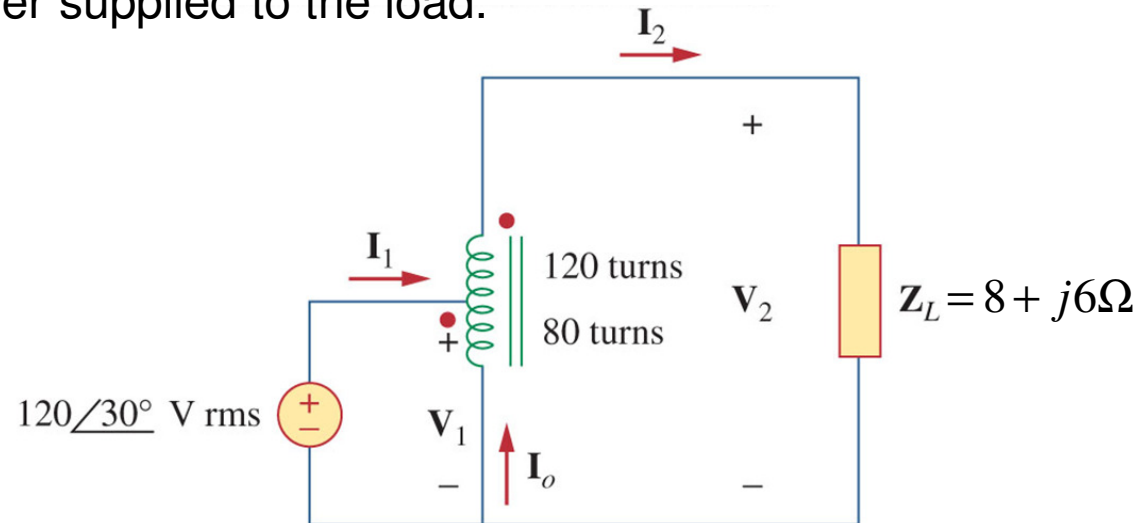
### Example 13.11 (Textbook)

For the autotransformer below, find: (a) the currents  $I_1$ ,  $I_2$ ,  $I_o$ , (b) the complex power supplied to the load.



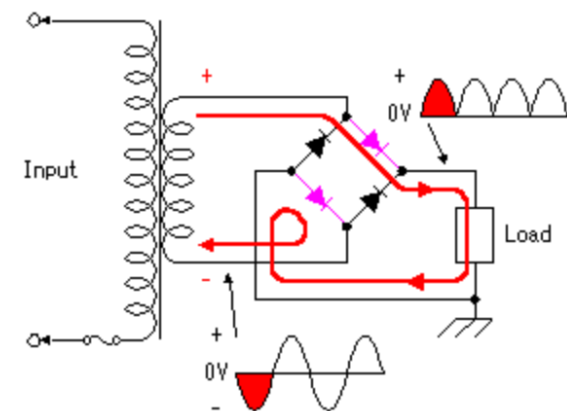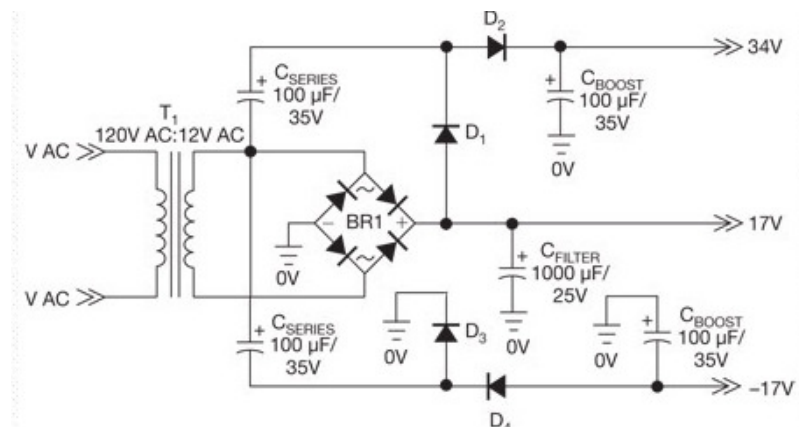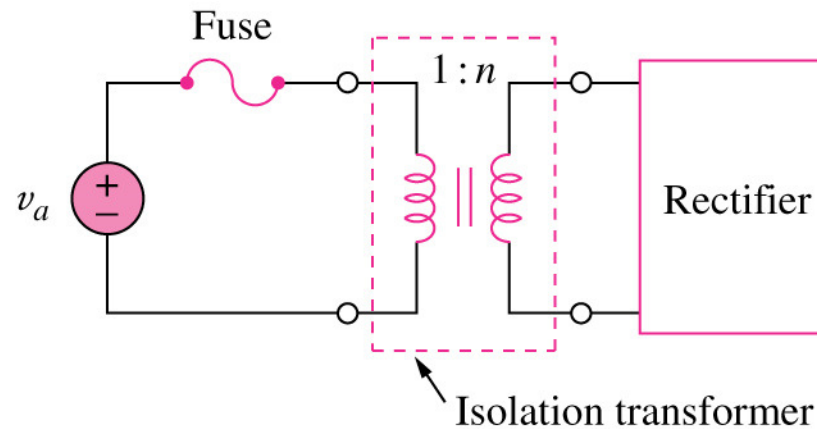
## 13.9 Applications (1)

- Transformer as an Isolation Device to isolate ac supply from a rectifier


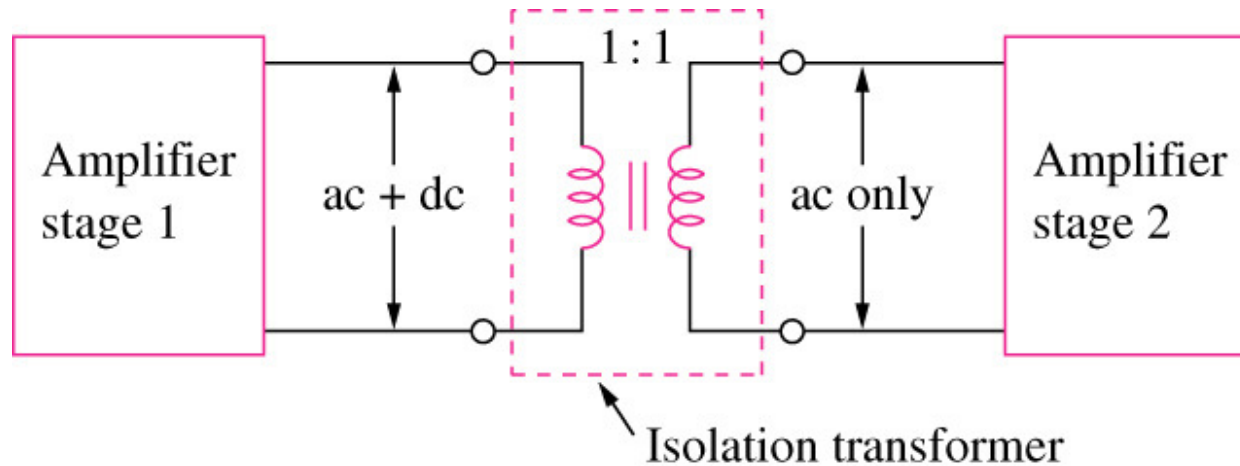
## 13.9 Applications (2)


- Transformer as an Isolation Device to isolate dc between two amplifier stages.



- Biasing is the application of a DC voltage to a transistor amplifier to produce a desired mode of operation.
- Each amplifier stage can be biased separately to operate in a particular mode.


## 13.9 Applications (3)

- Transformer as a Matching Device

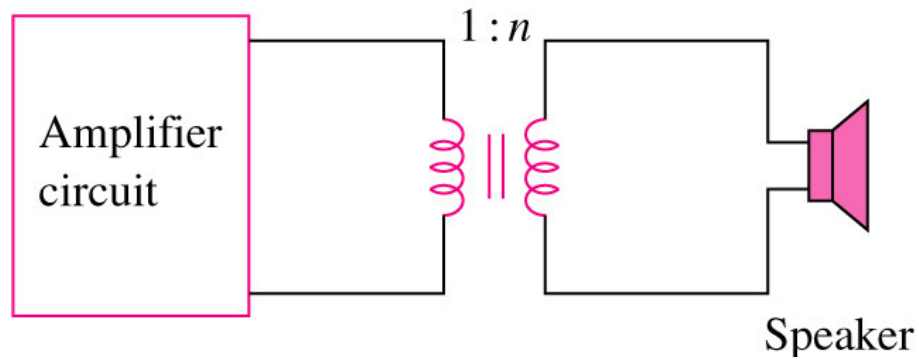

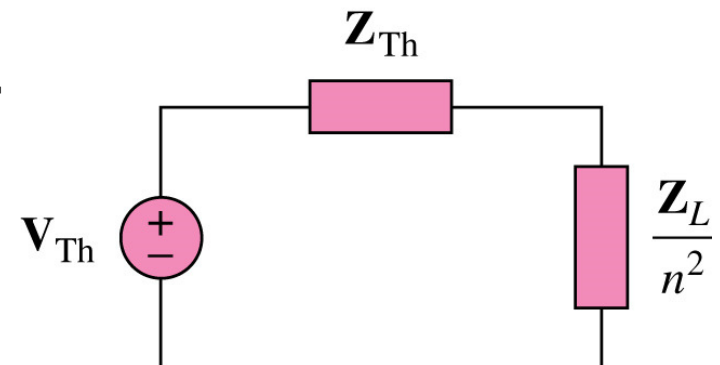**Equivalent circuit**

**Using an ideal transformer to  
match the speaker to the amplifier**



## 13.9 Applications (4)


### Practice Problem 13.16 (Textbook)

Calculate the turns ratio of an ideal transformer required to match a  $400\Omega$  load to a source with internal impedance of  $2.5k\Omega$ . Find the load voltage when the source voltage is  $30V$ .

Ans:  $n = 0.4$ ;  $V_L = 6V$

## 13.9 Applications (5)

- A typical power distribution system

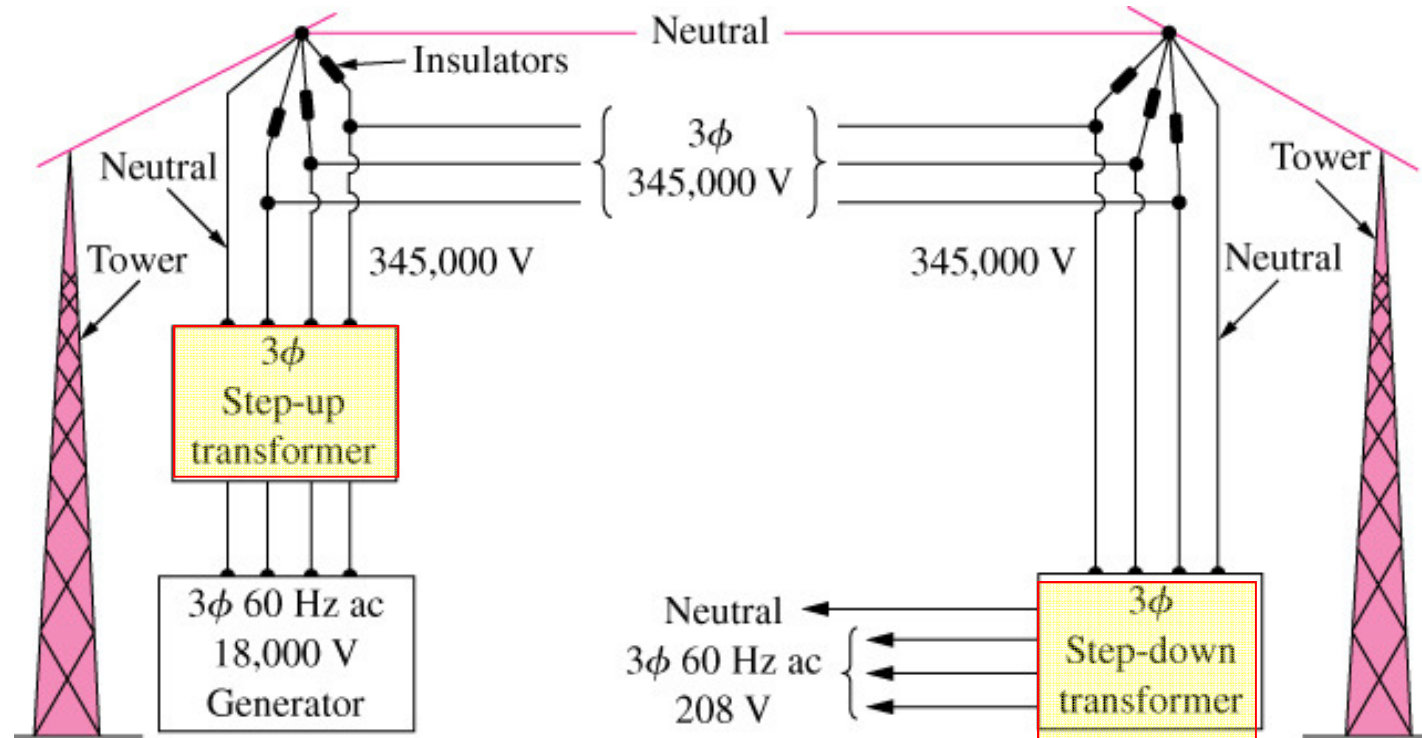

## Homework #3

**Due beginning of class Wednesday Feb 4, 2015**

- 13.30
- 13.35
- 13.42
- 13.50
- 13.53 (modified)
- Autotransformer (See handout)

**Exam over Chapter 13 on Monday Feb 9**



# Chapter 13

## Equation / Analysis Summary

- Series Aiding  $L = L_1 + L_2 + 2M$  / Opposing  $L = L_1 + L_2 - 2M$

- Dot Convention Model

- Coupling coefficient "k"  $M = k\sqrt{L_1 L_2}$

- Linear Transformer


- Input Impedance:

$$Z_{in} = Z_{primary} + \frac{\omega^2 M^2}{Z_{secondary}}$$

- Reflected Impedance:

$$Z_{reflected} = \frac{\omega^2 M^2}{Z_{secondary}}$$

- Equivalent T or  $\pi$  Circuits:

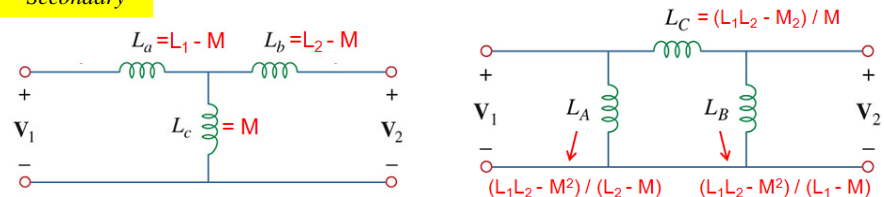

- Ideal Transformer

- $K = 1, L_1, L_2 \rightarrow \infty$


- Lossless ( $S_1 = S_2$ )

- Voltage / Current Relationship:

- Dots "same" = +n, Dots "diff" = -n

- Complex Power:  $S_1 = V_1 I_1^* = V_2 I_2^* = S_2$

**Turns Ratio**  
 $n = \frac{N_2}{N_1}$

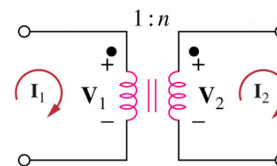

$$V_2 = nV_1$$

$$I_2 = \frac{I_1}{n}$$

$$Z_{in} = \frac{Z_L}{n^2}$$


$$P_{ave} = |I_2|^2 R_L$$

- Autotransformer

- Adjustable "tap"

- No electrical Isolation

- Voltage Divider like relationship

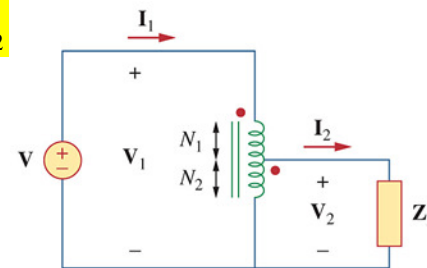

$$V_2 = \frac{N_2}{N_1 + N_2} V_1$$

$$I_2 = \frac{N_1 + N_2}{N_2} I_1$$

# Chapter 13


## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers
- 13.9 Applications
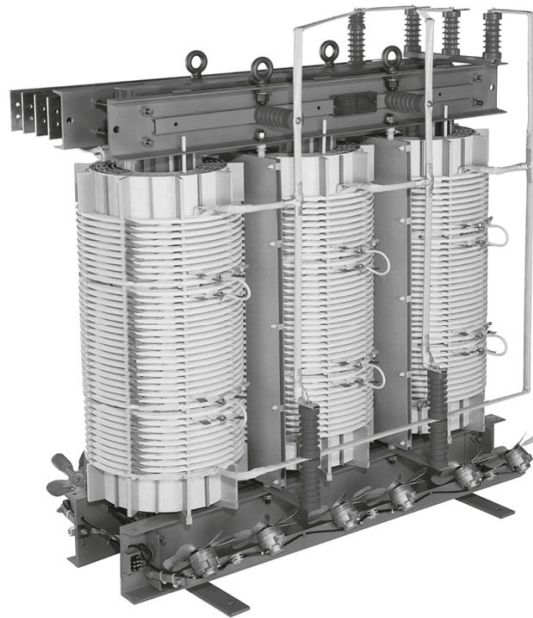
## 13.1 What is a transformer? (1)

- It is an electrical device designed on the basis of the concept of magnetic coupling
- It uses magnetically coupled coils to transfer energy from one circuit to another
- It is the key circuit elements for stepping up or stepping down ac voltages or currents, impedance matching, isolation, etc.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)



(b)


ECE 202 Ch 13

Courtesy of: (a) Electric Service Co., (b) Jensen Transformers
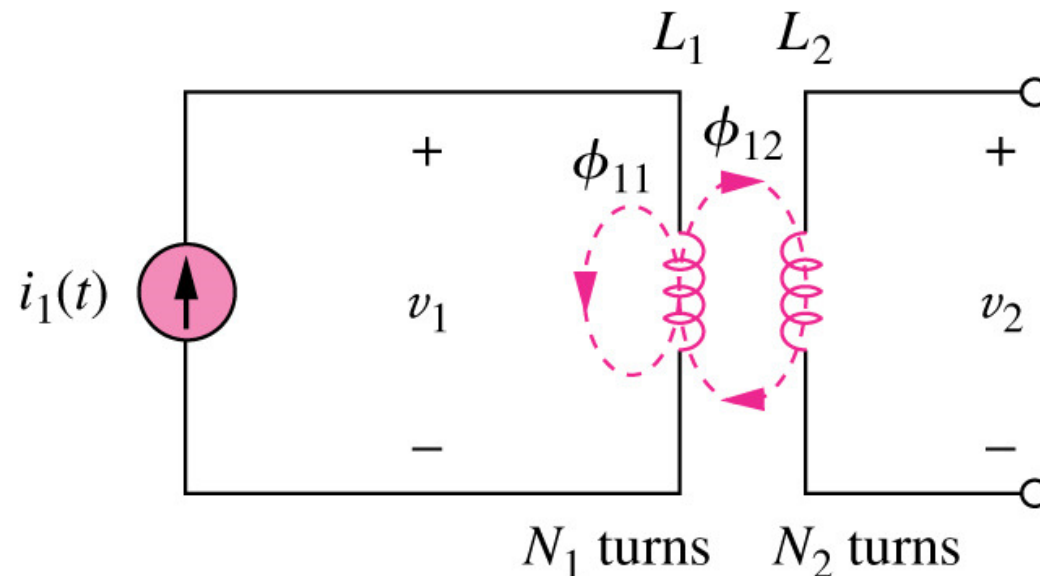
## 13.2 Mutual Inductance (1)


- Mutual Inductance

- When two inductors (or coils) are in close proximity of each other, the magnetic flux caused by current in one coil links with the other coil, thereby inducing voltage in the latter.


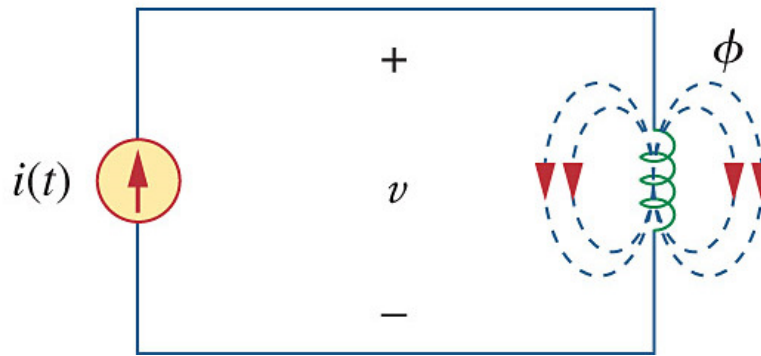
## 13.2 Mutual Inductance (2)

- First consider a single inductor, a coil with  $N$  turns:



When current  $i$  flows through the coil, a magnetic flux  $\Phi$  is produced around it.

- According to Faraday's law, the voltage  $v$  induced in the coil is proportional to the number of turns  $N$  and the time rate of change of magnetic flux  $\Phi$ :

$$v = N \frac{d \phi}{d t}$$

## 13.2 Mutual Inductance (3)

- Voltage induced in the coil given by:
- But the flux  $\Phi$  is produced by current  $i$  so that any change in  $\Phi$  is caused by a change in the current:
- Recall the voltage-current relationship for an inductor:
- The “Self” inductance  $L$  of the inductor is thus given by:
- Self-inductance  $L$  relates the voltage induced in a coil by a time-varying current in the same coil.

$$v = N \frac{d \phi}{d t}$$


$$v = N \frac{d \phi}{d i} \frac{d i}{d t}$$

$$v = L \frac{d i}{d t}$$

$$L = N \frac{d \phi}{d i}$$
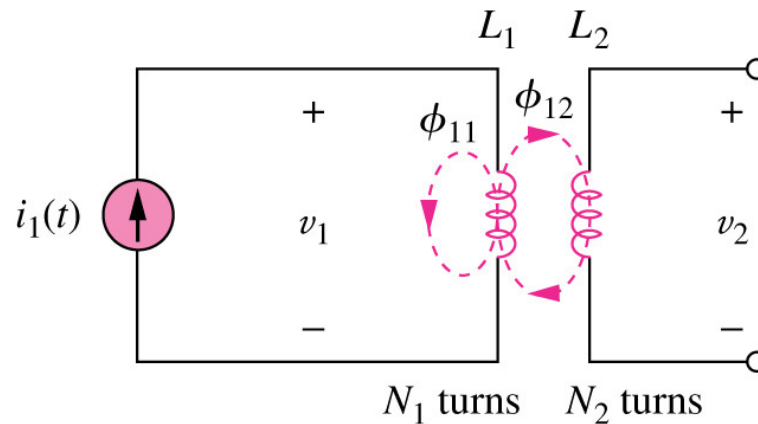
## 13.2 Mutual Inductance (4)

- Now consider two coils with self-inductances  $L_1$  and  $L_2$  that are in close proximity of each other:



Coil 1 has  $N_1$  turns

Coil 2 has  $N_2$  turns.


*Assume coil 2 carries no current.*

- The total magnetic flux  $\Phi_1$  emanating from coil 1 has two components:
  - $\Phi_{11}$  links only coil 1
  - $\Phi_{12}$  links both coils

$$\phi_1 = \phi_{11} + \phi_{12}$$
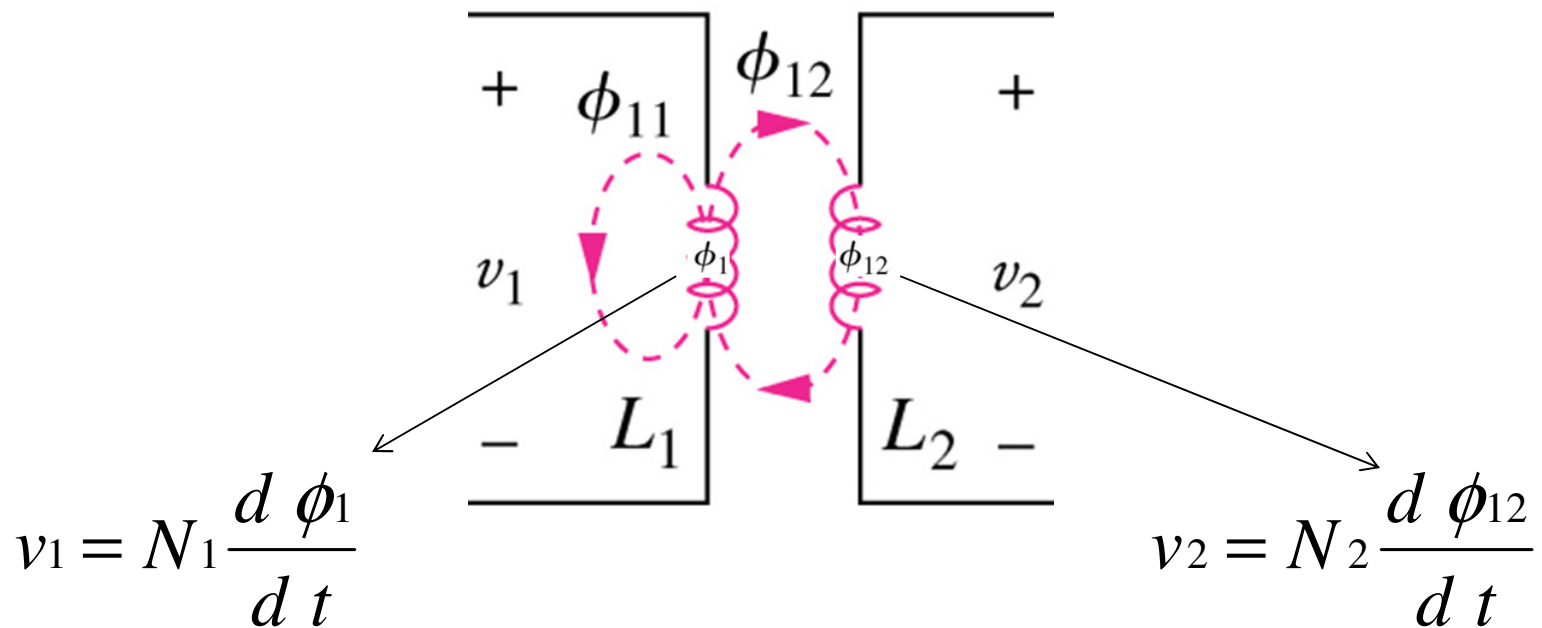
## 13.2 Mutual Inductance (5)


- Although the two coils are physically separated, they are magnetically coupled.
- The voltage induced in each coil is proportional to the flux in each coil.




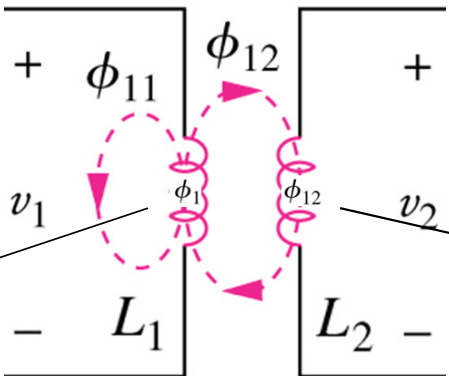
## 13.2 Mutual Inductance (6)

- The voltage equations can be rewritten as follows:



$v_2$  is the open-circuit mutual voltage (or induced voltage) across coil 2

$$v_1 = N_1 \frac{d \phi_1}{d t}$$

$$v_2 = N_2 \frac{d \phi_{12}}{d t}$$

$$v_1 = N_1 \frac{d \phi_1}{d i_1} \frac{d i_1}{d t}$$

$$v_2 = N_2 \frac{d \phi_{12}}{d i_1} \frac{d i_1}{d t}$$

$$v_1 = L_1 \frac{d i_1}{d t}$$


$$v_2 = M_{21} \frac{d i_1}{d t}$$

$L_1$  is the self-inductance of coil 1

$M_{21}$  is the mutual inductance of coil 2 with respect to coil 1
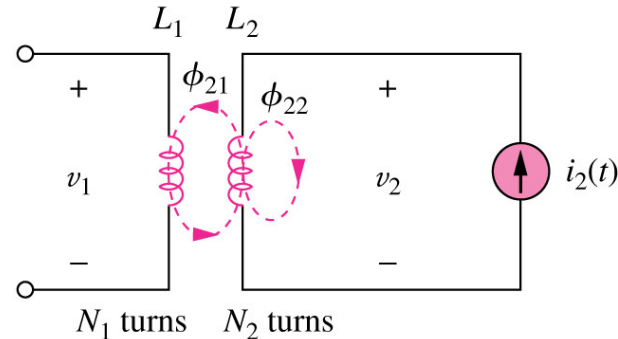
## 13.2 Mutual Inductance (7)

- Suppose now we let current  $i_2$  flow in coil 2 while coil 1 carries no current:



- The magnetic flux  $\Phi_2$  emanating from coil 2 comprises flux  $\Phi_{22}$  that links only coil 2 and flux  $\Phi_{21}$  that links both coils:

$$\phi_2 = \phi_{21} + \phi_{22}$$

- The resulting symmetry is true:


$$v_2 = L_2 \frac{d i_2}{d t} \quad v_1 = M_{12} \frac{d i_2}{d t} \quad M_{12} = N_1 \frac{d \phi_{21}}{d i_2}$$

## 13.2 Mutual Inductance (8)

- $M_{12} = M_{21} = M$  ; The “Mutual inductance” between the coils
- Mutual inductance  $M$  is measured in Henrys (just like inductors)
- Mutual inductance only exists when inductors or coils are in close proximity and the circuits are driven by time-varying sources
- Although mutual inductance  $M$  is always a positive quantity, the mutual voltage  $M \, di/dt$  may be negative or positive, just like the self-induced voltage  $L \, di/dt$  (determined by “Dot” convention)
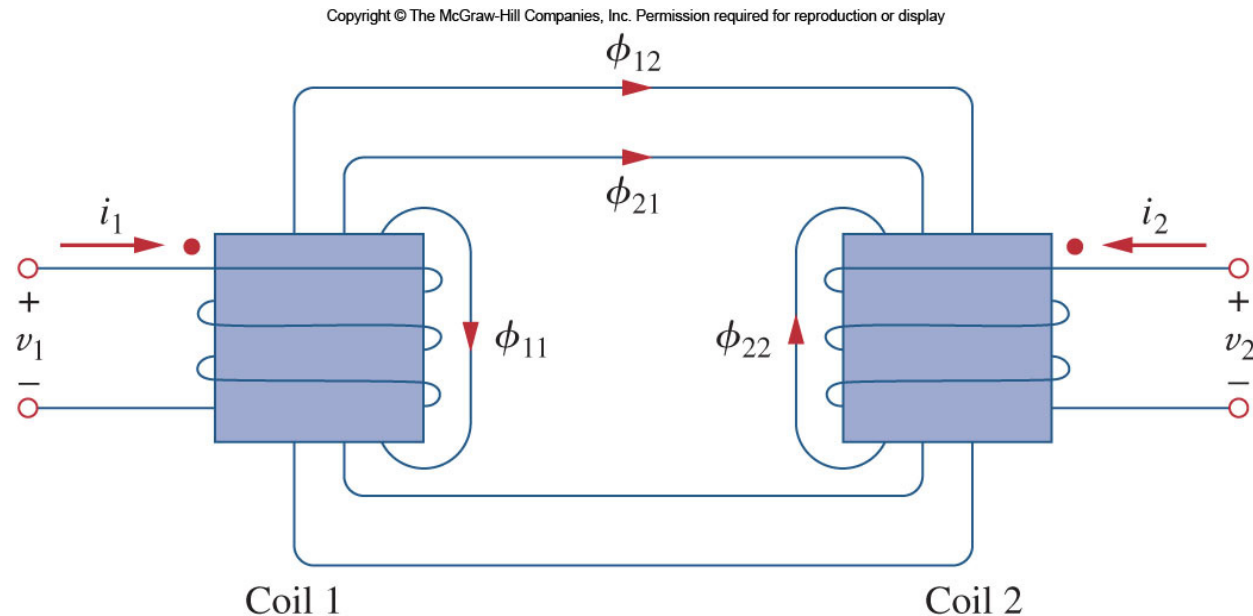
## 13.2 Mutual Inductance (9)

- Self-induced voltage polarity is determined by the reference direction of the current and the reference polarity of the voltage,
- The polarity of the mutual voltage is not as easy to determine (depends on winding direction of the coils).
- We use the dot convention to determine





## 13.2 Mutual Inductance (10)

### “Dot Convention”

- If a current **enters** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **positive** at the dotted terminal of the second coil.



Voltage is  
“Negative”

Enters the  
“Un-Dotted” side

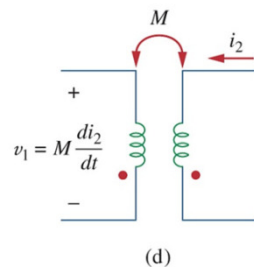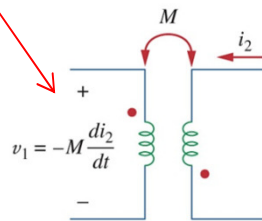

Enters the “Dot”

Voltage is  
“Positive”

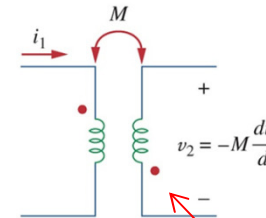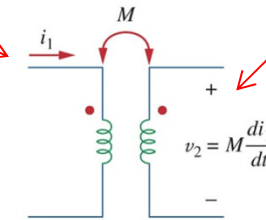

Voltage is  
“Positive”  
At “Dotted”  
Terminal


- Alternatively, if a current **leaves** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **negative** at the dotted terminal of the second coil.

## 13.2 Mutual Inductance (11)
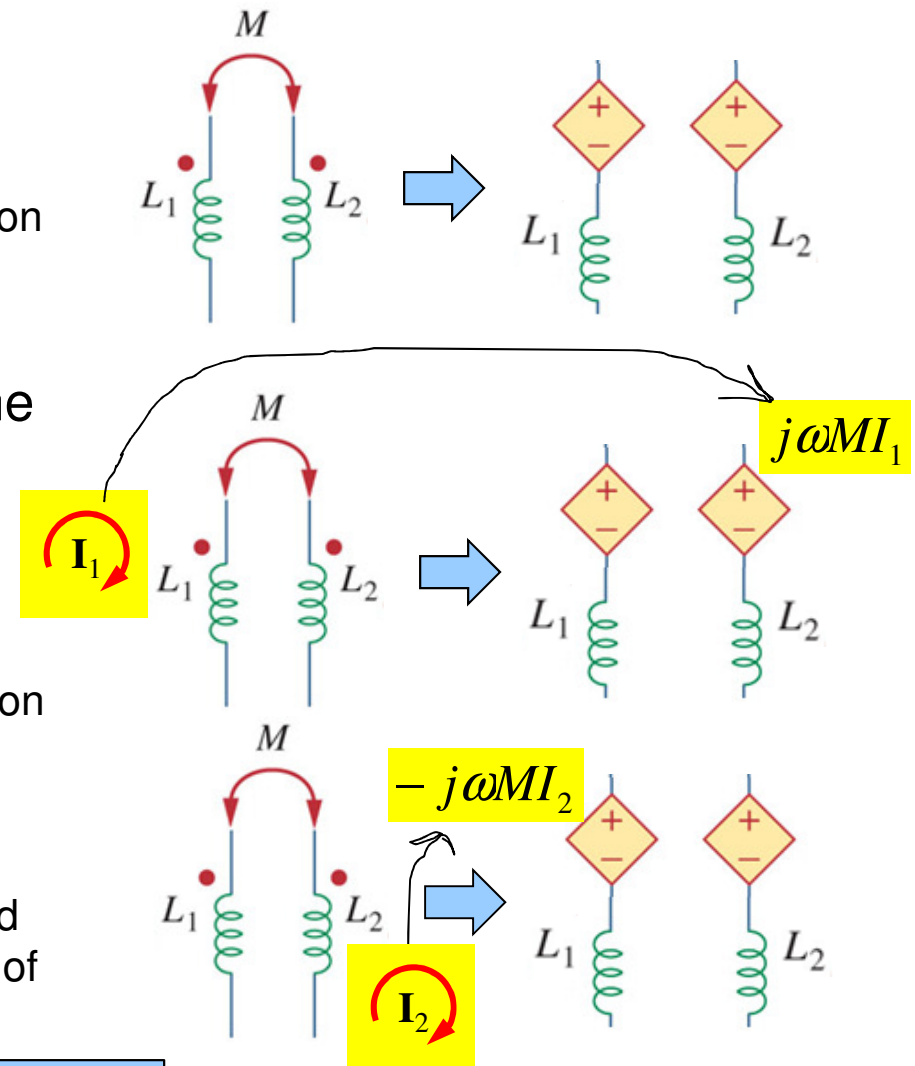
### “The Model” (Phasor domain)

- Replace the “Dot” with a controlled voltage source.
  - Place on same side as the Dot
  - Positive terminal in same direction as the Dot
- Now look at the current entering each dot to determine the magnitude of the voltage source
  - If the current enters the dotted terminal, it will induce a positive voltage in the controlled source on the opposite terminal of  $j\omega M(I)$
  - If the current enters the “un-dotted” terminal, it will induce a negative voltage in the controlled source on the opposite terminal of  $-j\omega M(I)$


Note: This method differs slightly from the text



KEY CONCEPT !

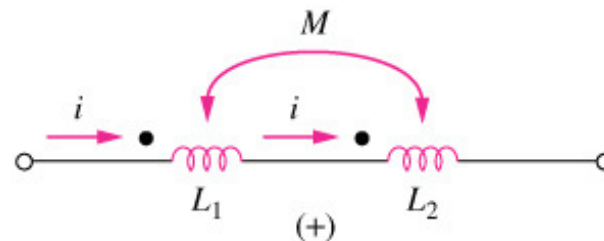
## 13.2 Mutual Inductance (12)

Dot convention for coils in series; the sign indicates the polarity of the mutual voltage



$$L = L_1 + L_2 + 2M$$

(series - aiding connection)

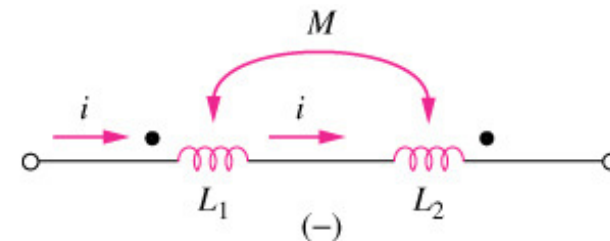

$$L = L_1 + L_2 - 2M$$

(series - opposing connection)


We can show this using the model!

## 13.2 Mutual Inductance (13)

### Example Problem 13.1
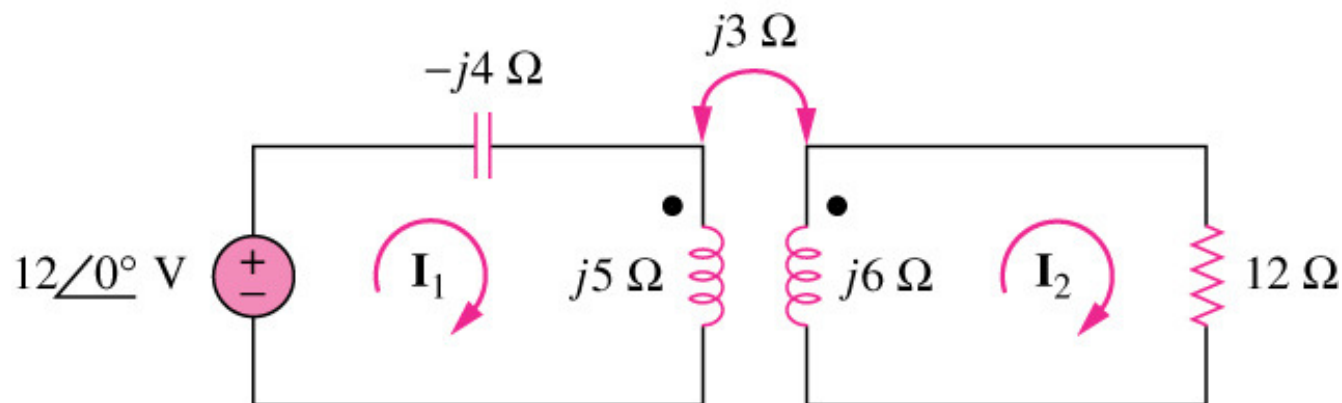
#### Example 13.1 (Textbook)

Calculate the phasor currents  $I_1$  and  $I_2$  in the circuit shown below.





Ans:  $I_1 = 13.02 \angle -49.40^\circ \text{ A}$ ;  $I_2 = 2.91 \angle 14.04^\circ \text{ A}$



## 13.2 Mutual Inductance (14)

### Example Problem 13.1

First, replace with the model:

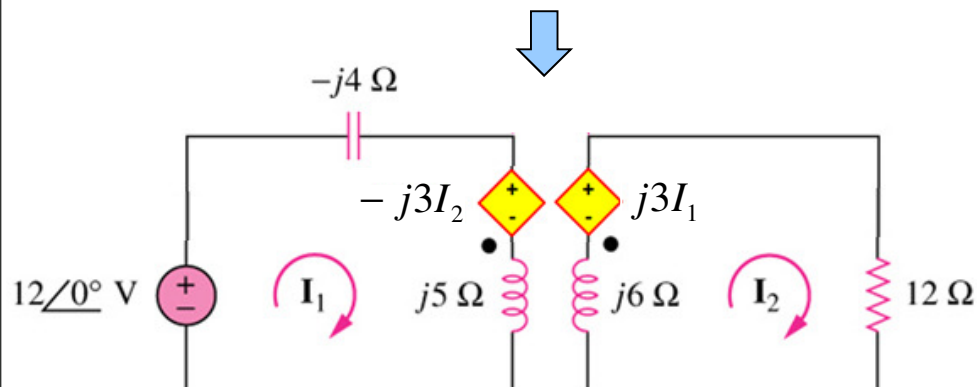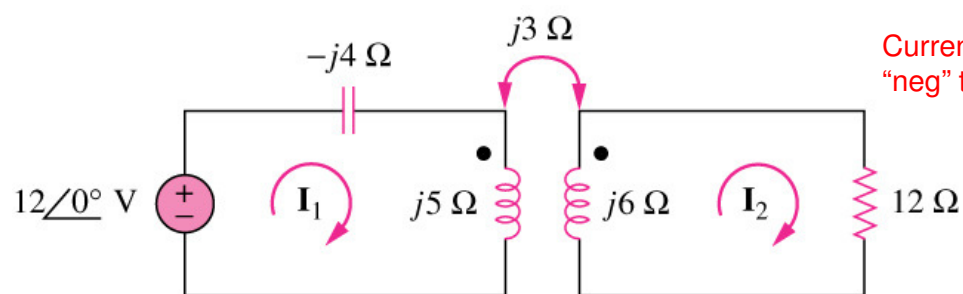

Then, solve Loop Equations:

Current enters "neg" terminal

Current enters "+" terminal but value is  $-j3I_2$

**Loop  $I_1$**

$$-12 - j4I_1 + (-j3I_2) + j5I_1 = 0$$

$$jI_1 - j3I_2 = 12$$

Current enters "neg" terminal

**Loop  $I_2$**

$$j6I_2 - j3I_1 + 12I_2 = 0$$

$$-j3I_1 + (12 + j6)I_2 = 0$$

NOTE:

$I_1$  goes "into" the dot  $\rightarrow$  Induced voltage on the second coil is "Positive"

$I_2$  goes "into" the un-dotted side  $\rightarrow$  Induced voltage on the first coil is "Negative"

**Pay Attention to Sign Conventions !**

## 13.2 Mutual Inductance (15)

### Example Problem 13.1

Lastly, solve 2 equations, 2 unknowns (expected you know this):

$$\text{Loop } I_1 \longrightarrow jI_1 - j3I_2 = 12 \longrightarrow jI_1 = 12 + j3I_2 \Rightarrow I_1 = 3I_2 - j12$$

$$\text{Loop } I_2 \longrightarrow -j3I_1 + (12 + j6)I_2 = 0 \quad I_1 = 3(2.824 + j0.706) - j12$$

$$\text{Substitution: } -3(12 + j3I_2) + (12 + j6)I_2 = 0$$

$$\div \text{ by } 3 \quad -12 - j3I_2 + (4 + j2)I_2 = 0$$

$$\text{Collect Terms: } (4 - j)I_2 = 12$$

$$\text{Solve for } I_2 \quad I_2 = \frac{12}{(4 - j)} = 2.824 + j0.706 = 2.91 \angle 14.04^\circ \text{ A}$$

Find  $I_1$  (Substitute back to Eq1)



$$I_1 = 8.471 + j2.118 - j12$$

$$I_1 = 8.471 - j9.882 = 13.02 \angle -49.40^\circ \text{ A}$$

Think about where we could have made mistakes!

- Applying the model incorrectly (wrong sign convention)
- Incorrect Phasor notation ( Understand:  $j\omega M \leftrightarrow j3$  ;  $j\omega L \leftrightarrow j5$  ;  $1/j\omega C \leftrightarrow -j4$  )
- Incorrect sign convention for loop equations
  - Current entering negative terminal of a voltage source
- Understanding of complex numbers!
  - Familiarity with your calculators handling of complex numbers
  - Converting from rectangular to polar


Review / Understand these concepts to avoid these mistakes

## 13.2 Recommended Viewing:

- Watch these videos illustrating solving mutual inductance problems:
  - <http://www.youtube.com/watch?v=tD35a-uzd34>
  - <http://www.youtube.com/watch?v=hzU4XKQYTWw>
  - <http://www.youtube.com/watch?v=OqSvesTtnUo>
- Uses the model described previously to solve mutual inductance problems.

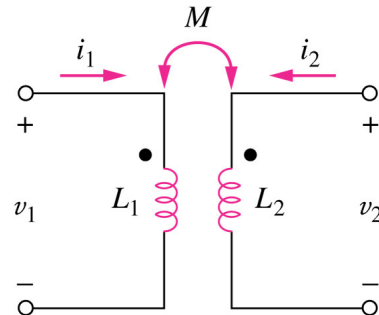
## 13.3 Energy in a Coupled Circuit (1)

- The instantaneous energy  $w$  stored in the circuit is:




$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

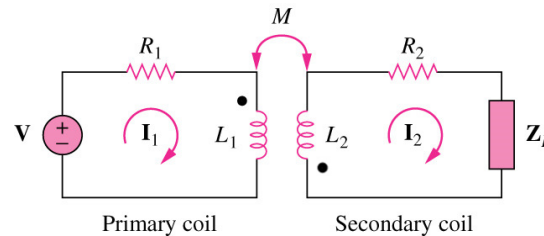- If **both** currents enter (or **both** leave) the dotted terminal the mutual term is (positive):



$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

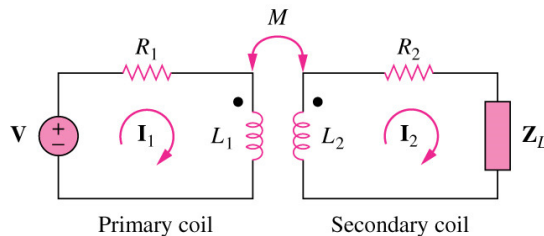- Otherwise the mutual term is (negative):



$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$

## 13.3 Energy in a Coupled Circuit (2)


- The coupling coefficient,  $k$ , is a measure of the magnetic coupling between two coils;  $0 \leq k \leq 1$ .

$$M = k\sqrt{L_1 L_2}$$


$K = 1$  coils perfectly coupled

$K < 0.5$  coils loosely coupled

$K > 0.5$  coils tightly coupled

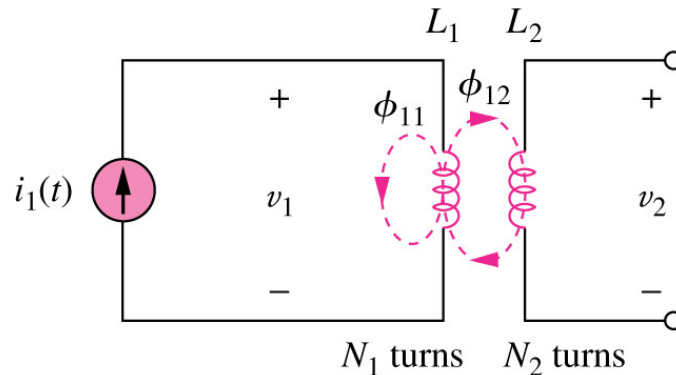
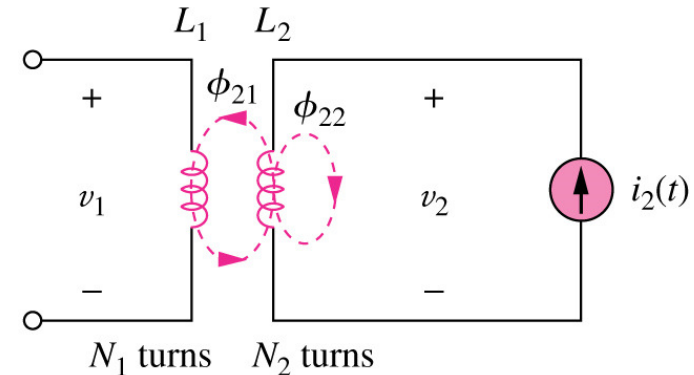
$$K = \frac{\phi_{12}}{\phi_{11} + \phi_{12}}$$




$$K = \frac{\phi_{21}}{\phi_{21} + \phi_{22}}$$

## 13.3 Energy in a Coupled Circuit (3)

### Example 13.3
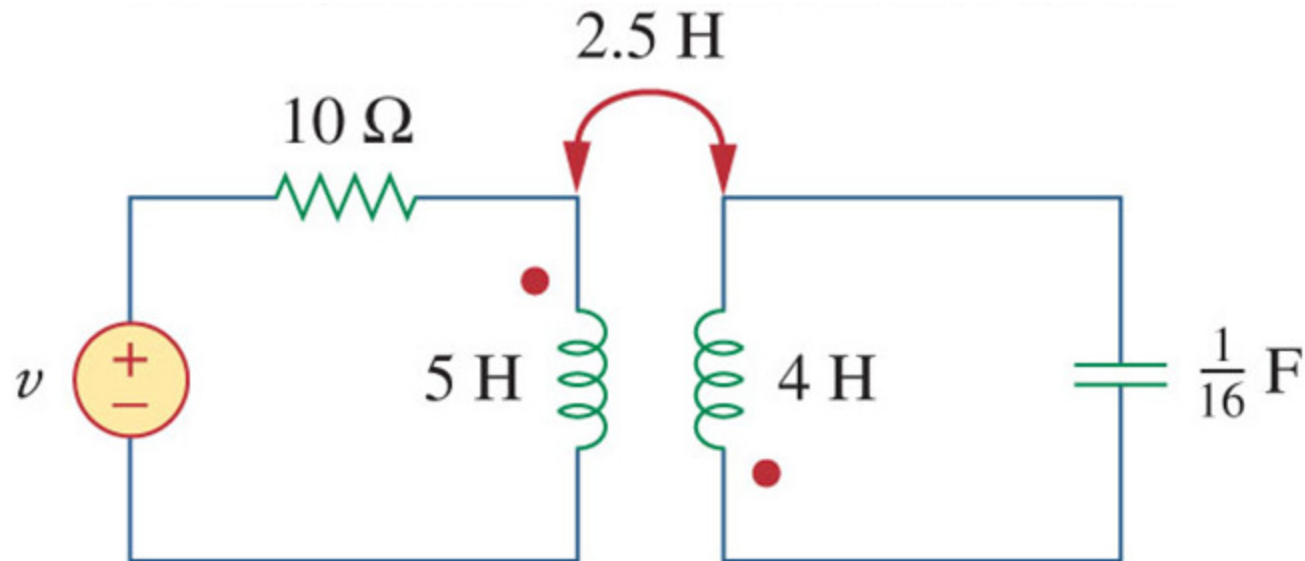
### Example 13.3 (Textbook)


Consider the circuit below. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time  $t = 1\text{ s}$  if  $v = 60\cos(4t + 30^\circ)\text{ V}$ .



Ans:  $k=0.56$ ;  $w(1)=20.73\text{ J}$

# 13.3 Energy in a Coupled Circuit (4)

## Example 13.3

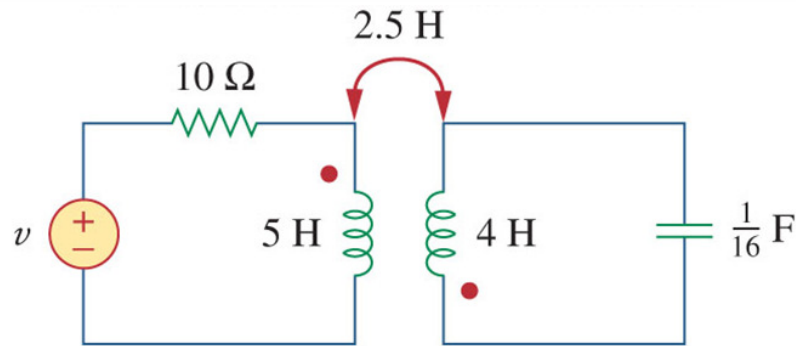


To find k, use the relation between  $L_1$ ,  $L_2$ , and  $M$ :

$$L_1 = 5 ; L_2 = 4 ; M = 2.5$$


$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2.5}{\sqrt{(5)(4)}} = 0.56$$

Apply the "Model"

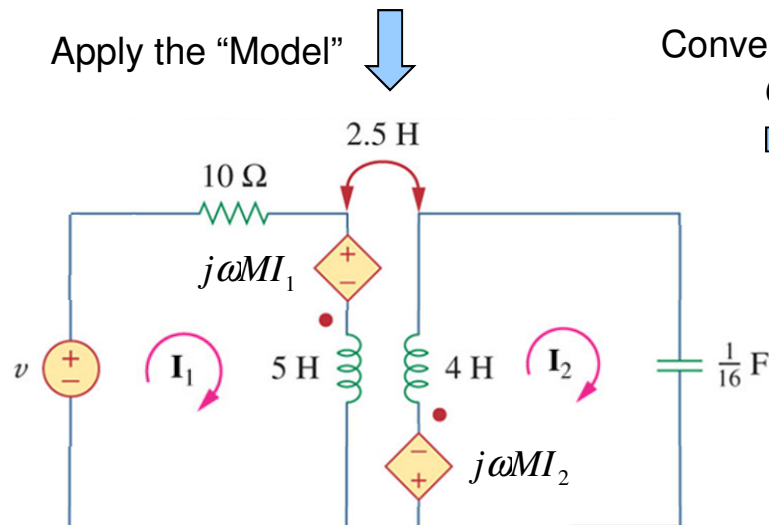

Convert to Phasor

$$\omega = 4$$

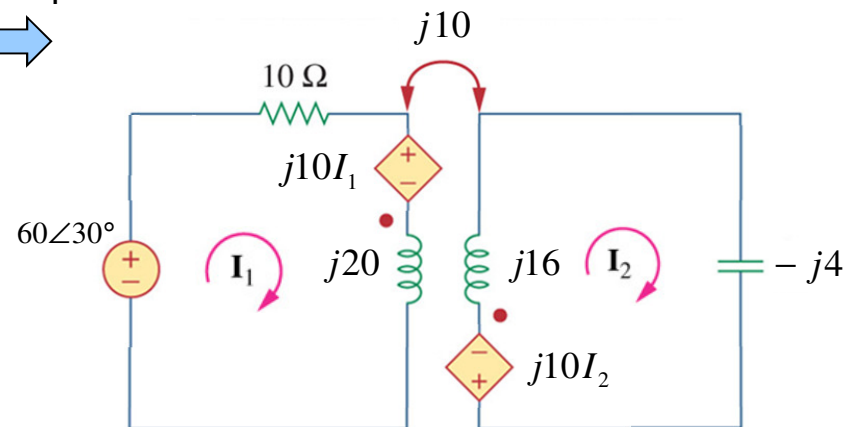

Solve Mesh equations for  $I_1$  and  $I_2$

## 13.3 Energy in a Coupled Circuit (5)

### Example 13.3

From Mesh analysis:

$$I_1 = 3.905 \angle -19.4^\circ \text{ A}$$

$$I_2 = 3.254 \angle 160.6^\circ \text{ A}$$

At  $t = 1$ , the value of  $\omega t = (4)(1) = 4$  radians =  $229.2^\circ$

To find the energy at  $t = 1$ :

$$i_1 = 3.905 \cos(\omega t - 19.4^\circ)$$

$$i_2 = 3.254 \cos(\omega t + 160.6^\circ)$$

$$i_1 = 3.905 \cos(229.2^\circ - 19.4^\circ) = -3.389$$

$$i_2 = 3.254 \cos(229.2^\circ + 160.6^\circ) = 2.824$$

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

Positive since current (as defined) enters **both** dots

$$w = \frac{1}{2} (5)(-3.389)^2 + \frac{1}{2} (4)(2.824)^2 + 2.5(-3.389)(2.824) = 20.73 \text{ J}$$



# Homework #2

Due in class Monday, January 26, 2015

- 13.1
- 13.7
- 13.9
- 13.24


# Chapter 13

## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers**
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers
- 13.9 Applications
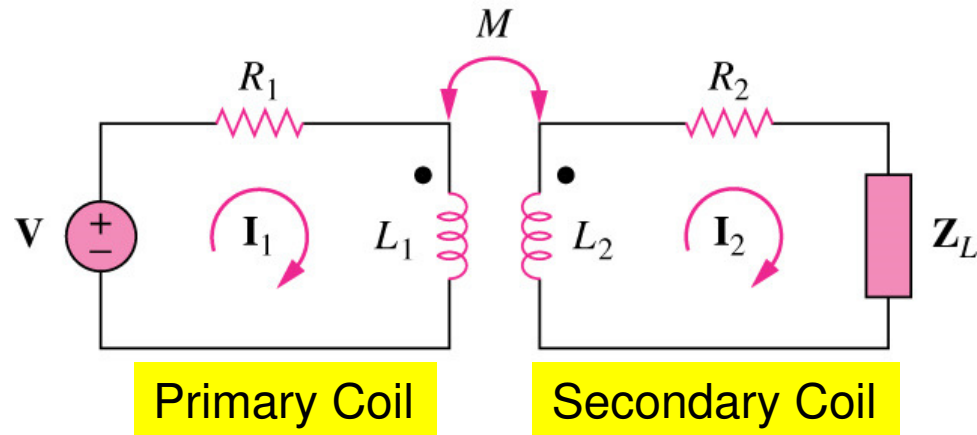
## 13.4 Linear Transformers (1)

- A transformer is generally a four-terminal device comprising two (or more) magnetically coupled coils. Below is a “simple” model:




- The coil connected to the voltage source is called the **primary winding**.
- The coil connected to the load is called the **secondary winding**.
- Resistances  $R_1$  and  $R_2$  are included to account for the losses in the coils.
- A transformer is said to be linear if the coils are wound on a magnetically linear material for which the permeability is constant.
  - Air, plastic, Bakelite, wood, etc.
  - Most materials are magnetically linear.

## 13.4 Linear Transformers (2)
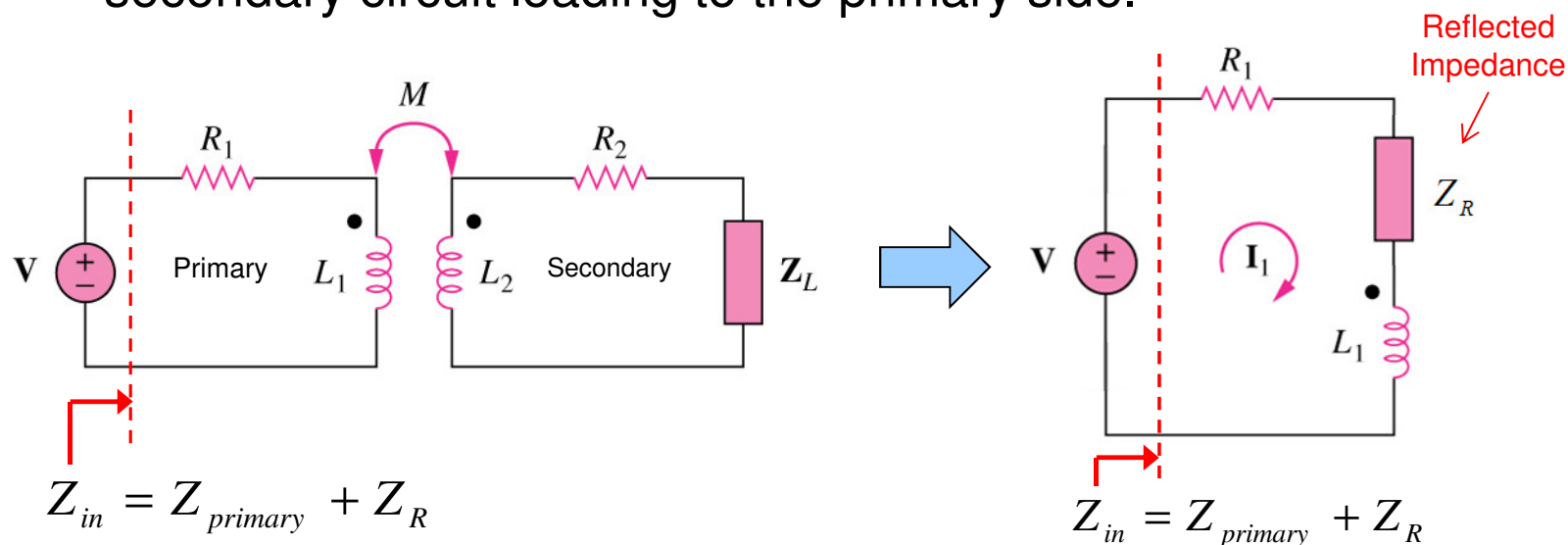
### Reflected Impedance


- Often we are interested in the input impedance  $Z_{in}$  seen by the source.
  - For example, may want to match  $Z_{in}$  to the source impedance for maximum power transfer!
- To simplify our analysis we can break  $Z_{in}$  up into:
  - $Z_{primary}$  -- The impedance of the “primary” circuit ( $Z_{primary} = R_1 + j\omega L_1$ )
  - $Z_R$  -- The “reflected” impedance back to the “primary”.
- The “reflected” impedance  $Z_R$  is the contribution of the secondary circuit loading to the primary side.



## 13.4 Linear Transformers (2)

### Reflected Impedance

To obtain the input impedance  $Z_{in}$  as seen from the source:

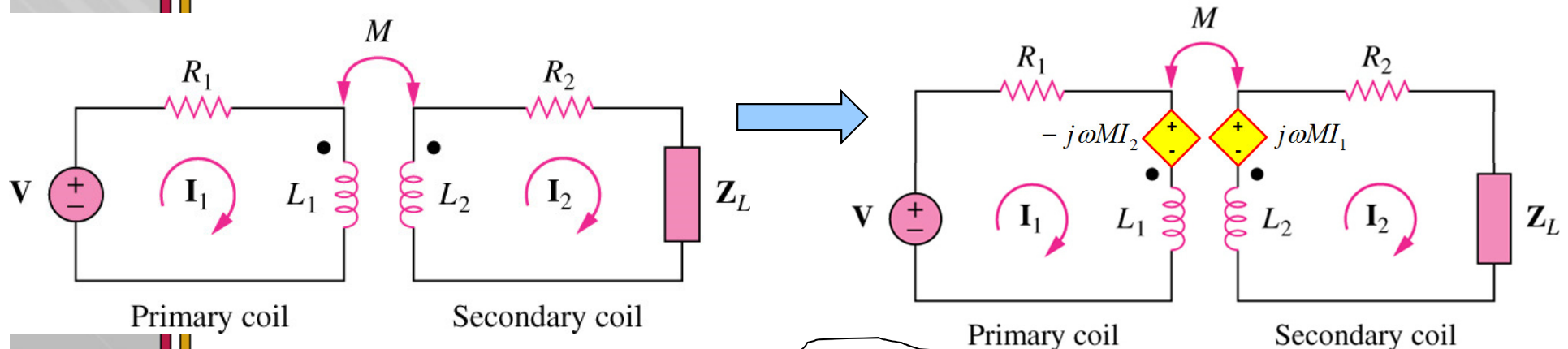

Mesh 1:  $V = (R_1 + j\omega L_1)I_1 - j\omega M I_2$  Current enters positive terminal so it is  $+$  ( $-j\omega M I_2$ )

Mesh 2:  $0 = -j\omega M I_1 + (R_2 + j\omega L_2 + Z_L)I_2$  Current enters negative terminal so it is  $-$  ( $j\omega M I_1$ )

From Mesh 2:

$$I_2 = \frac{j\omega M}{R_2 + j\omega L_2 + Z_L} I_1$$

Substituting into Mesh 1 gives:

$$V = (R_1 + j\omega L_1)I_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} I_1$$

**Reflected Impedance**


$$Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

$$V = Z_{primary} I_1 + Z_{reflected} I_1$$

# 13.4 Linear Transformers (3)

## Reflected Impedance (Another way of looking at it !)

Obtain input impedance  $Z_{in}$  as seen from the source:

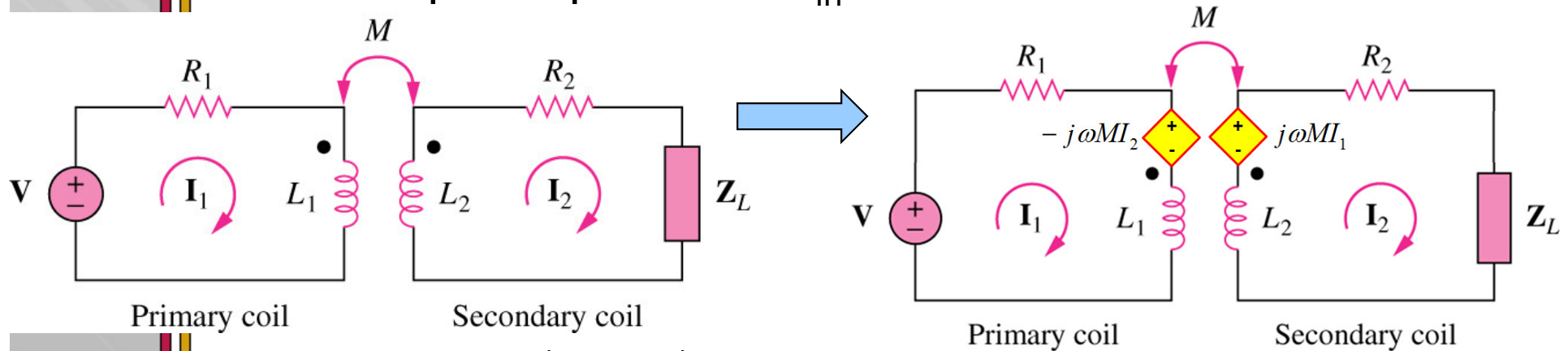

Mesh 1:  $V = (Z_{primary})I_1 - j\omega MI_2$

Mesh 2:  $0 = -j\omega MI_1 + (Z_{Secondary})I_2$

$Z_{Secondary}$  = the total series impedance in the secondary loop

From Mesh 2:

$$I_2 = \frac{j\omega M}{Z_{Secondary}} I_1$$

**Reflected Impedance**

$$Z_R = \frac{\omega^2 M^2}{Z_{Secondary}}$$

Substituting into Mesh 1 gives:


$$V = Z_{primary} I_1 + \frac{\omega^2 M^2}{Z_{Secondary}} I_1$$

$$V = Z_{primary} I_1 + Z_{reflected} I_1$$

## 13.4 Linear Transformers (4)
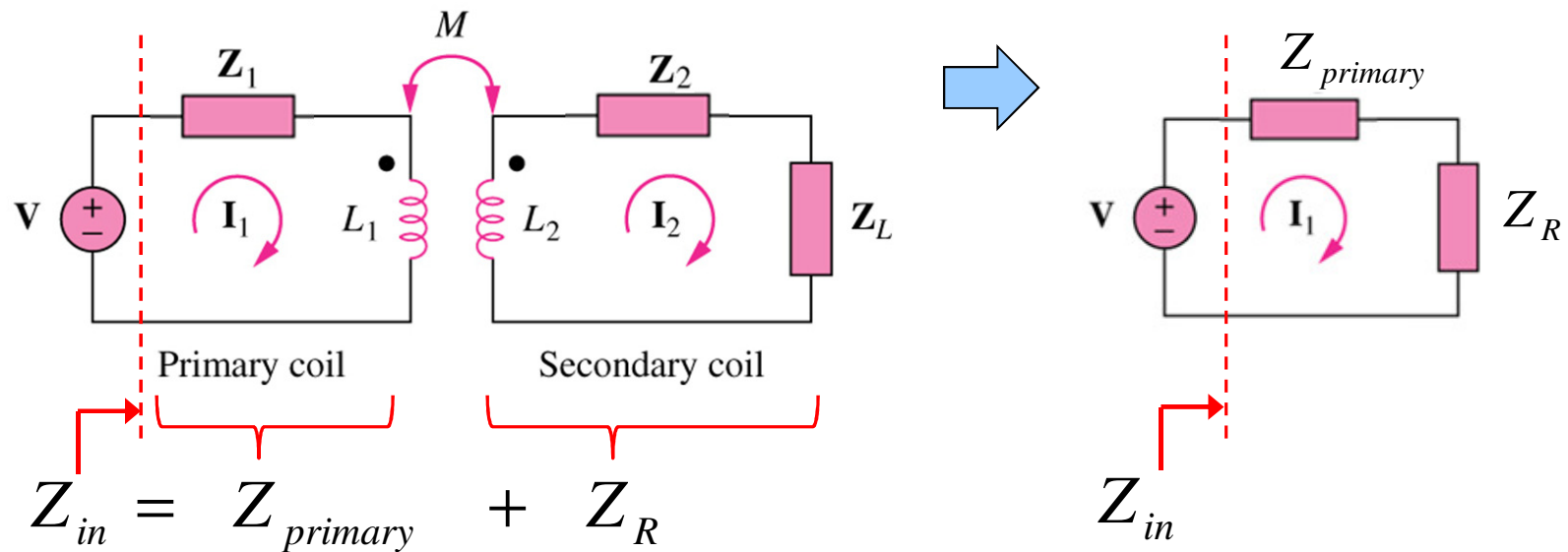
### Reflected Impedance

- The input impedance can be broken into two parts as follows:



- Series Impedance in Primary Coil:  $Z_{primary} = Z_1 + j\omega L_1$
- Series Impedance in Secondary Coil:  $Z_{secondary} = Z_2 + Z_L + j\omega L_2$
- Input Impedance:  $Z_{in} = Z_{primary} + \frac{\omega^2 M^2}{Z_{secondary}}$


*Note:  $Z_{in}$  will be the same if the dot on  $L_2$  is switched*

## 13.4 Linear Transformers (5)

### Example 13.4
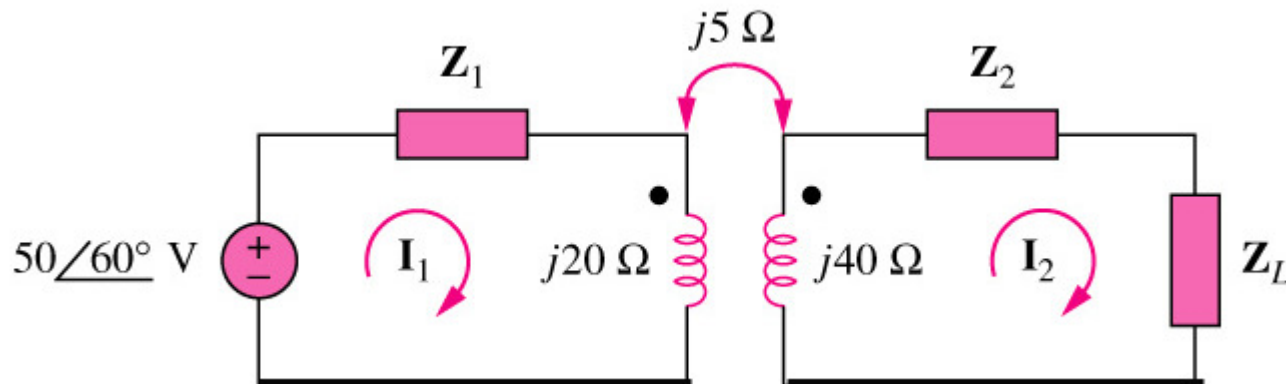
### Example 13.4 (textbook)

In the circuit below, calculate the input impedance and current  $I_1$ . Take  $Z_1=60-j100\Omega$ ,  $Z_2=30+j40\Omega$ , and  $Z_L=80+j60\Omega$ .




Ans:  $Z_{in} = 100.14\angle -53.1^\circ\Omega$ ;  $I_1 = 0.5\angle 113.1^\circ\text{A}$



## 13.4 Linear Transformers (5)

### Example 13.4

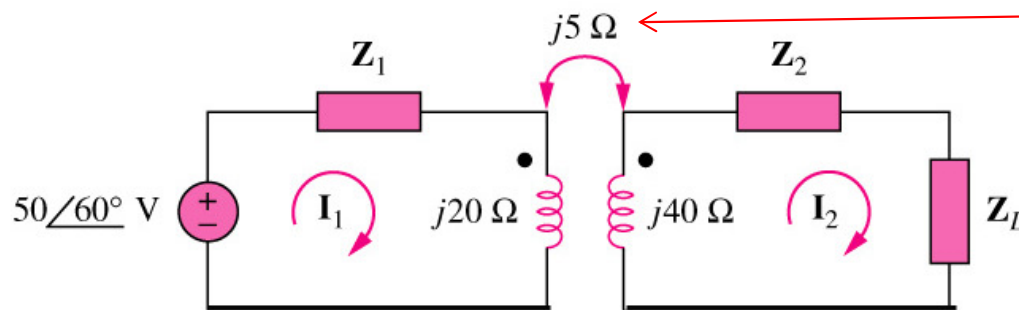

**Note:**

$$j\omega M = j5$$

$$\omega M = 5$$

$$(\omega M)^2 = 25$$

- The series impedance in the primary coil:

$$Z_{primary} = (60 - j100) + j20 = 60 - j80$$

- The series impedance in the secondary coil:

$$Z_{secondary} = (30 + j40) + (80 + j60) + j40 = 110 + j140$$

- Input Impedance given by:


$$Z_{in} = Z_{primary} + \frac{\omega^2 M^2}{Z_{Secondary}} = (60 - 80j) + \frac{25}{(110 + j140)} = 60.09 - j80.11$$

- Current  $I_1$  given by: 
$$I_1 = \frac{V_s}{Z_{in}} = \frac{50 \angle 60^\circ}{60.09 - j80.11} = \frac{50 \angle 60^\circ}{100.14 \angle -53.1^\circ}$$


## 13.4 Linear Transformers (6)
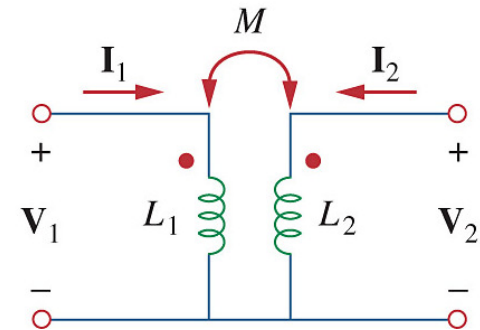
### Equivalent T and $\pi$ Circuits:


- It is sometimes convenient to replace a magnetically coupled circuit with an equivalent circuit with no magnetic coupling.
- We can replace the linear transformer with an equivalent T or  $\pi$  circuit that has no mutual inductance.



T Circuit

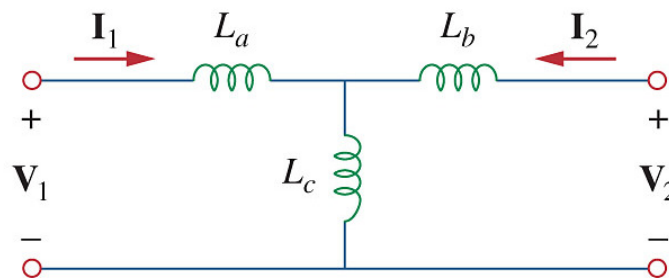


$\pi$  Circuit

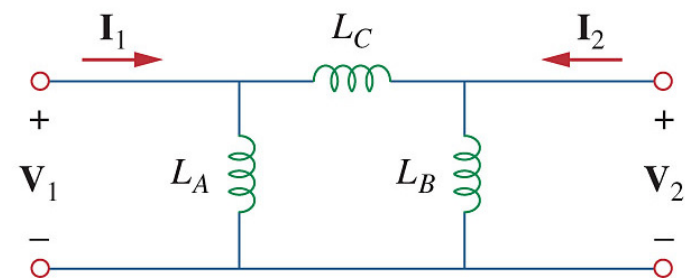

## 13.4 Linear Transformers (7)

### Equivalent T Circuit:


Linear Transformer Circuit

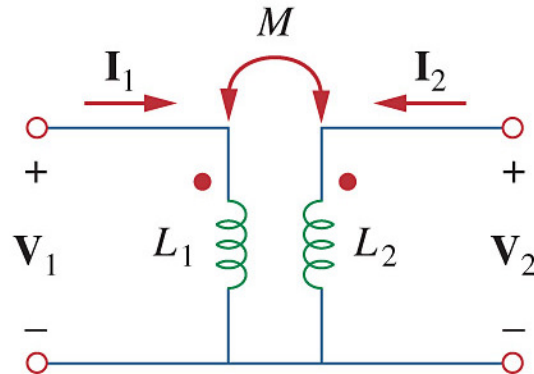

Mesh Analysis of this transformer circuit results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Equivalent T Network

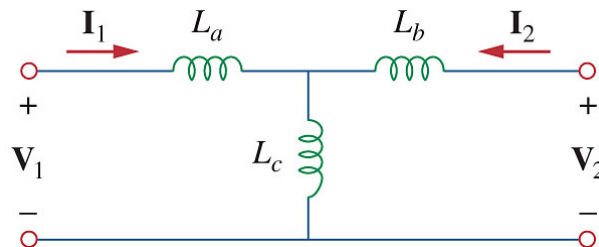

Mesh Analysis of the equivalent T network results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


Equating the terms gives the following relationships:

$$L_a = L_1 - M \quad L_b = L_2 - M \quad L_c = M$$

## 13.4 Linear Transformers (8)

### Equivalent T Circuits (Swapped Dots):


Linear Transformer Circuit

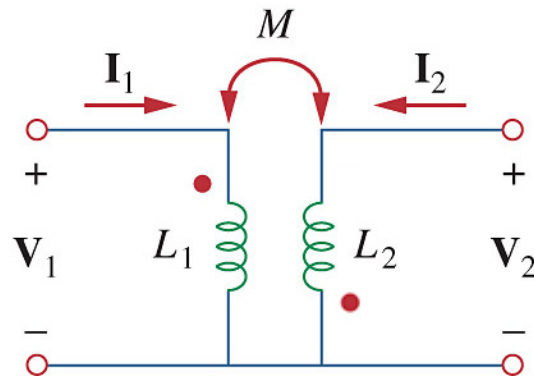

Mesh Analysis of this transformer circuit results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & -j\omega M \\ -j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Equivalent T Network

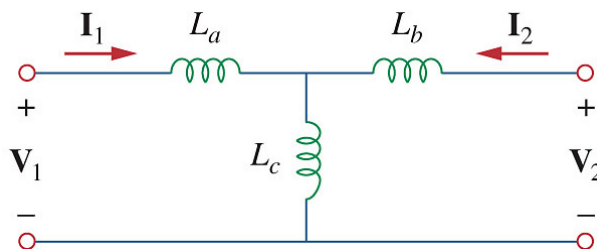

Mesh Analysis of the equivalent T network results in the following:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


Equating the terms gives the following relationships:

$$L_a = L_1 + M \quad L_b = L_2 + M \quad L_c = -M$$

## 13.4 Linear Transformers (9)

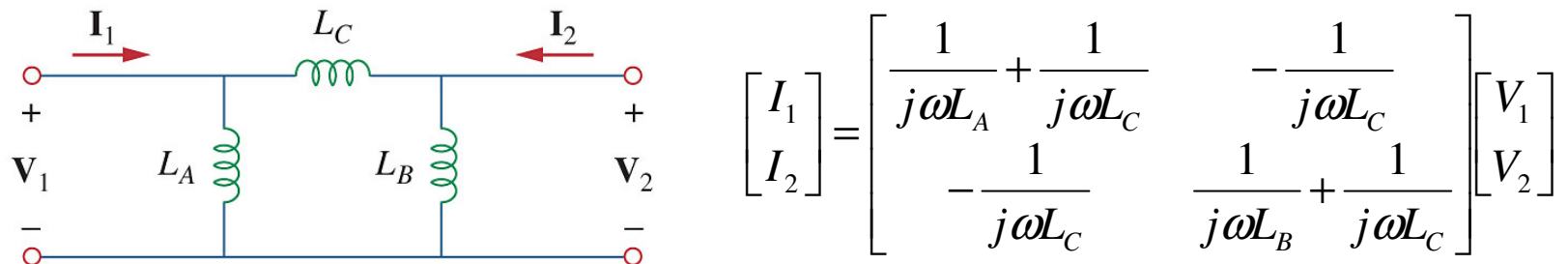
### Equivalent $\pi$ Circuit:

Similarly, for the  $\pi$  network nodal analysis provides:




Equivalent  $\pi$  Network

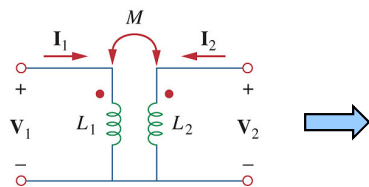By equating terms in admittance matrices, for the  $\pi$  equivalent network we obtain (note if dots are different, replace with  $-M$ ):



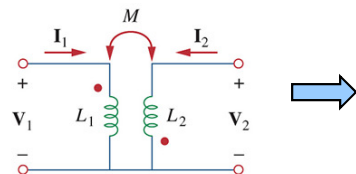
$$L_A = \frac{L_1 L_2 - M^2}{L_2 - M} ; L_B = \frac{L_1 L_2 - M^2}{L_1 - M} ; L_C = \frac{L_1 L_2 - M^2}{M}$$




$$L_A = \frac{L_1 L_2 - M^2}{L_2 + M} ; L_B = \frac{L_1 L_2 - M^2}{L_1 + M} ; L_C = \frac{L_1 L_2 - M^2}{-M}$$

# 13.4 Linear Transformers (10)


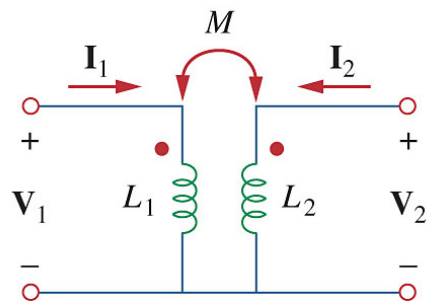
## Equivalent T or $\pi$ Circuits Summary




T Circuit

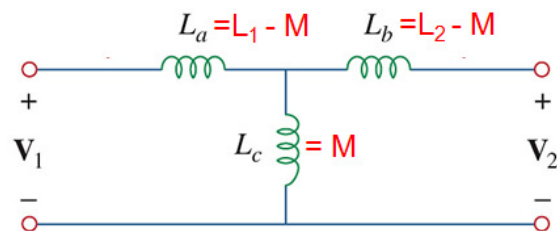


$\pi$  Circuit

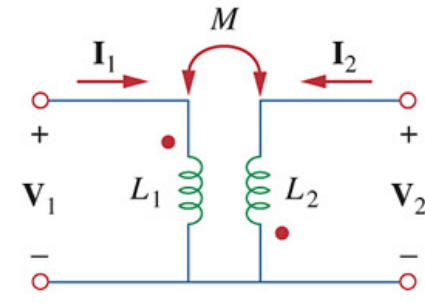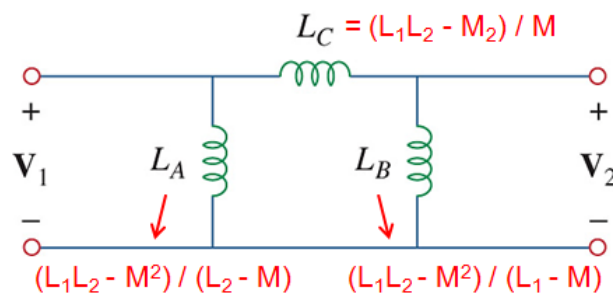

T Circuit

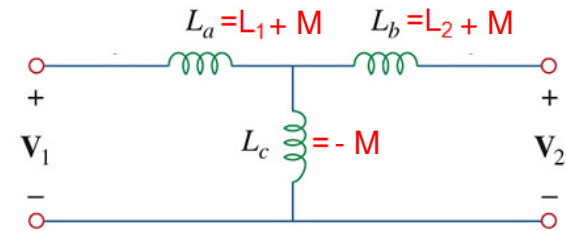



$\pi$  Circuit

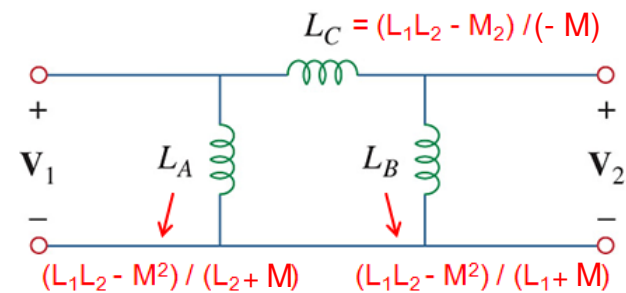

# 13.4 Linear Transformers (11)
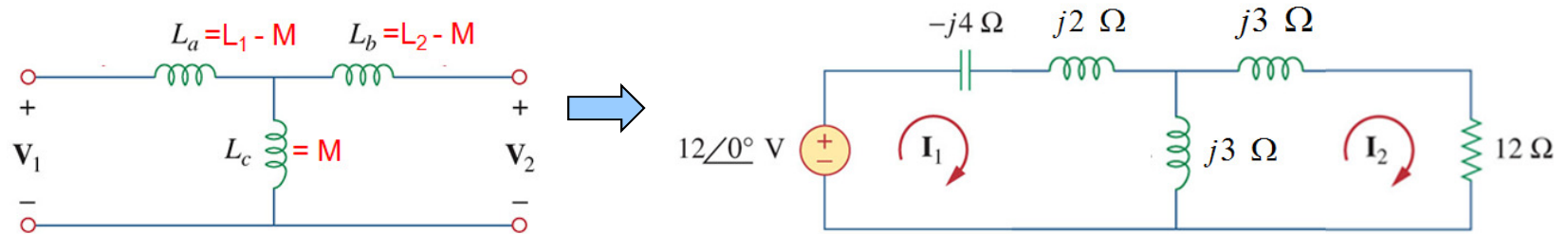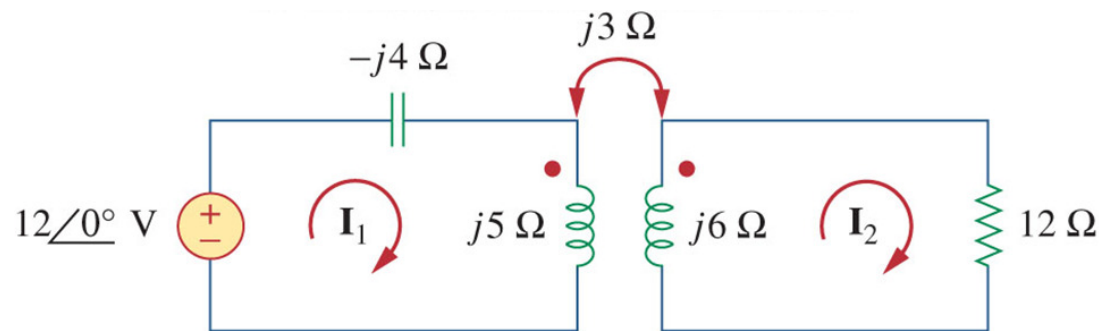
## Practice Problem 13.6

Find  $I_1$  and  $I_2$  using the T equivalent circuit



$$\text{Mesh } I_1: -12\angle 0^\circ - j4I_1 + j2I_1 + j3(I_1 - I_2) = 0 \qquad jI_1 - j3I_2 = 12\angle 0^\circ$$

$$\text{Mesh } I_2: j3(I_2 - I_1) + j3I_2 + 12I_2 = 0 \qquad -j3I_1 + (12 + j6)I_2 = 0$$

# Chapter 13



## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers**
- 13.6 Ideal Autotransformers
- 13.9 Applications


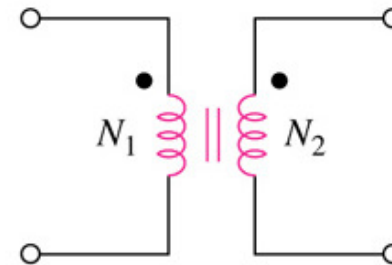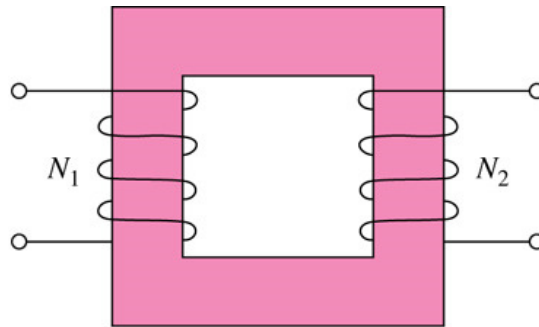
## 13.5 Ideal Transformers (1)

- An ideal transformer has perfect coupling ( $k=1$ ).
- It consists of two or more coils with a large number of turns wound on a common core of high permeability.



- Because of the high permeability of the core, the flux links all the turns of both coils, thereby resulting in a perfect coupling.

## 13.5 Ideal Transformers (2)

“Dot’s the same polarity”

Recall the coupled circuit:

$$V_1 = j\omega L_1 I_1 + j\omega M I_2 \quad (1)$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2 \quad (2)$$


Solving for  $I_1$  in (1):  $I_1 = \frac{V_1 - j\omega M I_2}{j\omega L_1} \quad (3)$

Substituting (3) into (2):  $V_2 = j\omega L_2 I_2 + \frac{M V_1}{L_1} - \frac{j\omega M^2 I_2}{L_1}$

$M = \sqrt{L_1 L_2}$  For perfect coupling ( $k=1$ ):

$$V_2 = j\omega L_2 I_2 + \frac{\sqrt{L_1 L_2} V_1}{L_1} - \frac{j\omega L_1 L_2 I_2}{L_1} = \sqrt{\frac{L_2}{L_1}} V_1 = n V_1$$

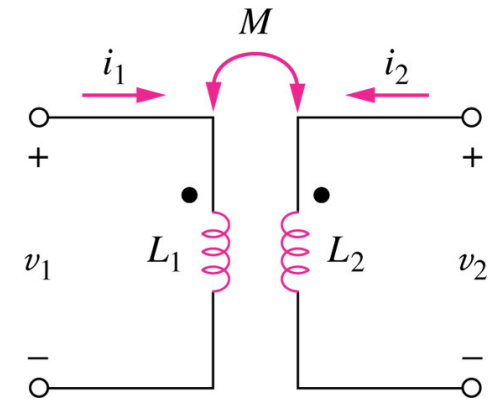Therefore:  $V_2 = n V_1$  where  $n = \sqrt{L_2 / L_1}$  = turns ratio



## 13.5 Ideal Transformers (3)

“Dot’s opposite each other”

Mesh Equations give the following:

$$V_1 = j\omega L_1 I_1 - j\omega M I_2 \quad (1)$$

$$V_2 = -j\omega M I_1 + j\omega L_2 I_2 \quad (2)$$


Solving for  $I_1$  in (1):  $I_1 = \frac{V_1 + j\omega M I_2}{j\omega L_1} \quad (3)$

Substituting (3) into (2):  $V_2 = j\omega L_2 I_2 - \frac{M V_1}{L_1} - \frac{j\omega M^2 I_2}{L_1}$

$M = \sqrt{L_1 L_2}$  For perfect coupling ( $k=1$ ):

$$V_2 = j\omega L_2 I_2 - \frac{\sqrt{L_1 L_2} V_1}{L_1} - \frac{j\omega L_1 L_2 I_2}{L_1} = -\sqrt{\frac{L_2}{L_1}} V_1 = -n V_1$$

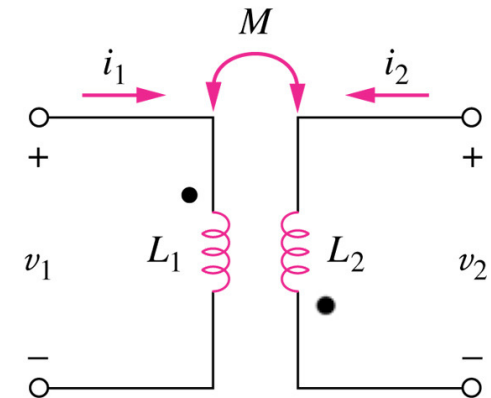Therefore:  $V_2 = -n V_1$  If dot is swapped at output




## 13.5 Ideal Transformers (4)

### Properties

- A transformer is said to be **ideal** if it has the following properties:
  1. Coils have very large reactances ( $L_1, L_2, M \rightarrow \infty$ )
  2. Coupling coefficient is equal to unity ( $k=1$ )
  3. Primary and secondary coils are lossless ( $R_1 = R_2 = 0$ )
- An ideal transformer is a unity-coupled ( $k=1$ ) lossless transformer in which the primary and secondary coils have infinite self-inductances ( $L_1 \& L_2 \rightarrow \infty$ ).
- Iron core transformers are close approximations to ideal transformers and are used in power systems and electronics.
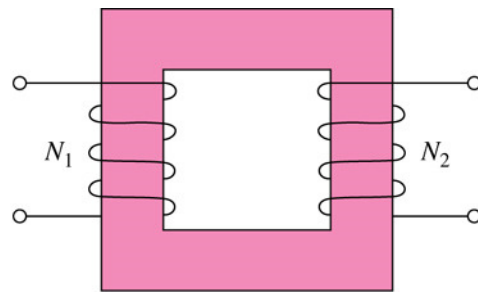
## 13.5 Ideal Transformers (5)

- When a sinusoidal voltage is applied to the primary winding, the same magnetic flux  $\Phi$  goes through both windings.



$$v_1 = N_1 \frac{d\phi}{dt} \quad ; \quad v_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = n = \text{Turns ratio or transformation ratio}$$

- Using the phasor voltages rather than the instantaneous voltages:


$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$

## 13.5 Ideal Transformers (6)

- Power conservation:  $v_1 i_1 = v_2 i_2$
- The energy supplied to the primary must equal the energy absorbed by the secondary, since there are no losses in an ideal transformer.

- In phasor form:
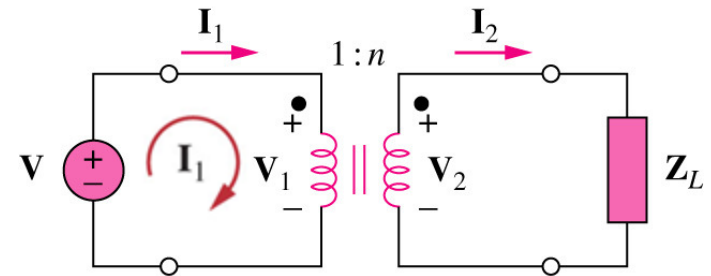
$$\frac{I_1}{I_2} = \frac{V_2}{V_1} = n$$



- $n=1 \rightarrow$  isolation transformer ( $V_2 = V_1$ )
- $n>1 \rightarrow$  step-up transformer ( $V_2 > V_1$ )
- $n<1 \rightarrow$  step-down transformer ( $V_2 < V_1$ )


## 13.5 Ideal Transformers (7)

- Transformer ratings are usually specified as  $V_1 / V_2$
- Power companies often generate at some convenient voltage and use the step-up transformer to increase the voltage so that the power can be transmitted at very high voltage and low current over transmission lines, resulting in significant cost savings. Near residential consumers, step-down transformers are used to bring the voltage down to 120 V.
- It is important to get the proper polarity of the voltages and the direction of the currents for the transformer.
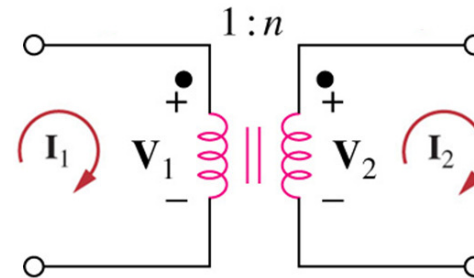
# 13.5 Ideal transformers (8)


V and I relationships (simpler way to remember)

Given this standard  
definition for Voltages  
and currents




**Note:** This definition  
of  $I_2$  differs from the  
text.

Dots "Same" → "+"

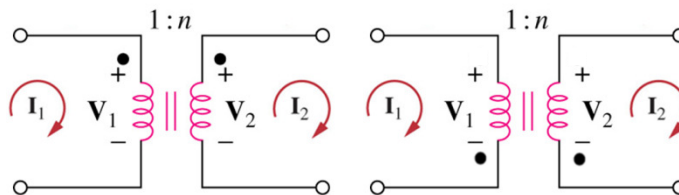

Dots "Different" → "-"

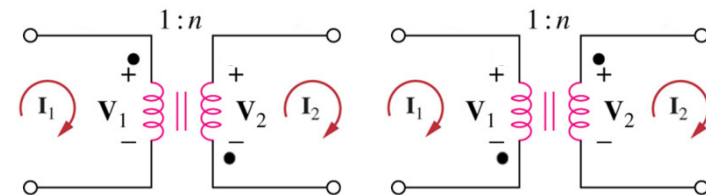

$$V_2 = nV_1$$

$$I_2 = \frac{I_1}{n}$$

$$Z_{in} = \frac{Z_L}{n^2}$$

Reflected  
Impedance →

*Note: The larger the turns ratio  
The larger "n"  
The larger "N<sub>2</sub>"  
The larger V<sub>2</sub>*

**Turns Ratio**

$$n = \frac{N_2}{N_1}$$

$$V_2 = -nV_1$$

$$I_2 = -\frac{I_1}{n}$$


$$Z_{in} = \frac{Z_L}{n^2}$$



## 13.5 Ideal Transformers (9)
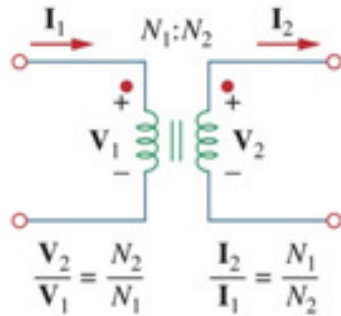
### V and I relationships

- Expressing  $V_1$  in terms of  $V_2$  and  $I_1$  in terms of  $I_2$  or vice versa:



$$V_1 = \frac{V_2}{n} \quad V_2 = nV_1$$

$$I_2 = \frac{I_1}{n} \quad I_1 = nI_2$$

Positive, if Voltage “**same**” polarity at dot

Positive, if current “**different**” polarity at dot

- Complex Power is:

$$S_1 = V_1 I_1^* = \frac{V_2}{n} (nI_2)^* = V_2 I_2^* = S_2$$


Complex Conjugate of  $I_2$

- Complex power supplied to the primary is delivered to the secondary without loss.
- The ideal transformer is **lossless** and absorbs **no power**.

## 13.5 Ideal Transformers (10)
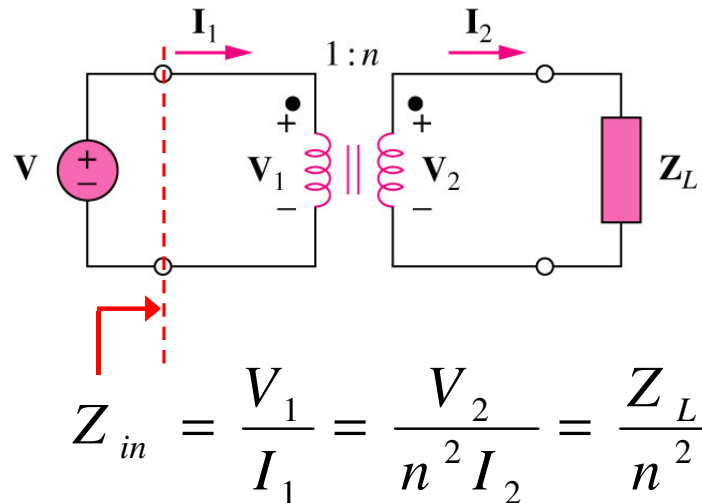
### Reflected impedance

- The input impedance as seen by the source is:




- The input impedance is also called the reflected impedance since it appears as if the load impedance is reflected to the primary side.
- The ability of the transformer to transform a given impedance to another allows impedance matching to ensure maximum power transfer.

## 13.5 Ideal Transformers (11)
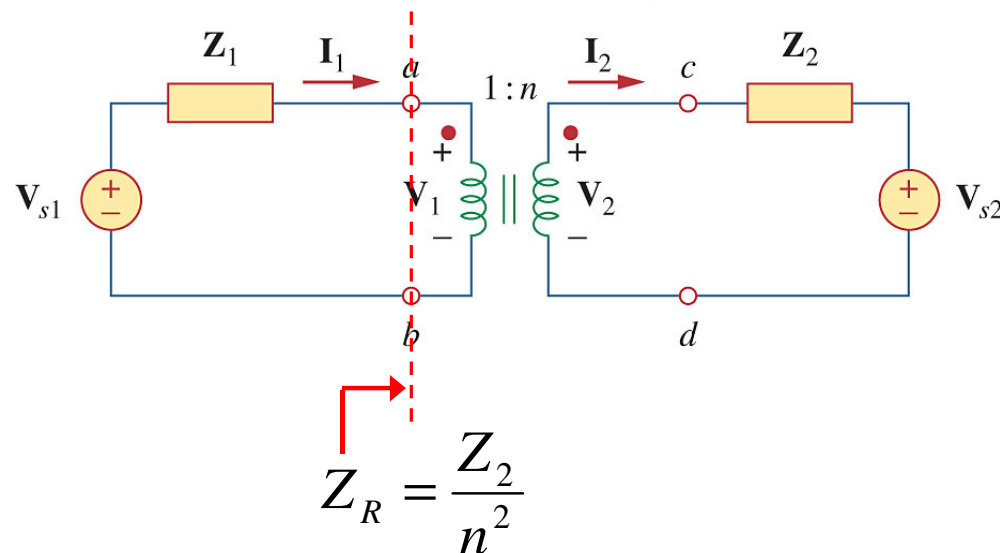
### Equivalent circuit analysis


- In analyzing a circuit containing an ideal transformer, it is common practice to eliminate the transformer by reflecting impedances and sources from one side of the transformer to the other.
- Suppose we want to reflect the secondary side of the circuit to the primary side:



# 13.5 Ideal Transformers (12)
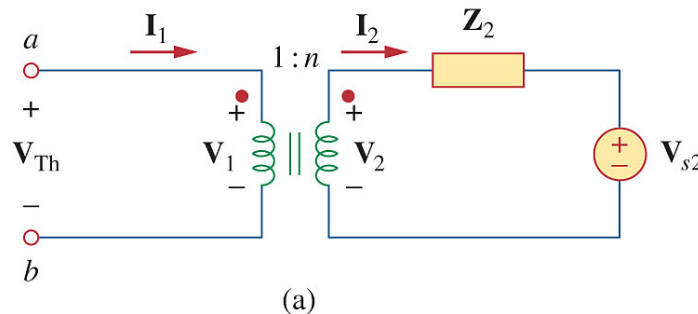
## Equivalent circuit analysis

- We find the Thevenin equivalent of the circuit to the right of a-b:
- Obtaining  $V_{th}$  from “open circuit voltage”:





$$I_1 = 0 = I_2 \quad \text{Since a-b is open}$$

$$V_2 = V_{s2}$$


$$V_{Th} = V_1 = \frac{V_2}{n} = \frac{V_{s2}}{n}$$

- Obtaining  $Z_{Th}$  (remove the voltage source in the secondary and insert a unit source at a-b terminals.)
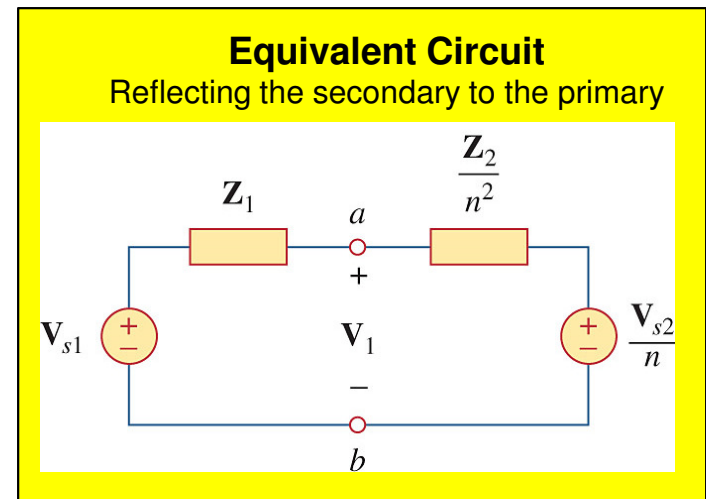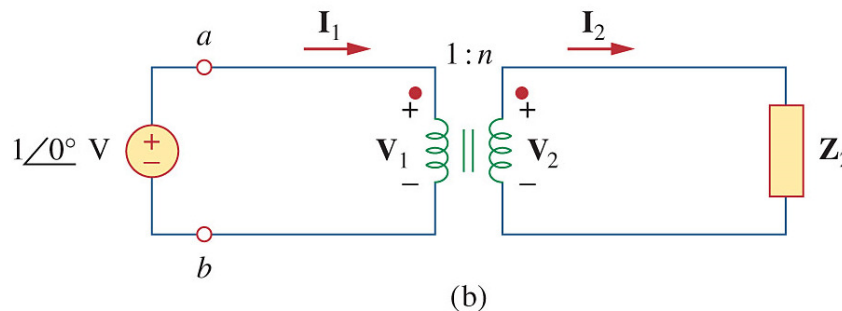
$$Z_{Th} = \frac{V_1}{I_1} = \frac{V_2}{n^2 I_2} = \frac{Z_2}{n^2}$$




## 13.5 Ideal Transformers (13)

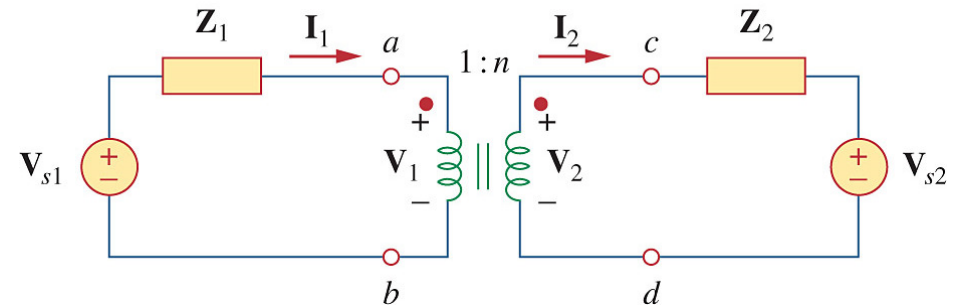


- The general rule for eliminating the transformer and reflecting the secondary circuit to the primary side:

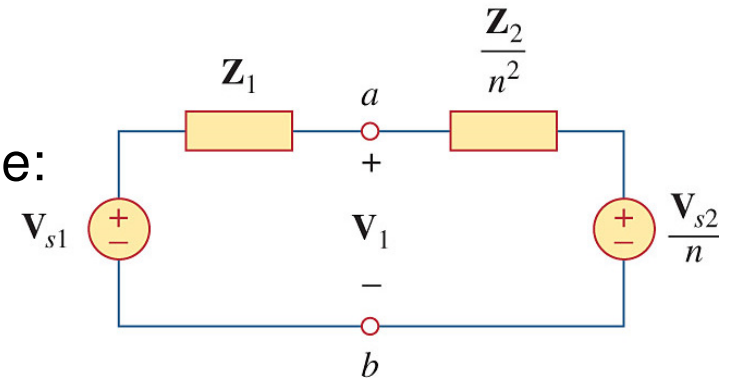- Divide the secondary impedance by  $n^2$
- Divide the secondary voltage by  $n$
- Multiply the secondary current by  $n$



- The general rule for eliminating the transformer and reflecting the secondary circuit to the primary side:

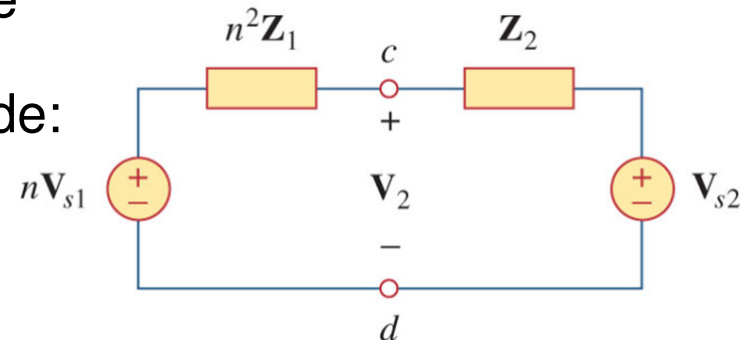
- Multiply the primary impedance by  $n^2$
- Multiply the primary voltage by  $n$
- Divide the primary current by  $n$




## 13.5 Ideal Transformer (14)
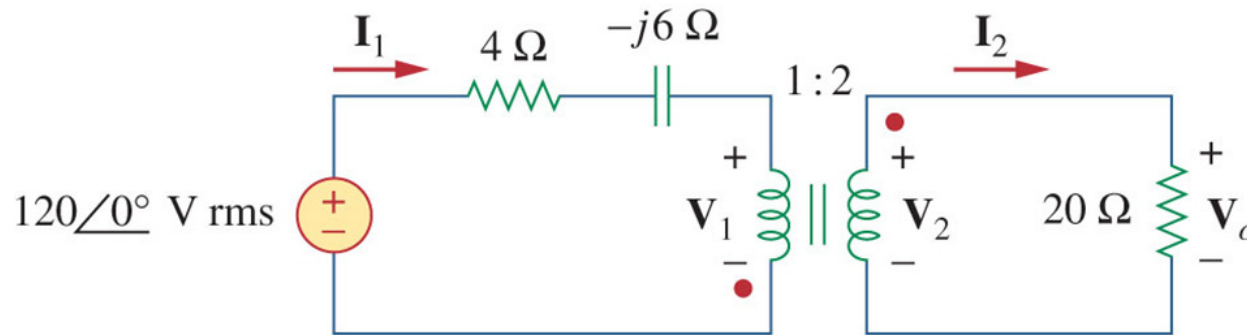
### Example 13.8 (Textbook)

For the ideal transformer, find: (a) the source current  $I_1$ , (b) the output voltage  $V_o$ , and (c) the complex power supplied by the source



## 13.5 Ideal Transformer (14)

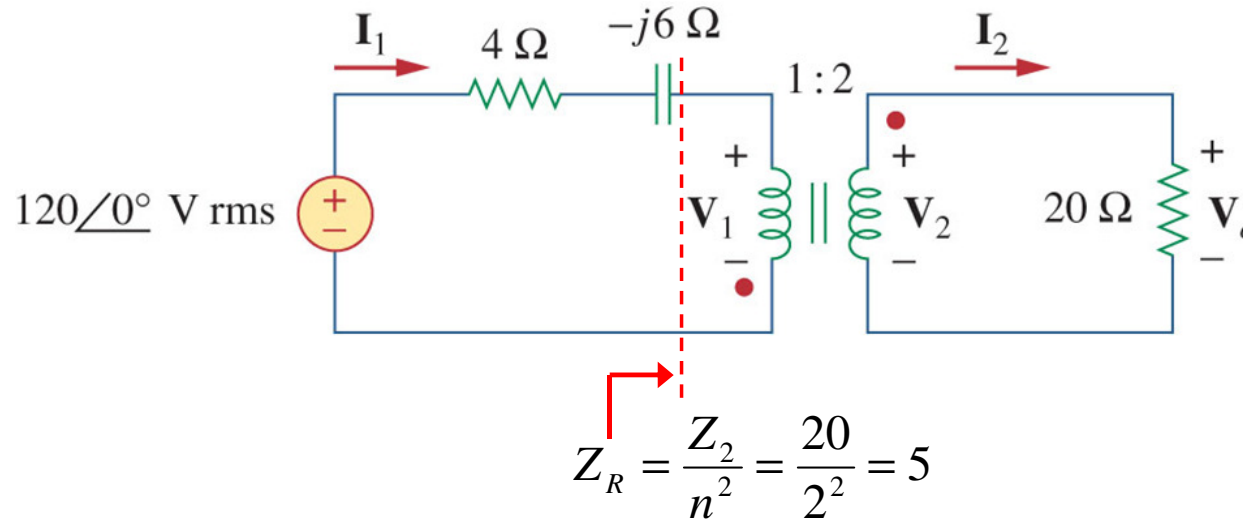

Impedance seen by the Voltage source is:

$$Z_{in} = (4 - j6) + 5 = 9 - j6 = 10.82 \angle -33.69^\circ \Omega$$

Input current  $I_1$  is:

$$I_1 = \frac{V_s}{Z_{in}} = \frac{120 \angle 0^\circ}{10.82 \angle -33.69^\circ} = 11.09 \angle 33.69^\circ \text{ A}$$

$$I_2 = -\frac{I_1}{n} = \frac{-11.09 \angle 33.69^\circ}{2} = 5.55 \angle -146.31^\circ \text{ A}$$

$$V_o = 20I_2 = 20(5.55 \angle -146.31^\circ) = 110.9 \angle -146.31^\circ \text{ V}$$

# Chapter 13


## Magnetically Coupled Circuits

- 13.1 What is a transformer?
- 13.2 Mutual Inductance
- 13.3 Energy in a Coupled Circuit
- 13.4 Linear Transformers
- 13.5 Ideal Transformers
- 13.6 Ideal Autotransformers**
- 13.9 Applications**



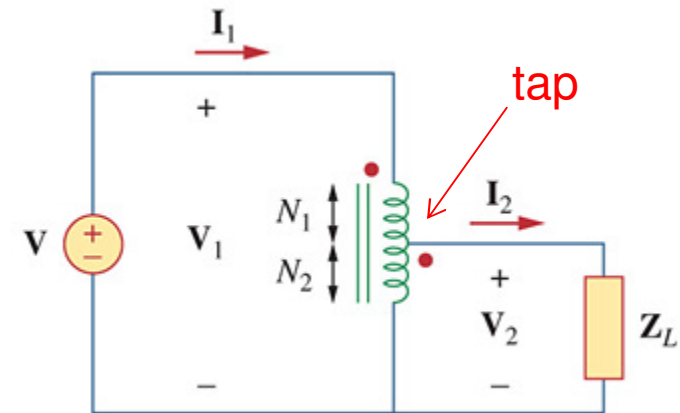
## 13.6 Ideal Auto-Transformers (1)

- An **autotransformer** is a transformer in which both the primary and the secondary are in a single winding
- A connection point called a *tap* separates the primary and secondary.
- The tap is often adjustable to provide a desired turns ratio.
- An adjustable tap provides a variable voltage to the load
- A disadvantage of the autotransformer is it provides *no electrical isolation*




Step Down Auto-Transformer

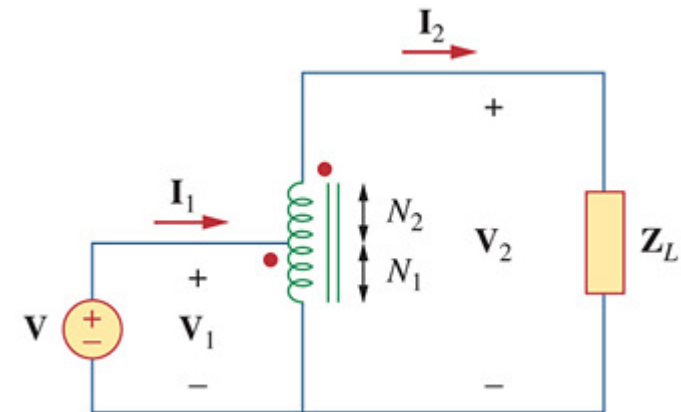

Step Up Auto-Transformer
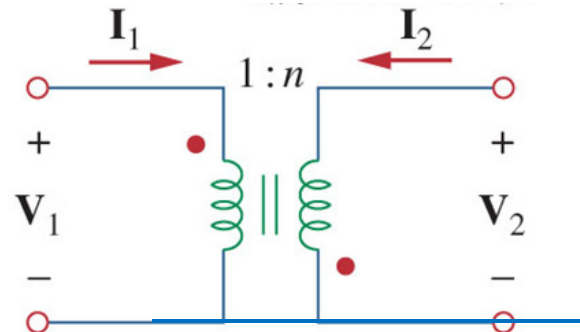
## 13.6 Ideal Auto-Transformers (2)


- In analyzing the autotransformer, consider the following circuit:



From earlier we know the following relationship

$$V_2 = -nV_1$$

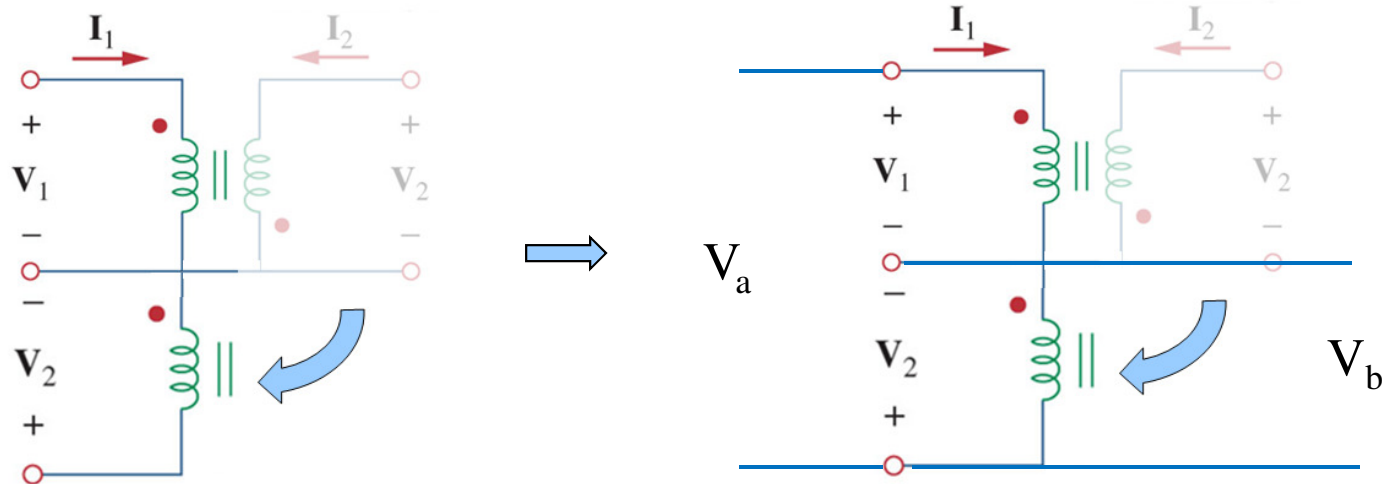- If we flip the secondary side underneath the primary, we can create an autotransformer as shown



## 13.6 Ideal Auto-Transformers (3)


- Analysis of this circuit provides the following results:

Primary Side

$$V_a = V_1 - V_2$$

$$V_a = V_1 + nV_1$$

$$V_a = (1+n)V_1$$

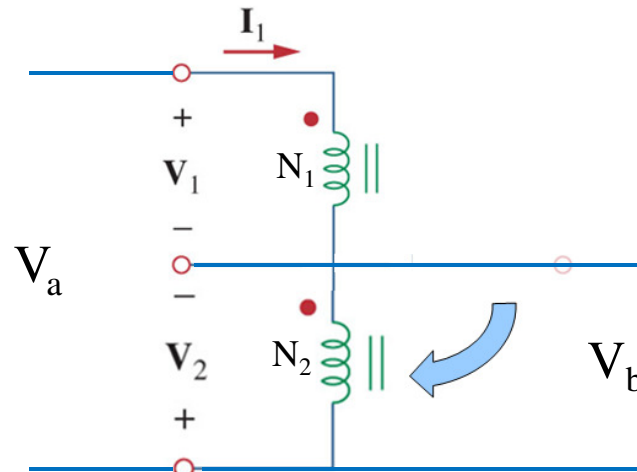

Secondary Side

$$V_b = -V_2 = nV_1$$

Ratio Primary/Secondary


$$\frac{V_a}{V_b} = \frac{1+n}{n} = \frac{N_1 + N_2}{N_2} \quad \Rightarrow$$

Notice, this looks like  
a Voltage Divider !


$$V_b = \left( \frac{N_2}{N_1 + N_2} \right) V_a$$
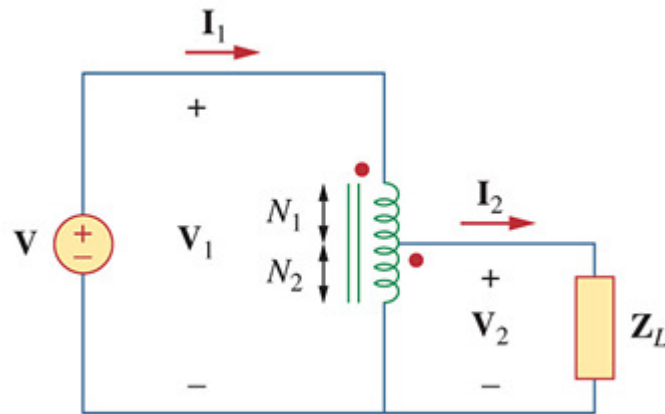
## 13.6 Ideal Auto-Transformers (4)

- The voltage / current relationships for the lossless ideal autotransformer are as follows:



Step Down Auto-Transformer

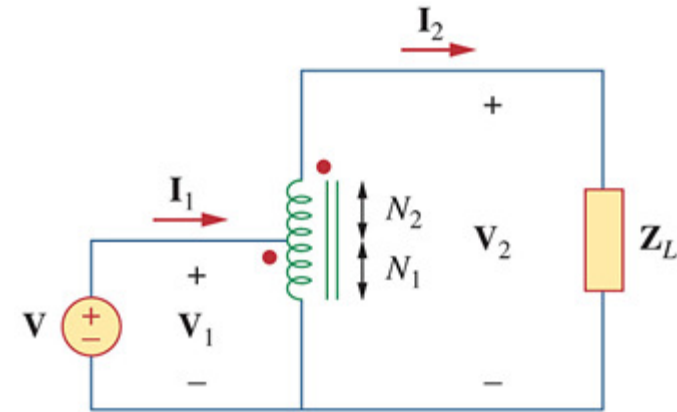

Step Up Auto-Transformer

$$V_2 = \frac{N_2}{N_1 + N_2} V_1$$

Similar to  
Voltage Divider  
equation

$$V_2 = \frac{N_1 + N_2}{N_1} V_1$$

$$I_2 = \frac{N_1 + N_2}{N_2} I_1$$

Inverse Relation

$$I_2 = \frac{N_1}{N_1 + N_2} I_1$$

$$Z_{in} = \left( \frac{N_1 + N_2}{N_2} \right)^2 Z_L$$


Derive from V/I

$$Z_{in} = \left( \frac{N_1}{N_1 + N_2} \right)^2 Z_L$$

## 13.6 Ideal Auto-Transformers (5)



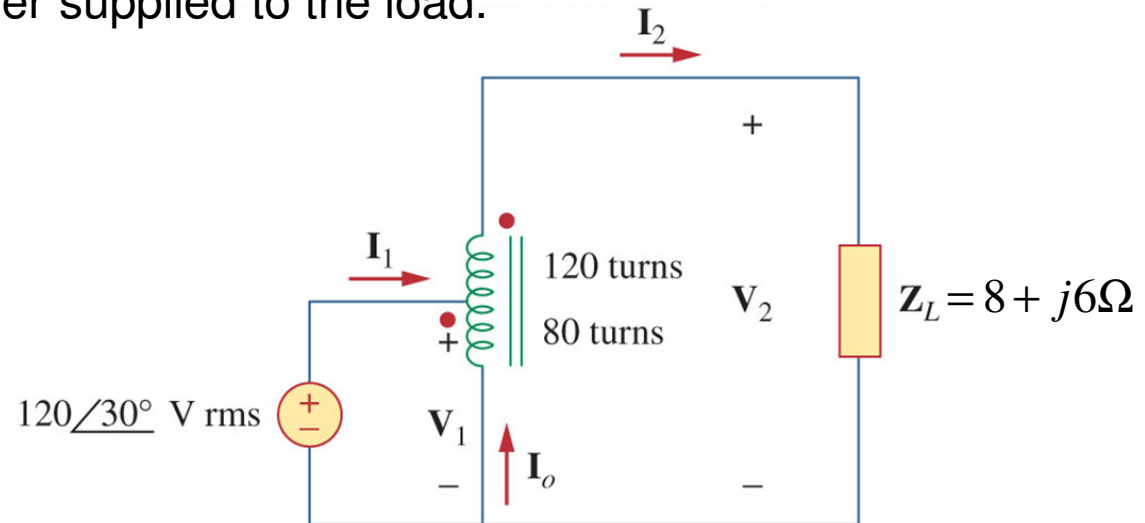
### Example 13.11 (Textbook)

For the autotransformer below, find: (a) the currents  $I_1$ ,  $I_2$ ,  $I_o$ , (b) the complex power supplied to the load.



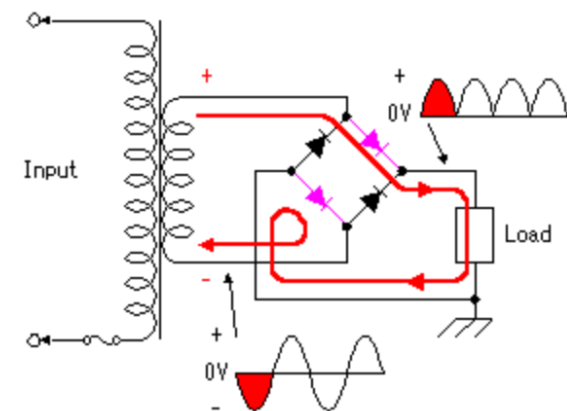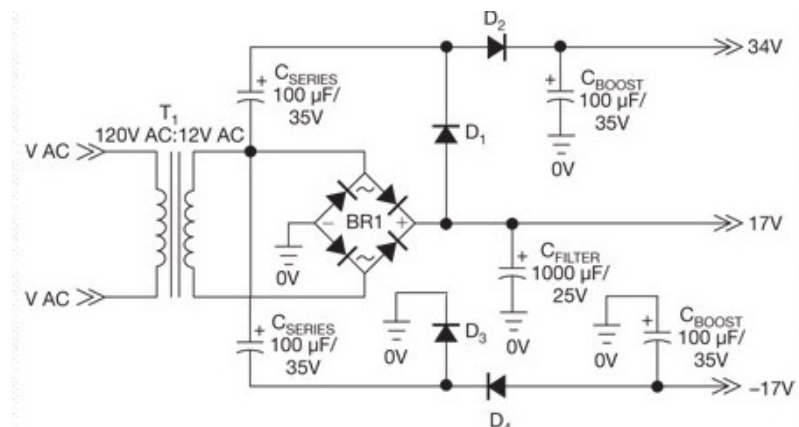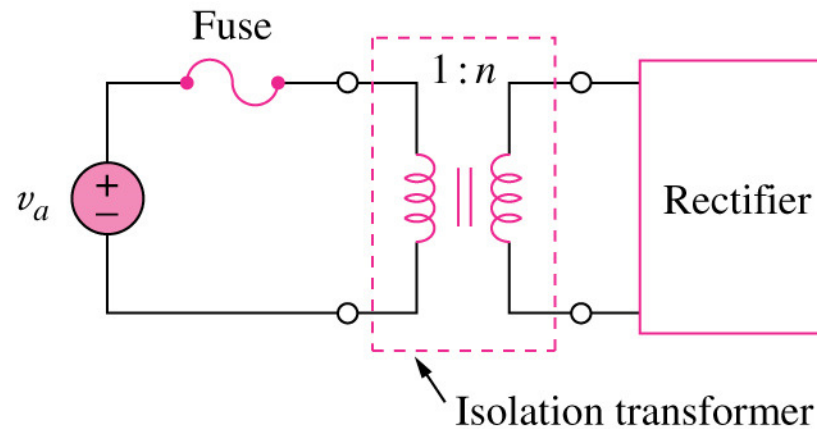
## 13.9 Applications (1)

- Transformer as an Isolation Device to isolate ac supply from a rectifier


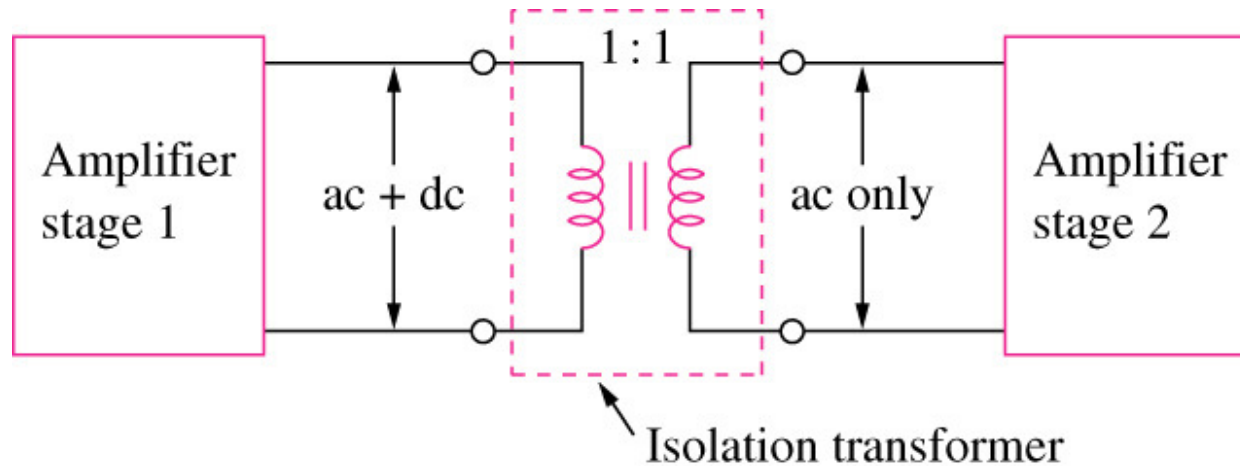
## 13.9 Applications (2)


- Transformer as an Isolation Device to isolate dc between two amplifier stages.



- Biasing is the application of a DC voltage to a transistor amplifier to produce a desired mode of operation.
- Each amplifier stage can be biased separately to operate in a particular mode.


## 13.9 Applications (3)

- Transformer as a Matching Device

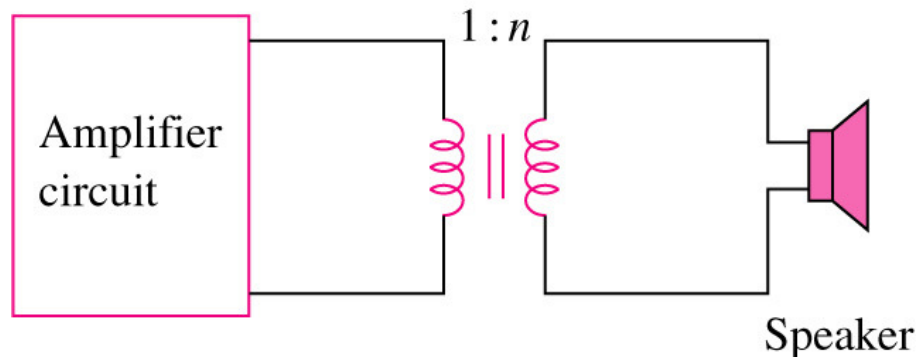

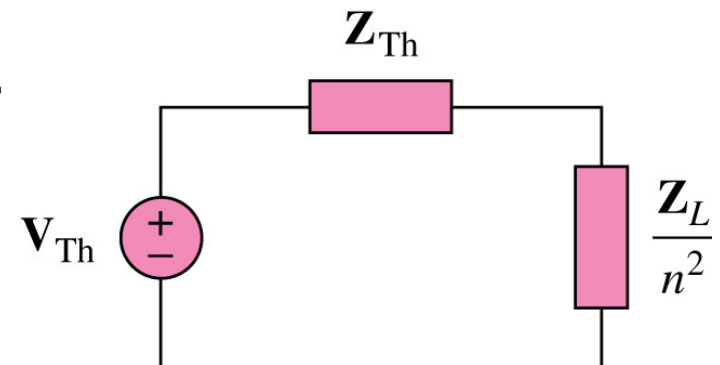**Equivalent circuit**

**Using an ideal transformer to  
match the speaker to the amplifier**





## 13.9 Applications (4)


### Practice Problem 13.16 (Textbook)

Calculate the turns ratio of an ideal transformer required to match a  $400\Omega$  load to a source with internal impedance of  $2.5k\Omega$ . Find the load voltage when the source voltage is  $30V$ .

Ans:  $n = 0.4$ ;  $V_L = 6V$

## 13.9 Applications (5)

- A typical power distribution system

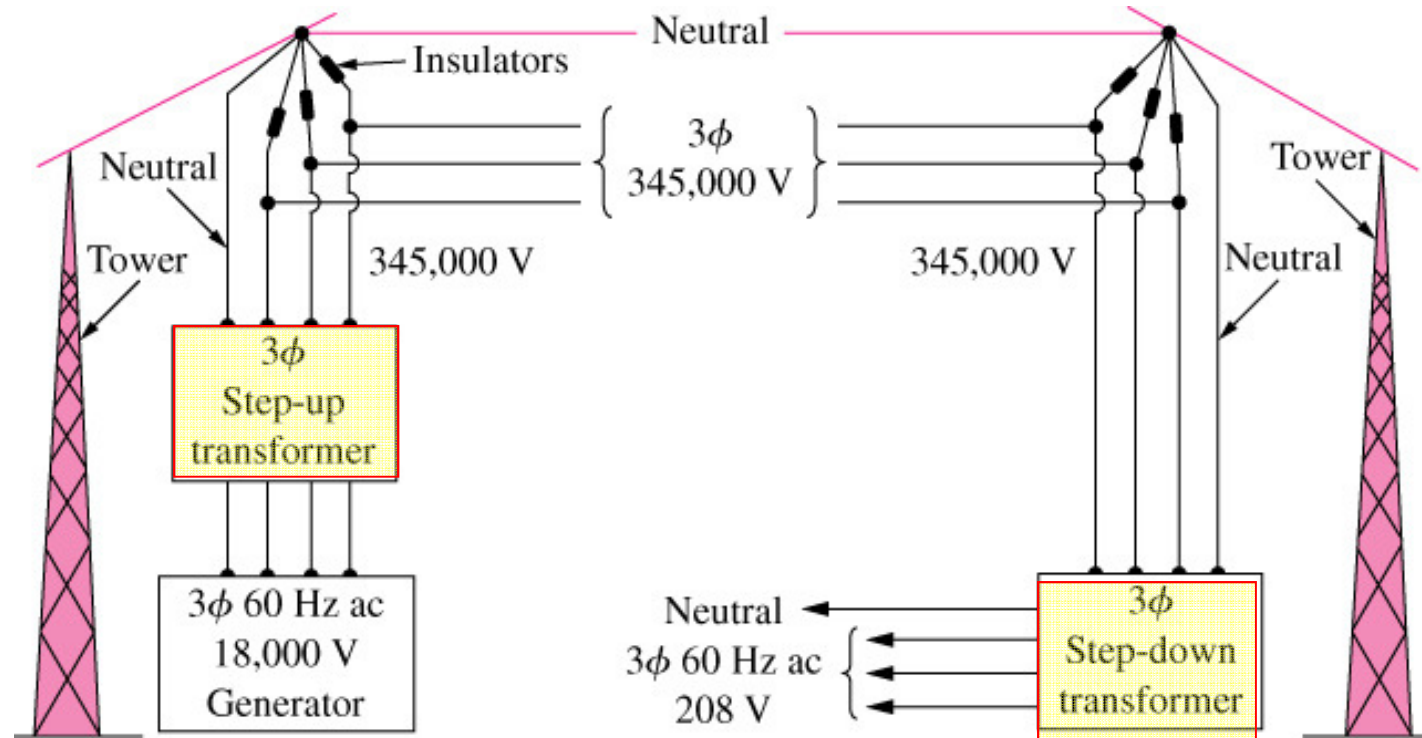

## Homework #3

**Due beginning of class Wednesday Feb 4, 2015**

- 13.30
- 13.35
- 13.42
- 13.50
- 13.53 (modified)
- Autotransformer (See handout)

**Exam over Chapter 13 on Monday Feb 9**

# Chapter 13

## Equation / Analysis Summary

- Series Aiding  $L = L_1 + L_2 + 2M$  / Opposing  $L = L_1 + L_2 - 2M$

- Dot Convention Model

- Coupling coefficient "k"  $M = k\sqrt{L_1 L_2}$

- Linear Transformer


- Input Impedance:

$$Z_{in} = Z_{primary} + \frac{\omega^2 M^2}{Z_{secondary}}$$

- Reflected Impedance:

$$Z_{reflected} = \frac{\omega^2 M^2}{Z_{secondary}}$$

- Equivalent T or  $\pi$  Circuits:

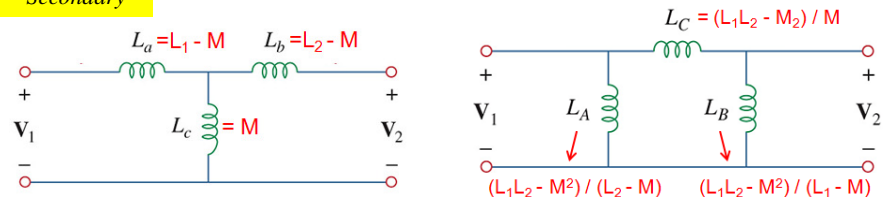

- Ideal Transformer

- $K = 1, L_1, L_2 \rightarrow \infty$

- Lossless ( $S_1 = S_2$ )


- Voltage / Current Relationship:

- Dots "same" = +n, Dots "diff" = -n

- Complex Power:  $S_1 = V_1 I_1^* = V_2 I_2^* = S_2$

- Autotransformer

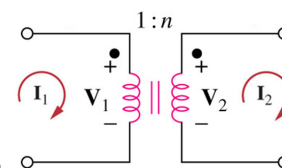- Adjustable "tap"
- No electrical Isolation
- Voltage Divider like relationship




$$V_2 = nV_1$$

$$I_2 = \frac{I_1}{n}$$

$$Z_{in} = \frac{Z_L}{n^2}$$

$$P_{ave} = |I_2|^2 R_L$$

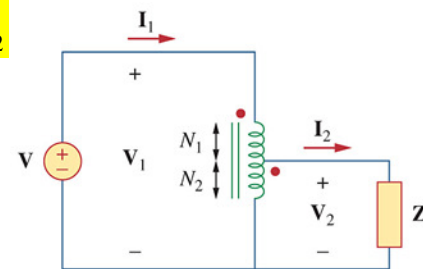

$$V_2 = \frac{N_2}{N_1 + N_2} V_1$$

$$I_2 = \frac{N_1 + N_2}{N_2} I_1$$