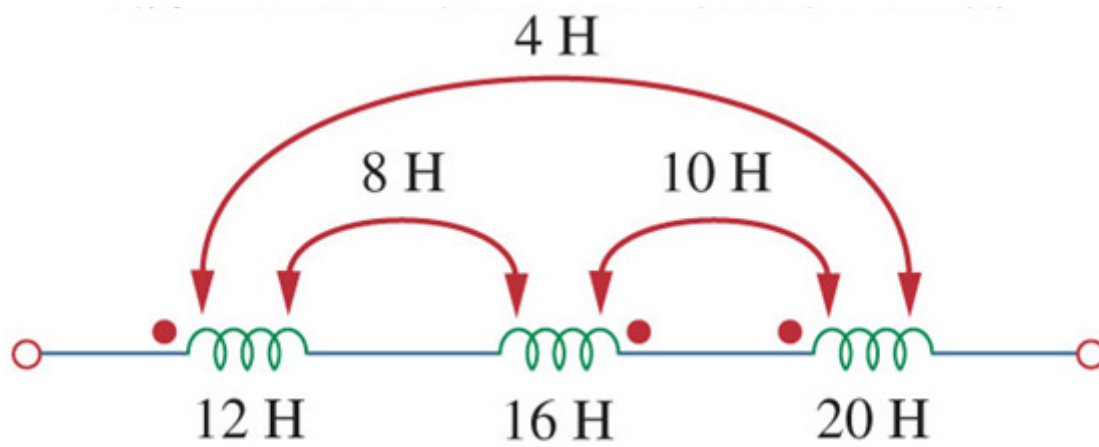



### Problem 13.1

For the three coupled coils, calculate the total inductance:



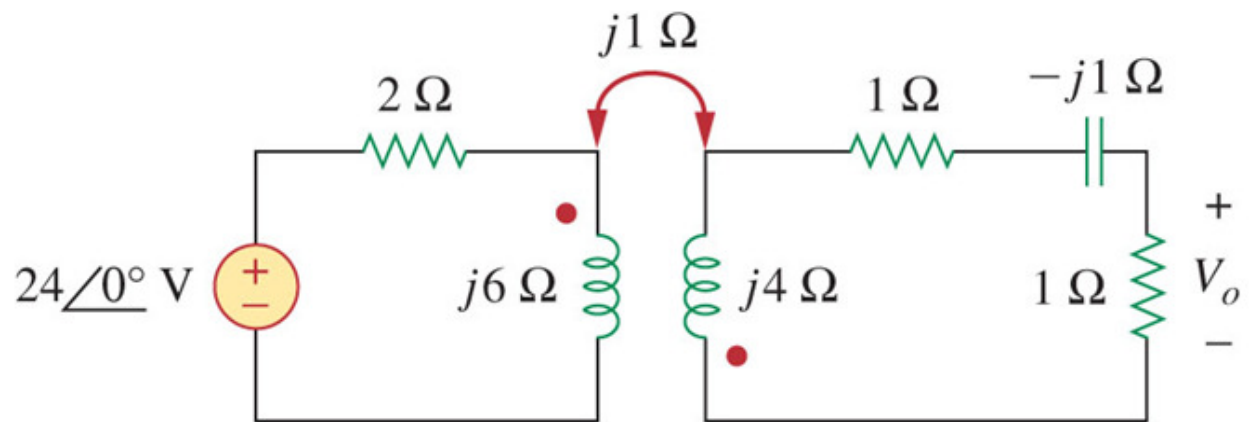
### Problem 13.7

For the circuit shown below find  $V_o$ .



### Problem 13.9

Find  $V_x$  for the circuit below:

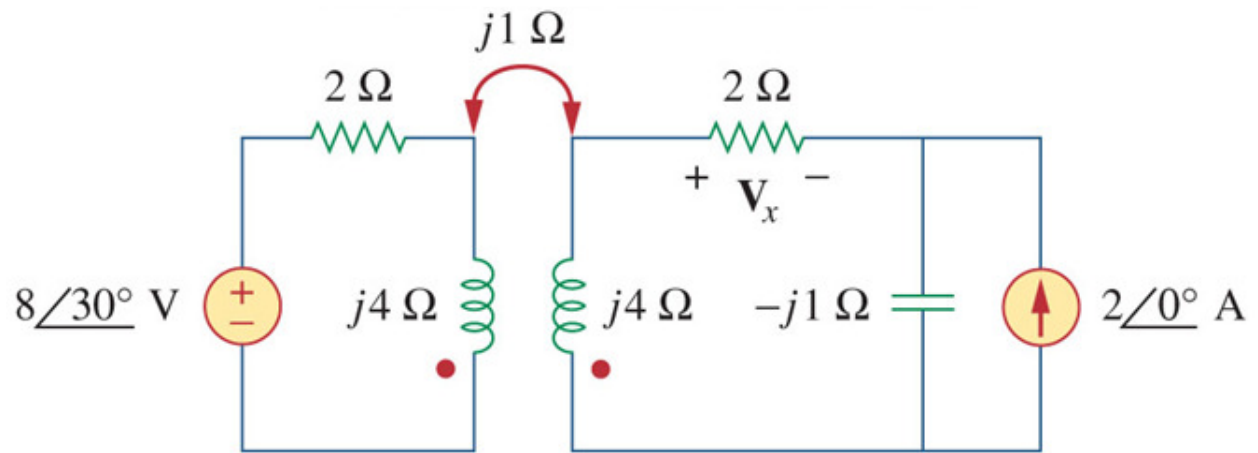

## Problem 13.24

In the circuit below:

- (a) Find the coupling coefficient
- (b) Calculate  $v_o$
- (c) Determine the energy stored in the coupled inductors at  $t = 2$  sec.

