

IUPUI ECE 202 Spring 2015:

Exam #2 (SOLUTIONS)


Name: _____

1. (15 points) For the following transfer function:
 - a. (10 Points) Draw the magnitude Bode plot
 - b. (3 Points) What type of filter is this (High Pass, Low Pass, Band Pass, or Band Stop) and what are the cutoff / corner frequencies (in rad/s)?
 - c. (2 Points) Is this an Active or Passive filter?

$$H(s) = \frac{1000s}{(s+2)(s+10)^2}$$

$$\text{a.) } H(s) = \frac{1000s}{(s+2)(10+s)^2} = \frac{1000s}{2(1+\frac{s}{2})10(1+\frac{s}{10})10(1+\frac{s}{10})}$$
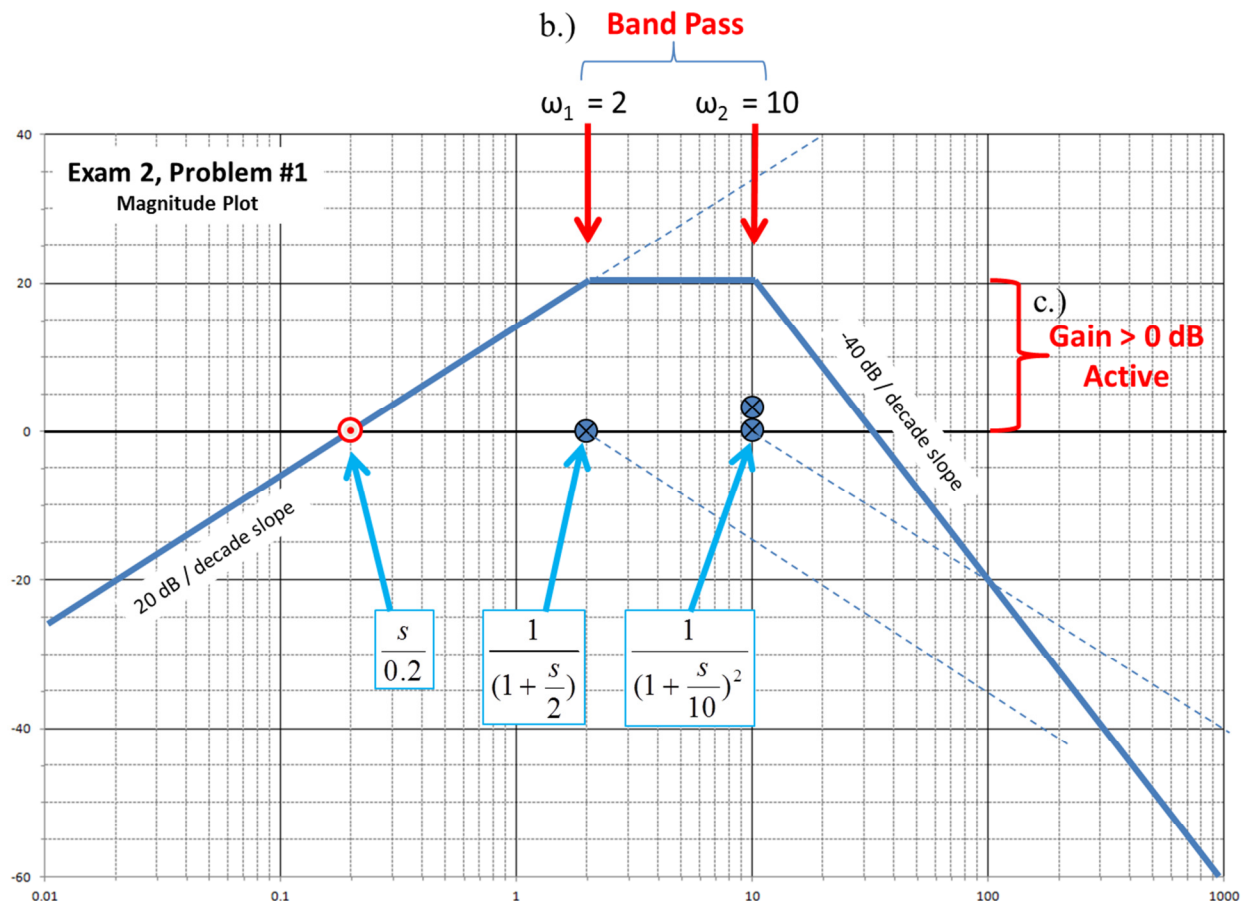
$$H(s) = \frac{5s}{(1+\frac{s}{2})(1+\frac{s}{10})^2} = \frac{\frac{s}{0.2}}{(1+\frac{s}{2})(1+\frac{s}{10})^2}$$



2. (20 points) Design a **parallel RLC** circuit to act as an audio band pass filter for the frequency range of **63.2 to 100 Hz** (*Band 4 of a 16 band graphic equalizer*). The filter should pass signals contained within this band and have **8 Ohm** impedance at resonance.

- (4 Points) Determine the **center frequency** and the quality factor "**Q**"
- (8 Points) Determine the component values for **R**, **L**, and **C** and **Draw the Circuit**
- (6 Points) Scale this filter up to *Band 7* so its center frequency is now at **317 Hz** and find the new values **R'**, **L'**, and **C'**.
- (2 Points) For this new circuit find the new bandwidth **B'**

Alternate Solution:

a.) $B_{\text{Hz}} = 100 - 63.2 = 36.8 \text{ Hz}$

$$f_o = \sqrt{f_1 f_2} = \sqrt{(63.2)(100)} = 79.5 \text{ Hz}$$

$$Q = \frac{\omega_o}{B} = \frac{f}{B_{\text{Hz}}} = \frac{79.5}{36.8} = 2.16$$

$$\omega_1 = 2\pi \times f_1 = 2\pi \times 63.2 = 397.1 \text{ rad/s}$$

$$\omega_2 = 2\pi \times f_2 = 2\pi \times 100 = 628.3 \text{ rad/s}$$

$$\omega_o = \sqrt{\omega_1 \omega_2} = \sqrt{(397.1)(628.3)} = 499.5 \text{ rad/s}$$

$$B = \omega_2 - \omega_1 = 628.3 - 397.1 = 231.2 \text{ rad/s}$$

$$Q = \frac{\omega_o}{B} = \frac{499.5}{231.2} = 2.16$$

b.) $R = 8 \Omega$

$$Q = \frac{R}{\omega_o L} = \omega_o RC$$

$$L = \frac{R}{\omega_o Q} = \frac{R}{(2\pi f_o)Q} = \frac{8}{(2\pi \times 79.5)(2.16)} = 7.41 \times 10^{-3} \text{ H or } 7.41 \text{ mH}$$

$$C = \frac{Q}{\omega_o R} = \frac{2.16}{(2\pi \times 79.5)(8)} = 540.6 \times 10^{-6} \text{ F or } 540.6 \mu\text{F}$$

c.) $K_m = 1$ no change in magnitude


$$K_f = \frac{f'}{f} = \frac{317}{79.5} = 3.99 \quad \text{or} \quad \frac{\omega'}{\omega} = \frac{2\pi \times 317}{499.5} = 3.99$$

$$R' = 8 \Omega$$


$$C' = \frac{1}{K_f} C = \frac{540.6 \mu\text{F}}{3.99} = 135.6 \mu\text{F}$$

$$L' = \frac{1}{K_f} L = \frac{7.41 \text{ mH}}{3.99} = 1.86 \text{ mH}$$

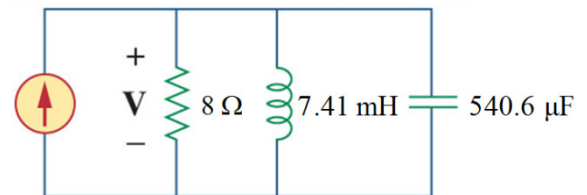d.) $B' = K_f B = 3.99 \times (36.8 \text{ Hz}) = 146.8 \text{ Hz or } 922.6 \text{ rad/s}$



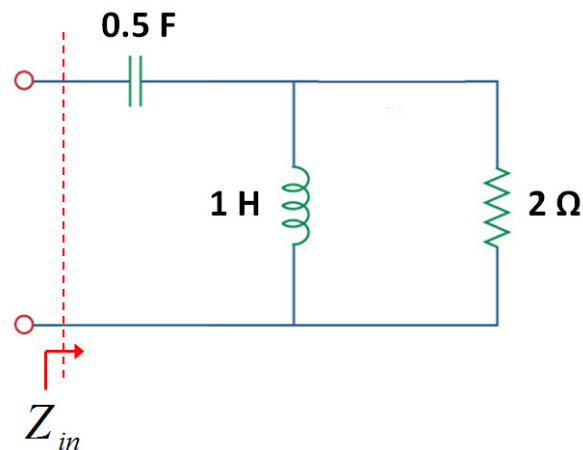3. (15 points) Find the resonant frequency for the circuit shown below:



$$Z_{in} = \frac{1}{j\omega C} + j\omega L \parallel R = \frac{1}{j\omega(0.5)} + \frac{(j\omega)(2)}{2 + j\omega}$$

$$Z_{in} = -j\frac{2}{\omega} + \frac{2j\omega}{2 + j\omega} \cdot \frac{(2 - j\omega)}{(2 - j\omega)} = -j\frac{2}{\omega} + \frac{2\omega^2 + 4j\omega}{2^2 + \omega^2}$$

$$Z_{in} = \frac{2\omega^2}{4 + \omega^2} + j\left(\frac{4\omega}{4 + \omega^2} - \frac{2}{\omega}\right)$$

$$\text{Im } Z_{in} = \frac{4\omega}{4 + \omega^2} - \frac{2}{\omega} = 0 \quad \text{At resonance}$$

$$\frac{4\omega}{4 + \omega^2} = \frac{2}{\omega}$$


$$4\omega^2 = 2(4 + \omega^2)$$

$$2\omega^2 = 4 + \omega^2$$


$$\omega^2 = 4$$

$$\omega = 2$$

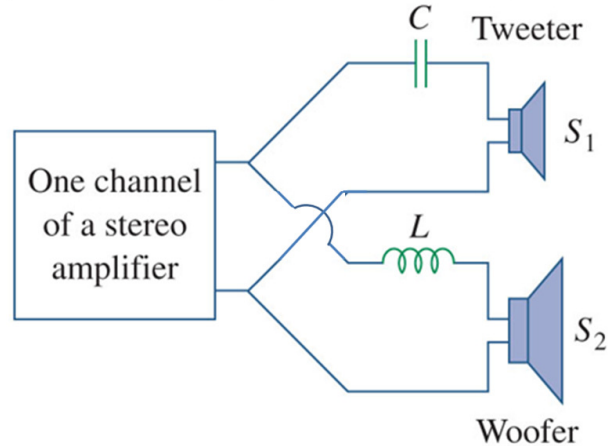4. (15 points) Design a crossover circuit for a speaker with a Woofer & Tweeter shown below. Assume the impedance of each speaker is $8\ \Omega$ and let the crossover frequency be $2.5\ \text{KHz}$. Determine the values for C and L . (assume no interaction between the two branches).



TWEETER CIRCUIT:

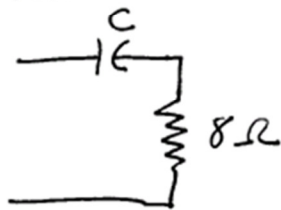

HIGH PASS FILTER

$$f_c = 2.5 \times 10^3 \text{ Hz}$$

$$\omega_c = 2\pi f_c = 15.7 \times 10^3 \frac{\text{rad}}{\text{s}}$$

$$\omega_c = \frac{1}{RC}$$

$$C = \frac{1}{\omega_c R}$$

$$C = \frac{1}{(15.7 \times 10^3)(8)} = \boxed{7.96 \times 10^{-6} \text{ F}} = \boxed{7.96 \mu\text{F}}$$

WOOFER CIRCUIT



LOW PASS FILTER
 $f_c = 2.5 \text{ kHz}$

$$\omega_c = 2\pi f_c = \frac{R}{L}$$

$$L = \frac{R}{2\pi f_c}$$

$$L = \frac{8}{2\pi \cdot (2.5 \times 10^3)} = \boxed{509.3 \times 10^{-6} \text{ H}} = \boxed{509.3 \mu\text{H}}$$


5. (20 points) Design and **active** filter to give the frequency response shown below. Use only one OPAMP in the circuit. Determine the **component values** and **draw the circuit**.

(Note the response is shown in Hz !)


$$GAIN = +6dB$$

$$6dB = 20 \log_{10} K$$

$$K = 10^{\frac{6}{20}} = 2$$

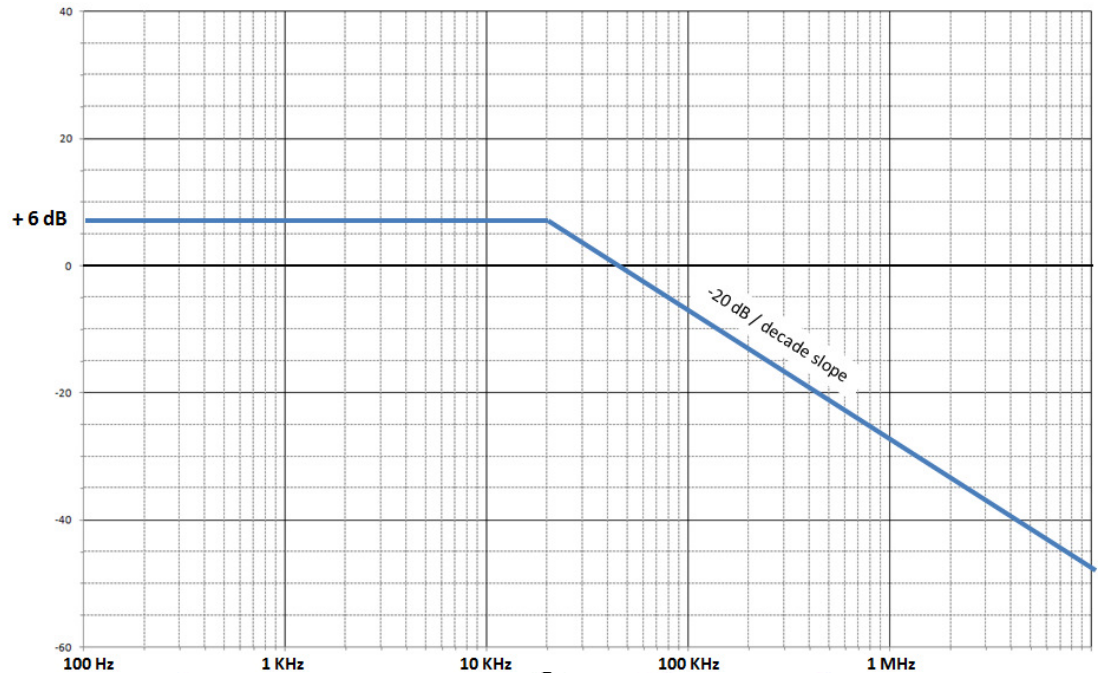

LOW PASS FILTER.

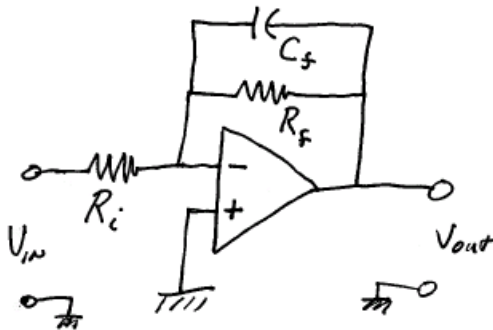

$$f_c = 20 \text{ kHz}$$

$$\omega_c = 2\pi f_c = 2\pi \cdot 20 \text{ kHz}$$

$$\omega_c = 125.7 \times 10^3 \text{ rad/sec}$$

$$\text{VOLTAGE GAIN} = \frac{R_f}{R_i} = 2$$

CHOOSE ONE RESISTOR, CALCULATE THE OTHER.

$$\text{i.e. } R_i = 10 \text{ k}\Omega \Rightarrow R_f = 20 \text{ k}\Omega$$

CAPACITANCE FOUND BY:

$$\omega_c = \frac{1}{R_f C_f} \Rightarrow C_f = \frac{1}{\omega_c R_f} = \frac{1}{(125.7 \times 10^3)(20 \times 10^3)} = \frac{1}{2514} = 397.9 \times 10^{-12} \text{ F} = 397.9 \text{ pF}$$

∴ MAY HAVE DIFFERENT VALUES DEPENDING ON CHOICE OF R_i , R_f .

6. (15 Points) For the circuit shown below:

a) (8 Points) Find the transfer function $H(s)$.

b) (4 Points) Put $H(s)$ in proper Bode form $(1 + \frac{s}{p_1}) \dots$ and find the cutoff frequency(s).

c) (3 Points) What type of filter is this (High Pass, Low Pass, Band Pass, or Band Stop)?

$$a.) H(s) = -\frac{Z_f}{Z_i} = -Z_f \left(\frac{1}{Z_i} \right)$$

$$Z_f = R \parallel \frac{1}{sC_f}$$

$$Z_f = \frac{R(\frac{1}{sC_f})}{R + \frac{1}{sC_f}} = \frac{R}{sRC_f + 1}$$

$$Z_i = R + \frac{1}{sC_i}$$

$$H(s) = -\left(\frac{R}{sRC_f + 1} \right) \cdot \frac{1}{R + \frac{1}{sC_i}} = \frac{-sRC_i}{(sRC_f + 1)(sRC_i + 1)}$$

$$= \frac{-5s}{(s \cdot 1 \cdot 1 + 1)(s \cdot 1 \cdot 5 + 1)} = \boxed{\frac{-5s}{(s+1)(5s+1)}} \quad \text{Zero offset at 0.2}$$

$$b.) H(s) = \frac{-5s}{(1+s)(1+\frac{s}{1/5})} = \frac{-\frac{s}{0.2}}{(1+s)(1+\frac{s}{0.2})} = \boxed{\frac{-\frac{s}{0.2}}{(1+s)(1+\frac{s}{0.2})}}$$

$$\boxed{\omega_1 = 0.2 ; \omega_2 = 1.0}$$

$$p=1 \quad p=0.2$$

c.) BAND PASS

