


IUPUI ECE 202 Spring 2015:

Homework #4 (Due in class: Feb 18, 2015)      Name: \_\_\_\_\_


---

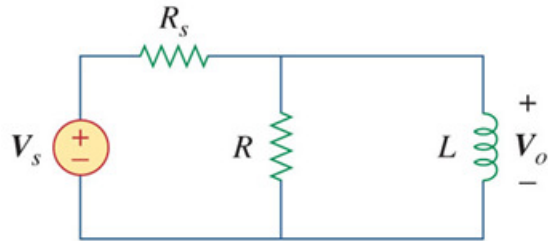1. (Prob. 14.5 in text) For each of the circuits shown below, find the transfer function:

$$\mathbf{H}(s) = \mathbf{V}_o(s) / \mathbf{V}_s(s)$$



(a)

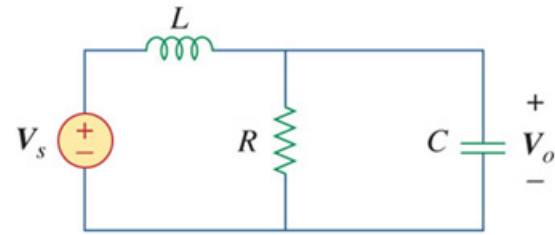


(b)

IUPUI ECE 202 Spring 2015:  
Homework #4 (Due in class: Feb 18, 2015) Name: \_\_\_\_\_

---

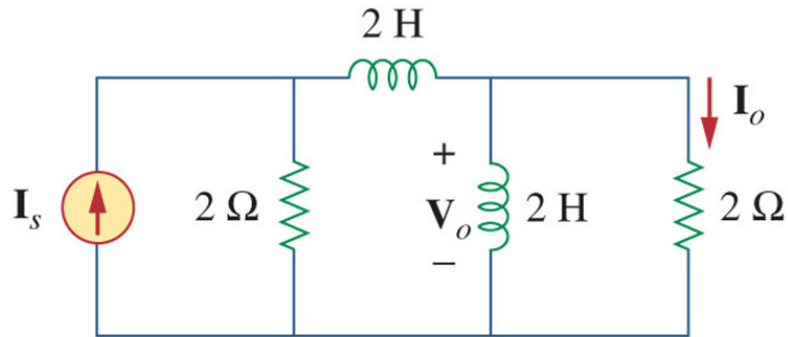2. (Prob. 14.6 from Text) For the circuit shown below, find the transfer function:

$$\mathbf{H}(s) = \mathbf{I}_o(s) / \mathbf{I}_s(s)$$



IUPUI ECE 202 Spring 2015:


Homework #4 (Due in class: Feb 18, 2015)      Name: \_\_\_\_\_

---

3. (Prob. 14.17 from Text) Sketch the magnitude and phase Bode plots for the following transfer function:

$$G(s) = \frac{s}{(s+2)^2(s+1)}$$


**Magnitude Plot**

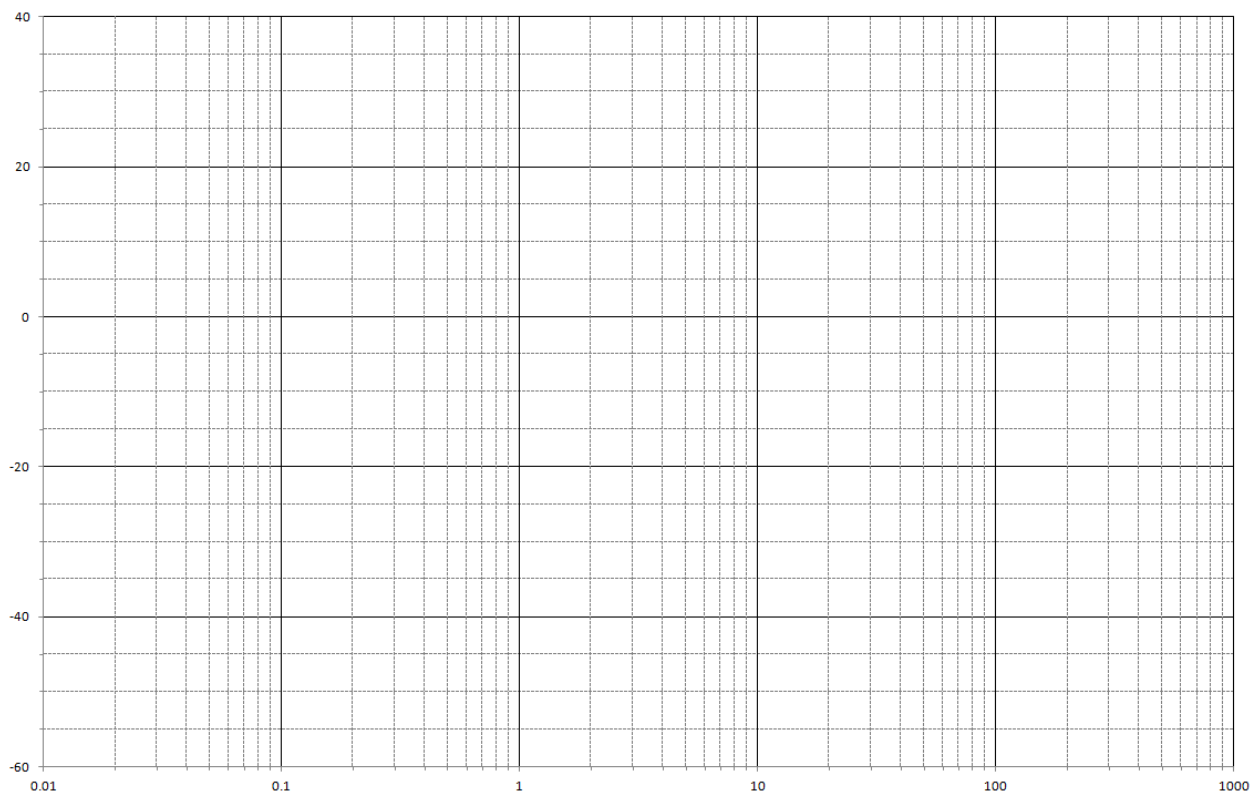

IUPUI ECE 202 Spring 2015:  
Homework #4 (Due in class: Feb 18, 2015) Name:

---

**Phase Plot**

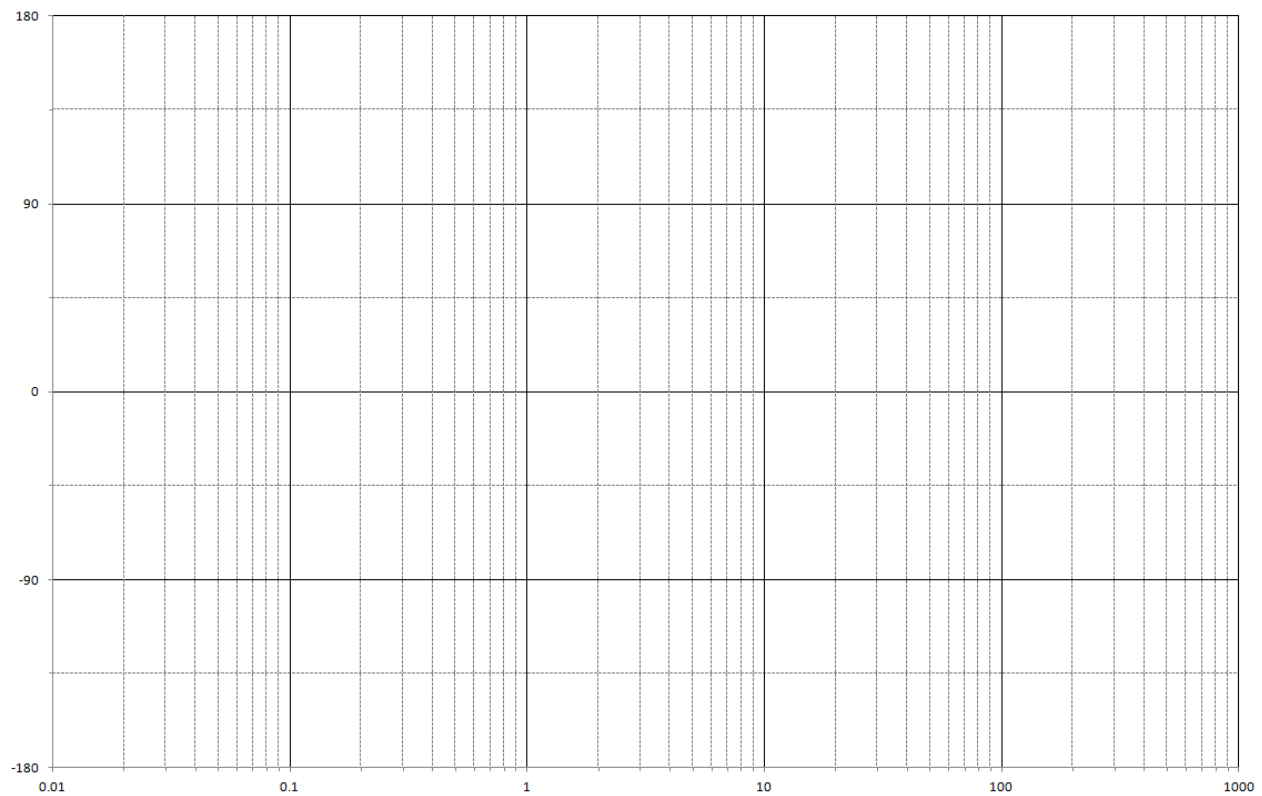

IUPUI ECE 202 Spring 2015:


Homework #4 (**Due in class: Feb 18, 2015**)      Name: \_\_\_\_\_

---

4. (Prob. 14.19 from Text) Sketch the magnitude and phase Bode plots for the following transfer function:

$$H(s) = \frac{80s}{(s+10)(s+20)(s+40)}$$


**Magnitude Plot**

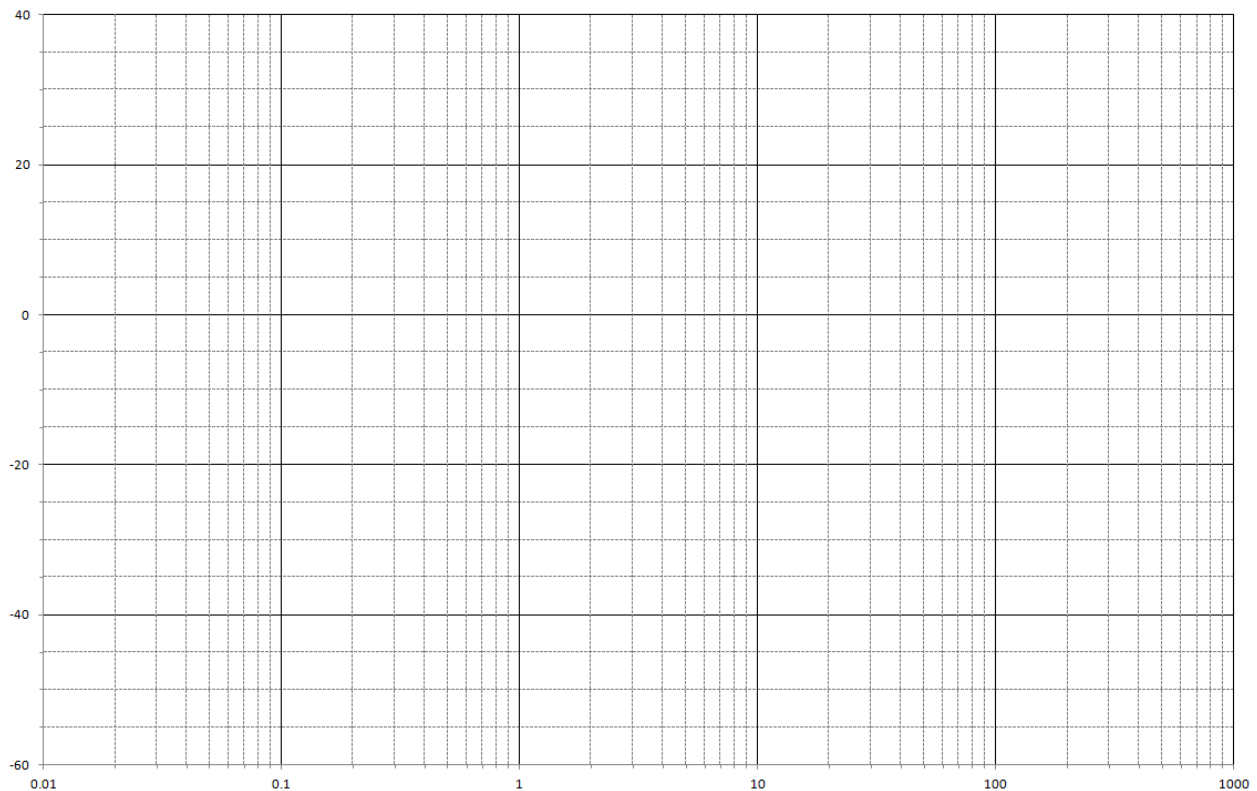

IUPUI ECE 202 Spring 2015:  
Homework #4 (Due in class: Feb 18, 2015) Name:

---

**Phase Plot**

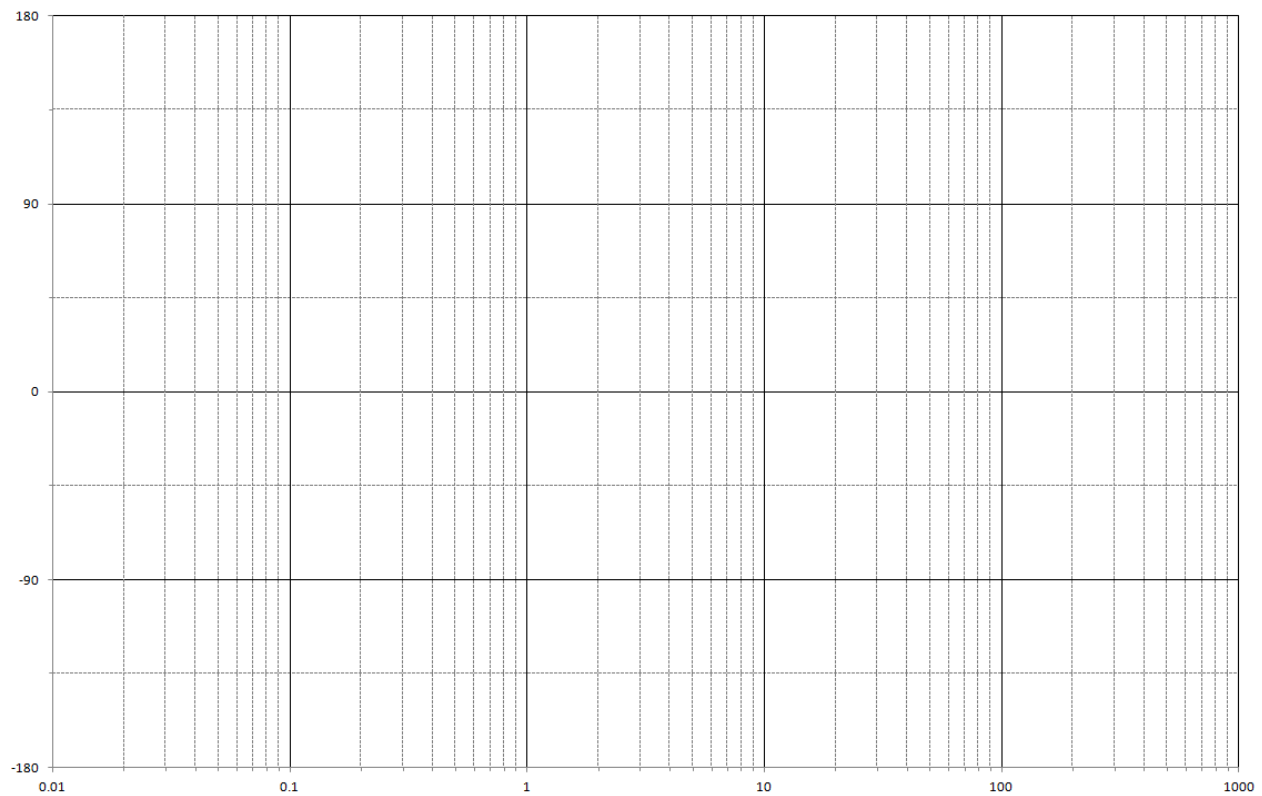


IUPUI ECE 202 Spring 2015:

Homework #4 (**Due in class: Feb 18, 2015**)      Name: \_\_\_\_\_

---

5. (Prob. 14.22 from Text)

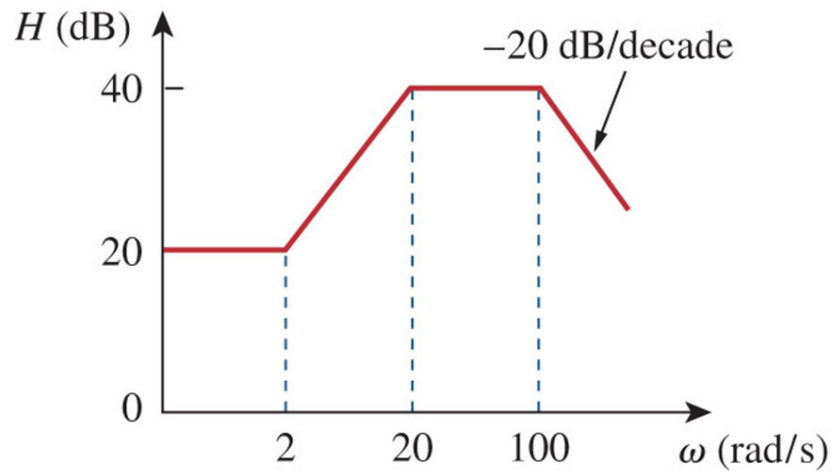- a. **Part 1:** Find the transfer function  $H(\omega)$  with the Bode magnitude plot as shown below:



- b. **Part II:** Use MATLAB to generate the Bode plot from your derived transfer function