
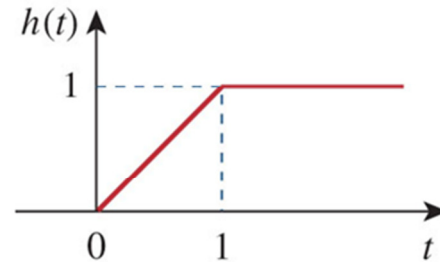


IUPUI ECE 202 Spring 2015:



Homework #8 (SOLUTION KEY) Name: _____

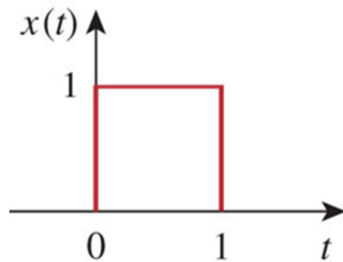1. (Prob. 15.43a in text) Find $y(t) = x(t) * h(t)$ (convolution of $x(t)$ and $h(t)$) for $x(t)$ and $h(t)$ in the figure below:
- Solve using the graphical method (evaluate the integral to find the area under the curve).
 - Solve by multiplying in the s-domain (use the Laplace Transform & Inverse Laplace transform):



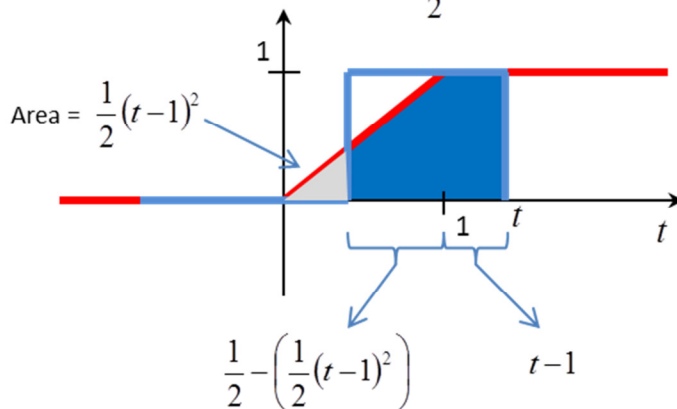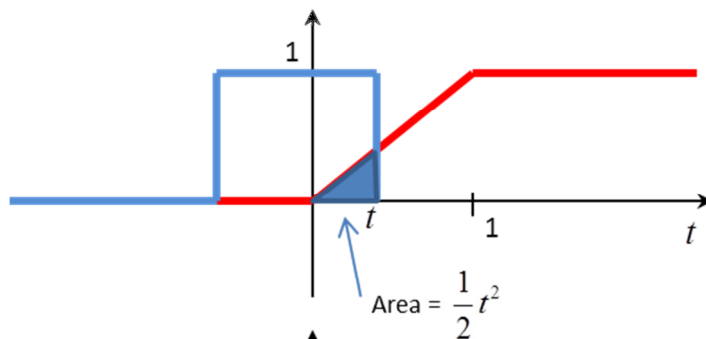a) Graphical Solution:

Fold $x(t)$, shift, slide, multiply and find area under curve



$$\text{Area} = \frac{1}{2} - \left(\frac{1}{2}t^2 + \frac{1}{2} - t\right) + (t-1)$$

$$-\frac{1}{2}t^2 + 2t - 1$$

$$y(t) = \begin{cases} \frac{1}{2}t^2 & 0 \leq t < 1 \\ -\frac{1}{2}t^2 + 2t - 1 & 1 \leq t < 2 \\ 1 & 2 \leq t < \infty \end{cases}$$

b) Laplace Solution:

The signals $x(t)$ and $h(t)$ can be described as follows:

$$x(t) = u(t) - u(t-1)$$

$$h(t) = \underbrace{tu(t)}_{\substack{\uparrow \\ \text{+ ramp at } t=0}} - \underbrace{(t-1)u(t-1)}_{\substack{\uparrow \\ \text{- ramp at } t=1 \text{ (Cancels previous slope)}}}$$

Converting to S-domain:

$$X(s) = \frac{1}{s} - \frac{1}{s}e^{-s} = \frac{1}{s}(1 - e^{-s})$$

$$H(s) = \frac{1}{s^2} - \frac{1}{s^2}e^{-s} = \frac{1}{s^2}(1 - e^{-s})$$

Multiplying together to get the output:

$$Y(s) = X(s)H(s) = \frac{1}{s^3}(1 - e^{-s})(1 - e^{-s})$$

$$Y(s) = X(s)H(s) = \frac{1}{s^3}(1 - 2e^{-s} + e^{-2s})$$

From Laplace Table $\mathcal{L}^{-1}\left[\frac{1}{s^3}\right] = \frac{1}{2}t^2u(t)$

Time Delay Property $\mathcal{L}^{-1}\left[-\frac{1}{s^3}2e^{-s}\right] = \frac{1}{2}(-2)(t-1)^2u(t-1)$

$$y(t) = \frac{1}{2}t^2u(t) - (t-1)^2u(t-1) + \frac{1}{2}(t-2)^2u(t-2)$$


$$y(t) = \frac{1}{2}t^2u(t) - (t^2 - 2t + 1)u(t-1) + \frac{1}{2}(t^2 - 4t + 4)u(t-2)$$

$$y(t) = \begin{cases} \frac{1}{2}t^2 & 0 \leq t < 1 \\ -\frac{1}{2}t^2 + 2t - 1 & 1 \leq t < 2 \\ 1 & 2 \leq t < \infty \end{cases}$$

IUPUI ECE 202 Spring 2015:


Homework #8 (SOLUTION KEY) Name: _____

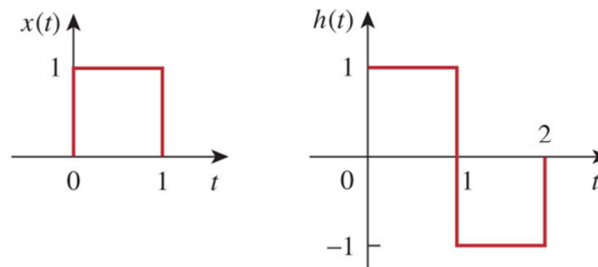2. (Prob. 15.44a from Text) Find $y(t) = x(t) * h(t)$ (convolution of $x(t)$ and $h(t)$) for $x(t)$ and $h(t)$ in the figure below:
- Solve using the graphical method (evaluate the integral to find the area under the curve).
 - Solve by multiplying in the s-domain (use the Laplace Transform & Inverse Laplace transform):



a.) Graphical Solution

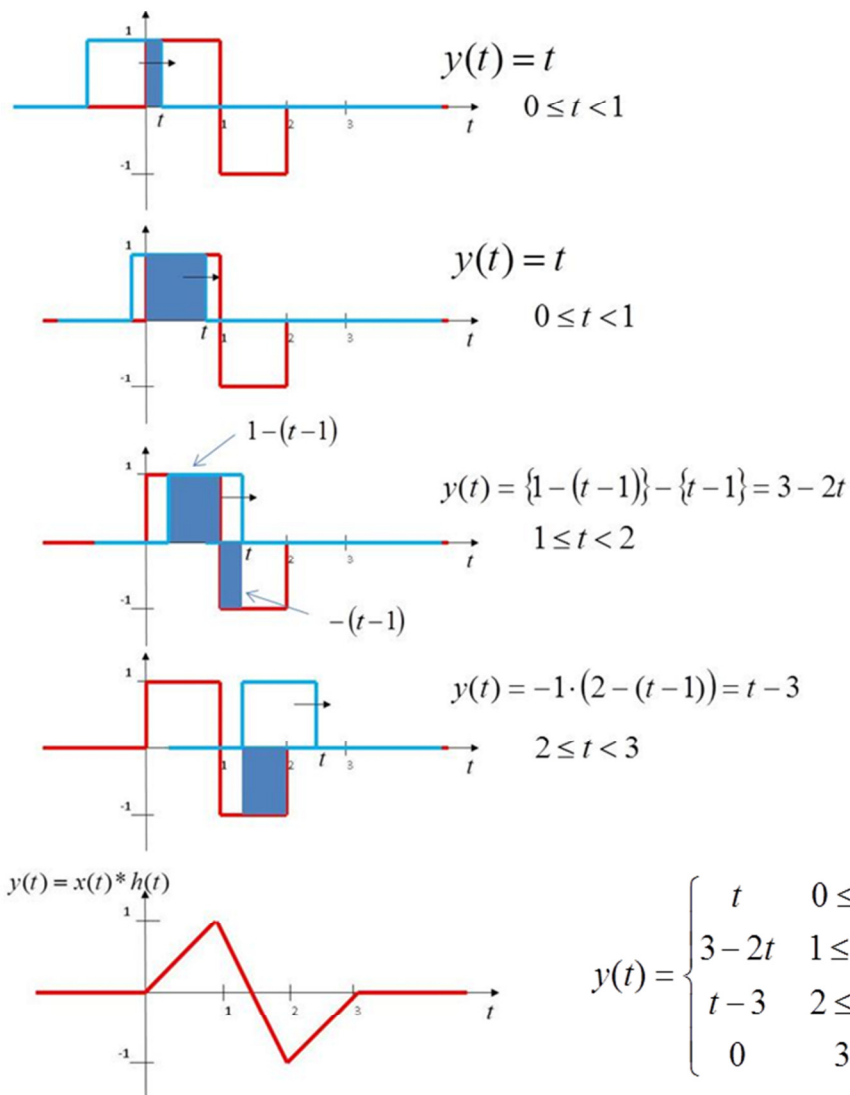Fold $x(t)$, shift, slide, multiply and find area under curve



b.) Laplace Solution:

The signals $x(t)$ and $h(t)$ can be described as follows:

$$x(t) = u(t) - u(t-1)$$

$$h(t) = u(t) - 2(t-1)u(t-1) + u(t-2)$$

Converting to S-domain:

$$X(s) = \frac{1}{s} - \frac{1}{s}e^{-s} = \frac{1}{s}(1 - e^{-s})$$

$$H(s) = \frac{1}{s} - \frac{2}{s}e^{-s} + \frac{1}{s}e^{-2s} = \frac{1}{s}(1 - 2e^{-s} + e^{-2s})$$

Multiplying together to get the output:

$$Y(s) = X(s)H(s) = \frac{1}{s^2}(1 - e^{-s})(1 - 2e^{-s} + e^{-2s})$$

$$Y(s) = \frac{1}{s^2}(1 - 2e^{-s} + e^{-2s} - e^{-s} + 2e^{-2s} - e^{-3s})$$

$$Y(s) = \frac{1}{s^2}(1 - 3e^{-s} + 3e^{-2s} - e^{-3s})$$

Inverse Laplace Transform:


$$y(t) = tu(t) - 3(t-1)u(t-1) + 3(t-2)u(t-2) - (t-3)u(t-3)$$

$$y(t) = \begin{cases} t & 0 \leq t < 1 \\ 3-2t & 1 \leq t < 2 \\ t-3 & 2 \leq t < 3 \\ 0 & 3 \leq t \end{cases}$$

IUPUI ECE 202 Spring 2015:
Homework #8 (SOLUTION KEY)


Name: _____

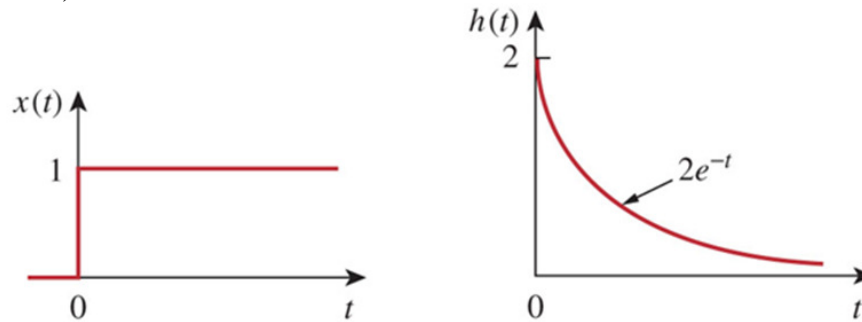3. (Prob. 15.43b from Text) Find $y(t) = x(t) * h(t)$ for the paired $x(t)$ and $h(t)$ below using two methods:
- Solve using the graphical method (evaluate the integral to find the area under the curve).
 - Solve by multiplying in the s-domain (use the Laplace Transform & Inverse Laplace transform):



- (a) For $t > 0$, the two functions overlap as shown in Fig. (c).

$$y(t) = x(t) * h(t) = \int_0^t (1) 2e^{-\lambda} d\lambda = -2e^{-\lambda} \Big|_0^t$$

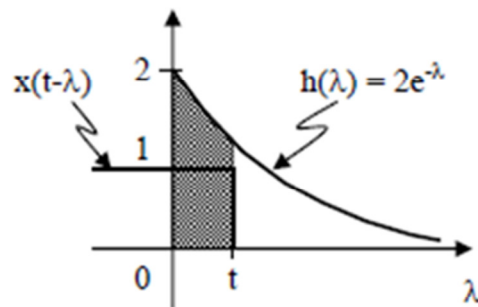

(c)

Therefore

$$y(t) = 2(1 - e^{-t}), \quad t > 0$$

(b)

$$x(t) = u(t) \quad h(t) = 2e^{-t}u(t)$$



$$X(s) = \frac{1}{s} \quad H(s) = \frac{2}{s+1}$$

$$Y(s) = X(s)H(s) = \frac{2}{s(s+1)} = \frac{k_0}{s} + \frac{k_1}{(s+1)} = \frac{2}{s} - \frac{2}{(s+1)}$$

$$y(t) = \mathcal{L}^{-1} \left[\frac{2}{s} - \frac{2}{(s+1)} \right] = 2(1 - e^{-t}) \quad t > 0$$

IUPUI ECE 202 Spring 2015:
Homework #8 (SOLUTION KEY) Name: _____

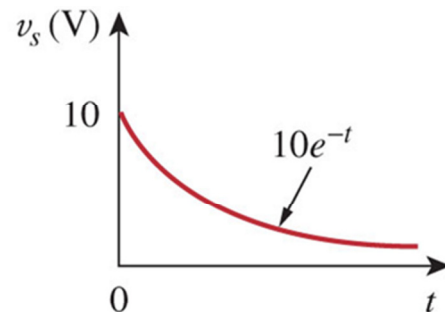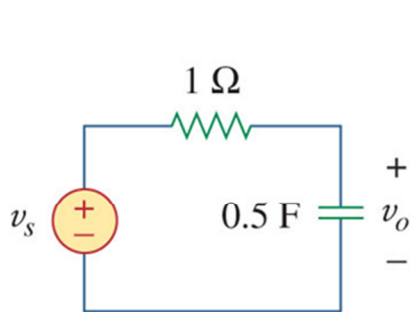4. (Practice problem 15.14 from Text) Use convolution to find $v_o(t)$ in the circuit below in figure (a) when the excitation is the signal shown in figure (b). Verify your answer by performing the equivalent operation in the s-domain.




First convert circuit to s-domain and find the transfer function (Voltage Divider):

$$V_o(s) = \frac{2/s}{1 + 2/s} V_s(s) = \frac{2}{s+2} V_s(s) \Rightarrow H(s) = \frac{2}{s+2}$$

Convert the transfer function to the time domain
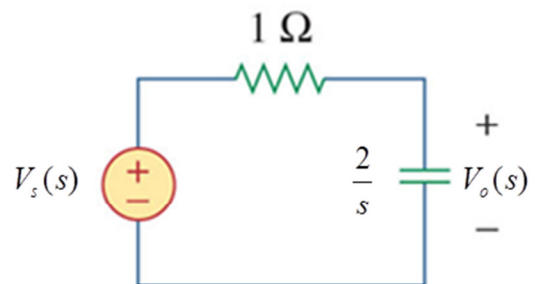
$$h(t) = \mathcal{L}^{-1}\left[\frac{2}{s+2}\right] = 2e^{-2t}u(t)$$



Perform the convolution using the integral equation

$$v_o(t) = v_s(t) * h(t) = \int_0^t v_s(t-\lambda)h(\lambda)d\lambda = \int_0^t (10e^{-(t-\lambda)})(2e^{-2\lambda})d\lambda = 20 \int_0^t e^{-t}e^{-\lambda}d\lambda = 20e^{-t}(-e^{-\lambda})\Big|_0^t$$

$$v_o(t) = 20e^{-t}(1 - e^{-t}) = 20(e^{-t} - e^{-2t}) \quad t > 0$$

Verify by performing in the s-domain:

$$H(s) = \frac{2}{s+2} \quad V_s(s) = \mathcal{L}[10e^{-t}] = \frac{10}{s+1}$$


$$V_o(s) = V_s(s)H(s) = \left(\frac{10}{s+1}\right)\left(\frac{2}{s+2}\right) = \frac{20}{(s+1)(s+2)} = \frac{k_0}{s+1} + \frac{k_1}{s+2} = \frac{20}{s+1} - \frac{20}{s+2}$$

$$v_o(t) = 20\mathcal{L}^{-1}\left[\frac{1}{s+1} - \frac{1}{s+2}\right] = 20(e^{-t} - e^{-2t}) \quad t > 0$$


IUPUI ECE 202 Spring 2015:
Homework #8 (SOLUTION KEY)

Name: _____

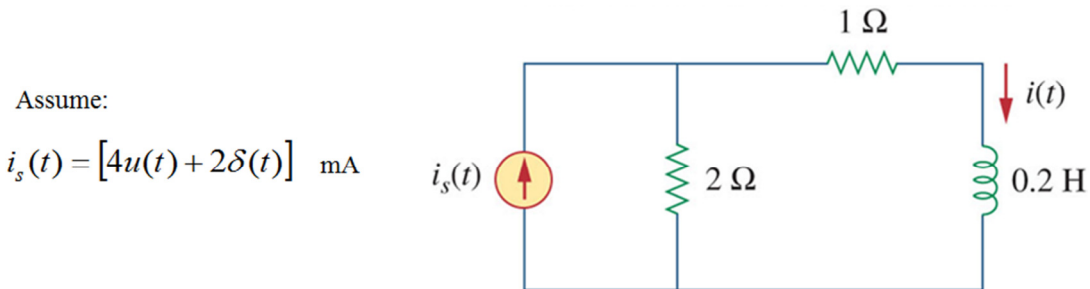
5. (Prob. 16.14 from Text) Find $i(t)$ for $t > 0$ for the circuit shown below:



First convert circuit to s-domain:

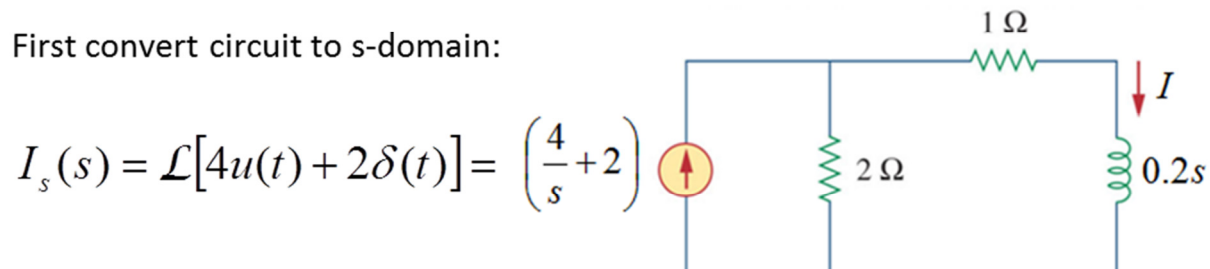

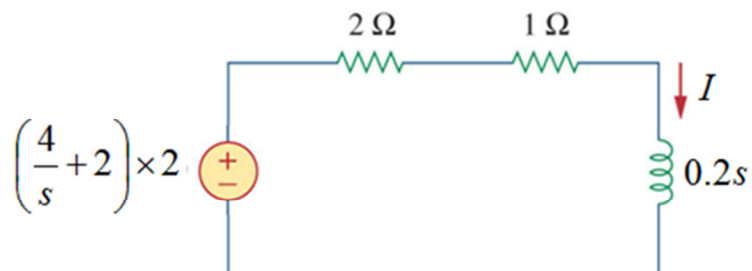Use source transformation
to convert current source
to a voltage source:



Solve circuit for I:

$$I = \frac{\left(\frac{8}{s} + 4\right)}{2 + 1 + 0.2s} = \frac{8 + 4s}{s(3 + 0.2s)} = \frac{20s + 40}{s(s + 15)} = \frac{k_0}{s} + \frac{k_1}{(s + 15)}$$

$$I = \left(\frac{8}{3}\right)\frac{1}{s} + \left(\frac{52}{3}\right)\frac{1}{(s + 15)}$$


$$k_0 = \frac{20(0) + 40}{(0 + 15)} = \frac{40}{15} = \frac{8}{3}$$

$$k_1 = \frac{20(-15) + 40}{-15} = \frac{-260}{-15} = \frac{52}{3}$$

$$i(t) = \mathcal{L}^{-1}\left[\left(\frac{8}{3}\right)\frac{1}{s} + \left(\frac{52}{3}\right)\frac{1}{(s + 15)}\right] = \left(\frac{8}{3}\right)u(t) + \left(\frac{52}{3}\right)e^{-15t}u(t) \text{ mA} \quad t > 0$$

IUPUI ECE 202 Spring 2015:
Homework #8 (SOLUTION KEY) Name:

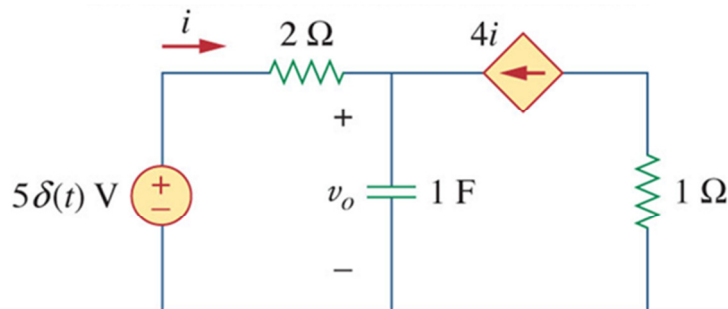6. (Prob. 16.16 from Text) The capacitor in the circuit below is initially uncharged. Find $v_o(t)$ for $t > 0$:



First convert circuit to s-domain:


Mesh for I_1 :

$$I_1(2) + \frac{1}{s}(I_1 - I_2) - 5 = 0$$

However $I_2 = -4 I_1$

$$I_1(2) + \frac{5}{s}(I_1) = 5$$
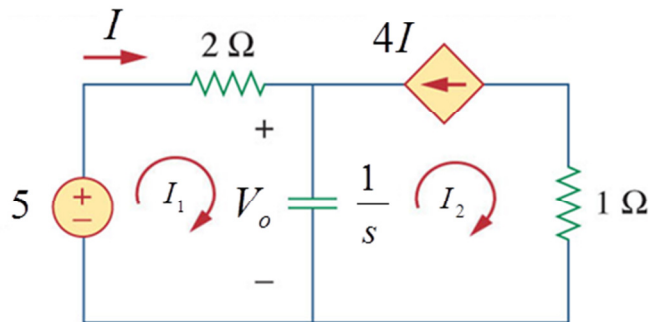
$$I_1 = \left(\frac{5}{2 + \frac{5}{s}} \right) = \frac{5s}{2s + 5} = \frac{2.5s}{s + 2.5}$$



Solve for Voltage across capacitor

$$V_o = \frac{1}{s}(I_1 - I_2) = \frac{5}{s}I_1 = \frac{5}{s} \left(\frac{2.5s}{s + 2.5} \right) = \frac{12.5}{s + 2.5}$$

$$v_o(t) = L^{-1} \left[\frac{12.5}{s + 2.5} \right] = 12.5e^{-2.5t} \quad t > 0$$