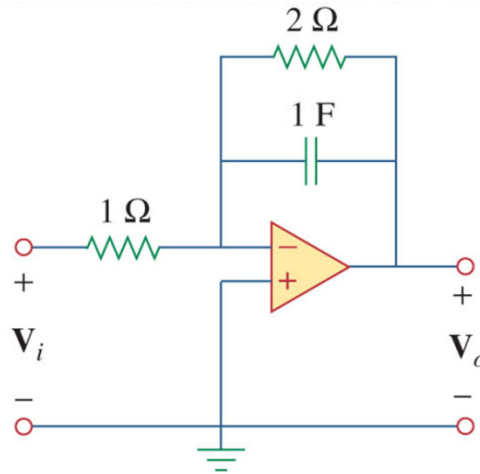


IUPUI ECE 202 Spring 2015:

Homework #6 (SOLUTIONS) Name: _____

1. (10 pts: Prob. 14.82 in text) Scale the **lowpass** active filter shown below so that its corner frequency increases from 1 rad/s to 200 rad/s. (Use a 1 μF capacitor).



Solution from the Author's Solution manual:

$$C' = \frac{C}{K_m K_f}$$

$$K_f = \frac{\omega'_c}{\omega} = \frac{200}{1} = 200$$

$$K_m = \frac{C}{C'} \cdot \frac{1}{K_f} = \frac{1}{10^{-6}} \cdot \frac{1}{200} = 5000$$

$$R' = K_m R = 5 \text{ k}\Omega, \quad \text{thus, } R'_f = 2R_i = 10 \text{ k}\Omega$$

However, this results in a corner frequency of 100 rad/s not 200 rad/s !!

The "error" is that the original corner frequency is actually 0.5 rad/s.

$$\omega_c = \frac{1}{R_f C_f} = \frac{1}{(2)(1)} = 0.5$$

Using this instead we get:

$$C' = \frac{C}{K_m K_f}$$

$$K_f = \frac{\omega'_c}{\omega_c} = \frac{200}{0.5} = 400$$

$$K_m = \frac{C}{C'} \cdot \frac{1}{K_f} = \frac{1}{1 \times 10^{-6}} \cdot \frac{1}{400} = 2500$$

$$R'_f = K_m R_f = (2500) \times (2) = 5 \text{ k}\Omega$$

$$R'_i = K_m R_i = (2500) \times (1) = 2.5 \text{ k}\Omega$$

Another solution:

To scale the circuit to result in a corner frequency of 200 rad/s and use a 1 μF capacitor:

$$\omega'_c = \frac{1}{R'_f C'_f}$$

$$R'_f = \frac{1}{C'_f \omega'_c}$$

$$R'_f = \frac{1}{(1 \times 10^{-6}) \times 200} = 5 \text{ k}\Omega$$

To find R_i to keep the same gain:

$$\text{Gain} = \frac{R_f}{R_i} = \frac{2}{1} = 2 = \frac{R'_f}{R'_i}$$


$$R'_i = \frac{R'_f}{2} = 2.5 \text{ k}\Omega$$

IUPUI ECE 202 Spring 2015:

Homework #6 (SOLUTIONS) Name: _____

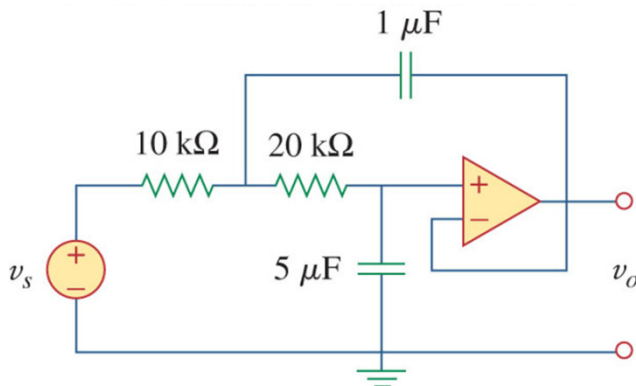2. (10 pts: Prob. 14.83 from Text) The op amp circuit in the figure below is to be magnitude-scaled by 100 and frequency-scaled by 10⁵. Find the resulting element values. (If Possible, use Pspice to verify)

Note: This is actually a fairly significant circuit, it's called a Sallen-Key filter and is a commonly used active filter design.




$$1\mu\text{F} \longrightarrow C' = \frac{1}{K_m K_f} C = \frac{10^{-6}}{100 \times 10^5} = \underline{0.1\text{pF}}$$

$$5\mu\text{F} \longrightarrow C' = \underline{0.5\text{pF}}$$

$$10\text{ k}\Omega \longrightarrow R' = K_m R = 100 \times 10\text{ k}\Omega = \underline{1\text{ M}\Omega}$$

$$20\text{ k}\Omega \longrightarrow R' = \underline{2\text{ M}\Omega}$$

From PSpice

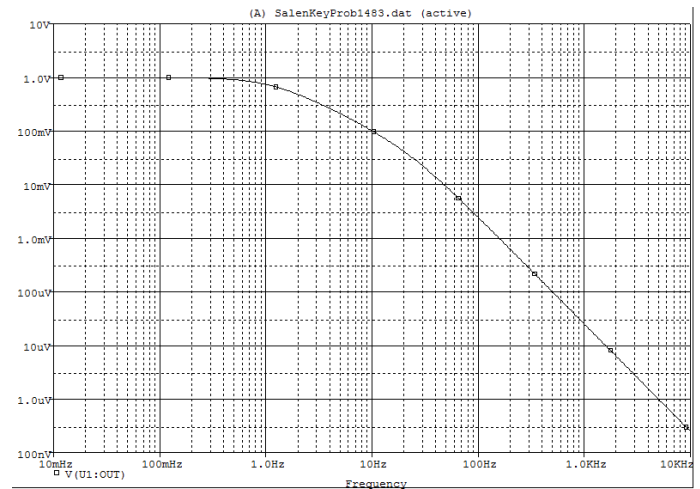

From website:

<http://sim.okawa-denshi.jp/en/OPstool.php>

Transfer Function



$$G(s) = \frac{1000}{s^2 + 150s + 1000}$$

Cut-off frequency
 $f_c = 5.03292121045[\text{Hz}]$

Quality factor
 $Q = 0.210818510678$

From PSpice

Sallen-Key Low-pass Filter

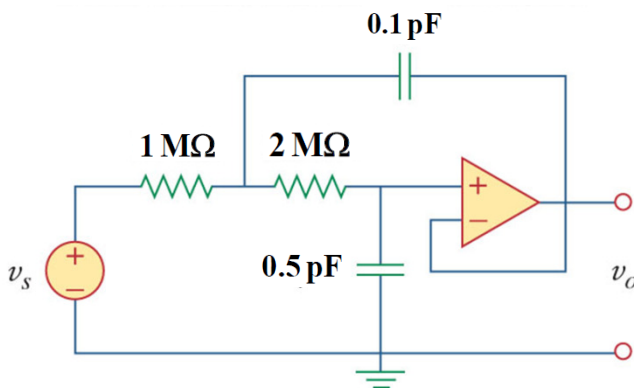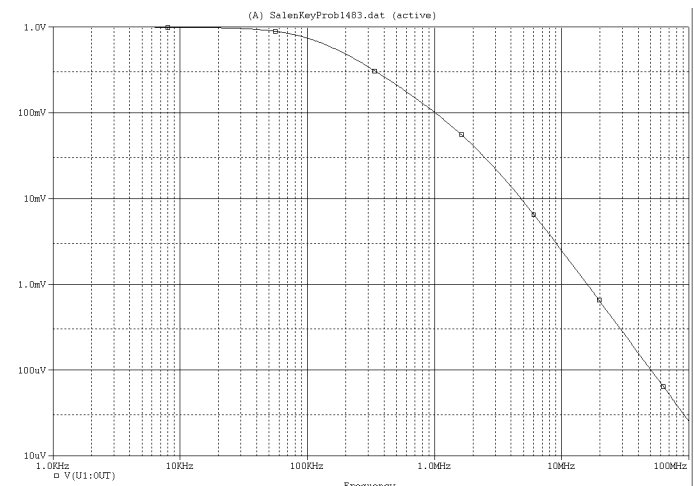

Sallen-Key Low-pass Filter

Cut-off frequency
 $f_c = 503292.121045[\text{Hz}]$


Quality factor
 $Q = 0.210818510678$

Damping ratio
 $\zeta = 2.37170824513$

IUPUI ECE 202 Spring 2015:

Homework #6 (SOLUTIONS) Name: _____

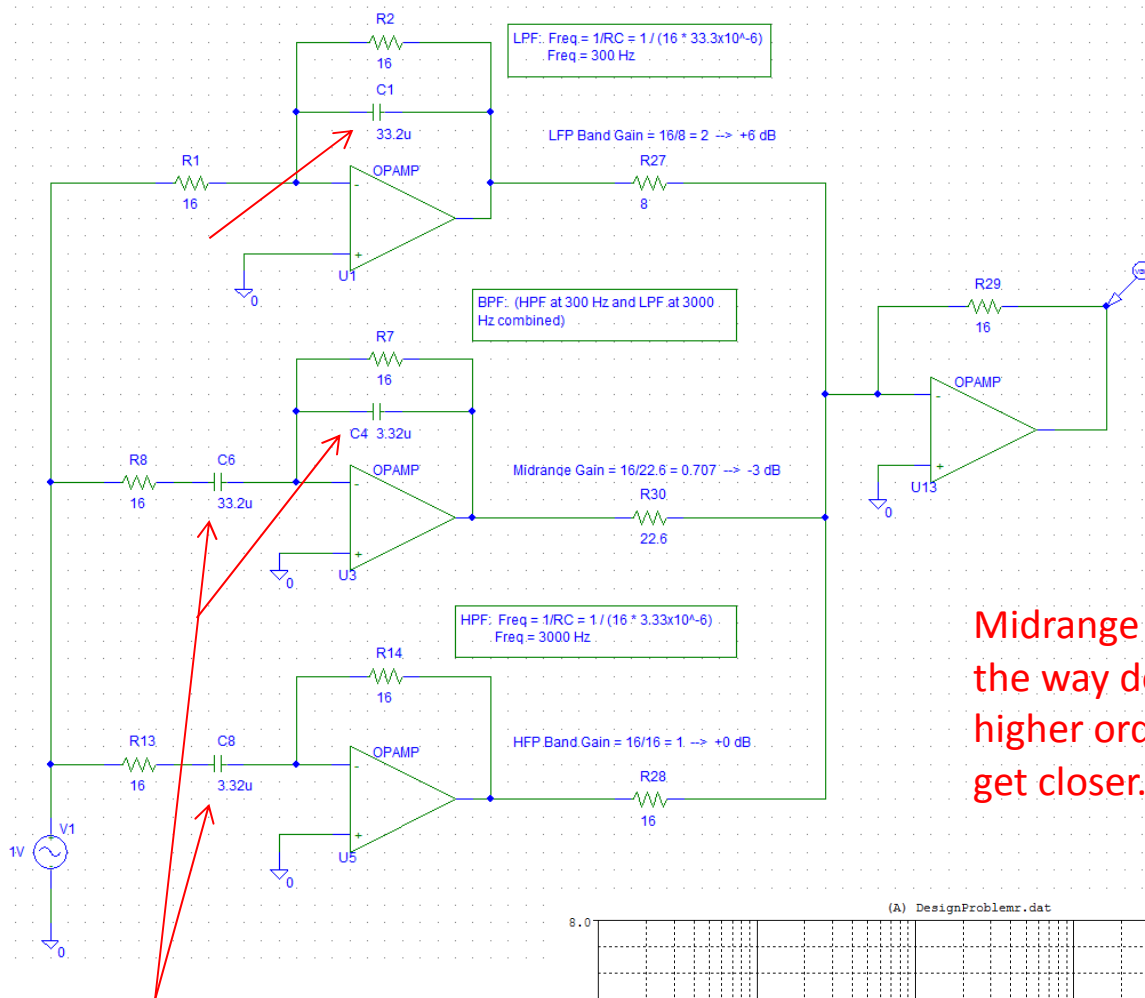3. (20 pts: Design Problem) Design a circuit to control the Base, Midrange, and Treble. Use 300 Hz as the crossover between the Base and Midrange and 3 KHz as the crossover between Midrange and Treble. Select resistor values to set the Base to +6 dB, the Midrange to -3 dB, and the Treble to +0dB Gain.



Midrange doesn't go all the way down to -3dB, higher order filter would get closer.

Time constants (Using 16 ohm resistor)


$$\omega_c = \frac{1}{RC}$$

$$R = 16 \Omega$$

$$C = \frac{1}{16 \times 2\pi f_c}$$

$$C_{LPF} = \frac{1}{(16) \times 2\pi \times 300} = 33.2 \mu F$$
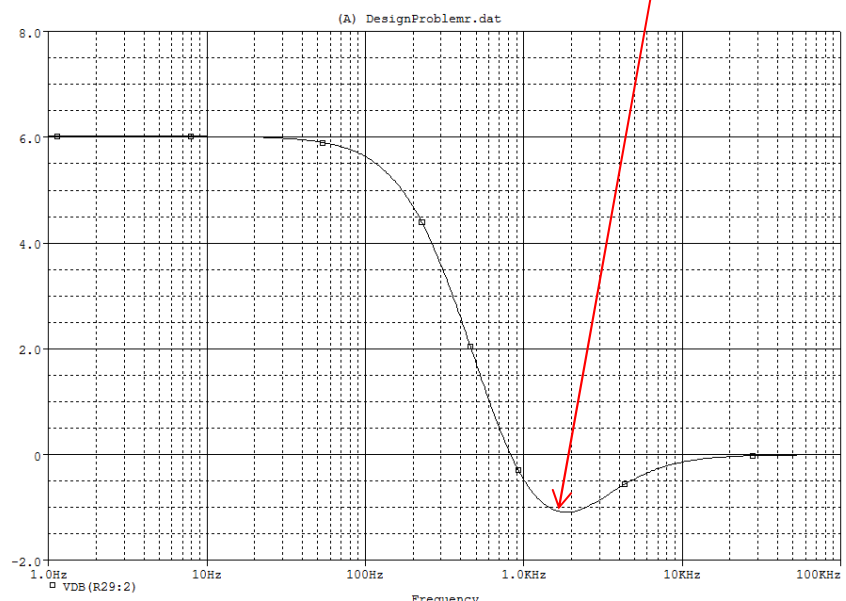
$$C_{HPF} = \frac{1}{(16) \times 2\pi \times 3000} = 3.32 \mu F$$



IUPUI ECE 202 Spring 2015: Homework #6 (SOLUTIONS) Name:

Another Solution:

