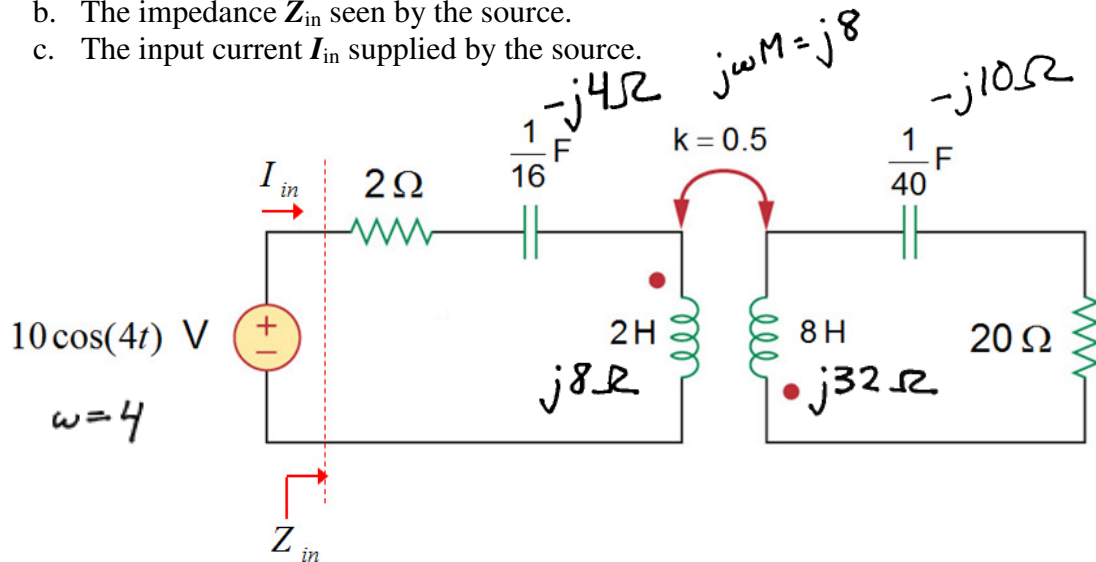


1. (20 points) For the circuit shown, determine:
- The mutual inductance M .
 - The impedance Z_{in} seen by the source.
 - The input current I_{in} supplied by the source.



$$a) M = k\sqrt{L_1 L_2} = 0.5\sqrt{2 \times 8} = \boxed{2}$$

$$b) Z_{in} = Z_{primary} + \frac{(\omega M)^2}{Z_{secondary}} = (2 - j4 + j8) + \frac{(2 \cdot 4)^2}{(20 + j32 - j10)}$$


$$= (2 + j4) + (1.448 - j1.5928) = \boxed{3.448 + j2.4072 \Omega}$$

$$= \boxed{4.205 \angle 34.92^\circ \Omega}$$

$$c) I_{in} = \frac{10 \angle 0^\circ}{4.205 \angle 34.92^\circ} = \boxed{2.378 \angle -34.92^\circ A}$$

$$\approx \boxed{1.9498 - j1.3613 A}$$

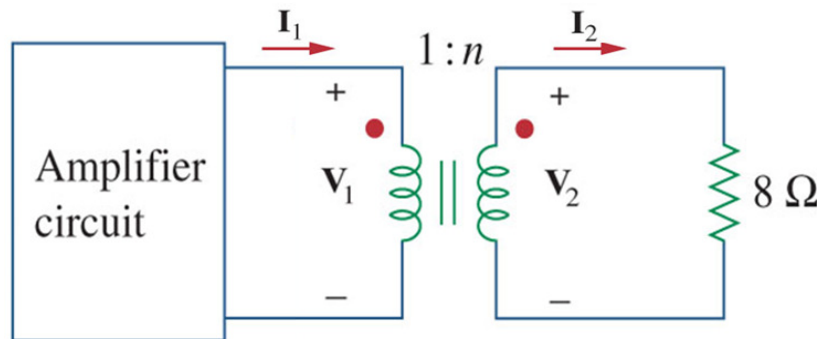3. (25 points) A transformer is used to match an amplifier with an $8\ \Omega$ load. The Thevenin equivalent of the amplifier is: $V_{th} = 10\ V_{rms}$, and $Z_{th} = 128\ \Omega$.
- Find the required turns ratio n for maximum power supplied to the $8\ \Omega$ load.
 - Determine the currents I_1 and I_2 .
 - Determine the voltages V_1 and V_2 .
 - Find the average power ($P_{ave} = I_{rms}^2 R$) in the $8\ \Omega$ load at this turns ratio.
 - If the amplifier signal was biased at 5 V DC (that is 5 V DC is added to the signal) how would this affect the average power absorbed by the $8\ \Omega$ load?



- a) For maximum power transfer, set the input impedance $Z_{in} = Z_{th}$

$$Z_{in} = \frac{Z_L}{n^2} = \frac{8}{n^2} = 128 \Rightarrow n^2 = \frac{8}{128} = \frac{1}{16} \Rightarrow n = \frac{1}{4} = 0.25$$

b) $I_1 = \frac{V_{th}}{(Z_{th} + Z_{in})} = \frac{10}{(128 + 128)} = 0.0391\ A \quad \text{or} \quad 39.1\ mA$

$$I_2 = \frac{I_1}{n} = \frac{0.0391}{0.25} = 0.156\ A \quad \text{or} \quad 156\ mA$$


c) $V_1 = I_1 Z_{in} = (0.0391)(128) = 5.0\ V$ (Note: at max power = $\frac{1}{2} V_1$)

$$V_2 = n V_1 = (0.25)(5) = 1.25\ V$$

d) $P_{ave} = I_2^2 Z_L = (0.156)^2 (8) = 0.195\ W \quad \text{or} \quad 195\ mW$

- e) No affect, transformers isolate DC current. Only AC current is coupled into the secondary.

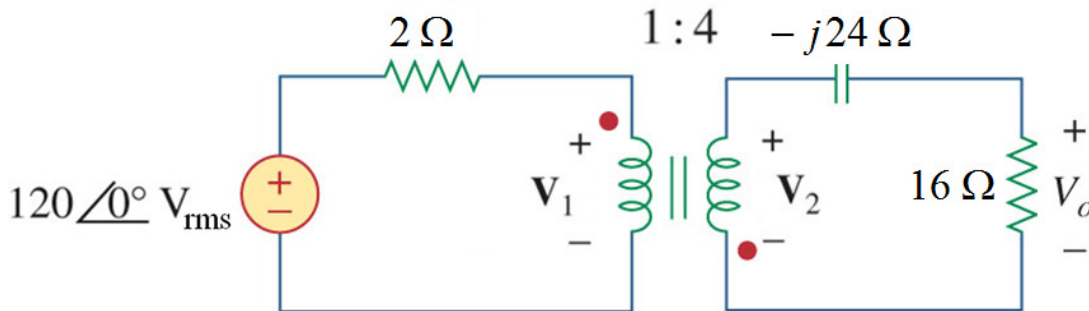4. (20 points) For the ideal transformer circuit shown,
- Find the voltage V_o across the $16\ \Omega$ resistor.
 - Find the complex power $S = V_{rms} I_{rms}^*$ supplied by the source.



4.) MESH #1: $2I_1 + V_1 = 120$

MESH #2: $(16 - j24)I_2 = V_2$

DOTS DIFFERENT

$$V_2 = -nV_1 = -4V_1$$

$$I_2 = -\frac{I_1}{n} = -\frac{I_1}{4}$$

SUBS FOR $V_2 I_2$: $(16 - j24)\left(-\frac{I_1}{4}\right) = -4V_1$

$$(4 - j6)I_1 = 4V_1 \Rightarrow (1 + j\frac{3}{2})I_1 = V_1$$

SUBS INTO #1: $2I_1 + (1 + j\frac{3}{2})I_1 = 120$

$$I_1 = \frac{120}{(3 - j\frac{3}{2})} = 32 + j16\text{ A}$$


$$I_2 = -\frac{I_1}{4} = -\frac{(32 + j16)}{4} = -8 - j4 = 8.944\angle -153.4^\circ$$

$$V_o = I_2 R = I_2 (16) = \boxed{\begin{matrix} -128 - j64\text{ V}_{rms} \\ 143.11\angle -153.4^\circ\text{ V}_{rms} \end{matrix}}$$

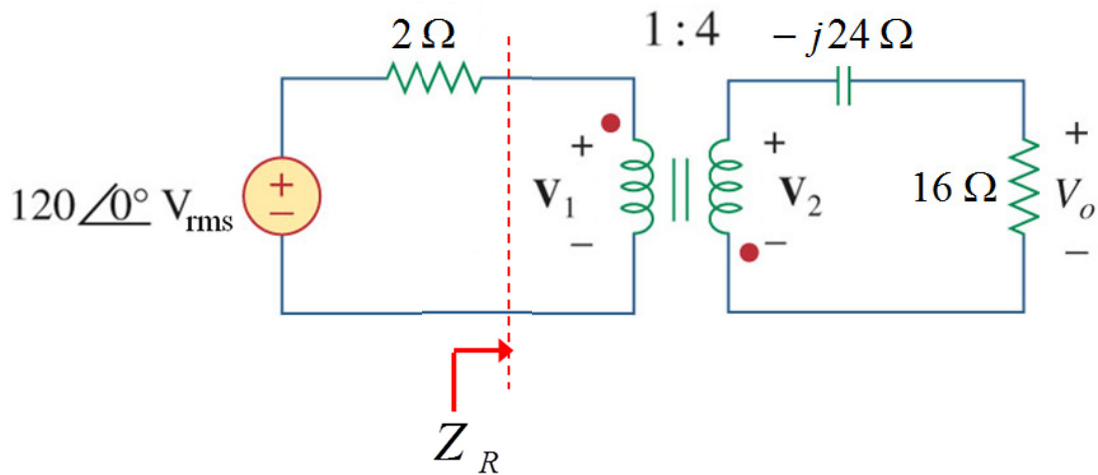b) $S = V I_{rms}^* = (120\angle 0^\circ) I_1^* = (120\angle 0^\circ)(32 - j16) = (120\angle 0^\circ)(35.77\angle -26.57^\circ)$

Page 4 of 5

$$\boxed{\begin{matrix} S = 4293.2\angle -26.59^\circ\text{ W} \\ S = 3840 - j1920\text{ W} \end{matrix}}$$



Alternate Solution using reflected impedance Z_R

$$a) \quad Z_R = \frac{Z_L}{n^2} = \frac{16 - j24}{4^2} = 1 - j1.5$$

Find the current I_1 on the primary side


$$I_1 = \frac{120}{2 + (1 - j1.5)} = 32 + j16 \text{ A}$$

$$I_2 = -\frac{I_1}{n} = -\frac{32 + j16}{4} = -8 - j4 \text{ A}$$

$$V_o = I_2(16) = (-8 - j4)(16) = -128 - j64 \text{ V or } 143.11 \angle -153.43^\circ \text{ V}$$

b) Find complex power same as before

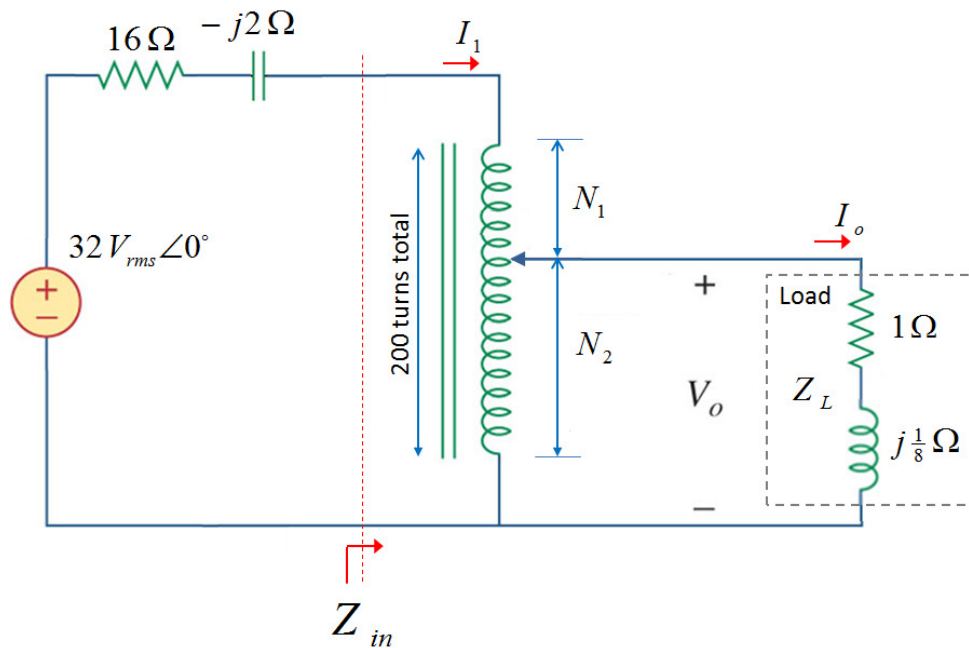5. (20 points) In the figure below the tap is initially to $N_2 = 50$.
- Find the impedance Z_{in} seen looking into the primary side.
 - Find the current I_o delivered to the load.
 - Find the complex power S delivered to the load.
 - Find the complex power S delivered to the load if $N_2 = 100$.



$$a) \quad Z_{in} = \left(\frac{N_1 + N_2}{N_2} \right)^2 Z_L = \left(\frac{200}{50} \right)^2 (1 + \frac{1}{8}j) = \boxed{(16 + j2)\ \Omega}$$

$$b) \quad I_1 = \frac{32}{(16 - j2 + Z_{in})} = \frac{32}{(16 - j2 + 16 + j2)} = \frac{32}{(16 + 16)} = 1.0\ \text{A}$$

$$I_o = \left(\frac{N_1 + N_2}{N_2} \right) I_1 = \frac{200}{50} (1.0) = \boxed{4.0\ \text{A}}$$

$$c) \quad S = V_o I_o^* = |I_o|^2 Z_L = (4)^2 (1 + j\frac{1}{8})$$

$$S = \boxed{16 + j2\ \text{W} \quad \text{or} \quad 16.125 \angle 7.125^\circ\ \text{W}}$$

$$d) \quad Z_{in} = \left(\frac{N_1 + N_2}{N_2} \right)^2 Z_L = \left(\frac{200}{100} \right)^2 (1 + \frac{1}{8}j) = (4 + j0.5) \, \Omega$$

$$I_1 = \frac{32}{(16 - j2 + Z_{in})} = \frac{32}{(16 - j2 + 4 + j0.5)} = \frac{32}{(20 - j1.5)}$$

$$I_1 = 1.59 + j0.119 \, \text{A} \quad \text{or} \quad 1.596 \angle 4.29^\circ \, \text{A}$$

$$I_o = \left(\frac{N_1 + N_2}{N_2} \right) I_1 = \frac{200}{100} (1.59 + j0.119)$$

$$I_o = 3.182 + j0.239 \, \text{A} \quad \text{or} \quad 3.191 \angle 4.289^\circ$$

$$S = V_o I_o^* = |I_o|^2 Z_L = (3.191)^2 (1 + j\frac{1}{8})$$

$$S = 10.18 + j1.27 \, \text{W} \quad \text{or} \quad 10.26 \angle 7.125^\circ \, \text{W}$$