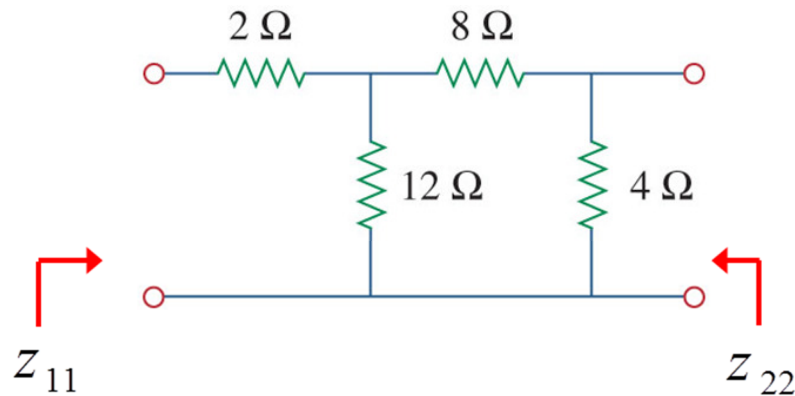


IUPUI ECE 202 Spring 2015:
Homework #10 (SOLUTIONS) Name: _____

1. (Prob. 19.1 in text) Obtain the z parameters for the network in the figure below:



First find z_{11} which is the open circuit input impedance:


$$z_{11} = 2 + 12 \parallel (8 + 4) = 2 + \frac{12(12)}{12 + 12} = 8 \ \Omega$$

Likewise find z_{22} which is the open circuit output impedance:

$$z_{22} = 4 \parallel (8 + 12) = \frac{4(20)}{4 + 20} = 3.333 \ \Omega$$

To find z_{21} apply a current source to the input I_1 and determine the voltage at the output and V_2 :

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

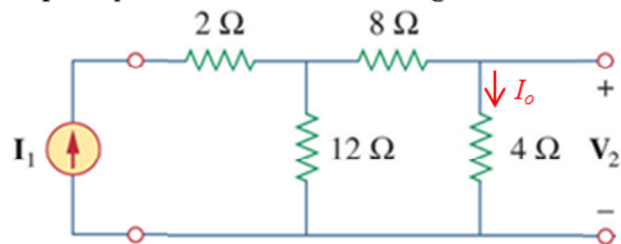

Use a current divider equation to find the current in the branch with the 8 Ω and 4 Ω resistors.

$$I_0 = \frac{12}{12 + (4 + 8)} I_1 = \frac{1}{2} I_1$$


$$V_2 = 4I_0 = 4\left(\frac{1}{2} I_1\right) = 2I_1$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{2I_1}{I_1} = 2 \ \Omega$$

IUPUI ECE 202 Spring 2015:
Homework #10 (SOLUTIONS) Name:

To find z_{12} apply a current source to the output I_2 and determine the voltage at the input and V_1 :

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

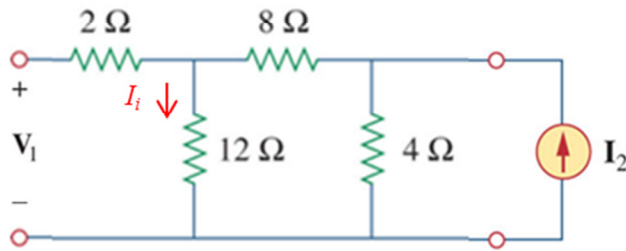

Use a current divider equation to find the current in the branch with the 8 Ω and 12 Ω resistors.

$$I_i = \frac{4}{4 + (8 + 12)} I_2 = \frac{1}{6} I_2$$



$$V_2 = 12I_i = 12\left(\frac{1}{6} I_2\right) = 2I_2$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{2I_2}{I_2} = 2 \Omega$$

Note: we could have also used the fact that since the circuit contains all R's, L's, and C's and has no dependant sources that the circuit is reciprocal and thus $z_{12} = z_{21}$.

$$[z] = \begin{bmatrix} 8 & 2 \\ 2 & 3.333 \end{bmatrix} \Omega$$

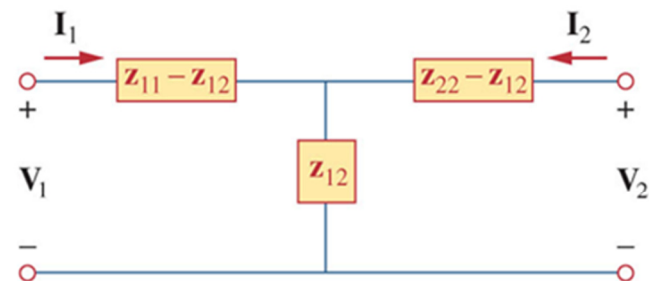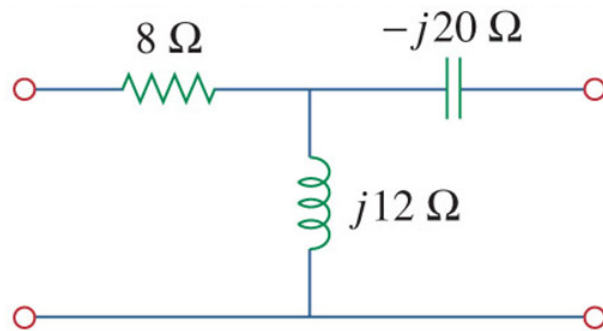2. (Prob. 19.3 from Text) Find the z parameters of the circuit below:




$$z_{12} = z_{21} = j12\ \Omega$$

$$z_{11} - z_{12} = 8 \Rightarrow z_{11} = 8 + z_{12} = 8 + j12\ \Omega$$

$$z_{22} - z_{12} = -j20 \Rightarrow z_{22} = -j20 + z_{12} = -j20 + j12 = -j8\ \Omega$$


IUPUI ECE 202 Spring 2015:
Homework #10 (SOLUTIONS) Name: _____

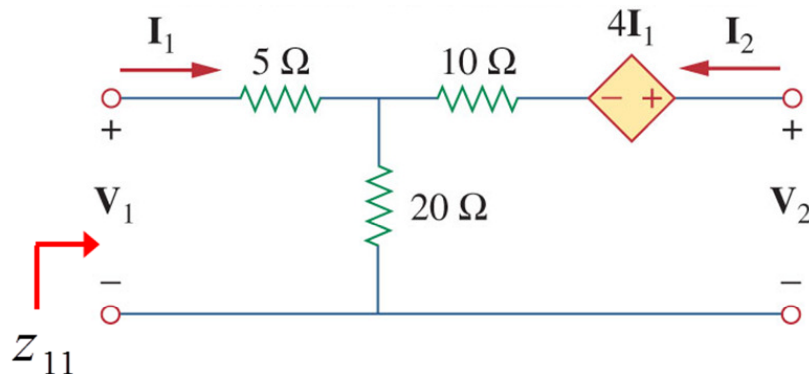3. (Prob. 19.6 from Text) Compute the z parameters of the circuit below:




To find z_{11} note that the $10\ \Omega$ resistor and dependent source contribute nothing since they are part of an open branch.

$$z_{11} = 5 + 20 = 25\ \Omega$$

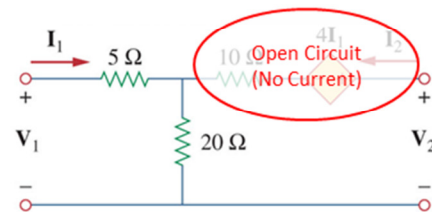

To find z_{22} note that since I_1 is zero, the dependant source is $4(0) = 0$ (short circuit) so the circuit can be replaced as follows if the input is open:

$$z_{22} = 10 + 20 = 30\ \Omega$$

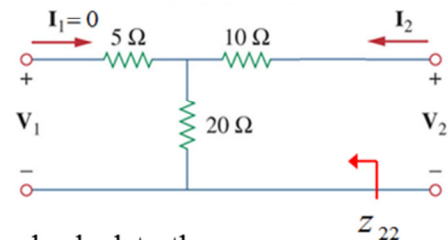


To find z_{21} we can place a 1 A current source at the input and calculate the output voltage V_2 :

$$I_1 = 1$$

Voltage across the $20\ \Omega$ is just:

$$V_{20\Omega} = 20I_1 = 20$$

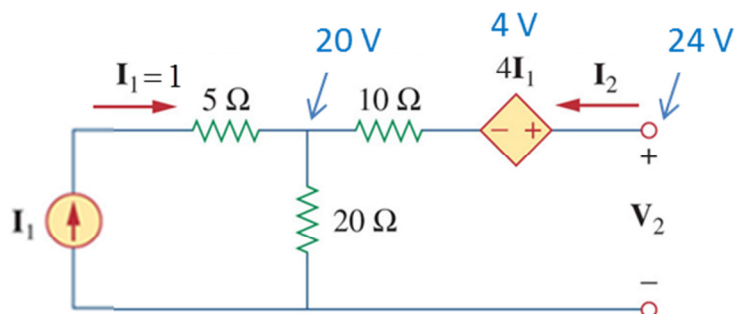

There is no current in the open branch so there is no voltage drop across the $10\ \Omega$ resistor, however the dependant source will raise the voltage at the output by 4 volts (see figure)

$$V_2 = 20 + 4I_1 = 24$$


$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{24}{1} = 24\ \Omega$$

IUPUI ECE 202 Spring 2015:
Homework #10 (SOLUTIONS) Name:

To find z_{12} we can place a 1 A current source at the output and calculate the input voltage V_1 :

Voltage across the $20\ \Omega$ is just:

$$V_{20\ \Omega} = 20I_1 = 20$$

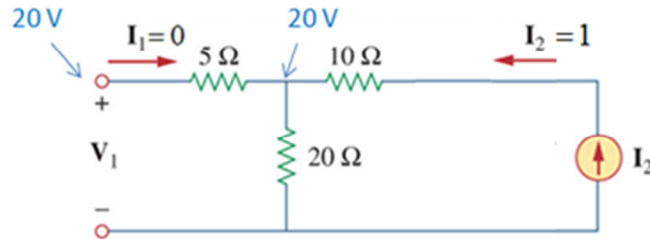

There is no current in the open branch so there is no voltage drop across the $5\ \Omega$ resistor, therefore the input voltage is the same as the voltage across the $20\ \Omega$ resistor.

$$V_2 = V_{20\ \Omega} = 20$$

$$z_{12} = \frac{V_1}{I_2} \bigg|_{I_1=0} = \frac{20}{1} = 20\ \Omega$$

$$[z] = \begin{bmatrix} 25 & 20 \\ 24 & 30 \end{bmatrix} \Omega$$