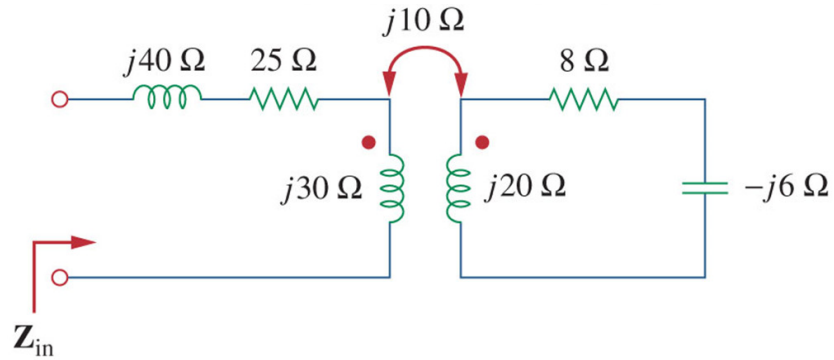


IUPUI ECE 202 Spring 2015:


Homework #3 (Due in class: Feb 4, 2015) Name: _____

1. (Prob. 13.30 in text) For the circuit shown, find the input impedance by:
- Using the concept of reflected impedance Z_R
 - Replacing the linear transformer by its T equivalent circuit




IUPUI ECE 202 Spring 2015:
Homework #3 (Due in class: Feb 4, 2015) Name: _____

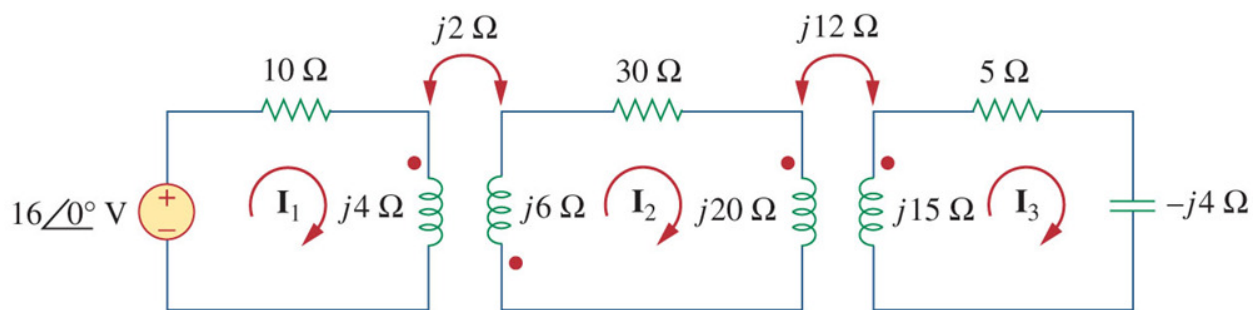2. (Prob. 13.35 from Text) Find currents \mathbf{I}_1 , \mathbf{I}_2 , and \mathbf{I}_3 in the circuit below:




IUPUI ECE 202 Spring 2015:
Homework #3 (Due in class: Feb 4, 2015) Name: _____

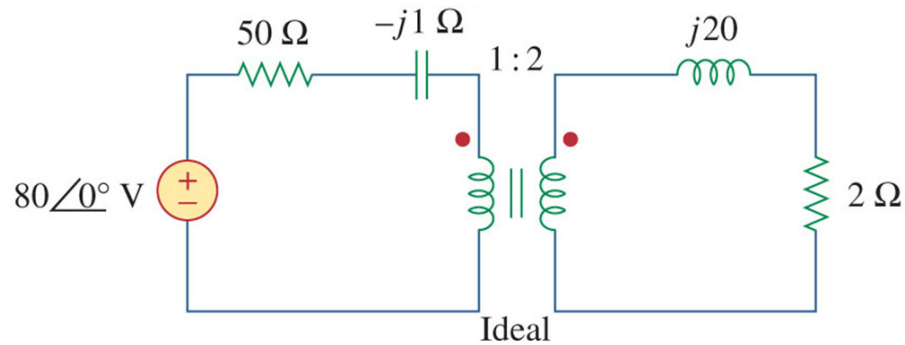3. (Prob. 13.42 from Text) For the circuit shown, determine the power absorbed by the $2\ \Omega$ resistor. (Assume the 80 V is a rms value).




IUPUI ECE 202 Spring 2015:
Homework #3 (Due in class: Feb 4, 2015) Name: _____

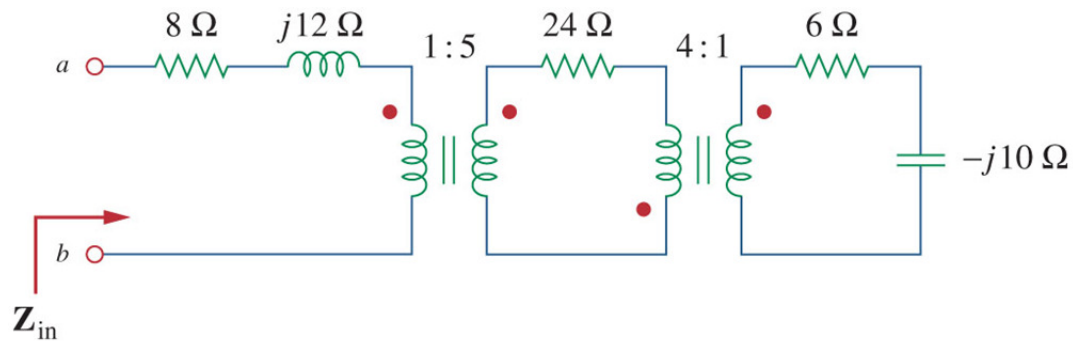4. (Prob. 13.50 from Text) Calculate the input impedance for the network below:



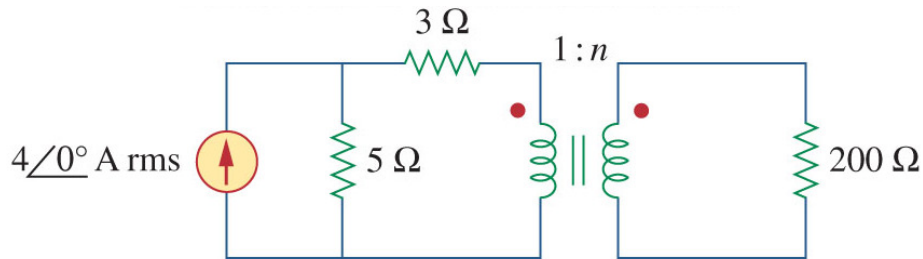5. ("Based on" Prob. 13.53 from Text) Refer to the figure below for the following:
- Find the turns ratio n for maximum power supplied to the $200\ \Omega$ load.
 - Find the average power ($P_{ave} = I_{rms}^2 R$) in the $200\ \Omega$ load at this turns ratio.
 - Find the average power in the $200\ \Omega$ load if the turns ratio $n = 6$.



IUPUI ECE 202 Spring 2015:

Homework #3 (Due in class: Feb 4, 2015) Name: _____

6. An audio amplifier with an internal Thevenin impedance of $16\ \Omega$ uses a source matching autotransformer shown below to match an $8\ \Omega$ speaker for maximum power transfer.
- Find the location of the tap N_2 for maximum power transfer to the speaker.
 - Find the Voltage V_o and Current I_o delivered to the speaker.
 - Find the average power P_{ave} delivered to the speaker.
 - Find the location of the tap N_2 if we replaced speaker with a $4\ \Omega$ speaker.
 - Find the average power P_{ave} delivered to the $4\ \Omega$ speaker.

