
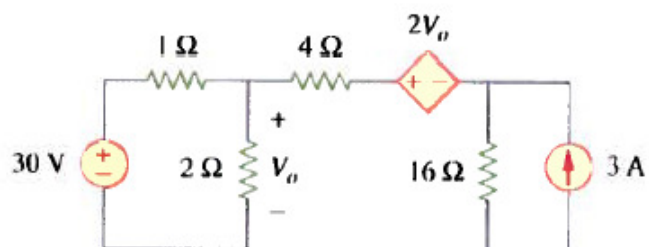


**3.23** Use nodal analysis to find  $V_o$  in the circuit of Fig. 3.72.

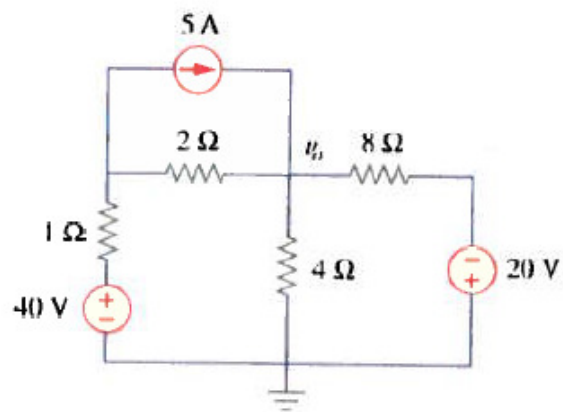


**Figure 3.72**  
For Prob. 3.23.

**3.51** Apply mesh analysis to find  $v_o$  in the circuit of Fig. 3.96.




**Figure 3.96**  
For Prob. 3.51.

**4.41** Find the Thevenin and Norton equivalents at terminals  $a$ - $b$  of the circuit shown in Fig. 4.108.

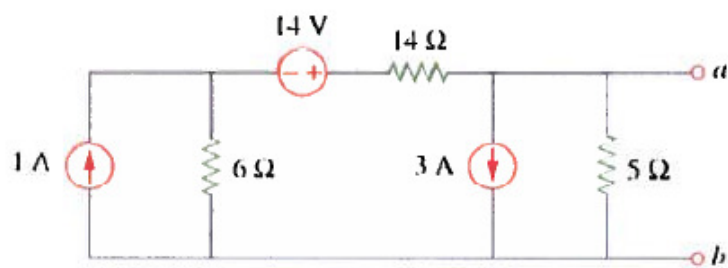


**Figure 4.108**  
For Prob. 4.41.

**5.27** Find  $v_o$  in the op amp circuit of Fig. 5.65.

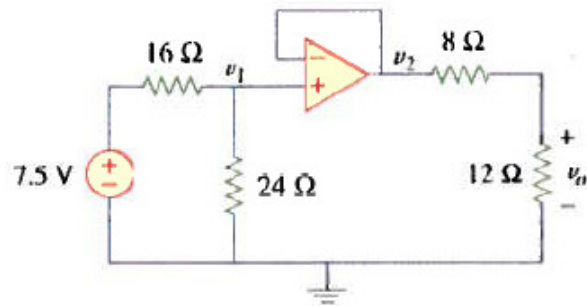


**Figure 5.65**  
For Prob. 5.27.

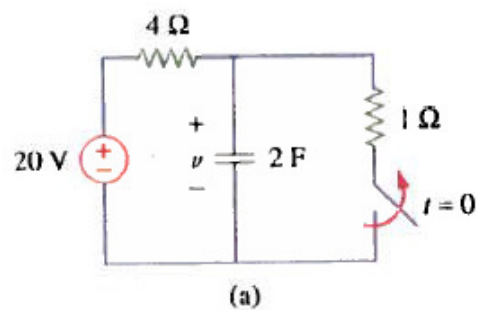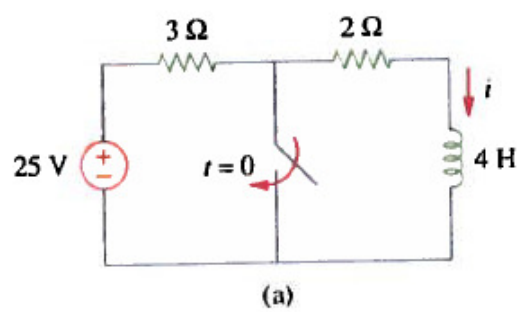
**7.39** Calculate the capacitor voltage for  $t < 0$  and  $t > 0$  for each of the circuits in Fig. 7.106.



**7.53** Determine the inductor current  $i(t)$  for both  $t < 0$  and  $t > 0$  for each of the circuits in Fig. 7.119.



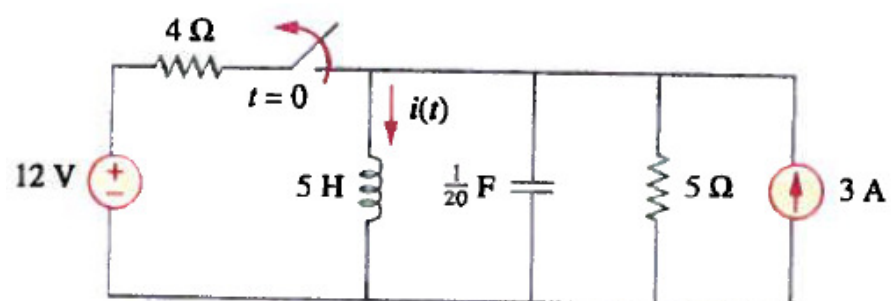8.49 Determine  $i(t)$  for  $t > 0$  in the circuit of Fig. 8.96.



**10.1** Determine  $i$  in the circuit of Fig. 10.50.

