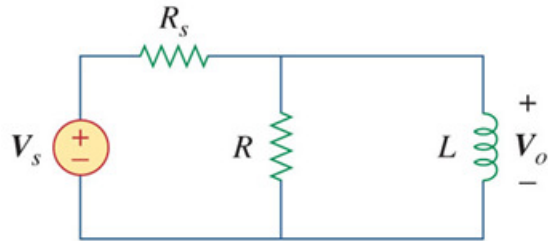



IUPUI ECE 202 Spring 2015:
Homework #4 (SOLUTIONS) Name: _____

1. (Prob. 14.5 in text) For each of the circuits shown below, find the transfer function:

$$\mathbf{H}(s) = \mathbf{V}_o(s) / \mathbf{V}_s(s)$$



(a)

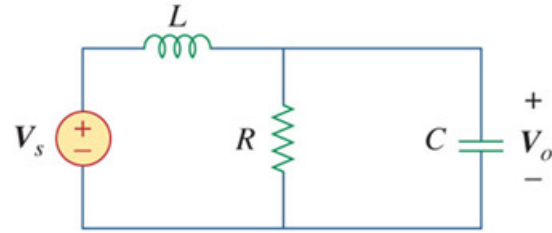

(b)

$$(a) \text{ Let } Z = R // sL = \frac{sRL}{R + sL}$$

$$V_o = \frac{Z}{Z + R_s} V_s$$

$$H(s) = \frac{V_o}{V_s} = \frac{Z}{Z + R_s} = \frac{\frac{sRL}{R + sL}}{R_s + \frac{sRL}{R + sL}} = \frac{sRL}{RR_s + s(R + R_s)L}$$

$$(b) \text{ Let } Z = R // \frac{1}{sC} = \frac{R \times \frac{1}{sC}}{R + \frac{1}{sC}} = \frac{R}{1 + sRC}$$



$$V_o = \frac{Z}{Z + sL} V_s$$

$$H(s) = \frac{V_o}{V_i} = \frac{Z}{Z + sL} = \frac{\frac{R}{1 + sRC}}{sL + \frac{R}{1 + sRC}} = \frac{R}{s^2 LRC + sL + R}$$

IUPUI ECE 202 Spring 2015:
Homework #4 (SOLUTIONS) Name: _____

2. (Prob. 14.6 from Text) For the circuit shown below, find the transfer function:

$$H(s) = I_o(s) / I_s(s)$$

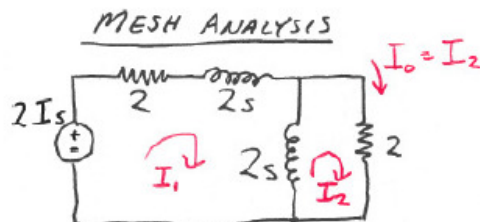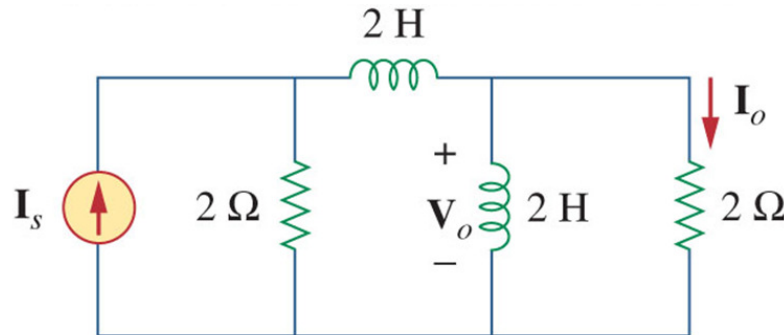

MESH I_1 : $2I_s = (2 + 2s)I_1 + 2sI_1 - 2sI_2$
 $I_s = (1 + 2s)I_1 - sI_2$

MESH I_2 : $0 = -2sI_1 + (2 + 2s)I_2$
 $I_1 = \frac{(1+s)}{s} I_2$

SUB I_1 into I_1 MESH EQⁿ

$$I_s = \frac{(1+2s)(1+s)}{s} I_2 - sI_2$$

$$sI_s = (1 + 3s + 2s^2)I_2 - s^2I_2$$

$$sI_s = (s^2 + 3s + 1)I_2$$

SINCE $I_2 = I_o$

$$\boxed{\frac{I_o}{I_s} = \frac{s}{s^2 + 3s + 1} = H(s)}$$

Node Voltage

NODE V_s :

$$I_s = \frac{V_s}{2} + \frac{V_s - V_o}{2s}$$

$$2sI_s = sV_s + V_s - V_o$$

$$2sI_s = (1+s)V_s - V_o$$

NODE V_o :

$$0 = \frac{V_o - V_s}{2s} + \frac{V_o}{2s} + \frac{V_o}{2}$$

$$0 = V_o - V_s + V_o + sV_o$$

$$V_s = (2+s)V_o$$

SUBSTITUTION V_o NODE INTO V_s NODE

$$2sI_s = (1+s)(2+s)V_o - V_o$$

$$= (2 + 3s + s^2 - 1)V_o$$

$$2sI_s = (s^2 + 3s + 1)V_o$$

SINCE $V_o = 2I_o$

$$2sI_s = (s^2 + 3s + 1)2I_o$$

SAME

$$\boxed{\frac{I_o}{I_s} = \frac{s}{s^2 + 3s + 1} = H(s)}$$

IUPUI ECE 202 Spring 2015:
Homework #4 (**SOLUTIONS**) Name: _____

3. (Prob. 14.17 from Text) Sketch the magnitude and phase Bode plots for the following transfer function:

$$G(s) = \frac{s}{(s+2)^2(s+1)}$$


First put into proper (1+s/a) form:

$$\text{Gain } K = 0.25 \rightarrow 20\log_{10}(0.25) = -12 \text{ dB}$$

$$G(s) = \frac{s}{(2)^2 \left(1 + \frac{s}{2}\right)^2 \left(1 + \frac{s}{1}\right)} = \frac{\left(\frac{1}{4}\right)s}{\left(1 + \frac{s}{2}\right)^2 \left(1 + \frac{s}{1}\right)}$$


Zero at the origin (Offset 4)
2 Poles at 2
1 Pole at 1

Magnitude Plot

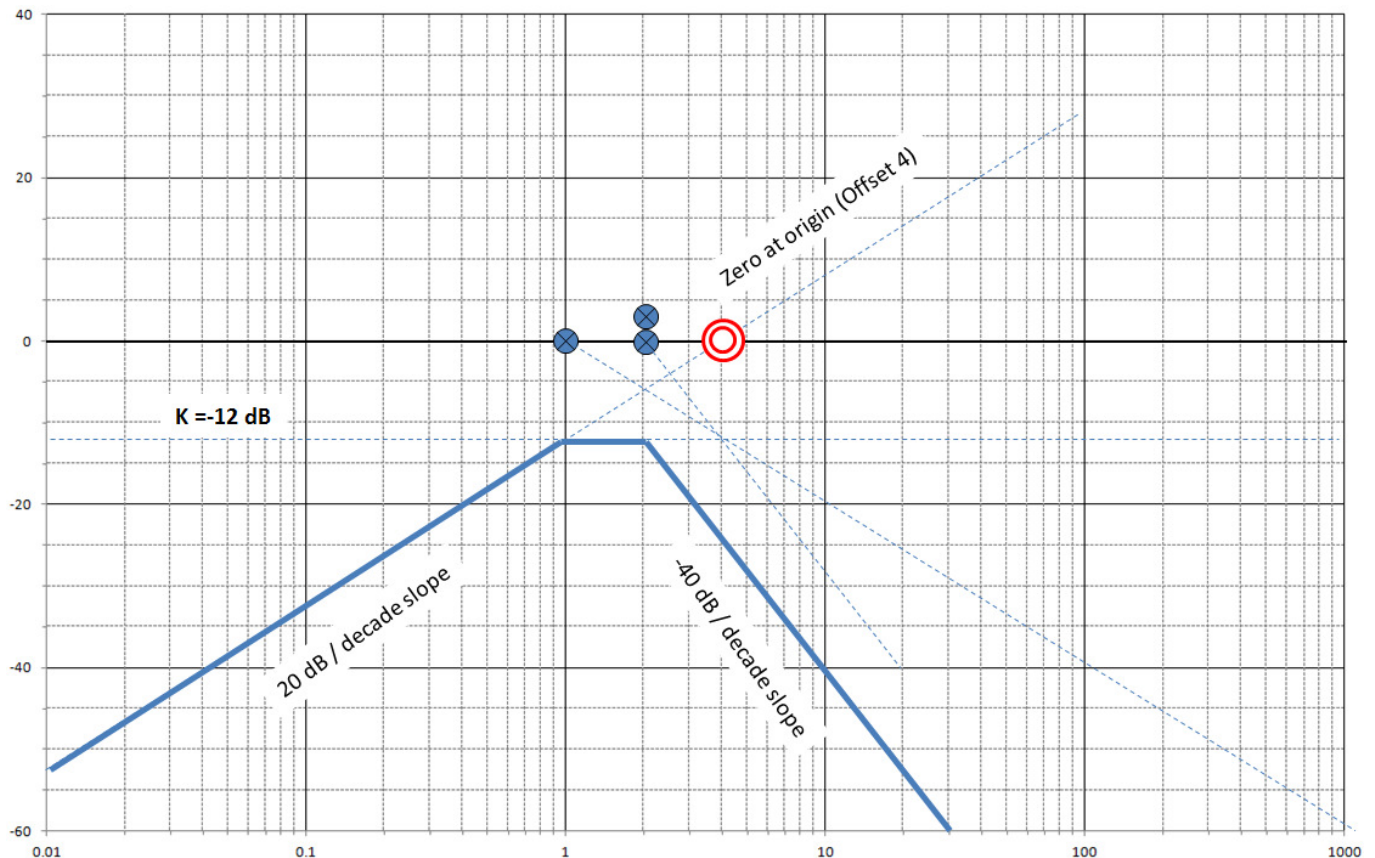

IUPUI ECE 202 Spring 2015:
Homework #4 (SOLUTIONS) Name: _____

Phase Plot

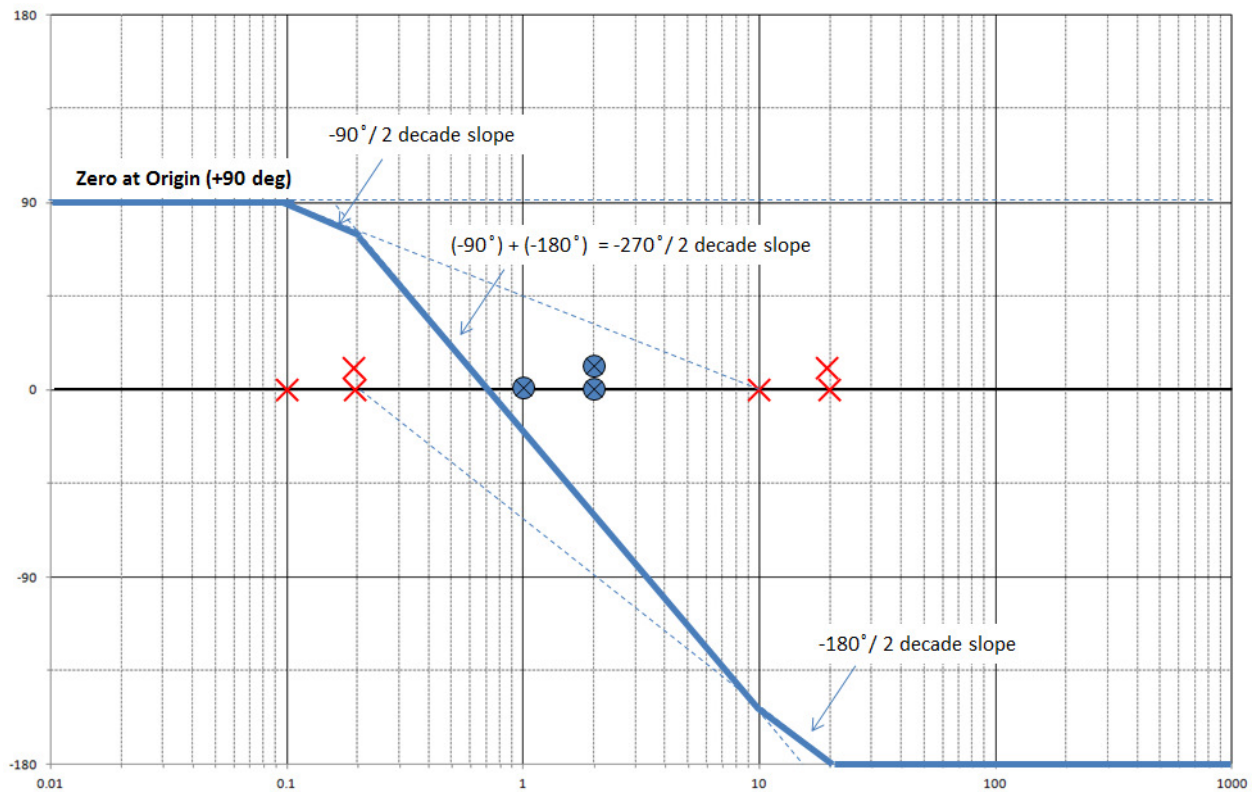

Notice:

$$G(s) = \frac{\left(\frac{1}{4}\right)s}{\left(1 + \frac{s}{2}\right)^2 \left(1 + \frac{s}{1}\right)}$$

→ +90	One Zero
→ -90	Three Poles
-90	
-90	
-180	Phase as $\omega \rightarrow \infty$

IUPUI ECE 202 Spring 2015:

Homework #4 (SOLUTIONS) Name: _____

4. (Prob. 14.19 from Text) Sketch the magnitude and phase Bode plots for the following transfer function:

$$H(s) = \frac{80s}{(s+10)(s+20)(s+40)}$$


First put into proper $(1+s/a)$ form:

$$H(s) = \frac{80s}{10\left(1+\frac{s}{10}\right)20\left(1+\frac{s}{20}\right)40\left(1+\frac{s}{40}\right)} = \frac{\frac{1}{100}s}{\left(1+\frac{s}{10}\right)\left(1+\frac{s}{20}\right)\left(1+\frac{s}{40}\right)}$$

Poles at 10, 20, and 40


Zero at the origin (Offset 100)

Magnitude Plot

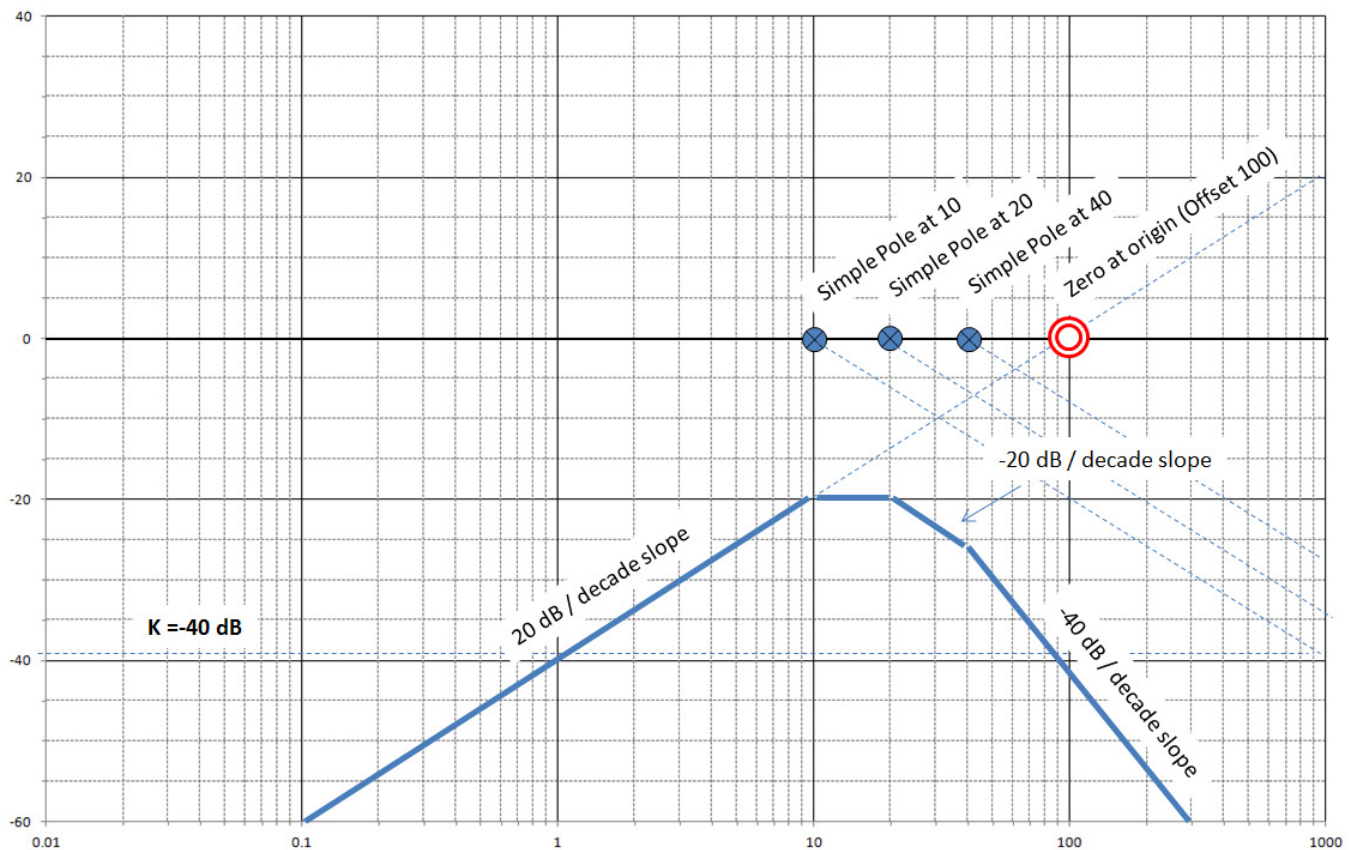

IUPUI ECE 202 Spring 2015:
Homework #4 (SOLUTIONS) Name: _____

Phase Plot

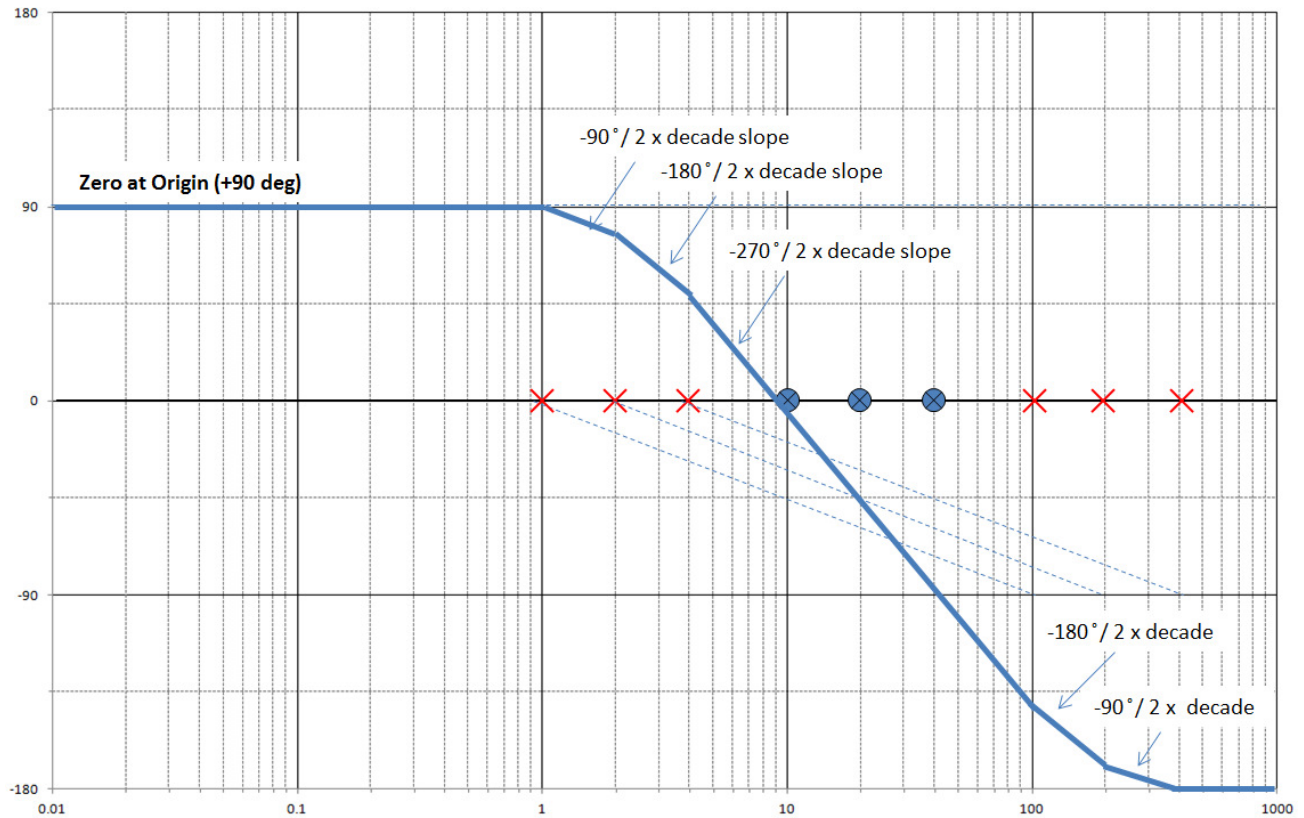

Notice:

$$H(s) = \frac{\frac{1}{100}s}{\left(1 + \frac{s}{10}\right)\left(1 + \frac{s}{20}\right)\left(1 + \frac{s}{40}\right)}$$


→ +90	One Zero
→ -90	Three Poles
-90	
-90	
<hr style="width: 100px; margin-left: 0;"/> -180	Phase as $\omega \rightarrow \infty$

IUPUI ECE 202 Spring 2015:

Homework #4 (SOLUTIONS) Name: _____

5. (Prob. 14.22 from Text)

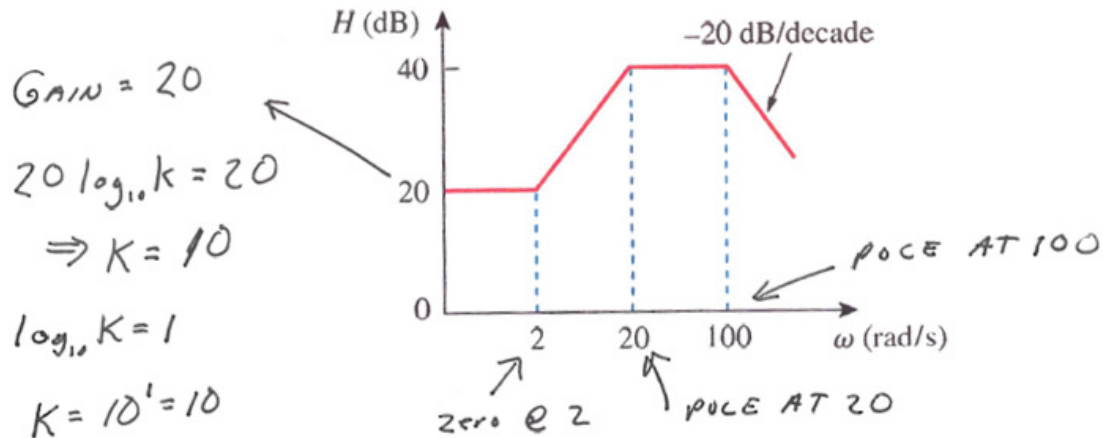a. **Part 1:** Find the transfer function $H(\omega)$ with the Bode magnitude plot as shown below:



$$H(s) = \frac{10 \left(1 + \frac{s}{2}\right)}{\left(1 + \frac{s}{20}\right) \left(1 + \frac{s}{100}\right)} = \frac{10 \left(\frac{1}{20}\right) (20 + s)}{\left(\frac{1}{20}\right) (20 + s) \left(\frac{1}{100}\right) (100 + s)}$$

$$H(s) = \frac{10,000 (2 + s)}{(20 + s)(100 + s)} \quad \text{sub } s = j\omega \text{ for } H(\omega)$$

b. **Part II:** Use MATLAB to generate the Bode plot from your derived transfer function

