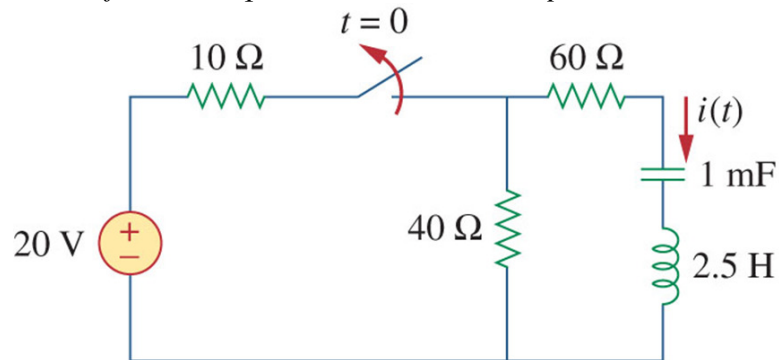


IUPUI ECE 202 Spring 2015:
Homework #9 (SOLUTION KEY) Name: _____

1. (Prob. 16.20 in text) Find $i(t)$ for $t > 0$ in the circuit below:


Hint: Should be able to factor the quadratic into a double pole.



First find initial conditions
(circuit for $t < 0$)

$$V_1 = \frac{40}{40 + 10}(20) = 16 \text{ V}$$

$$V_c = V_1 = 16 \text{ V}$$

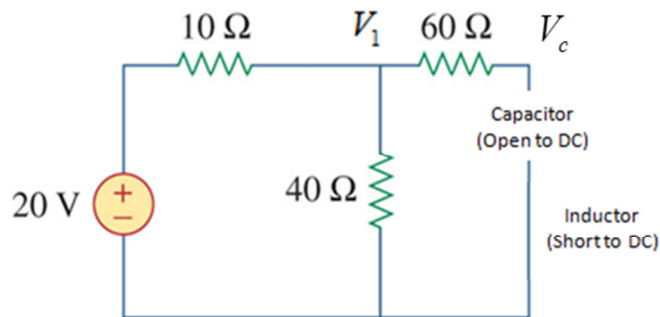

Initial capacitor voltage is 16 V. Now use Laplace Model of Capacitor with initial conditions. Model circuit for $t > 0$

Loop equation:


$$I(40) + I(60) + I\left(\frac{10^3}{s}\right) + \frac{16}{s} + I(2.5s) = 0$$

$$I\left(100 + \frac{10^3}{s} + 2.5s\right) = -\frac{16}{s}$$

$$I(2.5s^2 + 100s + 1000) = -16$$

$$I(s^2 + 40s + 400) = \frac{-16}{2.5} = -6.4$$

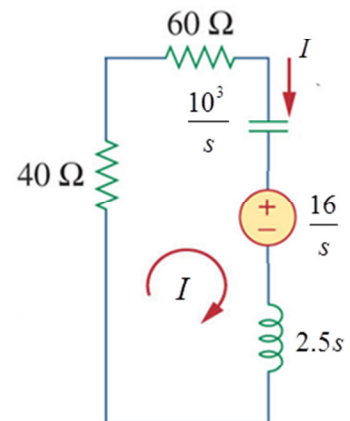
$$I = \frac{-6.4}{(s^2 + 40s + 400)} = \frac{-6.4}{(s + 20)^2}$$



$$i(t) = \mathcal{L}^{-1}\left[\frac{-6.4}{(s + 20)^2}\right] = -6.4te^{-20t} \text{ A for } t > 0$$

IUPUI ECE 202 Spring 2015:
Homework #9 (SOLUTION KEY) Name: _____

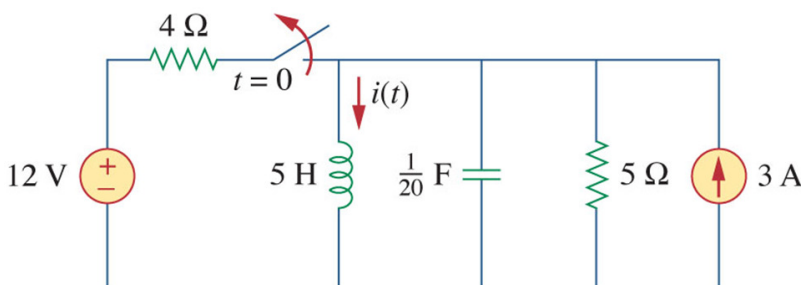
2. (Prob. 16.43 from Text) Find $i(t)$ for $t > 0$ in the circuit below:



First find initial conditions (circuit for $t < 0$). Capacitor is like an open, inductor like a short. Initial voltage across capacitor = 0. Initial current through inductor is $3 + 12/4 = 6$ Amps

$$i_l(0^-) = \frac{12}{4} + 3 = 6$$

$$v_c(0^-) = 0$$

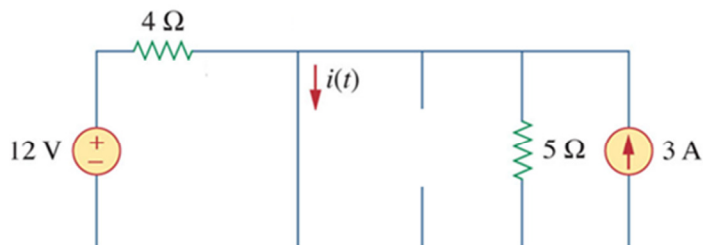

Next use the initial conditions to construct the $t > 0$ model of the circuit. Sum the currents into the single node to find V :


$$V \left(\frac{1}{5s} + \frac{s}{20} + \frac{1}{5} \right) + \frac{6}{s} = \frac{3}{s}$$

$$V \left(\frac{1}{5} + \frac{s^2}{20} + \frac{s}{5} \right) = -3$$

$$V(4 + s^2 + 4s) = -60$$

$$V = \frac{-60}{s^2 + 4s + 4} = \frac{-60}{(s+2)^2}$$

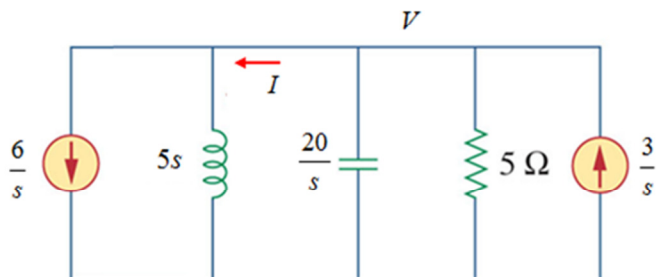Current I is the sum of the current through the inductor and initial condition current source



$$I = \frac{-60}{(s+2)^2} \cdot \frac{1}{5s} + \frac{6}{s} = \frac{6}{s} - \frac{12}{s(s+2)^2} = \frac{6}{s} + \frac{k_0}{s} + \frac{k_1}{(s+2)^2} + \frac{k_2}{(s+2)}$$

Substitute 1 in for s to find the last k_2

Residue method

$$6 - \frac{12}{(0+2)^2} = 6 + k_0 \Rightarrow k_0 = -3$$

Residue method

$$-\frac{12}{-2} = k_1 = 6$$

$$\frac{6}{1} - \frac{12}{1(1+2)^2} = \frac{6}{1} - \frac{3}{1} + \frac{6}{(1+2)^2} + \frac{k_2}{(1+2)}$$

$$-4 = -9 + 2 + k_2 \Rightarrow k_2 = 3$$


$$I = \frac{6}{s} - \frac{3}{s} + \frac{6}{(s+2)^2} + \frac{3}{(s+2)}$$

$$i(t) = 3u(t) + 6te^{-2t} + 3e^{-2t} \text{ A for } t > 0$$


IUPUI ECE 202 Spring 2015:
Homework #9 (SOLUTION KEY) Name: _____

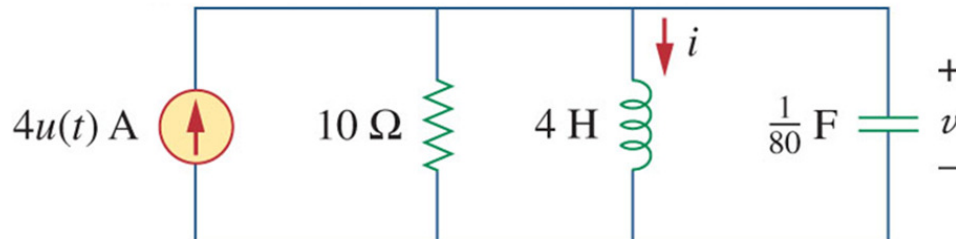3. (Prob. 16.63 from Text) Consider the parallel RLC circuit shown below. Find $v(t)$ for $t > 0$ given the following initial conditions: $v(0) = 5$ V and $i(0) = -2$ A:

Hint: May need to use the "Complete the square" method



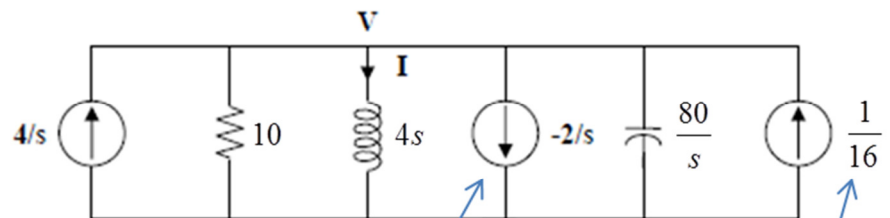First construct the s-domain form of the circuit with the initial conditions:



Summing current into the node

$$\frac{4}{s} + \frac{2}{s} + \frac{1}{16} = V \left(\frac{1}{10} + \frac{1}{4s} + \frac{s}{80} \right)$$

$$6 + \frac{s}{16} = V \left(\frac{s}{10} + \frac{1}{4} + \frac{s^2}{80} \right)$$

$$480 + 5s = V(8s + 20 + s^2)$$

$$V = \frac{5s + 480}{(s^2 + 8s + 20)}$$

Inductor Initial Condition

$$\frac{i_L(0^-)}{s} = -\frac{2}{s}$$

Capacitor Initial Condition

$$v_C(0^-)C = 5 \left(\frac{1}{80} \right) = \frac{1}{16}$$

Completing the square

$$s^2 + 8s + 20 = s^2 + 2as + (a^2 + \omega^2)$$

$a = 4$

$20 = 4^2 + \omega^2 \Rightarrow \omega = 2$

$$V = \frac{5s + 480}{(s + 4)^2 + 2} = \frac{5(s + 4) + 460}{(s + 4)^2 + 2} = \frac{5(s + 4)}{(s + 4)^2 + 2} + \frac{(230)(2)}{(s + 4)^2 + 2}$$

$$v(t) = 5\mathcal{L}^{-1} \left[\frac{(s + 4)}{(s + 4)^2 + 2} \right] + 230\mathcal{L}^{-1} \left[\frac{(2)}{(s + 4)^2 + 2} \right] = 5e^{-4t} \cos(2t) + 230e^{-4t} \sin(2t) \text{ V for } t > 0$$