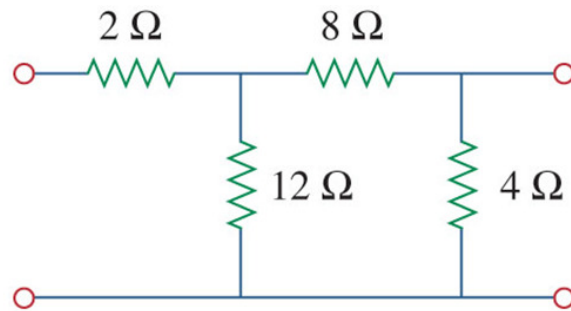



IUPUI ECE 202 Spring 2015:
Homework #10 (Due in class: April 13, 2015) Name: _____

1. (Prob. 19.1 in text) Obtain the z parameters for the network in the figure below:



IUPUI ECE 202 Spring 2015:
Homework #10 (Due in class: April 13, 2015) Name: _____

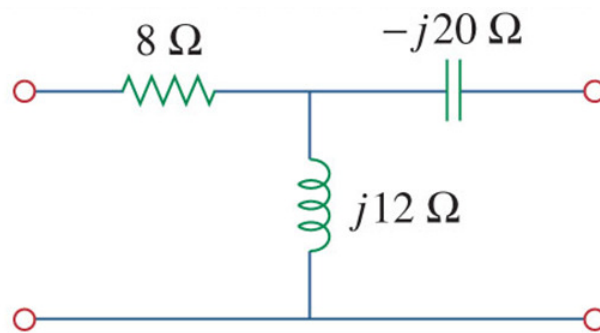2. (Prob. 19.3 from Text) Find the z parameters of the circuit below:



IUPUI ECE 202 Spring 2015:
Homework #10 (Due in class: April 13, 2015) Name: _____

3. (Prob. 19.6 from Text) Compute the z parameters of the circuit below:

