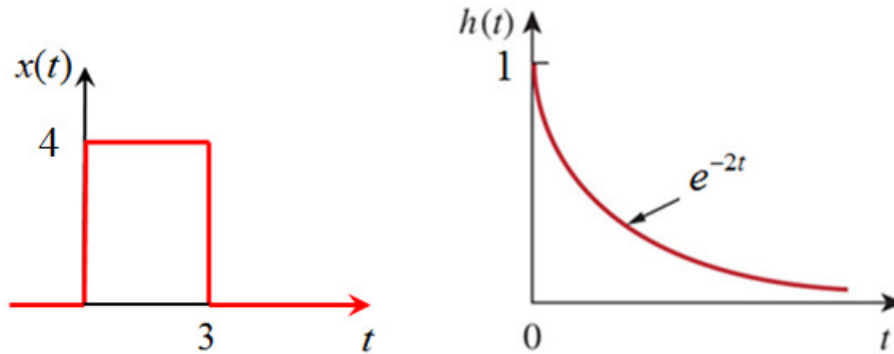


1. (25 points) Find $y(t) = x(t) * h(t)$ for the paired $x(t)$ and $h(t)$ below using two methods:
- Perform the **convolution** (either graphical method or by direct use of the convolution integral).
 - Solve by converting to the **s-domain** then back to time domain to find $y(t)$. (The Laplace Transform Pairs tables and Laplace Transform Properties tables are provided at the back of this exam).



a) for $0 \leq t < 3$
$$y(t) = \int_0^t (4)e^{-2\lambda} d\lambda = \left(-\frac{4}{2} \right) e^{-2\lambda} \Big|_0^t = (-2)(e^{-2t} - 1) = 2(1 - e^{-2t})$$

for $3 \leq t < \infty$
$$y(t) = \int_{t-3}^t (4)e^{-2\lambda} d\lambda = \left(-\frac{4}{2} \right) (e^{-2t} - e^{-2(t-3)}) = 2e^{-2t}(e^6 - 1)$$

$$y(t) = \begin{cases} 0 & t \leq 0 \\ 2(1 - e^{-2t}) & 0 < t \leq 3 \\ 2e^{-2t}(e^6 - 1) & 3 < t \end{cases}$$

b) $x(t) = 4(u(t) - u(t-3))$ $X(s) = \frac{4}{s} - \frac{4}{s}e^{-3s}$ $H(s) = \frac{1}{s+2}$

$$Y(s) = X(s)H(s) = \frac{4}{s(s+2)} - \frac{4}{s(s+2)}e^{-3s} = F(s) - F(s)e^{-3s}$$

$$F(s) = \frac{4}{s(s+2)} = \frac{k_0}{s} + \frac{k_1}{s+2} = \frac{2}{s} - \frac{2}{s+2} \Rightarrow f(t) = 2(1 - e^{-2t})u(t)$$


$$y(t) = \mathcal{L}^{-1}[F(s) - F(s)e^{-3s}] = f(t)u(t) - f(t-3)u(t-3) \quad \text{Time Delay Property}$$

$$y(t) = 2(1 - e^{-2t})u(t) - 2(1 - e^{-2(t-3)})u(t-3) = 2(1 - e^{-2t})u(t) - 2(1 - e^{-2t}e^6)u(t-3)$$

2. (30 points) Assume the source is connected to the circuit shown below for a very long time prior to the switch being opened at $t = 0$. For the circuit shown:

- Find the initial voltage $v_c(0^-)$ across the capacitor and initial current $i_l(0^-)$ through the inductor prior to the opening of the switch.
- Find $I(s)$ at $t > 0$ (after the switch has opened).
- Find $i(t)$ at $t > 0$.



Initial Conditions (circuit at $t < 0$)

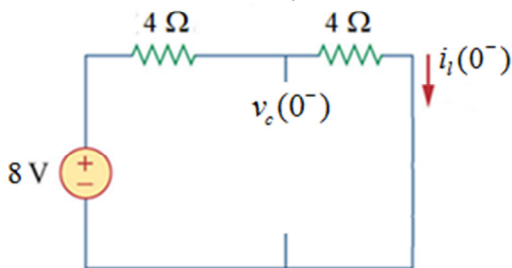

a)

$$v_c(0^-) = \frac{4}{4+4}(8) = 4$$

$$i_l(0^-) = \frac{(8)}{4+4} = 1$$

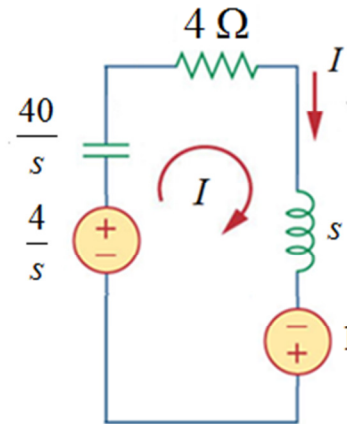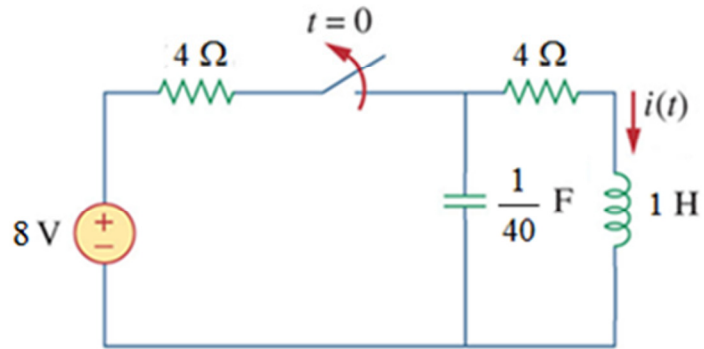

Find circuit at $t > 0$, translate to s-domain

$$b) \quad I \left(\frac{40}{s} + 4 + s \right) = 1 + \frac{4}{s}$$

$$I(s^2 + 4s + 40) = s + 4$$

$$I = \frac{s+4}{(s^2 + 4s + 40)} = \frac{s+4}{(s+2)^2 + 6^2}$$

Use "completing the square" method and numerator "trick" we discussed in lecture notes

$$s^2 + 4s + 40 = s^2 + 2as + (a^2 + \omega^2)$$

$$a = 2$$

$$40 = 2^2 + \omega^2 \Rightarrow \omega = 6$$



$$c) \quad I = \frac{(s+2)+2}{(s+2)^2 + 6^2} = \frac{(s+2)}{(s+2)^2 + 6^2} + \left(\frac{2}{6} \right) \frac{6}{(s+2)^2 + 6^2}$$

$$i(t) = e^{-2t} \cos 6t + \frac{1}{3} e^{-2t} \sin 6t \text{ A for } t > 0$$

| $f(t)$ | $F(s)$ |
|-------------------------|-------------------------------------|
| $e^{-at} \sin \omega t$ | $\frac{\omega}{(s+a)^2 + \omega^2}$ |
| $e^{-at} \cos \omega t$ | $\frac{s+a}{(s+a)^2 + \omega^2}$ |

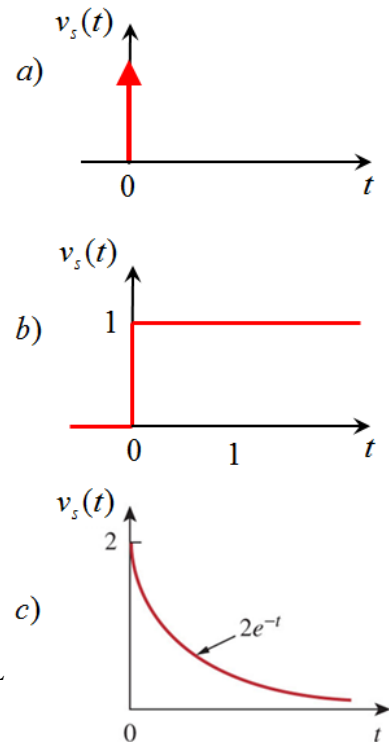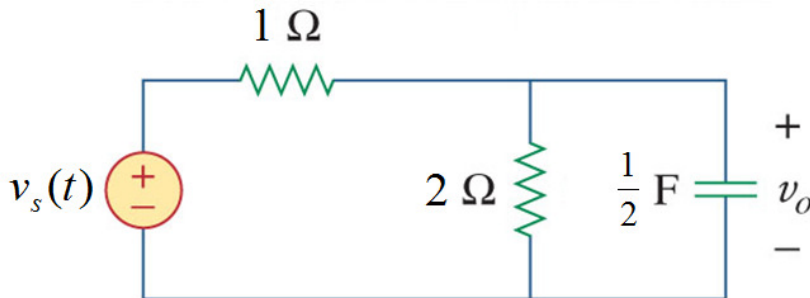3. (25 points) For the circuit shown below find the transfer function $H(s) = V_o(s) / V_s(s)$ and use to find the following outputs (assume the circuit has no initial energy):

- Find the output $v_o(t)$ given the input $v_s(t)$ is an impulse $\delta(t)$
- Find the output $v_o(t)$ given the input $v_s(t)$ is a unit step $u(t)$
- Find the output $v_o(t)$ given the input $v_s(t)$ is $2e^{-t}u(t)$



Find the impedance of the resistor and capacitor in parallel Z_L

$$Z_L = \frac{2\left(\frac{2}{s}\right)}{2 + \left(\frac{2}{s}\right)} = \frac{4}{2s + 2} = \frac{2}{s + 1}$$

Transfer function $H(s) = V_o(s) / V_s(s)$ is just a voltage divider equation:

$$H(s) = \frac{V_o}{V_s} = \frac{Z_L}{1 + Z_L} = \frac{2/(s+1)}{1 + 2/(s+1)} = \frac{2}{(s+1) + 2} = \boxed{\frac{2}{s+3}}$$

$$a) \quad V_o(s) = V_s(s)H(s) = \mathcal{L}[\delta(t)] \frac{2}{s+3} = (1) \frac{2}{s+3} = \frac{2}{s+3}$$

$$\boxed{v_o(t) = \mathcal{L}^{-1}\left[\frac{2}{s+3}\right] = 2e^{-3t}u(t)}$$

$$b) \quad V_o(s) = \mathcal{L}[u(t)] \frac{2}{s+3} = \left(\frac{1}{s}\right) \frac{2}{s+3} = \frac{k_0}{s} + \frac{k_1}{s+3} = \frac{2/3}{s} - \frac{2/3}{s+3}$$

$$\boxed{v_o(t) = \mathcal{L}^{-1}\left[\frac{2/3}{s} - \frac{2/3}{s+3}\right] = \frac{2}{3}(1 - e^{-3t})u(t)}$$

$$c) \quad V_o(s) = \mathcal{L}[2e^{-t}u(t)] \left(\frac{2}{s+3}\right) = \left(\frac{2}{s+1}\right) \left(\frac{2}{s+3}\right) = \frac{k_0}{s+1} + \frac{k_1}{s+3} = \frac{2}{s+1} - \frac{2}{s+3}$$

$$\boxed{v_o(t) = \mathcal{L}^{-1}\left[\frac{2}{s+1} - \frac{2}{s+3}\right] = 2(e^{-t} - e^{-3t})u(t)}$$

4. (20 points) Given a function $Y(s)$:

$$Y(s) = \frac{5(s+1)}{s(s+2)(s+3)}$$

- a) Use the initial value theorem to find $y(0)$
 b) Use the final value theorem to find $y(\infty)$
 c) Find the inverse Laplace Transform $y(t)$ and **verify** the answers from parts **a** & **b**.

$$a) \quad y(0) = \lim_{s \rightarrow \infty} sY(s) = \lim_{s \rightarrow \infty} s \frac{5(s+1)}{s(s+2)(s+3)} = \lim_{s \rightarrow \infty} \frac{5(s+1)}{(s+2)(s+3)} = 0$$

$$b) \quad y(\infty) = \lim_{s \rightarrow 0} sY(s) = \lim_{s \rightarrow 0} s \frac{5(s+1)}{s(s+2)(s+3)} = \frac{5(0+1)}{(0+2)(0+3)} = \frac{5}{6}$$

$$c) \quad \frac{5(s+1)}{s(s+2)(s+3)} = \frac{k_0}{s} + \frac{k_1}{s+2} + \frac{k_2}{s+3}$$

$$k_0 = \frac{5(0+1)}{(0+2)(0+3)} = \frac{5}{6}$$

$$k_1 = \frac{5((-2)+1)}{(-2)((-2)+3)} = \frac{5(-1)}{(-2)(1)} = \frac{5}{2}$$

$$k_3 = \frac{5((-3)+1)}{(-3)((-3)+2)} = \frac{5(-2)}{(-3)(-1)} = \frac{-10}{3}$$

$$Y(s) = \left(\frac{5}{6}\right) \frac{1}{s} + \left(\frac{5}{2}\right) \frac{1}{s+2} + \left(\frac{-10}{3}\right) \frac{1}{s+3}$$

$$y(t) = \left(\left(\frac{5}{6}\right) + \left(\frac{5}{2}\right)e^{-2t} + \left(\frac{-10}{3}\right)e^{-3t} \right) u(t) = \left(\frac{5}{6}\right) (1 + 3e^{-2t} - 4e^{-3t}) u(t)$$

$$y(0) = \left(\frac{5}{6}\right) + \left(\frac{5}{2}\right)e^0 + \left(\frac{-10}{3}\right)e^0 = \frac{5}{6} + \frac{5}{2} + \frac{-10}{3} = \frac{5}{6} + \frac{15}{6} + \frac{-20}{6} = 0$$

$$y(\infty) = \lim_{t \rightarrow \infty} y(t) = \left(\frac{5}{6}\right) + \left(\frac{5}{2}\right)e^{-\infty} + \left(\frac{-10}{3}\right)e^{-\infty} = \frac{5}{6} + 0 + 0 = \frac{5}{6}$$