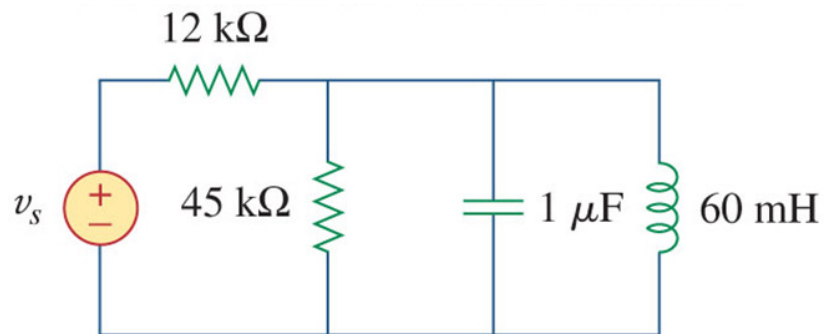


IUPUI ECE 202 Spring 2015:
Homework #5 (Due in class: Feb 25, 2015) Name: _____

1. (Prob. 14.29 in text) Let $v_s = 20 \cos(at)$ V in the circuit below. Find resonant frequency ω_o , quality factor \mathbf{Q} , and bandwidth \mathbf{B} , as seen by the capacitor.




IUPUI ECE 202 Spring 2015:

Homework #5 (**Due in class: Feb 25, 2015**) Name: _____

2. (Prob. 14.35 from Text) A parallel RLC circuit has $R = 5 \text{ k}\Omega$, $L = 8 \text{ mH}$, and $C = 60 \text{ }\mu\text{F}$. Determine the following:
- a. The resonant frequency ω_o
 - b. The bandwidth **B**
 - c. The quality factor **Q**

IUPUI ECE 202 Spring 2015:
Homework #5 (Due in class: Feb 25, 2015) Name:

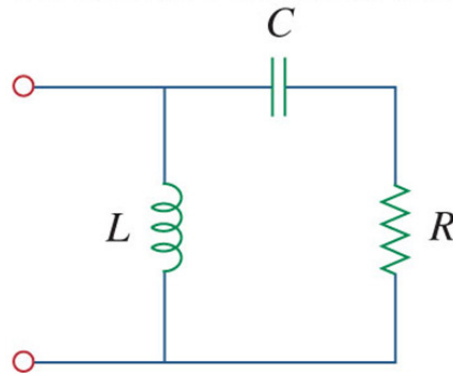3. (Prob. 14.38 from Text) Find the resonant frequency of the circuit in the figure below.



IUPUI ECE 202 Spring 2015:

Homework #5 (**Due in class: Feb 25, 2015**) Name: _____

4. (Prob. 14.53 from Text) Design a series RLC type **bandpass** filter with cutoff frequencies of 10 kHz and 11 kHz. Assuming $C = 80 \text{ pF}$ (80×10^{-12}), find R , L , and Q . **Draw** the circuit

IUPUI ECE 202 Spring 2015:
Homework #5 (**Due in class: Feb 25, 2015**) Name:

5. (Prob. 14.54 from Text) Design passive **bandstop** filter with $\omega_o = 10$ rad/s and $Q = 20$.
Draw the circuit.

IUPUI ECE 202 Spring 2015:
Homework #5 (**Due in class: Feb 25, 2015**) Name:

6. (Prob. 14.67 from Text) Design an **active lowpass** filter with dc gain of 0.25 and corner frequency of 500 Hz. (Remember $\omega = 2\pi f$)

IUPUI ECE 202 Spring 2015:
Homework #5 (Due in class: Feb 25, 2015) Name:

7. (“Based on” Prob. 14.68 from Text) Design an **active highpass** filter with dc voltage gain of +6 dB and corner frequency of 3000 Hz. (Remember $\omega = 2\pi f$)